

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

JULY 1977 / \$1.25

BATTERY MONEY-SAVER

"Zap" New Life Into Dead NiCd Batteries

AUDIO

Tape Recorder Hygiene

HOW TO MAINTAIN RECORDERS IN PEAK CONDITION

Build a Low-Cost Pink Noise Generator

A VALUABLE AUDIO TEST TOOL

COMMUNICATIONS

Deciphering Utility Code Broadcasts Without Knowing Morse Code!

TEST REPORTS

Radio Shack STA-2000

Stereo FM/AM Receiver

Koss K-145 Stereo Headphones

Cobra 29XLR 40-Channel AM

CB Mobile Transceiver



Two Fantastic Video Projects



BUILD DON LANCASTER'S LATEST "TV TYPEWRITER"

It's a \$35 Interface Board



GRAPHICS COMES TO THE "ELF" MICROCOMPUTER!

This One's Less Than \$25

Introducing the mobile that can move you out of the world of the ordinary and into the world of the serious CB'er. The Cobra 138XLR Single Sideband. Sidebanding puts you in your own private world. A world where there's less congestion. More privacy. More time to talk.



It's all possible because instead of 40 channels you get your choice of 120 channels. Both AM and SSB. And instead of 4 watts of legal power you get 12 watts of legal power. So you get almost double the range of AM.

With the 138XLR Single Sideband there's less background noise and less interference. So there's cleaner, clearer reception. Because like all Cobras, the 138XLR SSB is engineered to punch through loud and clear. Even in crowded metropolitan areas.

And like all Cobras it comes equipped with such standard features as an easy-to-read LED channel indicator. Switchable noise blanking and limiting. An RF/signal strength meter. And Cobra's exclusive DynaMike gain control.

You'll find the 138XLR SSB wherever Cobras are sold. Which is almost everywhere. Because Cobra's got a nationwide network of dealers and Authorized Service Centers offering sales, installation, service and advice. So come on in. And move on up.



Punches through loud and clear.

Cobra Communications Products
DYNASCAN CORPORATION
6460 W. Cortland St., Chicago, Illinois 60635

Write for color brochure
EXPORTERS: Empire • Plainville, N.Y. • CANADA: Atlas Electronics • Toronto

CIRCLE NO. 9 ON FREE INFORMATION CARD

UPWARD MOBILITY.



Revolutionary breakthrough in CB antenna design




Photo courtesy of Edmund Scientific Co.

AVANTI Invents the Saturn™ Base

The reason the "Saturn" is so revolutionary is that it is absolutely the only combination vertical and horizontal omni-directional antenna. That's right, it needs no rotor! You can pick up mobiles (which are vertical) or horizontal and vertical beams.

The "Saturn", invented after years of research by Avanti engineers, is the latest development using AVANTI's unique CO-INDUCTIVE principle to give you the performance of two antennas combined into one.

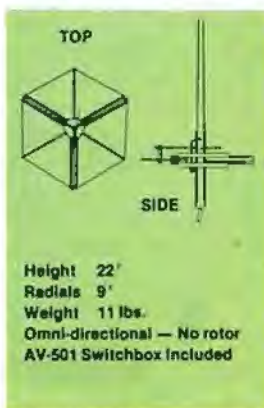The "Saturn" not only works on both polarities, but pounds out signals like an air hammer and picks them up like a magnet. Both polarities offer high gain figures.



Patent Pending

Avanti makes a complete line of high performance base and mobile CB antennas from \$11.95 to \$404.00. Write for free Avanti catalog.

Those of you who are worried about sun spots and "skip" can relax too. This antenna really helps. When the sun spots cause a signal shift, you can often change polarity (just like our P.D.L. or Moonraker) and still pick up the desired channel with no loss of transmission.

The P.D.L. and Moonraker made dual polarity famous as the only antennas to have during the last sun spot cycle, and this time around any serious C.B.'er will want to have the "Saturn."

In fact, having a "Saturn" and a "P.D.L." or "Moonraker" will put you in the elite group of C.B.'ers who "always seem to get out better."

avanti®

AVANTI RESEARCH AND DEVELOPMENT, INC.,
340 Stewart Avenue, Addison, IL 60101

© Copyright 1977, All rights reserved

Creators of the famous

CIRCLE NO. 6 ON FREE INFORMATION CARD



MIDLAND POWER

IT'S WHAT YOU GET WHEN YOU RUN WITH NUMBER 1. MIDLAND CB.



WE GOT TO THE TOP ON PURE GUTS.

Consistency. If one word can sum up Midland's rise to Number 1 in CB, that's it.

We've got to know that the ten-thousandth Midland will

perform every watt and ohm as reliably as the first Midland off the line.

To make sure, we use computer technology throughout the manufacture of all our new 40-channel models.

In the assembly and integration of our state-of-the-art circuitry.

In the ultra-fine tuning of those circuits.

And in the final testing of your new 40-channel Midland CB, so you know it'll deliver,

right out of the box.

Add to that Midland's 15 years' experience in CB, Midland's warranty and convenient authorized service centers, coast to coast.

Pure guts. Pure reliability. Pure Midland Power. That's what you get when you run with Number 1.

For your free, full-color, 24-page 1977 Midland CB brochure, write: Midland International, P.O. Box 12737, North Kansas City, Mo. 64116



MIDLAND CB

A member of the Beneficial Corporation family.

Shop for these active living products from Midland International: Benchmark Tools • Goodwin Sporting Goods • Medallion Car-Sound Products • Midland Television • Young World Toys.

CIRCLE NO. 28 ON FREE INFORMATION CARD

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

FEATURE ARTICLES

RC CIRCUIT QUIZ	Robert P. Balin	26
NOISE FILTERING FOR HI-FI	Julian D. Hirsch	32
PIXIE ANIMATION PROGRAM	Edward C. Deveau	42
END THAT "UTILITY FUTILITY"	Harry L. Helms, Jr.	53
<i>DX'ing CW without knowing Morse code.</i>		
TAPE RECORDER HYGIENE	Craig Stark	56
<i>The importance of taking care of your machine and tapes.</i>		
AN INTRODUCTION TO GYRATOR THEORY	Bryan T. Morrison	58
"ZAP" NEW LIFE INTO DEAD NiCd BATTERIES	Douglas C. Myers	60
THE WORLD OF ELECTRONICS	Frank Bolle	67
AVERAGE, PEAK, AND RMS VALUES	Hector French	68
HOBBYIST COMPUTER CLUBS		91

CONSTRUCTION ARTICLES

COSMAC ELF, PART IV	Joseph A. Weisbecker	41
<i>One added chip provides video interface and animated graphics.</i>		
ELECTRONIC "BELL" FOR A TVT-II	Denis J. Deutsch	46
BUILD THE TVT-6: A LOW-COST DIRECT VIDEO DISPLAY	Don Lancaster	47
<i>User-selectable line lengths; scrolling; and up to 4k on-screen characters.</i>		
BUILD A PINK NOISE GENERATOR FOR AUDIO TESTING	Dennis Bohn	66
BUILD A SOLAR CONTROLLER	Jerald M. Cogswell	69
PORTABLE 60-HZ "CLOCK" OSCILLATOR	Charles F. Smith	70
ONE-TOUCH DIODE TESTER	David Markegard	75

COLUMNS

STEREO SCENE	Ralph Hodges	22
<i>Instruments I Have Miked.</i>		
SOLID STATE	Lou Garner	77
<i>IC's For Test Instruments.</i>		
EXPERIMENTER'S CORNER	Forrest M. Mims	82
<i>The 556 Timer.</i>		
HOBBY SCENE	John McVeigh	84
CB SCENE	Ray Newhall	88
<i>The Anatomy of CBRS.</i>		
COMPUTER BITS	Hal Chamberlin	89
<i>Assemblers.</i>		

JULIAN HIRSCH AUDIO REPORTS

REALISTIC MODEL STA-2000 STEREO RECEIVER	33
KOSS MODEL K/145 STEREO HEADPHONES	36

ELECTRONIC PRODUCT TEST REPORTS

COBRA MODEL 29 XLR MOBILE 40-CHANNEL CB TRANSCEIVER	85
WAHL MODELS 7700 AND 7800 CORDLESS SOLDERING IRONS	86

DEPARTMENTS

EDITORIAL	Art Salsberg	4
<i>Solar Energy News Notes.</i>		
LETTERS		6
OUT OF TUNE		7
<i>"Bicycle Speedometer" (March 1977); "LED Racing Game" (March 1977); "Digistart Lock" (April 1977).</i>		
NEW PRODUCTS		12
NEW LITERATURE		16
NEWS HIGHLIGHTS		38
TIPS & TECHNIQUES		92
OPERATION ASSIST		93
ELECTRONICS LIBRARY		95

POPULAR ELECTRONICS, July 1977, Volume 12, Number 1. Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S. and Possessions, \$12.00; Canada, \$15.00; all other countries, \$17.00 (cash orders only, payable in U.S. currency). Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada, and for payment of postage in cash.

POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature.

COPYRIGHT © 1977 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.

Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to Jerry Schneider, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.

Forms 3579 and all subscription correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

EDGAR W. HOPPER
Publisher

ARTHUR P. SALSBERG
Editorial Director

LESLIE SOLOMON
Technical Editor

JOHN R. RIGGS
Managing Editor

IVAN BERGER
Senior Editor

ALEXANDER W. BURAWA
Features Editor

EDWARD I. BUXBAUM
Art Director

JOHN McVEIGH
Associate Editor

ANDRE DUZANT
Technical Illustrator

PATRICIA GERRIER-BROWN
Production Editor

Contributing Editors
HAL CHAMBERLIN, LOU GARNER
GLENN HAUSER, JULIAN HIRSCH
RALPH HODGES, FORREST MIMS
RAY NEWHALL, WILFRED SCHERER

JOSEPH E. HALLORAN
Advertising Director

JOHN J. CORTON
Advertising Sales

LINDA BLUM
Advertising Service Manager

PEGI McENEANEY
Executive Assistant

STANLEY NEUFELD
Associate Publisher

ZIFF-DAVIS PUBLISHING COMPANY
Popular Electronics
Editorial and Executive Offices
One Park Avenue New York, New York 10016
212-725-3500

Herchel B. Sartor, President
Furman Hobbs, Executive Vice President
John R. Emery, Sr. Vice President, Finance and Treasurer
Phillip T. Heffernan, Sr. Vice President
Edward D. Muhlefeld, Sr. Vice President, Sports Division
Philip Sine, Sr. Vice President
Frank Pomerantz, Vice President, Creative Services
Arthur W. Butzow, Vice President, Production
Lawrence Sporn, Vice President, Circulation
George Morrissey, Vice President
Sydney H. Rogers, Vice President
Sidney Holtz, Vice President
Albert S. Traim, Vice President
Philip Korsant, Vice President
Paul H. Chook, Vice President
Edgar W. Hopper, Vice President
Charles B. Seton, Secretary
William Ziff, Chairman
W. Bradford Briggs, Vice Chairman

Midwestern Office
The Patis Group, 4761 West Touhy Ave.
Lincolnwood, Illinois 60466, 312-679-1100
Thomas Hockney, Michael Neri, Gerald E. White
Western Office
9025 Wilshire Boulevard, Beverly Hills, CA 90211
213-273-8050, Bradshaw 2-1161
Western Advertising Manager: Bud Dean
Japan: James Yagi
Oji Palace Aoyama, 5-25, Minami Aoyama
6 Chome, Minato-Ku, Tokyo 407-1930/6821,
582-2851



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



Editorial

SOLAR ENERGY NEWS NOTES

¶ A recent energy policy study by the MITRE Corp. concludes that nuclear power is the economical choice for at least the remainder of the century. . . . If other than economic considerations are counted, coal might eventually prove more attractive. . . . Solar energy for heating houses will be practical in the near future in favorable situations, but there's little prospect for competitively priced solar power in this century. (A Fusion Energy Foundation spokesman, however, says that the total study was justification to cut the Clinch River Tenn. fast-breeder reactor program.)

¶ In contrast, the latest paper from Worldwatch Institute (*Energy: The Solar Prospect*) concludes that subsidizing energy forms other than solar makes devices for the latter appear relatively costly. Removing subsidization would, according to the paper, make solar resources able to provide 40 percent of the world's energy needs by the end of the twentieth century. Researchers at the University of New Mexico, in a study prepared for the Joint Economic Committee of Congress, also claim that solar energy could compete with other energy sources (by 1990).

¶ President Carter asked Congress to downplay the future use of nuclear energy in his overall energy conservation/production proposals.

¶ At IBM Corp.'s Palo Alto facilities, powerful computers are exploring solutions to the problems of tapping the sun as a widespread and economical source of energy.

¶ Carl Pepper's amazing solar heating machine provides 55 percent of the heating needs in his 3200-square-foot home in Granton, Ontario, Canada. Cost is said to be \$1300, with projected savings in fuel oil of more than \$3000/year by 1996. The builder sells solar construction plans for \$10 and a differential thermostat for \$60, the latter said to be reversible for cooling the house in the summer. (See *Harrowsmith*, Jan./Feb. 1977 issue, \$1.00, published by Camden House Publishing, Camden East, Ontario, Canada, KOK-1J0.)

¶ An advertiser in *Newsday*, a Long Island, N. Y., newspaper, offers swimming-pool solar energy heaters for \$1900.

¶ A selection of texts on solar energy: *The Solar Energy Handbook*, Time-Wise Publications, P. O. Box 4140, Pasadena, CA 91106 (87 pages, soft cover, \$3.95, plus \$.50 handling); *Solar Energy Directory*, Centerline Corp., 401 S. 36th St., Phoenix, AZ 85034 (108 pages, soft cover, \$7.50); *Wind/Solar Energy*, by Edward Noll, Howard W. Sams & Co., Inc., Indianapolis, IN 46268 (208 pages, soft cover, \$7.95); *Solar Cells*, (IEEE Press Selected Reprints), John Wiley & Sons, Inc., 605 Third Ave., New York, NY 10016 (504 pages, \$29.95 cloth, \$8.95 soft cover).

Judging from the response to our annual tongue-in-cheek "April Hobby Scene," which included an implausible solar cell project, there's an extremely high level of interest in solar energy. Perhaps these serious observations will partially whet it. As an aside, I wonder what the new budget for energy research will be. Solar thermal research for fiscal-year 1976 was budgeted for only 89-million dollars; not much by any standard, and only some 4.5 percent of the total revised energy R & D budget. However, the Carter administration's new energy package seems to promise that solar devices will soon have their day in the sun.

Art Salsberg

Do-it-yourself JBL.



Take the guts of what makes JBL JBL and adapt it to your own ideas of what a loudspeaker system should be.

Mix and match with forty-seven individual JBL components—horns, lenses, dividing networks, transducers, everything.

And when you've found your perfect sound, we'll help you find somewhere to put it: The JBL Enclosure Construction Kit, with complete plans for building your own loudspeaker enclosure from scratch.

See your authorized JBL Loudspeaker Components dealer for the start of a great new team in sound: You and JBL.





DOCTORS SAY NOT TO WORRY

No matter how "spacey" the rest of the world got, I could always depend on good ole PE to be swimming in the "real" world of parts specifications and product news. Then I saw April's "How to DX Earth Radio From Outer Space." I still talk to myself and my hands shake, but the doctors tell me not to worry. Just kidding, I can't begin to tell you how much I enjoy reading your magazine. —Michael Swaney, Erie, PA.

ETC HAS ROM MONITOR

I read with interest the April 1977 Computer Bits column and was not pleased that the only remark about our product was an unfavorable comparison with a competitor, especially when this remark was based on misinformation. The Model ETC-1000 Basic System includes a 40-key keyboard that is operated by a monitor system that permits the user to effectively operate a minimum system or to initialize and perform other housekeeping operations in systems with terminal interfaces. Our terminal monitor version comes in two packages, the 8k and 16k configuration (the latter including an assembler), and disassembler, Basic, cassette I/O, Utilities, and a variety of other program packages. —E.S. Bjornsson, Electronic Tool Co., Hawthorne, CA.

Our apologies for the erroneous description of the ETC-1000. The ROM monitor system indeed uses 40 buttons to allow calling routines from the monitor without need of a terminal. Debugging is simplified by using a built-in break-point routine, and included is a thorough memory diagnostic system.

"DIGISTART'S" COLLAPSING FIELD

After reading the "Digistart" (April 1977) article, I noticed a minor omission in the circuit that might cause operating problems. When the Q1 transistor cuts off, the collapsing field of the K1 coil could induce a large enough back emf to destroy the transistor. To remedy this, it is suggested that a diode be installed across the relay's coil in reverse bias. To be on the safe side, the rectifier diode should be rated at no less than 100 PIV at 1 ampere. —Alan Bradford, Derry, NH.

"APRIL FOOL" IS 2-WAY STREET

We were intrigued with the high-efficiency solar cell described in the April Hobby Scene. Because the corresponding ketone (3,7-dimethylpentadecan-2-one) is available in

large quantities, at least in the midwest, by ether extraction from the saliva of pregnant sows, this seemed like the logical starting point. Reduction of this ketone with sodium borohydride gave the alcohol that, upon treatment with propionyl chloride in pyridine, gave the desired propionate ester in good yield.

The solar cell was then constructed pretty much as described, except that a glass spray bottle could not be used to apply the compound to the sand. This is because the chemical also reacts with the silica in the glass and the resulting deoxygenation process is violent. A plastic bottle, however, works quite well. The cell actually is more efficient than the one described, providing about 87% conversion. —Dr. C.T.C. Creedy and co-workers, Charles F. Kettering Research Laboratory, Yellow Springs, OH.

You stated that car-radio frequency drift was due to the Doppler effect and that the problem should be corrected with a phase-locked loop. My God, tell the fool to slow down! For an audible Doppler shift to occur in the commercial AM band (let's say 5 Hz, to be conservative), this person would have to be driving faster than 5000 mph. By helping him to keep his radio tuned, you are aiding and abetting this reckless and unlawful operation of a motor vehicle. —Walter Satre, Chairman, Electrical & Electronics Technology Dept., Vermont Technical College, Randolph Center, VT.

In discussing the well-known effect of radiation pressure from car stereo speakers in the April Hobby Scene, Marcia Swampfelder overlooked the most important application of them all: swinging the speakers forward to assist in braking. Such dynamic air braking does not wear down the tires and has been used effectively for years in fire engines. When close to the fire, the driver swings his siren around to hasten the stop. You can determine the precise moment when he does this from the change in pitch, caused by the Doppler effect, provided you are not close to the fire. —Harry E. Stockman, Arlington, MA.

DX'ING EARTH ON CHANNEL 68

The statement that there is only one channel 68 in North America in "How to DX Earth Radio From Outer Space" (April 1977) is incorrect. Independent station WBTB TV in Newark, NJ operates on channel 68. —John J. Dynarski, Carteret, NJ

FREQUENCY READOUT PROJECT A HIT

I wish to thank POPULAR ELECTRONICS and author David L. Mattis for the "Digital Frequency Readout for Shortwave Receivers" (February 1977). After connecting it to my receiver, it was surprisingly accurate and stable. I can set my receiver to a predetermined frequency and just wait for the signal to fade in. Also, the display is especially bright and clear and can be read from clear across the room.

Incidentally, the hookup point given in the

article is incorrect for my 1973 Lafayette Radio Model HA-600A receiver. The correct tie point is the junction of C31 and R16. The circuit board in the receiver is already drilled to permit such a connection. —Stephen E. Franklin, Ellicott City, MD

I built the "Digital Frequency Readout" project from a kit supplied by Mattis Electronics and am delighted with it. I was impressed by the fine kit of parts supplied. Everything was included and the project worked immediately upon completion. —D.C. Mead, Greensboro, NC

AN ERROR IN SWITCHING

In "Build a Digital Bicycle Speedometer" (March 1977), it is stated that, to calibrate the project one must "depress S2 and adjust R2 until the display indicates the wheel's diameter." Since S2 is the power switch, the instructions should read: "depress S3 . . ." —Rick Stievenart, Carbon, IN.

THANKS FOR THE "ELF"

My thanks to Joe Weisbecker for designing the "COSMAC Elf Microcomputer" (August 1976). I built my micro using slide switches, discrete LED's, and a 555 timer IC for economy. (In my project, the 555 timer can be placed in either of two positions in a 16-pin DIP socket to give me either a high or a low clock.)

The basic construction technique I used in assembling my Elf was Wire Wrap, with two bus strips for power distribution. My main problem during assembly was trying to find 22-pin Wire Wrap sockets. Since I couldn't find them anywhere, I had to build my own from Molex Soldercons, Vector J pins, and epoxy cement. My next project is to build my Elf with a hex keyboard and 1024 words of memory. —Charles J. Billwiller, Rancho Cordova, CA.

SLIDE SYNCER STEERS MOTORBOAT

I enjoyed building "The 35-mm Slide Syncer" (November 1976). Found the circuit to be so stable that I plan to use two of them in a programmable steering system for my motorboat. The only "bug" in the system is that it will trigger from some momentary signals other than its center-frequency signal. This problem can be eliminated by increasing the value of C6 to 20 or 30 μ F.

I also found that the circuit refused to trigger at low signal levels. I discovered that by paralleling R2 with a 50,000-ohm potentiometer, this second problem could be eliminated. These modifications ensure excellent circuit operation. —Mark Irgang, New York, NY.

MORE SOLAR VIEWING SAFETY

"Propagation Forecasts For Radio Communications" (November 1976) contains an error regarding the use of the Kodak #4 neu-

tral-density filter which could have serious consequences. The safest way to view the sun through binoculars or a telescope is by projection. If direct viewing is required, it should be done only through full-aperture filters of the deposited-metal-film type such as that shown on the telescope in Fig. 3 of the article. These filters effectively block all harmful radiation.

Another method is to use one or more layers of black and white (not color) film that has been exposed to direct sunlight and then developed. These are suitable for direct viewing but not photography because they degrade the image.

Another area of danger is in the use of the so-called "sun filters" supplied with many inexpensive telescopes. These filters are meant to be used on the eyepiece. Since they will be near the focal plane of the main objective lens or mirror, it is possible that sufficient heat could be built up in the filter to cause it to crack. The damage to the eye would occur before the observer could move away from the eyepiece.—John Hudak, Vice President, Hamilton Centre of the Royal Astronomical Society of Canada, Ontario, Canada.

ANOTHER CLASS OF AMPLIFIER

We read with interest "Classes of Audio Amplifiers" (March 1977) and noted that although the article covered classes A through G, it failed to mention the class K "reference


shift" amplifier. The class-K amp is similar to the class-A amp except that the average direct current to the power amplifier is controlled as a function of the audio level. Thus, no more power is consumed than is necessary to minimize distortion for a particular audio level. This makes its average efficiency appreciably higher than for the class-A amplifier. The principal virtue of the class-K amplifier is that it yields about twice the power output of a class-A system, using the same tube or transistor. Of course, the class-K system is not suitable for hi-fi without special refinements because of difficulties in handling transients. But it performs well in voice applications, such as in modulating communication equipment.—Dale Hileman, WB6NTR, Topanga, CA

Out of Tune

In "Bicycle Speedometer" (March 1977), the segment-I pin of IC2 in Fig. 1 was incorrectly identified as pin 16; it should be pin 10.

In "LED Racing Game" (March 1977), pins 7 and 8 of IC13 in Fig. 4 are reversed. Also, pin 16 of IC6, IC7, and IC8 must be connected to the +5-volt bus (see Fig. 6). If you add a 4700-ohm, 1/4-watt resistor to IC9 through

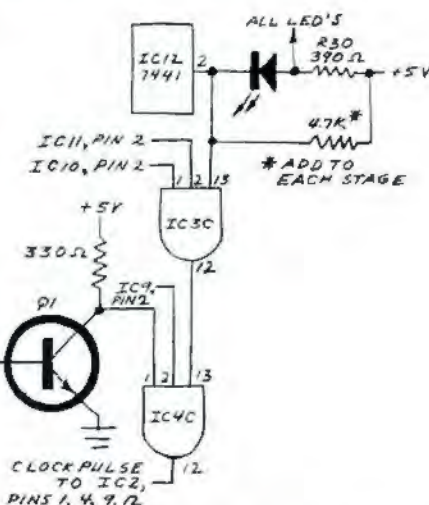IC12 as shown here, the two unused 7411 gates can be used to block the clock pulse



when any one of the four players reaches the finish first. This will eliminate any doubt as to the winner if all four players wish to race at the same time.

In the "Digistart Lock" (April 1977), contact bounce problems in flip-flop A can be reduced by connecting pin 1 (J) to +5V and pin 4 (K) to gnd. On IC5, the Q output is pin 1. For more stability in the one-shot multivibrator, change R6 to 39,000 ohms (1/4-watt) and C1 to 120 μ F.

Great Jumpers are here!

State of the art flat cable connector assemblies . . . at affordable prices.

Great Jumpers come to you fully pre-assembled and fully pre-tested. Cable strain reliefs are integral to the molded-on connectors. And we've designed in complete line-by-line probeability with probe access ports behind each contact.

Our connectors are industry standard; two parallel rows of contacts, spaced every .1".

Great Jumpers come in five popular cable widths: 20, 26, 34, 40 and 50 lines wide, and in lengths ranging from 6" to 36".

Available now at the distributor near you who carries the A P Products Faster and Easier Line.

Our distributor list is growing daily. For the name of the distributor nearest you call Toll-Free 800-321-9668.

Send for our complete A P catalog, the Faster and Easier Book.

Faster and easier is what we're all about.



A P PRODUCTS INCORPORATED

Box 110-72 Corwin Drive, Painesville, Ohio 44077
(216) 354-2101 TWX: 810-425-2250

Learn to service Communications/CB equipment at home...with NRI'S COMPLETE COMMUNICATIONS COURSE

Learn design, installation and maintenance of commercial, amateur, or CB communications equipment.

The field of communications is bursting out all over. In Citizens Band alone, class D licenses grew from 1 to over 2.6 million in 1975, and the FCC projects about 15 million CB'ers in the U.S. by 1979. That means a lot of service and maintenance jobs . . . and NRI can train you at home to fill one of those openings. NRI's Complete Communications Course covers all types of two-way radio equipment (including CB), AM and FM



Transmission and Reception, Television Broadcasting, Microwave Systems, Radar Principles, Marine Electronics, Mobile Communications, and Aircraft Electronics.

The course will also qualify you for a First Class Radio Telephone Commercial FCC License or you get your tuition back.

Learn on your own 400-channel digitally-synthesized VHF transceiver.

You will learn to service all types of communication equipment, with the one unit that is designed mechanically and electronically to train you for CB, Commercial and Amateur communications: a digitally-synthesized 400-channel VHF transceiver and AC power supply. This 2-meter unit gives you "Power-On" training. Then we help you get your FCC Amateur License with



special instruction so you can go on the air.

The complete course includes 48 lessons, 9 special reference texts, and 10 training kits. Included are: your own electronics Discovery Lab, Antenna Applications Lab, CMOS Frequency Counter, and an Optical Transmission System. You'll learn at home, progressing at your own speed, to your FCC license and into the communications field of your choice.

NEW CB SPECIALIST COURSE NOW OFFERED



NRI now offers a special course in CB Servicing. You get 37 lessons, 8 reference texts, your own CB Transceiver, AC power supply and multi-meter . . . for hands-on training. Also included are 14 coaching units to make it easy to get your commercial radio telephone FCC license—enabling you to test, install, and service communications equipment.

NRI offers you five TV/Audio Servicing Courses

NRI can train you at home to service TV equipment and audio systems. You can



choose from 5 courses, starting with a 48-lesson basic course, up to a Master Color TV/Audio Course, complete with designed-for-learning 25" diagonal

solid state color TV and a 4-speaker SQ™ Quadraphonic Audio System. NRI gives you both TV and Audio servicing for hundreds of dollars less than the two courses as offered by another home study school.

All courses are available with low down payment and convenient monthly payments. All courses provide professional tools and "Power-On" equipment along with NRI kits engineered for training. With the Master Course, for instance, you build your own 5" wide-band triggered sweep solid state oscilloscope, digital color TV pattern generator, CMOS digital frequency counter, and NRI electronics Discovery Lab.



™Trademark of CBS Inc.

NRI's complete computer electronics course gives you real digital training.

Digital electronics is the career area of the future . . . and the best way to learn is with NRI's Complete Computer Electronics Course. NRI's programmable digital computer goes far beyond any "logic trainer" in preparing you to become a computer or digital technician. With the IC's in its new Memory Kit, you get the only home training in machine language programming . . . experience essential to trouble shooting digital computers. And the NRI programmable computer is just one of ten kits you receive, including a TVOM and NRI's exclusive electronics lab. It's the quickest and best way to learn digital logic and computer operation.

You pay less for NRI training and you get more for your money.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

More than one million students have enrolled with NRI in 62 years.

Mail the insert card and discover for yourself why NRI is the recognized leader in home training. No



salesman will call. Do it today and get started on that new career.

APPROVED UNDER GI BILL

if taken for career purposes Check box on card for details.



NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016



New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.

DYNACO INTEGRATED AMPLIFIER

The Model SCA-50 integrated amplifier is available from Dynaco/Dynakit either factory assembled or in kit form. It is rated at 25 watts/channel continuous average power with less than 0.5% THD with 8-ohm loads. The bass and treble control circuits are de-



signed to have little or no effect on the mid-range. The turnover in the bass control system is variable, while that in the treble system is fixed and has a hinge frequency that is higher than is usual. In the amplifier section, the output circuit is full complementary symmetry, and the bias supply thermally tracks the output transistors. A thump-suppression circuit (for turn-on/turn-off) is standard. In addition to the line fuse, protection includes separate fuses at each of the four power supply outputs, current limiting, and a thermal circuit breaker. \$149 kit; \$249 factory wired.

CIRCLE NO. 89 ON FREE INFORMATION CARD

RAYMALEE CB MOBILE ANTENNA

The Solar Hot Rod, from Raymalee, is a power-gain CB antenna featuring a self-contained solar-powered device with built-in solar storage. It clamps to the user's present mobile or base-station antenna with no addi-



tional wiring required. The Solar Hot Rod is said to provide 14 dB of signal gain to the receiver with less than 2 dB of noise gain. The Solar Power Supply is claimed to be able to maintain a fully charged supply, enough to provide several months operation in total darkness. \$89.95.

CIRCLE NO. 91 ON FREE INFORMATION CARD

AMCOMM 2-METER FM TRANSCEIVER

The Model S225 2-meter mobile FM transceiver from AMCOMM (American Communications Corp.) features a digital synthesizer that provides complete coverage of the 2-meter ham band in 5-kHz increments. Operating frequency is determined by three rotary



switches and is displayed to the nearest kilohertz on a six-digit LED display. Transmit offsets are switch selectable for +600 kHz, -600 kHz, +1 MHz and -1 MHz. R-F output power is continuously variable from 2 to 25 watts, with spurious harmonic output at -60 dB. Receiver sensitivity is rated at 0.5 μ V for 20 dB quieting. Local oscillator frequency stability is claimed to be ± 5 ppm. Audio output power is rated at 4 watts into the built-in 8-ohm speaker with less than 10% distortion. The transmitter is phase modulated (± 5 kHz with 100% modulation at 1000 Hz), and T/R switching is solid state. A Touch-Tone encoder is optional.

CIRCLE NO. 92 ON FREE INFORMATION CARD

OPTONICA FRONT-LOAD CASSETTE DECK

Sharp Electronic Corp.'s Optonica Model RT-2050U is a two-motor, front-loaded cassette deck. Wow and flutter is rated at 0.045% weighted rms, and S/N ratio is 64 dB with its Dolby noise-reduction system switched in. An automatic program find sys-



tem (APFS) enables the user to move to the next selection or to return to the start of the current selection simply by pushing a button. Among other features are: a space setter, peak level meters (respond to signals in 10 ms), electronic automatic stop, and three-position BIAS and EQUALIZER tape selection switches, pause switch, counter, stereo headphone jack, separate record level controls, and a ganged output control. \$299.95.

CIRCLE NO. 93 ON FREE INFORMATION CARD

MOTOROLA CB RADIO CARRYING CASE

A Universal Carrying Case for mobile CB transceivers has been introduced by the Motorola Communications Group Parts Dept. The case permits easy removal of a CB radio so it can be carried by the owner from an unattended vehicle. Separate compartments



in the case hold microphones, the power cable, and a portable antenna. The case is designed so a mobile radio can be operated without removing it from the case. Openings at the top and bottom of the case allow the speakers to be heard, while a large opening at the back permits antenna and power connections. The front flap folds down so that the transceiver controls and microphone jack are readily accessible. Covered with Texion vinyl that simulates genuine leather and equipped with a heavy-duty handle, the case measures 12" x 9" x 3" (30.5 x 23 x 7.6 cm).

CIRCLE NO. 94 ON FREE INFORMATION CARD

SENCORE AUDIO-VHF FREQUENCY COUNTER

Sencore's FC45 frequency counter offers continuous frequency check capability from audio through vhf (uhf-band coverage to 600 MHz with optional PR47 prescaler). A direct-reading eight-digit display with pushbutton




action makes the FC45 easy to use. Incorporates a crystal checker. Counter sensitivity is 25 mV average throughout the band; accuracy is 1 ppm, using a temperature-controlled oven. The basic unit comes with all testing leads at \$395. The PR47 prescaler is \$125.

CIRCLE NO. 95 ON FREE INFORMATION CARD

NAKAMICHI FM TUNER/PREAMPLIFIER

The Model 630 FM tuner/preamplifier from Nakamichi is said to provide an extremely low-noise, low-distortion preamplifier section. Noise is rated at 80 dB below 1 mV, and distortion is claimed to be virtually impossible to measure. A phono overload of 250 mV and a switch-selectable phono input sensitivity ensure compatibility with a wide variety of cartridges. The preamp section also provides tone and contour controls, tape deck monitor

Memories are made of this.

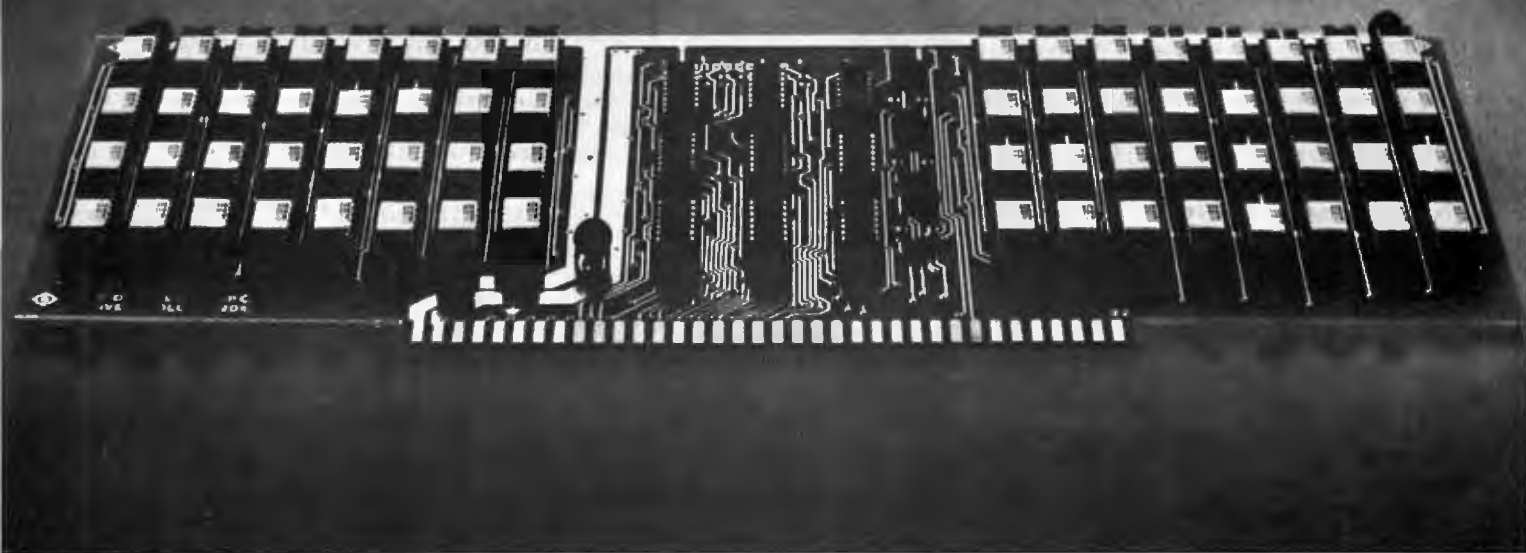

32K. One Card. One low price. Only from the Digital Group.

Now, on only one *fully static* card, the Digital Group has squeezed in a whopping 32K of memory. Which, with a little quick addition, means a full 64K architecture now requires only 2 boards instead of 8. That's a 4-to-1 space reduction ...and leaves one extra memory slot on the Digital Group's standard motherboard still available for future products.

All this and one low price, too.

It just may be the best news of all. Our full static, assembled and tested 32K memory board is only \$995. Now that's worth remembering. It's substantially less than our equivalent assembled 8K board prices. (Please note: We're initially offering this 32K board assembled only, but kit versions will soon be available, too—at even lower prices.)

Here's what you get.

Specifications:

- 32K on single card
- Speed—450ns. All of our current CPUs will operate at full-rated speed.
- Decoding—Lower or upper 32K bank
- Power—+5V only @ 4A
- Card size—12" x 5" (excluding connector fingers)

Features:

- May be intermixed on Digital Group systems with our 8K memory cards

- All data and address lines are buffered
- Fully static memories—EMM 4801 (450ns) or equivalent

Price:

32K board complete, assembled and tested \$995.00

For all the memorable details, just fill out the coupon below.
(Then all you have to remember is to mail it in.)

the digital group

P.O. Box 6528
Denver, Colorado 80206 (303) 777-7133

☐ I promise to mail this in, so add me to your mailing list!

Name _____

Address _____

City/State/Zip _____

☐ Remember me? I'm already on your mailing list, but I need the memory spec sheet desperately.



and copy facilities, and a high output head-phone amplifier. The FM tuner section features low-noise dual-gate MOSFETs, a six-element LC network, and a switch-selectable wide/narrow-band response. FM sensitivity is 8.75 dBf (1.5 μ V for 30 dB quieting), and a capture ratio of 1 dB. Incorporates a Dolby noise-reduction unit with 25- μ s deemphasis. \$600.00.

CIRCLE NO. 96 ON FREE INFORMATION CARD

IMSAI SINGLE-BOARD COMPUTER

IMSAI's new 8048 control computer is a completely programmable computer and hardware control system on one 8½" x 10" board. It is powered by a 5-V supply or 6-V battery and allows standard electric tools, instruments, and appliances to be attached and controlled directly without requiring any intervening hardware other than wire. The 8048 8-bit CPU contains 1k words of program memory, and the system has cassette interface,

RS232 current loop, and five relays. The control computer incorporates the Intel 8048/8748 microcomputer chip, which will accommodate three separate and unique memory stages: program memory, internal register memory, and external RAM. Input a program through the onboard keyboard, attach the device, and immediate control of the



devices is said to be obtained. Both kit and assembled versions are available: ROM version (\$249, kit; \$299, assembled), EROM version (\$399, kit; \$499, assembled). A 5-V power supply is \$99.

CIRCLE NO. 97 ON FREE INFORMATION CARD

CROWN ELECTRONIC CROSSOVER

The Crown Model VFX-2A is the successor to the Model VFX-2 electronic crossover. Internally, the VFX-2A uses six quad op amps in-



stead of the 10 dual op amps used in the earlier model to obtain better slew rates and handling of transients. Additionally, the new op amps are claimed to allow a greater range on the level control. One quad op amp operates as an isolation amplifier to eliminate impedance mismatching problems. Continuously variable filters, two per channel, can be used to perform either crossover or bandpass functions. Each filter in the dual-channel system is variable from 20 to 20,000 Hz with a fixed rolloff of 18 dB/octave. Output impedance is 300 ohms in both inverted and noninverted modes, with greater than 6 volts maximum into 600 ohms. IM distortion and noise are rated at 0.01% and more than 100 dB below the rated output with 0 dB of gain, respectively. \$329 for VFX-2A, \$49.95 for optional walnut-veneer cabinet.

CIRCLE NO. 98 ON FREE INFORMATION CARD

TRIPLETT PORTABLE DMM

A single switch provides five functions and 22 measurement ranges on the compact battery-powered Model 3000 digital multimeter from Triplett. The 3½-digit display features

Aircommand 40-channel CB.



From the people who bring you Marantz—the world's finest stereo systems—comes the Aircommand CB-640—the finest in 40-channel CB. With Aircommand you get over 25 years experience in outstanding 2-way communications products.

Full 6 Watts of audio power. Provides plenty of punch so your speaker cuts through freeway noise.

Dual-conversion super-heterodyne receiver with dual-cascaded ceramic filters. Together, both features provide the most complete rejection of unwanted signals, assuring you unsurpassed selectivity and sensitivity.

4 big Watts of RF power. Aircommand delivers the maximum power legally allowable to let you belt out the big sound. **100% modulation capability.** Even when you talk softly into the mike, your message cuts through loud and clear, thanks to one of the most advanced mike preamp and compressor designs in CB today. With Aircommand, you don't have to spend an extra \$30 to \$40 on a "power mike." You can't buy better modulation than Aircommand.

Specially tailored frequency response.

LED 40-channel selection display. Easy-to-read, night or day.

8-LED (light emitting diode) meter display. Provides an easy-to-read display of SWR (standing wave ratio), modulation, and incoming or outgoing signal strength—instantly, accurately.

Special emergency Channel 9 scan with exclusive Aircommand "beep" alert. No matter what channel you're on, a special Aircommand CB-640 circuit continuously and silently monitors Emergency Channel 9. When someone starts transmitting on Channel 9, a unique "beep" alerts you, so you can tune yourself in and give assistance.

Public address capability. The versatile Aircommand CB-640 public address package lets you (1.) Talk into the CB mike and out an exterior public address speaker. (2.) Attach a tape recorder to the auxiliary jack on the



seven-segment LED's with blinking over-range, auto-zeroing, and autopolarity indication. All decimal points light up when the battery is low. Ranges include: 0 to 0.2, 2, 20, 200, and 600 on both ac and dc volts; 0 to 2, 20, and 200 mA on ac and dc; 0 to 200, 20k, and 2M ohms on low-power ohms; and 0 to 2k, 200k, and 20M ohms on conventional ohms. Typical ratings include 0.9% dc accuracy, 10-megohm input resistance on all voltage ranges, and 600-volt overload protection on all ranges. The DMM is powered by four Ni-Cd cells, for which a battery-charger/eliminator is provided. Size is 5 3/8" x 3" x 1 3/8" (13.7 x 7.6 x 3.5 cm) and weight is 10 oz (310 g). \$140.

CIRCLE NO. 99 ON FREE INFORMATION CARD

INFINITY ELECTROSTATIC HEADPHONES

Infinity System's ES-1 headphone system consists of headphones with a claimed fre-

quency response of 20-25,000 Hz \pm 2 dB and an adapter containing a power supply and matching transformers. Other specs include: less than 0.3% THD at 100 dB SPL, 50 watts at 1 kHz maximum input, and 118 dB SPL maximum output. The low-mass conductive diaphragms are made of an extremely light material called "Polyurethin." The power supply is housed in a walnut enclosure, which is connected between the amplifier and speakers. Front-panel switching allows head-



phones to remain connected whether they or the speaker systems are being used. The headset weighs 9 ounces. The complete system is \$275.

CIRCLE NO. 100 ON FREE INFORMATION CARD

ONE-HAND SOLDERING

The Kager KL-3000 is Minitool's answer to the problem of one-hand soldering on electronic circuits. The gun has adjustable, auto-

matic feed of preset amounts of solder. It accepts various diameters and brands of solder wire, interchangeable elements and tips (20-30-40-60-watt elements available), and has optional accessories for practically any type of soldering work. The standard kit is \$49.50 with interchangeable heating elements \$13 each; soldering tips, \$7.30; solder reels \$2.25 and \$5.95 depending on size. Address: Minitool, 15076 Dickens Ave., San Jose, CA 95124.

ROYAL MOBILE AMPLIFIER

Royal Sound has a new mobile stereo high-fidelity power amplifier module, the RS-55, that's normally driven by speaker output leads of an FM/AM radio with cassette player. The module increases amplifier output for car audio equipment by providing a power output of 15 watts/channel. Self-contained, the RS-55 is ruggedly constructed to withstand shock and vibration. It also has sepa-



rate bass and treble controls, on/off switch, power indicator light, and quick-connect terminals, and can be mounted anywhere in a car or van. Operates on 12-volt dc negative-ground only. \$90.00

CIRCLE NO. 101 ON FREE INFORMATION CARD

...You never heard it so good!!!

CB-640 rear panel, and boom your tape out through the same external speaker. (3.) Mix your voice from the CB microphone with the program material on the tape recorder. Both voice and tape sound at the same time through the external speaker. (4.) Beam your received signal through the external speaker.

Built-in standing wave ratio circuitry. Measures the efficiency of the antenna system for optimum performance.

Other outstanding features include: Delta fine tuning control, digital synthesizer with phase-locked loop,

automatic noise limiting switch, noise blanking switch, squelch control, RF gain control.

Also available: Aircommand CB-140; Aircommand CB-340. All 3 units bring you state-of-art design, flawless craftsmanship and day-in, day-out reliability. Try them out now at your Superscope Aircommand dealer.

TM **Aircommand** by **SUPERSCOPE**



© 1977 Superscope, Inc., 20525 Nordhoff St., Chatsworth, CA 91311. Prices and models subject to change without notice.



New Literature

HEATHKIT CATALOG

The new 96-page Heathkit Catalog describes over 400 electronic kits. Product categories include amateur radio, hi-fi components, col-

or TV, test instruments, digital clocks, radio control equipment and auto accessories. Among the new products introduced are a 3-way bookshelf speaker system, a battery monitor device for radio control modelers, a two-way freezer alarm and a touch-control light switch. A section of fully assembled brand-name 40-channel CB radios has also been included. Address: Heath Co., Dept. 350-11, Benton Harbor, MI 49022.

EDMUND CATALOG

Edmund Scientific's 164-page Spring Catalog #772 contains over 4500 items for experimenters, students and hobbyists. Among the many items described are an AM/FM deluxe

wall radio; a storm alarm which is triggered by a signal from a local National Weather Service station; and a Sol-20 computer with Basic 5 language. Address: Edmund Scientific Co., 555 Edscorp Bldg., Barrington, NJ 08007.

WINEGARD CB ANTENNA CATALOG

Winegard Industries offers its first CB Antenna Catalog #770. The catalog illustrates the company's line of 40-channel CB mobile antennas and accessories, providing technical information and specifications. A listing of available antenna replacement parts is also included. Address: Winegard Industries, Inc., 3002A Winegard Dr., Burlington, IA 52601.

MOTOROLA HEP CATALOG

The new, 184-page edition of the HEP Semiconductor Cross Reference Guide and Catalog is offered by Motorola. Includes replacement HEP semiconductors for over 60,000 discrete devices and IC's, with 198 new products. Covers discrete silicon and germanium power transistors, thyristors, small-signal FET's and bipolar transistors, zeners, digital IC's, voltage regulator and op amps. The Educator II microcomputer power supply kits are also included. Address: HEP/MRO Operations Headquarters, Motorola Products, Inc., PO Box 20902, Phoenix, AZ 85036.

ADWAR VIDEO EDITING GUIDE

Adwar Video's 8-page guide offers advice on editing with half-inch tape and video cassette equipment. It begins with basic tips on avoiding quality losses and editorial confusion, and goes on to deal with scene edits; search and review; insert editing; and quality-enhancing modifications to VTR's. New video processing and portable field editing are also highlighted. Address: Adwar Video Corp., 100 5th Ave., New York, NY 10011.

SYNC TAPE RECORDERS & PLAYERS

A 4-page brochure from Audiotronics describes its line of SYNC Cassette tape recorders and players. The units, designed as aids for synchronized presentations of recorded audio tape to slide/filmstrip projectors, include Model 144S, which plays both superimposed and separate track synchronized cassette tapes. Another, Model 152-2, features an automatic stop program. The brochure illustrates each device and describes the different sync functions. A specification chart allows for easy comparison of models. Address: Audiotronics Corp., 7428 Bellaire Ave., N. Hollywood, CA 91605.

SPERRY MULTI-TESTER BROCHURE

Bulletin SP-73 (Issue B) from a.w. Sperry describes its line of V-Q-Ma-T multi-testers. The 7-page pocket-sized brochure provides detailed specifications, applications information, and a list of special features for each tester. Accessories are also described. Address: a.w. Sperry Instruments, Inc., 245 Marcus Blvd., Hauppauge, NY 11787.

ARE YOU READY TO RECEIVE THE WORLD? ALL NEW fully synthesized DR22 Receiver general coverage receiver from McKAY DYMEK \$995.



FEATURES

- Shortwave, CB, ham radio, ships at sea, overseas phone calls, etc.
- Hi Fi, SWL, commercial, industrial and government uses.
- High level RF front end for excellent intermodulation rejection and sensitivity.
- Crystal filters in first and second IF amplifiers, ceramic filter in third IF.
- Quartz crystal tuning accuracy at all frequencies, no crystals to buy.
- Built in power supply for 110-120 or 220-240 VAC switchable, 50-60 Hz.
- Solid state, phase locked, digital synthesis tuning.
- Extreme ease of tuning at all frequencies.
- No mechanical tuning dial error or backlash.
- Switch selectable 4 or 8 kHz RF bandwidth.
- Built in monitor speaker with external speaker connectors.

SPECIFICATIONS

■ Frequency coverage:	50 kHz to 29.7 MHz, continuous. Digital synthesis in 5 kHz steps, fine tune for ± 5 kHz.				
■ Reception modes:	AM, upper sideband, lower sideband, CW.				
■ Sensitivity for 10 dB S + N/N:		100 kHz	200 kHz	300 kHz-20MHz	20-29.7 MHz
	CW, SSB	10 μ V	2.0 μ V	0.5 μ V	1.0 μ V
	AM	30 μ V	6.0 μ V	1.0 μ V	2.0 μ V
■ RF Bandwidth:	-3dB @ 4 kHz or 8 kHz, and -60dB @ 10 kHz or 14 kHz				
■ Dimensions & Wt.:	(W x D x H) 17.5 x 14.5 x 5.1 inches. Shpg. Wt. 19 lbs.				

DR22 features and specifications unmatched under \$2900.



McKay Dymek Co.
675 N. Park Ave.
P.O. Box 2100
Pomona, CA 91766

Order factory direct, call
toll free today. Exclusive
rent/own plan available.



Nationwide
800/854-7769
California
800/472-1783

In Canada:
**Great Metropolitan
Sound Co. Ltd.**
120 Eglinton Avenue East
Toronto, Canada M4P 1E2
Tel. 416/484-0800

We've just made the impossible...

a professional 3½ digit DMM Kit for less than \$60.



The Sabtronics Model 2000 is an impossible \$59.95! And that price still includes phenomenal accuracy, range and professional features.

This all-new bench/portable multimeter, reading to ± 1999 , has a basic accuracy of $0.1\% \pm 1$ digit, and has five functions giving 28 ranges, 100% overrange and overload protection. So you know it's no toy!

Besides, what toys are as automatic as the 2000? With automatic overrange indication, automatic polarity, even automatic zeroing!

Yet the 2000 is easy to assemble. We send you all the parts you need, even the high-impact case. We also send you clear, step-by-step assembly instructions.

So you end up with a professional quality 3½ digit DMM for the unheard-of price of less than \$60. From Sabtronics, specialists in digital technology. And manufacturers of the impossible.

Order yours today!



Made in U.S.A.

sabtronics 
INTERNATIONAL INC.

P.O. Box 64683 Dallas, Texas 75206 (214) 369-7310

GUARANTEE:

Our guarantee to you; examine the 2000 DMM kit for 10 days. If you're not satisfied, return it unassembled for a full refund of purchase price.

SPECIFICATIONS: (condensed)

DC volts in 5 ranges: $100\mu\text{V}$ to 1000V
AC volts in 5 ranges: $100\mu\text{V}$ to 1000V
DC current in 6 ranges: 10nA to 2A
AC current in 6 ranges: 10nA to 2A
Resistance in 6 ranges: 1Ω to $20\text{M}\Omega$
Input Impedance: $10\text{M}\Omega$
Display: 9mm (.36") LED
Power requirements: 4.5 VDC to 6.5 VDC
(4 "C" cells - not included)
Size: 8"W x 6.5"D x 3.0"H.
(203W x 165D x 76H mm).

To: Sabtronics International, Inc.
P.O. Box 64683, Dallas, TX 75206

PE7

Please send me _____ Sabtronics Model 2000 DMM kit(s) at
\$59.95 each. _____ subtotal

Shipping and Handling, \$3.50 per unit* _____ subtotal

Texas Residents Add Sales Tax _____

TOTAL enclosed _____

Name _____

Street Address _____

City _____

State _____ Zip _____

*USA only. Canada, \$4.50. All Other Countries, \$9.00

Go after the best of everything.



Don't settle for less. Especially when it comes to electronics training... because everything else in your life may depend on it. That's why you ought to pick CIE!

You've probably seen advertisements from other electronics schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one...with the specialists...with CIE!

There's no such thing as bargain education.

If you talked with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

Because we're specialists, we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it...

Our step-by-step learning includes "hands-on" training.

At CIE, we believe theory is important. And our famous Auto-Programmed® Lessons teach you the principles in logical steps.

But professionals need more than theory. That's why some of our courses train you to use tools of the trade like a 5 MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a beauty of a 19-inch diagonal Zenith solid-state color TV you use to perform actual service operations.

Our specialists offer you personal attention.

Sometimes, you may even have a question about a specific lesson. Fine. Write it down and mail it in. Our experts will answer you promptly in writing. You may even get the specialized knowledge of all the CIE specialists. And the answer you get becomes a part of your permanent reference file. You may find this even better than having a classroom teacher.

Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up...no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.

Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back—the same day. You find out quickly how well you're doing!

CIE can prepare you for your FCC License.

For some electronics jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of your specific knowledge and skills!

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

For professionals only.

CIE training is not for the hobbyist. It's for people who are willing to roll up their sleeves and go to work...to build a career. The work can be hard, sure. But the benefits are worth it.

Send for more details and a FREE school catalog.

Mail the card today. If it's gone, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

☐ **YES...** I want the best of everything! Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information. PE-38

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G. I. Bill information: ☐ Veteran ☐ Active Duty

MAIL TODAY!



Stereo Scene

By Ralph Hodges

INSTRUMENTS I HAVE MIKED

I'LL BE honest and admit I haven't actually made recordings of all the instruments to be mentioned here. Sometimes I have assisted others while they recorded them, or fulfilled the function of interested observer and general nuisance at a session. And in many cases, my experience with any given instrument is hardly what you'd call exhaustive. I have only recorded a large orchestra once, for example. (I found it rather easy; beginner's luck, no doubt.)

Every once in a while I pick up a piece of data about a particular instrument or recording situation that seems directly pertinent to the logistical problem of placing microphones. Sometimes this datum immediately suggests a solution to a miking situation; other times, after further examination, it proves totally irrelevant. In either case, the information is good to have.

The few really useful *general* guidelines for placing microphones—the various ways to achieve a good stereo pickup, the maintaining of acoustic separation between mikes when you're multi-tracking, etc.—are ably covered in the several good books on studio technique now available. The indispensable rules of mike placement—pulling the mikes back to increase the contribution of room reverberation, avoiding the close-up use of cardioid mikes because of various frequency-response errors it can introduce, and so on—are surely well known to anyone who has taken the slightest interest in live recording. However, approaching a specific instrument, or assemblage of specific instruments, gives almost everyone pause, I think.

How do you begin? What's the first logical move? Having a definite approach, whether it is vital to the proper capturing of the sound or not, is confidence-building for all of us, and that's what I mean to focus on here.

Drums and Such. The bass drum, surprisingly, is evidently a highly directional instrument. I first learned this when I happened on an unguarded bass drum in a rehearsal room at the New England Conservatory of Music. Ecstatic, I hefted the heavy lead-loaded mallet, poised it well to the side of the drum head, swung from the hips and shoulders, and . . . nothing! After a while I realized that the drum heads, apparently moving in tandem, were giving rise to an almost perfect acoustic cancellation around the periphery of the drum, and I was therefore standing in a huge node. Not so an innocent passerby outside, who met the enormous pressure wave as it swept up the corridor.

From time to time I've encountered audible evidence of this cancellation node at considerable distances from the drum itself. So if you're ever puzzled as to why your mike is missing the near-infrasonic throb you expect from a bass drum, try turning the drum so that one head faces the mike directly. Conversely, if you're getting too much throb, turn the drum so that you get a more edge-on perspective.

Tympani (kettledrums) present no comparable problems, although they have a well-known tendency to shake the stage floor and any microphone stands on it, which may cause vibration pickup. Sometimes a failure to get the sound you want from a kettledrum is attributable to the way in which it's played. Striking the drum in the exact center of its head produces a rather ridiculous, overdamped "boomp." As the mallet progresses out toward the edge, the drum acquires that characteristic baleful, almost metallic timbre. A light roll at the very edge produces almost a rustle. Tympani are played either with sponge (or perhaps a spongy synthetic) or felt mallets; the sonic results from each are quite different. Felt mallets are exceedingly rare nowadays, however. Some recordists apparently fear that it's impossible to properly balance the tympani with the rest of the orchestra unless they are recorded with a separate mike(s) and mixed in later. It's not.

Professional recordists take elaborate pains with a drum set (kick drum, tom-tom, snare, and one or more cymbals), festooning it with microphones and stuffing towels in the kick drum. They all do it somewhat differently, so there are no general rules, except perhaps in the case of the cymbal. High-hat cymbals move considerably when they are played. If two differently placed microphones happen to be picking up the cymbal, and you intend to mix the outputs of these two mikes, you can wind up with a very weird Doppler effect that you may like, but which won't sound natural. (A two-mike pickup exaggerates the effect.) The best approach with a drum set is often a simple stereo pickup, balanced by ear.

The Strings. A celebrated concert violinist has said that a violin doesn't be-

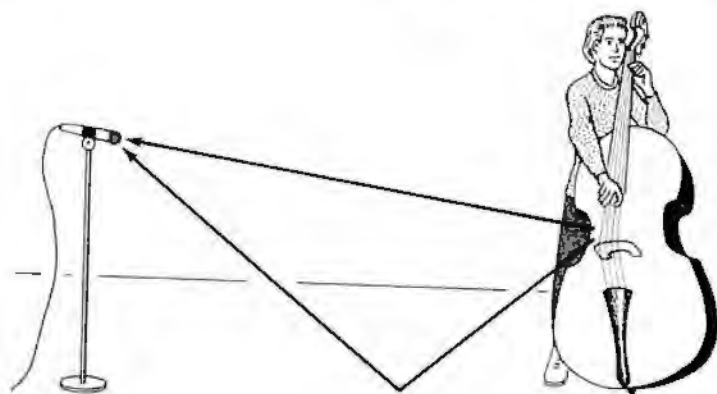


Fig. 1. Phase differences between direct and reflected signals present a problem when miking a string bass or cello.

Go with Realistic[®] no matter how you go!

Realistic CB is for people on the move. Whether you're driving an unfamiliar road, hiking away from camp, or working in the field, reliability is a prime concern with your walkie-talkie or mobile set. So come to Radio Shack — leading the way in quality CB since 1959.



walkin' and talkin'

Realistic's TRC-190 has exclusive range-boost: Grip the side-panels and your body adds extra signal power to the antenna system. Three watts input, with a high-low power switch to save on batteries during short-range use. Built-in automatic noise limiter, ceramic IF filter, IC audio circuitry — all for clean, low-interference sound. Adjustable squelch. Battery/RF meter. Built-in mike, speaker, plus a jack for optional push-to-talk mike. Power and antenna jacks so you can use the TRC-190 as a base or mobile station. Includes batteries, crystals for Channel 14, and you can add up to 5 more channels. Just \$84.50*.



ridin' and talkin'



The TRC-424 is our finest 40-channel set, and the built-in quality is obvious. Phase-locked loop circuitry for ultra-precise frequency control. Switchable noise blanker — the surest way to reduce pulse interference. Delta-tuning helps get off-channel signals. Adjustable RF gain and squelch. Channel selection is easier than ever with the large LED digital readout — one glance is all it takes. Add an external speaker and you've got a mobile public address system, too. with S/RF meter, dynamic plug-in mike, mounting bracket and power cables. First-class CB is even better when you can afford it! Get the new Realistic TRC-424. Just \$169.95*.



These two credit cards honored at most Radio Shacks.
*Prices may vary at individual stores and dealers.

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack[®]

A TANDY COMPANY • FORT WORTH, TEXAS 76107
OVER 5000 LOCATIONS IN NINE COUNTRIES

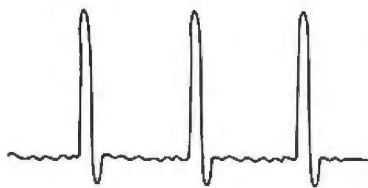


Fig. 2. Trumpet waveform miked on axis in anechoic chamber. From a Denon record made with pulse-code-modulation process.

gin to sound good until you're at least ten feet distant, so that the "garbage" has had a chance to fall away. Good miking advice too rarely taken. At their loudest, massed violins are never very loud compared with the real heavyweights in a symphony orchestra. In their upper registers, however, they have a penetrating tone that will often rise above the most astounding ruckus. If one balances too much in favor of the violins (a fault of many commercial recordings), the aforementioned penetrating tone will give the feeling of going right in to your eardrums.

For a natural-sounding recording, restraint in the handling of violins is admirable. They should not always be audi-

bly strong, and they should have a certain fragility, even thinness, of tone. Where possible, give them a chance to balance naturally with the rest of the orchestra. And don't ride gain on them to any excess.

The string bass, when miked from any distance, encounters problems from reflecting surfaces. Figure 1 shows how the first reflection from the floor bounces up to the microphone, causing a complex pattern of reinforcements and cancellations, all wavelength-dependent. A solid wall behind the instrument will produce much the same thing. When you're miking several basses, as in an orchestra, the most productive approach is usually to ignore these complications and press on regardless, hoping the randomness factor will solve your problems for you. For a single bass, as in a jazz combo, it's a frequent practice to mike the instrument quite closely, which will tend to get rid of the room and, hence, the reflections. Electric basses are almost invariably miked closely (at the amplifier's speaker), or even fed directly into the recorder, bypassing the amp.

Woodwinds. It may be obvious, but the proper place to mike a woodwind is not at the bell of the instrument where you'd expect most of the sound to emerge. In general, the right place for the mike is directly in front of the musician, as if he were going to speak into it. Usually he will play so that the bell is pointing toward the floor (or, in the case of the bassoon, toward the ceiling). This is fine. Move the mike(s) closer or farther away as appropriate, but don't try to get too close.

The Brass. The trouble with the brass is eloquently demonstrated by Figure 2, a drawing of an oscilloscope trace made by a trumpet in full cry. The vicious spikiness of this waveform will never be revealed by any VU meter, and yet it has to be taken into account because any significant tampering with this crest will be audible. In jazz clubs you'll often see a trumpet played directly into a microphone. Apparently, the sound-reinforcement system can usually take this onslaught in stride. But it's murder on tape. I tried to record this trumpet waveform with a good cassette machine. Finally, I had to drop the recording level down to the point where the meters (peak reading) were barely stirring, and still the waveform peaks were appreciably abbreviated.

Your defense against the brass, which can easily overload microphone pream-

plifiers and the built-in preamps of condenser mikes as well as tape, is to get away and off-axis. Discourage brass players from pointing their instruments directly at the microphone or put the mike where they can't conveniently aim at it. Even then, a French horn, which projects rearward in line with the player's elbow, and which often has his fist stuck up into its bell, can cause trouble. Distance is your only recourse then, and here it usually sounds good.

Piano. Don't we wish we could make consistently good piano recordings. The trouble is, the instrument is too big to close-mike with one microphone, and when we try to mix the output of several microphones there is inevitable trouble with interference. Other complications intrude as well.

Presently, for grand piano, I favor the stereo pickup shown in Figure 3. Note that the two mikes (cardioids or omnidirectionals, or a coincident pair embracing a moderate angle) are aimed down into the piano's case approximately in line with the instrument's lid. This theoretically avoids reflections from the lid



Fig. 3. This mike positioning for piano avoids pickup of direct reflections from bottom of lid.

(which I believe to be detrimental to clarity) from reaching the mikes directly. The mikes are brought forward or pulled back as necessary to provide that right touch of room reverberation.

There are many other ways of recording a piano that I'm itching to try as soon as I get the chance. Some of these are described in a Shure Brothers' publication, "The Music-Maker's Manual of Microphone Mastery." Although intended for sound reinforcement at live performances, you can extrapolate its advice into a recording situation with relative ease. It's free. (Shure Brothers, 222 Hartrey Ave., Evanston, IL 60204.)

The Sound Field. All of us are intrigued by the examples of recording

COMING UP IN
THE AUGUST

Popular Electronics®

BUILD THE "CABONGA"
ELECTRONIC DRUMS
SYNTHESIZER

MEASURE CAMERA SHUTTER
SPEED DIGITALLY

HOW TO PROTECT
MOS DEVICES
DURING INSTALLATION AND
SOLDERING

BUILD THE TVT-6: A LOW-COST
DIRECT VIDEO
DISPLAY—PART 2

TEST REPORTS
Heath AR-1515 Digital-Readout
Stereo FM/AM Receiver
Thorens TD-126C Turntable
President "Washington"
40-Channel CB Base Station

professionals and hope to emulate their results in time. Here's a piece of advice offered by several recording professionals I have talked to: Forget it! A professional recording session costs multi-dollars with every tick of the clock. There is scarcely time for aesthetic considerations or lengthy consideration of microphone repositioning. Ideally, a professional recordist would like to capture every instrument in complete isolation and later mix all the instruments together (along with appropriate reverberation) at his leisure. Hence he turns to the multi-miking approach, which by-and-large sacrifices all the good things—depth, spaciousness, authentic perspective—of a simple stereo pickup. If you don't believe me, read John Woram's book, *The Recording Studio Handbook* (Saga-more Publishing Co., 1120 Old Country Road, Plainview, N.Y.) for some frank discussion of the subject.

If you're an amateur recordist, and time is not pressing, you have the luxury of being able to attempt a miking of the "sound field"—the whole musical event, balanced naturally, and presented to the ultimate listener with startling realism and an impressive stereo panorama. It will not sound like a professional mix on one of the big labels, but if you're famil-

iar with the sound of live music you'll appreciate that it sounds, in many respects, better. Above all, have a good time, and fulfill yourself while inching toward capturing the full realism of the music. Even if the final goal cannot be wholly reached, you'd be surprised at how forgiving the human ear is.

More on Decontaminating Discs.

Dr. Bruce Maier, president of Discwasher, has favored us with some comments on the recent "Decontamination Squad" column (May 1977) that I'd like to share.

He observes that "It has been our experience that once you begin wet-playing a record you can never, never play the record dry again. After two wet plays, playing the record dry will blow you out of the room with surface noise."

"The reason is fairly complex," says Dr. Maier, offering some research conclusions concerning wet playing of discs:

(1) Wet playing causes an intense disequilibrium in temperatures between the vinyl at the stylus pressure point and the liquid layer on the disc surface. This temperature differential causes (by actual electron microscopy investigation) disorientation or cracking or injury to the surface molecular structure, just as you

might fracture a glass cup if you heated it when it contained cold water.

(2) Wet playing allows an interface layer of liquid to extract tiny amounts of surface stabilizer into a slurry. When this slurry is allowed to dry back onto the surface, there is a concomitant lack of stabilizers in the right place plus little globules in the wrong places.

(3) Wet playing literally shorts out some cartridges by wicking up the cantilever and causing the generator assemblies of some cartridges to corrode very quickly.

Dr. Maier disagrees with my suggestion that record-cleaning substances and lubricants can be evaluated by treating just 180 degrees of a record side and then listening for any difference between the two halves. He points out (quite rightly, I suspect) that the transition points between the halves will always be audible. Had my description been more complete, it would have been clear that the evaluator should listen for any differences between the two halves other than the noise occurring at the actual transition points, of which there should be two per revolution. As I suggested, the slower the playing speed, the easier it will be to distinguish the transition points from the rest of the disc surface. ◇

Treat yourself to a new direct reading DVM today.



DVM35

POCKET PORTABLE
ANALOG REPLACEMENT
3-digit, 1% DCV
Battery or AC
Only \$134



DVM36

LAB ACCURATE
POCKET PORTABLE
3½ digit, .5% DCV
Battery or AC
Only \$158



DVM32

BENCH & FIELD MASTER
3½ digit, .5% DCV
Battery or AC
Only \$198



DVM38

"PRIME" STANDARD AT
YOUR FINGERTIPS
3½ digit, .1% DCV
Auto-Ranging
Only \$348

A COMPLETE LINE OF DVMs TO FILL YOUR EVERY NEED OR WANT.

You can be sure more times in more circuits, under more adverse conditions, with greater versatility, accuracy, and meter protection than any other digital multimeters on the market today; and for less money, too. 10 Day Free Trial: Try any of these famous DVMs for 10 days. If the DVMs in use don't prove exactly what we say, return them to your Sencore FLPD Distributor.

SENCORE

JULY 1977

Want more information? We would like to tell you all about the Sencore DVMs by sending you a 24-page Sencore News, a six-page brochure, and the name of your nearest Sencore Distributor today... simply write or circle reader's service number.

3200 Sencore Drive, Sioux Falls, SD 57107



CIRCLE NO 46 ON FREE INFORMATION CARD











RC CIRCUIT QUIZ

BY ROBERT P. BALIN

Resistance-capacitance circuits are not always as simple as they might seem. For example, in dc circuits, the charging time of the capacitor, as controlled by the resistance, is used to determine oscillator frequency.

In ac circuits, the RC combination is used as a frequency-sensitive voltage divider or filter. And, in circuits involving both dc and ac components, it is used to block the dc component. Other examples could be given.

However, whenever the RC circuit has a different application, it seems to acquire a different name for its function. To test your knowledge of RC circuits, see if you can match the circuits (A to J) with the functions (1 to 10).
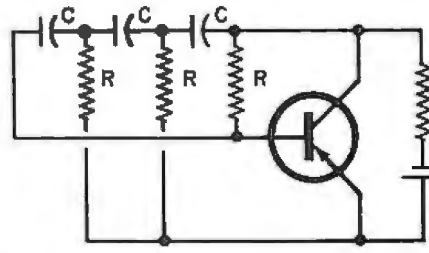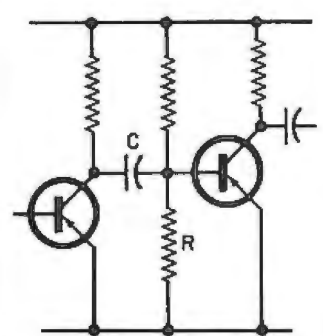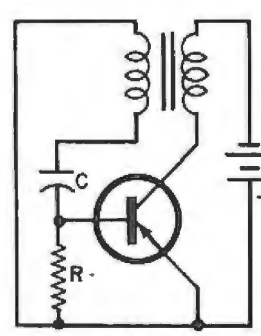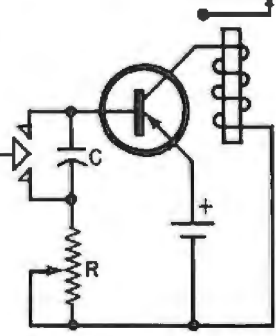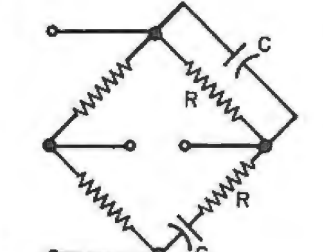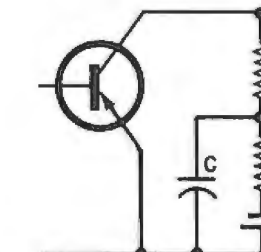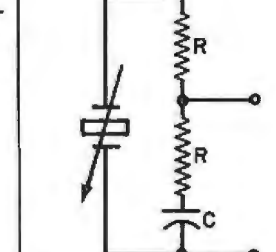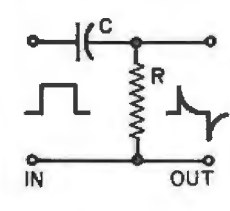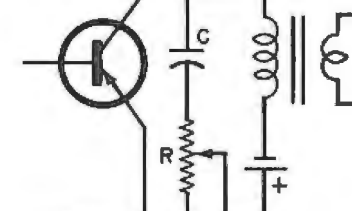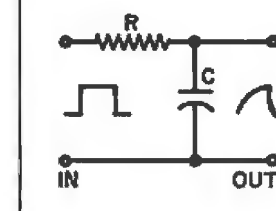
<ol style="list-style-type: none"> 1. Band Suppression Circuit 2. Coupling Circuit 3. Decoupling Circuit 4. Differentiator 5. Equalizer 6. Frequency Control 7. Integrator 8. Phase Shifting Circuit 9. Timing Control 10. Tone Control 	 <p>A.</p>	
 <p>B.</p>	 <p>C.</p>	 <p>D.</p>
 <p>E.</p>	 <p>F.</p>	 <p>G.</p>
 <p>H.</p>	 <p>I.</p>	 <p>J.</p>

ANSWERS: 1-E, 2-B, 3-F, 4-J, 5-G, 6-C, 7-H, 8-A, 9-D, 10-I

/ability.

It Comes Naturally With The Altair™ 8800b

The Altair 8800b from MITS: the second generation design of the microcomputer that started it all. The mainframe that has the abilities everyone is demanding from microcomputers today:

Expand-ability:

The Altair 8800b power supply and one-piece, 18-slot motherboard allow efficient and easy expandability for memory and I/O options. All Altair PC boards are designed to give you maximum capability/lowest power usage possible per board. This means that for each slot used you get more features and require less power, than with any of the "off-brand" Altair-bus-compatible boards.

Whether you buy an entire system up front or choose to expand gradually, it's easy to get the configuration you need with the complete family of Altair peripheral equipment, including floppy disk, line printer, audio cassette record interface, A/D converter, PROM programmer, serial and parallel I/O boards.

choice of four different memory boards and many others.

Reli-ability:

The unique design features of the Altair 8800b, which have set the standard for the microcomputer industry, make it the most reliable unit of its kind. The Altair 100-pin bus, the now-standard design used by many imitators, has been "standard" all along at MITS. The unique Front Panel Interface Board on the Altair 8800b isolates and filters front panel noise before it can be transmitted to the bus. The all-new CPU board utilizes the 8080A microprocessor, Intel 8224 clock generator and 8216 bus drivers.

Flex-ability:

Meeting the diversified demands of an ever-increasing microprocessor market requires flexibility: not just hardware flexibility but

software flexibility as well. MITS software, including the innovative Altair BASIC language, allows the full potential of the Altair 8800b computer to be realized.

8K ALTAIR BASIC has facilities for variable length strings with LEFT\$, RIGHT\$, and MID\$ functions, a concatenation operator, and VAL AND STR\$ functions to convert between strings and numbers.

Extended ALTAIR BASIC allows integer, single and double precision variables, automatic line numbering and renumbering, user-defined string functions, PRINT USING for formatted output and a powerful EDIT command for editing program files during or after entry. Extended statements and commands include IF... THEN... ELSE, LIST and DELETE program lines, SWAP variables and Trace On and Off for debugging.

Disk ALTAIR BASIC has all the features of Extended BASIC with the additional capability to maintain sequential and random access disk files. Utilities are provided for formatting disks and printing directories.

In all versions of ALTAIR BASIC you get the ease and efficiency of BASIC for the solution of real world problems.


Package II, an assembly language development system for the Altair 8800b, includes system monitor, text editor, assembler and debug.

Afford-ability:

Prices for the Altair 8800b start at \$840.00 for a kit and \$1100.00 for an assembled unit (all documentation included).

For a complete listing of prices on all Altair products and a free brochure, contact:

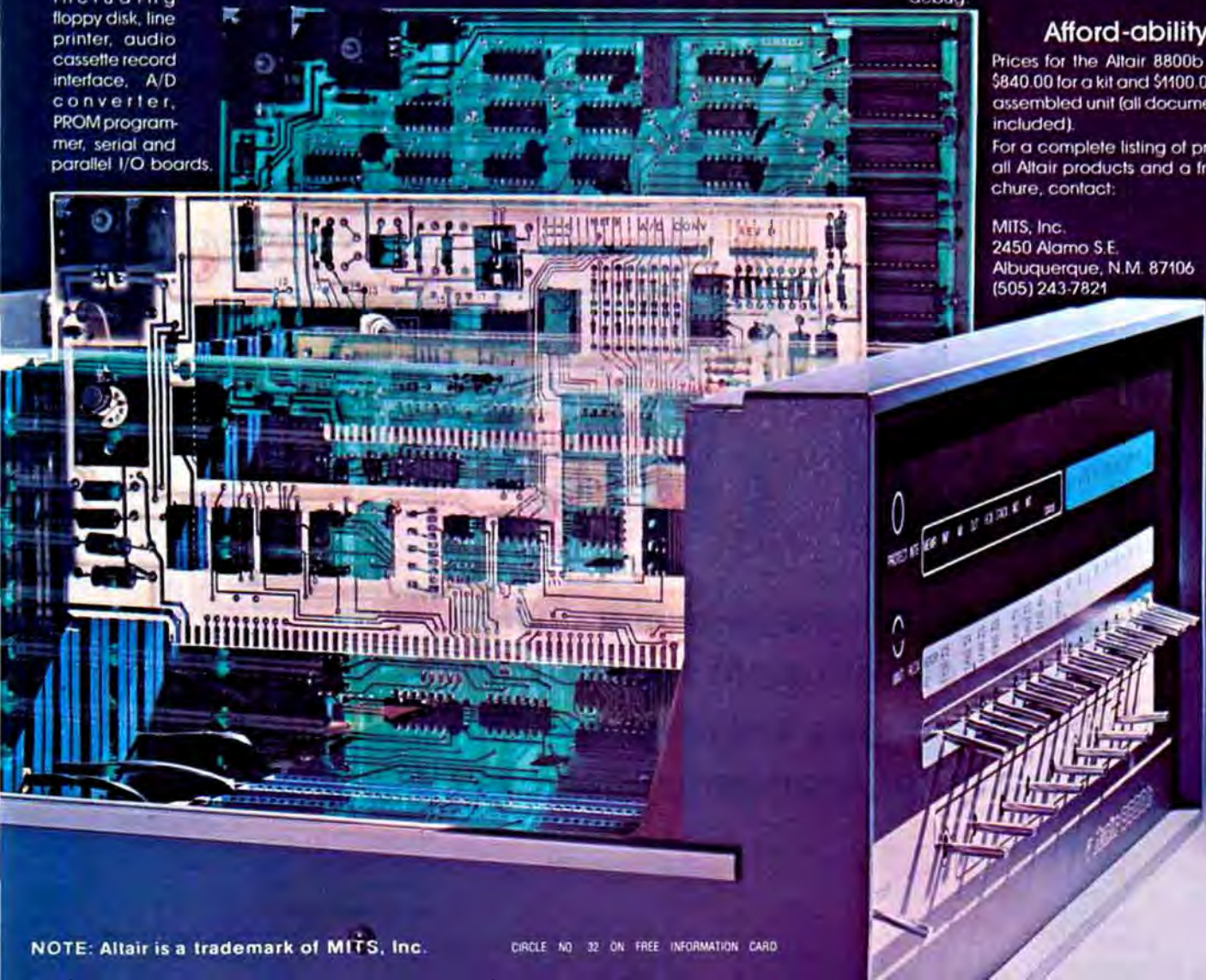MITS, Inc.
2450 Alamo S.E.
Albuquerque, N.M. 87106
(505) 243-7821



If you can't go to college for your career in electronics —read this!

**CREI brings college-level training
to you with eight educational
advantages, including special
arrangements for engineering degrees**

The best way to qualify for top positions and top pay in electronics is obviously with college-level training. The person with such training usually steps more quickly into an engineering level position and is paid considerably more than the average technician who has been on the job several years.

A regular college engineering program, however, means several years of full-time resident training—and it often means waiting several years before you can even start your career. This, of course, is difficult if you must work full time to support yourself and your family.

If your career in electronics is limited without college-level training, take a look at the advantages a CREI home study program can offer you.

1. Convenient Training

CREI brings the college to you. Through the convenience of home study, you receive exactly the same level of training you will find in any college or university offering programs in electronic engineering technology. With CREI, however, you can “go to college” whenever you have spare time at home or on the job.

2. Specialized Programs

With CREI, you enjoy the advantage of *specialized* training. That is, your program will include only those courses directly applicable to your career in electronics. We omit such courses as English, social studies and other subjects, which are usually required in resident schools. Therefore, with CREI, you move ahead faster to the more interesting and useful part of your training.

3. Practical Engineering

CREI programs give you a *practical engineering* knowledge of electronics. That is, each part of your training is planned for your “use on the job.” By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.

4. Engineering Degrees

CREI offers you a number of special arrangements for earning engineering degrees at recognized colleges and universities. You can earn college credit while you are taking your CREI program or apply later, whatever is best for your career plans.

Career Training at Home

5. Unique Laboratory

Only CREI offers you the unique Electronic Design Laboratory Program. This complete college laboratory makes learning advanced electronics easier and it gives you extensive practical experience in many areas of engineering, including design of electronic circuits. No other school offers this unique program. It is a better "Lab" than we have found in many colleges. And the professional equipment included in the program becomes yours to keep and use throughout your professional career.

6. Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

7. Prepared by Experts

Experts in industry and technical organizations of government develop CREI programs. Each part of your training is developed by a recognized expert in that area of electronics. That means you get the most up-to-date and practical instruction for your career.

8. Industry Recognition

That CREI training is recognized by industry and government is evident from the fact CREI provides training to advanced technical personnel in over 1,700 technical organizations. Many subsidize the training of their employees with CREI. If there is any question about the advantages of CREI training for you, ask your employer or any engineer to evaluate the outline of a CREI program for you.

Other Advantages

Of course, there are many other advantages to CREI training. For example, throughout your training, CREI's staff gives you personal instruction for each step of your program. And in many industrial areas, both in the U. S. and abroad, CREI Field Service Representatives provide a number of important personal services for your training and your career.

FREE Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog (if you are qualified). This fully illustrated, 80 page catalog describes in detail the programs, equipment and services of CREI.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

**Send for this FREE Book
describing your opportunities
and CREI college-level
programs in electronics**



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

*CREI programs
are approved
for training of
veterans and
servicemen under
the G.I. Bill.*



Audio Reports

NOISE FILTERING FOR HI-FI

From high fidelity's earliest days, audiophiles have faced the problem of dealing with the various effects that we lump together under the heading of "noise." Noise is defined in the current ANSI standard as "unwanted disturbances super-imposed upon a useful signal that tend to obscure its information content." In the case of sound reproduction systems, this is modified to exclude harmonic, subharmonic, and intermodulation distortion products, and flutter and wow.

For most hi-fi listeners, noise falls into two broad categories: high-frequency hiss or scratch and low-frequency noises, such as rumble or hum. All are essentially steady-state effects, though they are usually random in nature. Another category includes impulse noise, composed of discrete pulses that occur at regular or irregular intervals, such as automobile-ignition interference and record ticks or pops.

To some degree, all of these forms of noise are present at all times in reproduced music, and eliminating or reducing their objectionable qualities has been the goal of many talented engineers for decades. No panacea has yet been discovered for noise, but by attacking the problem on several fronts, it has been possible to greatly reduce its audible effects.

The basic problem is that the noise energy and the music program occupy the same frequency spectrum, often simultaneously. Noise may extend well beyond the program bandwidth or, as in the case of power line hum, may occupy a small discrete portion of the spectrum. The more successful noise-reduction systems operate by virtue of achieving a greater reduction of noise than of program content, though some sacrifice of the latter is unavoidable.

The simplest, oldest, and least-effective anti-noise technique is to use fixed low-pass or high-pass filters to attenuate noise energy outside the main spectrum of the program bandwidth. If bandwidth is limited (as in the case of 78-rpm records or AM radio) it is possible to cut off most of the hiss with little loss of program quality. The shellac-based 78-rpm phonograph records were noted for their high "scratch" level, and a fixed filter cutting off above 3000 or 4000 Hz could be very helpful. Since turntable rumble was concentrated at frequencies below 100 Hz, a filter cutting off at that frequency could clean up the bass reproduction without too much loss of content.

The wider bandwidth of LP records was fortunately (and not accidentally) combined with low-noise vinyl record materials so that the full frequency range could frequently be enjoyed without too much disturbance from noise. Nevertheless, even as records and playback systems were improved, one's enjoyment of a wide-range recording was increasingly likely to be marred by extraneous noises. The fixed filter, being by far the cheapest "cure," continued to be offered as a solution to this problem, although it usually solved nothing at all.

Unlike the situation with 78's, the recorded material on an LP disc usually had useful energy up to 10,000 Hz or higher. Cutting off the noise above 10,000 Hz was of no help, since the change could not be heard by most people. Cutting off an octave lower, at 5000 Hz, might produce a noticeable lowering of the hiss level, but would certainly dull the program to an undesirable degree. The low-frequency noise problem was much less severe. For one, most of it was under the listener's control, in the sense that using a better turntable would eliminate much of the rumble at its source. Since most speaker systems have considerably reduced output at very low frequencies, only the unfortunate combination of a poor turntable, good speaker system, and high listening level was likely to result in a disturbingly high rumble level.

We have been referring to filter action as "cutting off" at a certain frequency. If filters worked that way, they would be much more effective. Unfortunately, a real filter, the simple type used in home entertainment electronic products, attenuates the response gradually, on both sides of its cutoff frequency. Most filters used in hi-fi amplifiers or receivers have a cutoff slope of 6 dB/octave (which requires only a single resistor and capacitor, hence its popularity). The effect of the filter begins more than an octave below the cutoff frequency, at which point its response is down 3 dB. By the time the frequency has gone an octave or more above the cutoff point, the rate of attenuation approaches its ultimate value of 6 dB with each octave increase (doubling of frequency).

In fact, the typical filter response curve is virtually identical to the treble tone control response with the control set to minimum. The filter switch is thus a convenient substitute for the tone control—but it is

no more effective as a noise-reducing device! A similar situation exists at the low frequencies, with many rumble filters beginning to cut the frequency response as high as 150 or 200 Hz. Fortunately it is possible, by selecting a cutoff frequency between 50 and 100 Hz, to make a worthwhile reduction in rumble without undue loss of program content because most recorded music has little energy below 100 Hz.

For better results, filters can be made with a sharper cutoff action so that a greater proportion of noise can be removed without harmful effects on the program. It is not too expensive to build filters with a 12 dB/octave slope, and in some active filter configurations the cutoff "knee" can be made much sharper so that program material will be less affected. Some of the better amplifiers and receivers do have such filters, and if their cutoff frequencies are well chosen (and preferably selectable) they can be useful.

Nevertheless, no fixed filter, no matter how steep its attenuation slope or where its cutoff action begins, can do a really effective job of noise reduction without impairing program quality. A number of ingenious dynamic filters have been developed in which the attenuation and the frequency at which the filter becomes effective are controlled by the program itself. The psychoacoustic phenomenon of masking is used in the design of these filters. High-frequency hiss is audible only in the absence of high-frequency program content; when the music is loud or contains appreciable high-frequency energy, the hiss is masked and cannot be heard. Similarly at the low

end, rumble cannot be heard when the program is loud or contains strong low-frequency material.


It would seem logical to use a high-cut (low-pass) filter whose operating frequency and/or slope are controlled by the program so that its filtering action occurs only under conditions that allow the hiss to be heard. This logic is correct, but there is the problem of selecting the dynamic characteristics, including the basis for filter operation, its actual response characteristics, and the rate of attack and decay of the filtering. Failure to do this correctly will result in audible swishes and other clues that the filter is working; a noise reduction device whose action can be heard is not of much value.

There are a handful of add-on noise-reduction systems that truly do a fair-to-good job of minimizing noise without any noticeable effect on program material. A new NR accessory, announced by SAE recently, even claims to remove ticks and pops from record reproduction. But these are *accessories*.

As strongly implied, the fixed filters built into most receivers and amplifiers, especially those having 6-dB/octave slopes, are virtually worthless as noise-reduction devices. In spite of this, many receivers and amplifiers above the lowest price ranges include some sort of "filter," presumably because their designers feel that it is expected of them. Perhaps a counter-trend is under way, since we noted with interest that Radio Shack's deluxe Realistic Model STA-2000 receiver, reviewed in this issue, eschews *all* filters. We did not miss them for a moment. ◇

REALISTIC MODEL STA-2000 STEREO RECEIVER

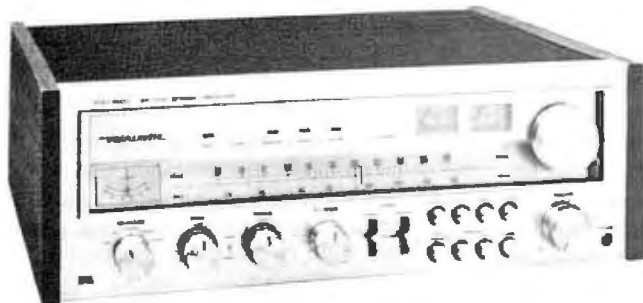Company's top-of-the-line, 75-W/channel receiver boasts notable features and smooth performance.



Radio Shack's Model STA-2000 heads the "Realistic" brand's list as its top AM/stereo FM receiver. Its amplifiers are rated to deliver 75 watts/channel into 8-ohm loads at less than 0.25% total harmonic distortion (THD) from 20 to 20,000 Hz. The front panel is satin-finished aluminum with matching control

knobs and switch buttons. A large clear glass window, behind which the dial scales are angled back for better visibility, dominates the upper two-thirds of the panel. All controls, except the large tuning knob, are located on the lower third of the panel. The single tuning meter indicates center-of-channel for FM and relative signal strength for AM.


The receiver measures 19"W × 16½"D × 6¾"H (48.3 × 41.9 × 17.5 cm)

and weighs 40 lb (18.2 kg). Supplied with genuine walnut-finished end plates, the receiver is catalog priced at \$499.95.

General Description. A row of colored indicator lights above the dial scales illuminate to identify the selected input (AM, FM, PHONO, AUX1, AUX2) and when a stereo FM station is being received. Two small meters above the dial scales monitor the output power of the audio channels. The meters are calibrated at decade intervals from 0.1 to 100 watts, based on 8-ohm loads.

In addition to the input SELECTOR switch, there are BASS and TREBLE tone controls with 21 detented positions, including a FLAT setting at the center, and a BALANCE control with a center detent. The volume control operates in steps with 41 detented positions. Tone controls are concentric, permitting individual channels to be adjusted.

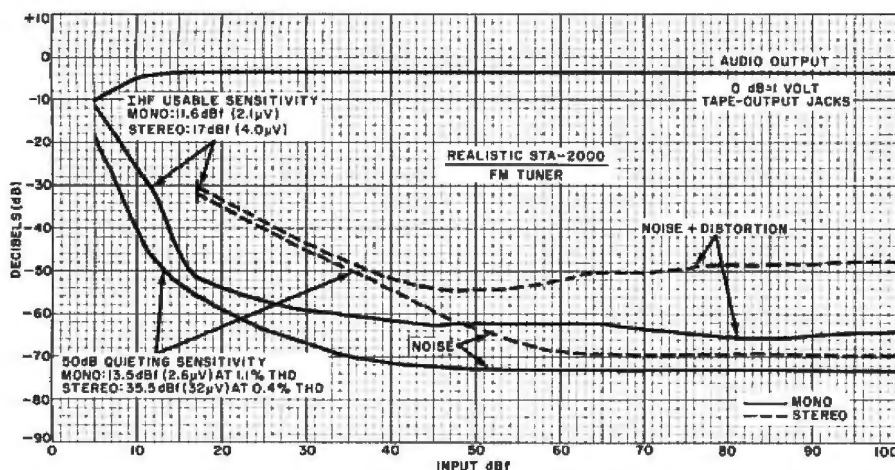Eight pushbutton switches are arranged in a two-row matrix. The upper



Noise and sensitivity curves for FM section of Realistic receiver.

row is for switching in and out an FM MPX FILTER (reduces noise in stereo reception by partially blending the channels at higher audio frequencies), FM MUTE circuit, MONO/STEREO mode, and LOUDNESS compensation. The lower row of switches contains switching for a 20-dB audio ATTENUATOR (for temporary interruption), A and B SPEAKERS selection, and POWER. Two lever switches are provided for controlling the tape recording functions for two tape decks. The DUBBING switch crossconnects the decks for copying a tape from either deck to the other or connects both decks for recording from the program source to which the SELECTOR switch is set. The MONITOR switch connects the playback from either deck or the selected source to the receiver's audio amplifiers.

On the rear apron of the receiver are insulated binding posts for the two pairs of speaker systems that can be accommodated. (The connectors are exceptionally easy to use and do not require the wire to be wrapped around the posts.) Their functions are duplicated by two pairs of phono jacks for speaker system cables equipped with phono plugs. The various signal input and output connectors are phono jacks, and the two sets of tape recorder connectors are duplicated in DIN sockets. Two sets of auxiliary outputs are also included. Preamp outputs and power amplifier inputs are brought out to separate phono jacks that are joined together by removable jumper links. There are antenna terminals for 75- and 300-ohm FM antennas as well as a wire-type AM antenna. There is also a fully hinged and pivoted AM ferrite rod antenna. The line cord has a capacitive coupling clip that can be connected to one of the 300-ohm FM antenna inputs so that the power line can be used as an antenna in strong sig-

nal areas. One of the two accessory ac outlets on the rear apron is switched.

Laboratory Measurements. During the one-hour preconditioning of the amplifier at one-third rated power, the metal cover above the output transistors became quite warm, but the receiver as a whole remained cool. The outputs of the amplifiers, when driving 8-ohm loads at 1000 Hz, clipped at 90 watts/channel. Into 4- and 16-ohm loads, the output was 106 and 55 watts, respectively.

The 1000-Hz THD was less than 0.01% from 0.1 to 20 watts. It increased very slowly to 0.05% at 80 watts. The IM distortion was between 0.03% and 0.1% from 0.1 to 80 watts. At outputs of a few milliwatts, the IM distortion increased to several tenths of a percent.

At the rated 75-watt output, the distortion was between 0.02% and 0.05% over most of the audible-frequency range and never exceeded 0.09%. It was much the same at lower output powers, measuring about 0.01% at middle frequencies and from 0.1% to 0.14% at 20,000 Hz. Through the AUX input, the amplifier's sensitivity was 50 mV for a reference 10-watt output with a 74-dB S/N ratio. The phono sensitivity was 0.83 mV with a 66-dB S/N ratio. The


phono input at 1000 Hz didn't overload until a very high 220 mV was reached.

The bass tone control had a variable turnover frequency. It provided a moderate boost or cut below 100 Hz at partial settings, with negligible effect at higher frequencies. The turnover frequency increased to about 500 Hz at the control's extremes. The treble control characteristics were hinged at about 3000 Hz. RIAA phono equalization was flat within ± 0.5 dB from 60 to 20,000 Hz, dropping slightly at lower frequencies to -2 dB at 30 Hz. Because the phono preamplifier stage effectively isolates the cartridge from the feedback components, the phono response was completely unaffected by the cartridge inductance.


The loudness compensation boosted only the low frequencies as the volume control setting was reduced. The boost at normal listening levels was slight, avoiding the unnaturally heavy sound that is typical of most loudness-compensation systems. The power meters provided only a rough approximation of the actual output, with typical errors being 50% to 100%. They had a fairly slow response time and were well damped, following average program levels to our satisfaction.

The FM tuner section had an IHF sensitivity of 11.6 dBf (2.1 μ V) in mono and 17 dBf (4.0 μ V) in stereo. The steep limiting curve yielded 50 dB of noise quieting at only 13.5 dBf (2.6 μ V) in mono, with 1.1% THD, and 35.5 dBf (32 μ V) in stereo, with 0.4% THD. The 1000-Hz distortion was about 0.08% in mono and 0.32% in stereo at a 65-dBf (1000 μ V) input. The stereo THD, with L - R channel modulation, was 0.75% at 100 Hz, 0.1% at 1000 Hz, and 0.2% at 6000 Hz. The S/N was 72.5 dB in mono and 69 dB in stereo.

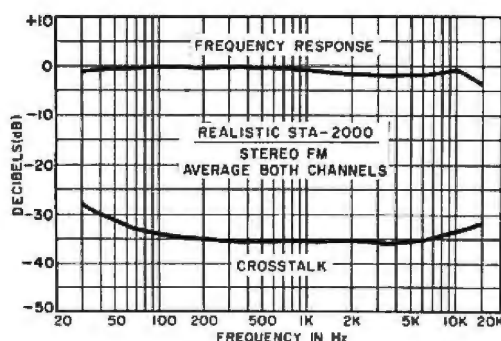
The FM frequency response had a slight dip in the midrange and high-frequency response, plus the usual drop at 15,000 Hz due to the multiplex pilot carrier filter. Overall, the response was still within ± 1 dB from 30 to 12,500 Hz,



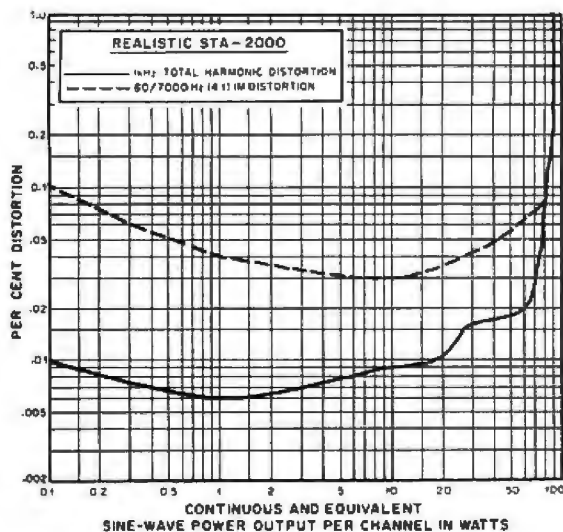Frequency response and crosstalk averaged for both channels in stereo FM.



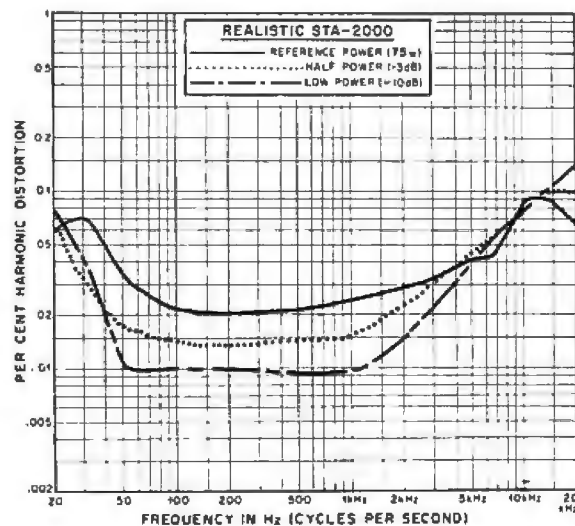Total harmonic distortion and 60/7000-Hz distortion.



Harmonic distortion at three power levels.

down about 3.7 dB from midrange levels at 15,000 Hz. The stereo channel separation was very uniform, about 35 dB over most of the audio range. It was a very good 27.5 dB at 30 Hz and 31.5 dB at 15,000 Hz.

FM capture ratio was 1.75 dB at 65 dBf and 1.9 dB at 45 dBf (100 μ V) inputs. The AM rejection was an exceptional 83 dB. Image rejection also measured 83 dB. The alternate-channel se-

lectivity was 76 dB, and adjacent-channel selectivity was 4.6 dB. Muting and automatic stereo switching thresholds were identical at 17.2 dBf (4 μ V). The 19-kHz pilot carrier leakage into the audio outputs was -70 dB, and tuner hum was a very low -75 dB. The AM tuner section appeared to be relatively sensitive, with a notable freedom from buzzing noises, and a wider-than-usual frequency response that was down 6 dB at

4500 Hz and 3.5 dB at 20 Hz, from the midrange levels.

User Comment. There are some interesting in-use observations to be made concerning this receiver that don't show up by examining specifications. For example, unwanted noises and switching transients have been eliminated with notable success. This is accomplished by effecting a slight delay

IN WIRE-WRAPPING HAS THE LINE...

HOBBY-WRAP-30 WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)



STRIP



WRAP



UNWRAP

OK MACHINE & TOOL CORPORATION

3450 CONNER STREET, BRONX, NEW YORK, N.Y. 10478 U.S.A. • PHONE (212) 694-6800

TELEX: 125091 TELEX: 232395

after power is applied, whereupon a relay connects the speakers to the output transistors. Furthermore, when the FM muting switch is activated, FM tuning action is completely free of transients and noise bursts.

The output transistors are protected against damage from overload, including short circuits, by a circuit that silences the receiver until it is reset by turning off the power for a few moments and then turning it on again. We verified the effectiveness of the overload protection by driving the receiver into shorted outputs, which immediately shut off the amplifiers without damaging them. It is also thermally protected against excessive operating temperatures, although we never reached such a condition.

Realistic has chosen to omit some "features" usually found in receivers of the Model STA-2000's price range that are of little value in any receiver such as low- and high-cut audio filters. Unless such filters have cutoff slopes of 12 dB/octave or more, they are useless for their intended purpose. However, the tape recorder dubbing connections, and the separate preamplifier outputs and power amplifier inputs that are indeed useful have been included. The same for its FM multiplex noise filter. We particularly like the large pushbutton switches as compared to rotary switches. They're most convenient to use. The 20-dB attenuator switch is a nice touch, permitting the user to lower volume temporarily without losing the

volume-setting place previously used.

Comparing the actual measured performance of this receiver to that of similar products we have evaluated, we find that the Model STA-2000 is at the least a competent performer in every respect and outstanding in many. It has the unmistakable "sound" of a good control amplifier, giving the sense of not having a device between the source and the speakers.

The physical smoothness and precision "feel" of the controls are consistent with the receiver's excellent performance. Though it is not a "super-power" receiver, the Model STA-2000 is more than powerful enough for the majority of users and is a very good value.

CIRCLE NO. 102 ON FREE INFORMATION CARD

KOSS MODEL K/145 STEREO HEADPHONES

Comfortable to wear with fine bass performance in moderate price range.



Heading a new line of low-cost "Slimline" stereo headphones from Koss is the Model

K/145. This circumaural headphone features rectangular ear cushions that exclude most outside sounds. Each earcup contains a dynamic driver with a 38-mm polyester diaphragm. The frequency range of the phones is specified at 20 to 20,000 Hz. Impedance is rated at 90 ohms at 1000 Hz, while sensitivity is specified at 0.25 volt at 1000 Hz (or 0.11 volt rms with pink noise) for a 100-dB sound pressure level (SPL). Harmonic distortion is claimed to be less than 0.5% at 1000 Hz and 100 dB SPL.

The phones are finished in textured

brown vinyl and come with a matching padded headband. A separate knurled wheel protruding slightly from each earcup allows independent volume level adjustment in the left and right channels. The cords that attach to the earcups come down to form a Y joint about 2' (60 cm) from the earcups before joining to the coiled cord that goes to the driving amplifier. The total length of the cord is 10' (about 3 meters). The phones weigh 1 lb (454 g), less cord. Price is \$45.

Laboratory Measurements. We tested the phones on a modified ANSI headphone coupler, the type used by Koss for making in-plant measurements. The bass frequency response was very flat and smooth, confirming the effectiveness of the "Pneumalite" ear cushions in sealing the phones to the ears. The output varied by only ± 1.5 dB from 20 to 300 Hz.

At higher frequencies, the output dropped at about a 6-dB/octave rate, to -20 dB in the 3000-Hz range. The usual high-frequency response irregularities were visible above 4000 Hz in our chart plots, including peaks at 5500 and 14,000 Hz. These irregularities can be due, at least in some degree, to the coupler and cannot be definitely attributed to the headphones themselves.

With a 0.25-volt drive at 1000 Hz applied through a source resistance of 100 ohms, the phones delivered their rated 100-dB SPL output. The total harmonic distortion at this level was between 0.1% and 0.2% from 300 to 10,000 Hz, which is well below the rated 0.5%. At lower frequencies, the THD increased, due to

the larger excursions of the diaphragm, to between 0.6% and 0.9% in the 20-to-100-Hz range. We also measured the distortion with the drive level increased to 1 volt, which corresponds to a 112-dB output at 1000 Hz. The THD at this level, although far in excess of normal listening levels, was 0.3% to 0.8% at most frequencies above 100 hertz and 1.8% at 20 hertz.

The impedance of the phones was a constant 90 ohms from 20 to 20,000 Hz with the level controls set to maximum. At the center positions of the controls, the impedance increased to 700 ohms, while at the minimum settings, it was about 1000 ohms.

User Comment. In our use tests, we found these snug-fitting phones to be comfortable to wear, even over prolonged listening periods. We noted that the sound quality is pleasant and listenable throughout, though it lacks the brilliance or crispness exhibited by, say, electrostatic types. (The latter are much costlier, of course.) However, we observed no apparent loss in the high-frequency range. The bass and lower mid-range were strong and solid.

In an overall evaluation of performance, we find these new Koss phones to be fine performers, though sounding a bit "soft" for our personal tastes. But other listeners may indeed prefer it this way. Since headphones, like speaker systems, are best judged subjectively by the listener, we strongly recommend a personal audition of these comfortable, relatively inexpensive phones.

CIRCLE NO. 103 ON FREE INFORMATION CARD

handic®



FREE!
FULL COLOR
CATALOG OF
handic
EQUIPMENT
Send today
for your free
copy.

Now you can buy Europe's No.1 CB in the U.S.A.

The country that created superior steel, jet fighters, automobiles and cameras has also created the world's finest CB equipment.

handic, from Sweden, is the best selling, most popular CB in all Europe.

It is a true system. Base stations, mobiles, hand-helds and accessories interface with one another as a system should.

handic CBs have not only met but exceeded all FCC specifications at their time of introduction. Including the extraordinarily handsome new 40 channel line.

Ruggedly made for tough Swedish geography and extreme weather conditions, yet stunningly designed, handic has drawn rave reviews from CB publications in the U.S.



handic USA, Inc., 14560 N.W. 60th Ave., Miami Lakes, FL 33014

- A handic 240 - in-dash 40 ch/5w Mobile CB/AM/FM Radio MPX (LED) - \$259.95
- B handic 230 - under-dash 40 ch/5w Mobile CB (LED) - \$199.95
- C handic 21 - 2 ch/1w Hand-held CB - \$59.95
- D handic 32 - 3 ch/2w Hand-held CB - \$69.95
- E handic 43C - 4 ch/3w Hand-held CB - \$89.95
- F handic 65C - 6 ch/5w Hand-held CB - \$109.95
- G UCB - Universal Cassette, Recharge/Power Holder for Hand-helds - \$19.95
- H handic S-12 - Selective Call for Base & Mobile - \$79.95
- I handic 305 - 3 ch/5w Mobile CB - \$79.95
- J handic 4005 - 40 ch/5w Base CB w/Sub-receive (LED) - \$279.95
- K handic 3605 - 40 ch/5w Base (LED) - \$249.95
- L handic 007 - 8ch/hi-lo band Scanner w/FM Radio - \$239.95
- M handic 006-H/L - 8ch/hi-lo band or UHF Scanner - \$149.95
- N handic 004-U - 4ch/hi-lo band or UHF Pocket Scanner - \$139.95
- O BK-305 - Power-pak for handic 305, 605, 006 - \$34.95
- P handic 60 - Base Power Mike - \$49.95

Please send the free handic color catalog and name of my nearest dealer. PE-777-LC

Name _____

Address _____

City _____

State _____

Zip _____

handic
USA Inc.



Telephone (305) 558-1522 Telex: 519139
Kennedy Building, 14560 N.W. 60th Ave.
Miami Lakes, Florida 33014 USA

news HIGHLIGHTS

Automotive Developments

Ford Motor Company recently announced plans to use the resources of major semiconductor producers to help in the design of future automotive models. Specially designed large-scale integrated circuits and microcomputers will shortly control many engine functions. Two new concepts which will be pioneered by Ford in 1978 include an electronically controlled carburetor and an electronic engine control system for spark timing and exhaust gas recirculation. The new devices, to be installed on a limited volume of 1978 models, are intended to improve fuel economy, emissions and performance. Chrysler and General Motors have also announced plans to use microprocessors in some auto models.

TV Color Organ

A new entertainment system developed by Atari, called "Video Music," electronically synchronizes images and colors to music from a stereo receiver. A cable which connects the Video Music to a stereo receiver and a switch box connected to the vhf antenna terminals of a television set allow the music signals to be conducted directly to the video screen. Five front-panel potentiometers and twelve pushbuttons on the Video Music enable the viewer to adjust the color, shape, brightness and size of the geometric image, producing an enormous number of possible picture combinations which pulse and beat to the rhythm of the music. Uses five IC's, two transistors and twelve diodes, and comes with an FCC-approved r-f switch box.

RCA To Market 4-Hour VTR

RCA has announced plans to market a home video-tape recorder made by the Matsushita Electric Industrial Co. of Japan. The new video tape recorder, called "VHS," will have a mode switch for either 2- or 4-hour recording with the same cassette, vhf and uhf tuners, and a clock for automatic recording. Moreover, a company spokesman said that optional microphones and cameras will be made available to allow consumers to produce home movies on the video tape cassettes. Thus, a VTR war for consumers' hearts appears to be shaping up between the VHS models and Sony's Betamax models, the latter, a two-hour video recorder to be marketed by the Zenith Corp. Too bad that standards are dissimilar.

An R-F People Finder

The Trakatron "Silent People Finder" by Interasonics Corp., New York, NY, is an electronic system that locates people in an office or plant without paging them. Each person has a transponder and is assigned a button on a console locator. A sensor is placed in certain desired areas. When the console's button is pressed, the proper signal goes throughout the covered areas. If the

person sought is in a room with a sensor, his or her transponder unit responds, whereupon a signal goes back to the console, giving the location and telephone extension (if any). The inquirer can then either go to the area indicated or call on the extension. Shades of 1984!

Digital Watch Firsts

Intertime Corporation has introduced the latest in diving equipment, an *underwater* digital watch. Named "Maritime," the watch uses LED's to display month, week, date, hours, minutes and continuous counting seconds. Activation of a single button displays red numerals designed for easy underwater visibility, and a ratchet bezel graduated in minutes is provided for elapsed time reference. The housing is Swiss made, produced from a solid block of stainless steel. It's equipped with double "O" rings to prevent water leakage and fogging, and has been factory tested to a depth of 600 ft. \$250.00.

Another innovative digital watch to be introduced is the "programmable message" model from the Solid State Products Division of Hughes Aircraft Company. The watch module features a personalized five-word, five-letter-per-word message programmed by the wearer and displayed in an electronic readout. The message can be changed as desired by the user, a procedure which takes less than five minutes. The five standard functions of month, date, hour, minute and second are also included, with five LED's providing the letter, symbol and number readouts. A spokesman for the company suggests that the watch can be used for important appointment reminders or medical instructions, among other applications.

Solar-Powered Calculator

"The Sun Man," a new solar battery-powered calculator recently introduced by Sharp Electronics, is believed to be the smallest such instrument on the market. With dimensions of 0.35" thin x 2.6" wide x 7.5" deep (9 mm x 66 mm x 109 mm), the solar-powered calculator is said to have a longer life span than the ordinary calculator battery, needing only two hours of window light to recharge. It performs six functions, and uses a liquid crystal display. \$99.95.


Antique-Radio Manuals

To assist antique-radio collectors in the usually frustrating search for technical literature, Supreme Publications has formed a department which will buy and sell old technical data. Original Rider manuals and old Sams, Supreme, and many factory service manuals are on hand, some dating back to the 20's. For information write to Supreme Publications, 1760 Balsam Rd., Highland Park, IL 60035.

HOW TO SAVE HUNDREDS OF DOLLARS ON PARTS. PAINLESSLY.

At CSC, we've developed a family of ingenious Design Mate™ test equipment that gives you professional quality and precision at very *un*professional prices. Each unit can save you money—and time—in a number of interesting ways.

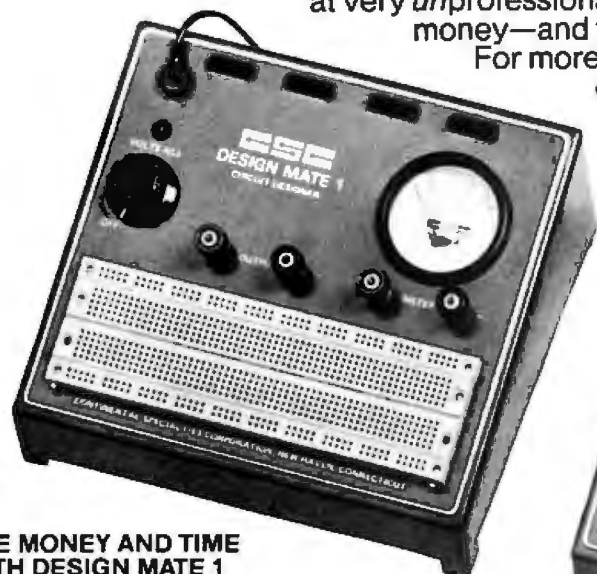For more information on these, or any other CSC products, see your dealer or write for our catalog and distributor list.



SAVE MONEY AND TIME WITH DESIGN MATE 1

This precision all-in-one unit combines a solderless plug-in breadboarding system with a built-in better-than-1%-regulated variable 5-15V supply and 0-15V voltmeter. Gives you everything you need to design and test circuits faster than you ever could before. Saves money by eliminating lead damage and heat damage to components. Lets you re-use parts over and over again, to save even more. All for just \$54.95*.



STRETCH YOUR BUDGET FURTHER WITH DESIGN MATE 2


Precision function generator lets you test all kinds of equipment, with 1Hz-100kHz signals. Low-distortion sine waves, high-linearity triangle waves, fast-rise-time square waves. Five decade ranges, accurate to 5% of dial setting, with variable 100mV-10V P-P output and constant 600-ohm impedance. At \$69.95*, it's a lot of signal for very little money.



SAVE MORE MONEY AND TIME WITH DESIGN MATE 3

Accurate R/C bridge helps you use "bargain" components. Quickly and easily measures resistance 10 ohms-10 meg; capacitance 10pF-1μF—both in decade ranges to within 5% of dial setting. Simple, 2-control operation and positive LED indication make measurements in seconds. At \$59.95*, it pays for itself in no time.

CONTINENTAL SPECIALTIES CORPORATION

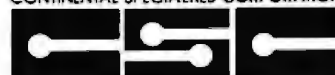

EASY DOES IT

44 Kendall Street, Box 1942
New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227
West Coast office: Box 7809, San Francisco, CA
94119 • 415-421-8872 TWX: 910-372-7992
Canada: Len Finkler Ltd., Ontario
Mexico: ELPRO, S.A., Mexico City 5-23-30-04



The 9-inch screen of the CT-VM monitor (\$175) shown here with Southwest's new CT-64 illustrates the terminal's 64-character lines, switchable control character printing, and word highlighting. At just \$500 for both, these matching units provide a complete CRT terminal with full cursor control, 110-1200 Baud serial interface, and many other features.

Now \$325 buys a 64-character terminal kit

Our new CT-64 terminal kit gives you scrolling, full cursor control, 128-character ASCII display (with both upper and lower case), and two 1K memory pages. It's usable with any 8-bit computer.

Add our optional fully assembled 12 MHz CT-VM monitor for another \$175 and you'll have the best CRT terminal buy offered anywhere.

The CT-64 gives you full cursor control, home-up and erase, erase to end of line or end of frame, cursor on/off, screen reversal, scroll or page, solid or blinking cursor, page selection, and end-of-page warning beeper.

The CT-64's features include:

- 64 or 32 characters per line (16 lines)
- Premium display with both upper and lower case letters, and descenders (g, j, etc.)
- Two 1K pages of 8-bit memory
- Scrolling or page mode operation
- 32 control character decoding
- Prints control characters (selectable)
- 128-character ASCII set
- 110/220 Volt 50-60 Hz power supply
- Highlights words with reversed background
- Optional 9-inch monitor with matching cover available
- Complete with keyboard, power supply, 110-1200 Baud serial interface, and case

Okay, Southwest, I know a bargain when I see it.

- ☐ Enclosed is \$500 for the whole works
(CT-64 terminal plus 12 MHz CT-VM monitor).
- ☐ Here's \$325 for the CT-64
- ☐ Send only data for now.
- ☐ Send me your \$395 MP-68 computer kit.

☐ or BAC # _____ Exp. Date _____

☐ or MC # _____ Exp. Date _____

Name _____ Address _____

City _____ State _____ ZIP _____



Southwest Technical Products Corp.
219 W. Rhapsody, San Antonio, Texas 78216

CIRCLE NO. 48 ON FREE INFORMATION CARD



**BREAKTHROUGH
PROJECT**

BY JOSEPH A. WEISBECKER

PART IV:

Build the PIXIE Graphic Display

Adding one chip to the Elf provides complete video interface and animated graphics capability for less than \$25.



If you own an Elf microcomputer (see POPULAR ELECTRONICS August 1976) or are planning to build one soon, the addition of a single IC and a handful of support components, and a change in the crystal frequency, can give you Pixie graphics. The entire graphics system is built into the new CDP 1861 LSI chip that sells for less than \$20 from RCA

parts distributors. (A complete kit is available; see Parts List.) The two other IC's in the optional add-on system are for a crystal oscillator that allows the graphics IC to generate the correct TV horizontal and vertical sync pulses.

The photo at the top of this page illustrates what can be done with the original 256 bytes of memory in the Elf when the

Pixie graphics system is added. In this article, we will show you how to install and program the Pixie system to produce this type of graphics.

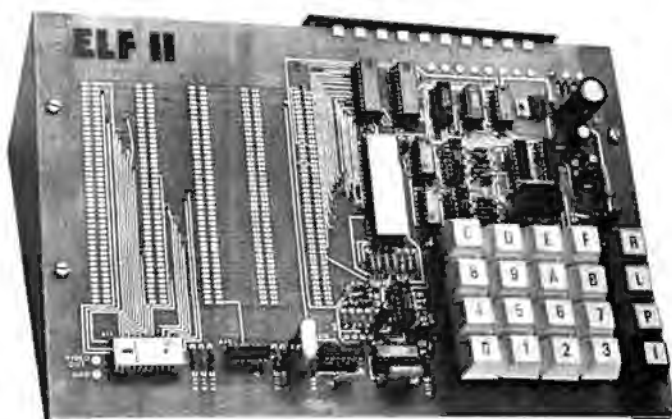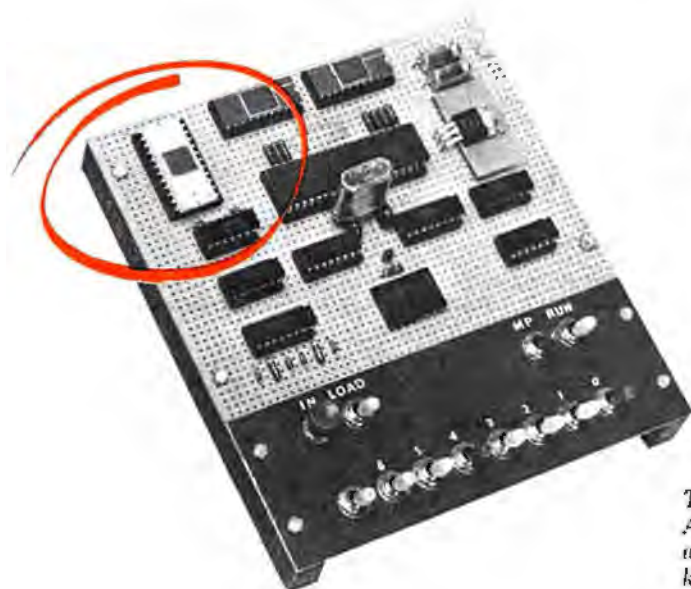Some Details. The unique Pixie graphics system employs the direct memory access (DMA) capability built into the 1802 microprocessor in the Elf



The basic Elf project originally published in the August 1976 issue of POPULAR ELECTRONICS is shown at left with Pixie components added. Elf II is a complete kit including a pc board, hexadecimal keypad, Pixie graphics components and expansion bus (see Parts List).

[illegible]

Fig. 1. Memory addresses of bytes mapped onto TV screen in sample program.

to work in conjunction with the new graphics IC. This allows you to display any 256-byte segment of memory on a CRT monitor or TV receiver. The output of the new chip is a 1-volt composite video/sync signal.

The selected segment of memory appears on-screen as an array of small squares that represent individual memory bits. If a memory bit is a 1, the appropriate square will be white, while if a bit is a 0, the square will be dark. Changing the bit pattern within the memory will change the pattern that appears on-screen. You can store several different bit patterns (pictures) in memory and,

TABLE I—TEST PROGRAM

Label	M	Bytes	Comments
Start	0000	90 B1 B2	R1=1, R2.1=00
	0003	B3 B4	R3.0, R4.0=00
	0005	F8 2D A3	R3.0=(main)
	0008	F8 3F A2	R2.0=(stack)
	000B	F8 11 A1	R1.0=(interrupt)
	000E	D3	P=3 (go to main)
Return	000F	72	restore D, R2+1
	0010	70	restore XP, R2+1
Interrupt	0011	22 78	R2-1, save XP @ M2
	0013	22 52	R2-1, save D @ M2
	0015	C4 C4 C4	no-op (9 cycles)
	0018	F8 00 B0	
	001B	F8 00 A0	
Refresh	001E	80 E2	R0=0000(refresh ptr) D=R0.0
	—	—	8 DMA cycles (R0+8)
	0020	E2 20 A0	R0-1, R0.0=D
	—	—	8 DMA cycles (R0+8)
	0023	E2 20 A0	R0-1, R0.0=D
	—	—	8 DMA cycles (R0+8)
	0026	E2 20 A0	R0-1, R0.0=D
	—	—	8 DMA cycles (R0+8)
	0029	3C 1E	go to refresh (EF1=0)
	002B	30 0F	go to return (EF1=1)
Main	002D	E2 69	X=2, turn TV on
	002F	3F 2F	wait for IN pressed
	0031	6C A4	set MX,D, R4.0=toggles
	0033	37 33	wait for IN released
	0035	3F 35	wait for IN pressed
	0037	6C	set MX,D=toggles
	0038	54 14	set M4=D, R4+1
	003A	30 33	go to M33

PIXIE ANIMATION PROGRAM

BY EDWARD C. DEVEAUX

THE PROGRAM given here can be used with the Pixie version of the Elf microcomputer to create animation graphics using only the original 256 bytes of memory. The interrupt routine uses the same timing as described in previous Elf articles. However, a counter has been added to this routine, and we load the refresh address into R0 from R4. The main line of the program has been completely rewritten and contains shift, roll, and INPUT switch read routines.

The shift routine shifts 16 lines of the display to the right one bit at a time; bits shifted off the rightmost byte are shifted back onto the display in the

```

LOC  COSMAC CODE  LNNO  SOURCE LINE
      1  .. AN 1802 ANIMATION PROGRAM by E. DEVEAUX
      2  ..
78    3  BEGSFT=#78  .. ADDRESS OF FIRST LINE SHIFTED.
      4  ..
      5  .. THIS PROGRAM PROVIDES VARIABLE SPEED
      6  .. ANIMATION OF THE IMAGE LOCATED AT #78 to
      7  .. #F7 IN MEMORY.
      8  .. SPEED CONTROL IS PROVIDED BY INPUT SWITCHES.
00    9  GHI R0  ..ZERO HIGH ORDER OF
01   10  PHI R1  ..R1 R2 R3.
02   11  PHI R2
03   12  PHI R3
04   13  PHI R4  ..R4 POINTS TO REFRESH
05   14  PLO R4  ADDRESS
06   15  LDI A.0(INTRPT)
08   16  PLO R1
09   17  LDI A.0(STACK)
0B   18  PLO R2
0C   19  LDI A.0(MAIN)
0E   20  PLO R3
0F   21  SEP R3  ..GO TO MAIN LINE
10   22  DC#01020300  ..STACK AREA
13   23  STACK =*-1
      24  ..
      25  ..THIS PROGRAM USES A MODIFIED VERSION
      26  ..OF THE INTERRUPT ROUTINE THAT APPEARED
      27  ..IN COSMAC ELF PART 4.
      28  ..
      29  ..A SHIFT ROUTINE HAS BEEN ADDED THAT MOVES THE
      30  .. STARSHIP FROM LEFT TO RIGHT ACROSS THE CRT.
      31  ..
14   32  RETURN;LDXA
15   33  RET  ..CYCLES
16   35  INTRPT;DEC R2  .. 2
17   36  SAV  ..4 R5 COUNTS REFRESH
18   37  DEC R2  ..6 CYCLES, USED TO
19   38  STR R2  ..8 DETERMINE WHEN TO
1A   39  INC R5  ..10 SHIFT /ROLL.
1B   40  NOP  ..13
1C   41  GHI R4  ..15 R4 TO R0

```


using software, display them successively onscreen to produce animation effects. Low-resolution alphanumerics can also be created.

Since the basic Elf has only 256 bytes of memory, we will show how to display the entire memory on the screen. The memory is mapped as shown in Fig. 1, in an array of 64 spots wide (eight bytes with eight bits/byte) by 32 spots high to make a total of 256 bytes.

The byte at M(0000) is displayed at the upper-left of the screen; each row on the screen is equivalent to eight memory bytes. Byte M(00FF) appears at the bottom-right of the screen.

Circuit Operation. The entire schematic diagram for the Pixie graphics display system is shown in Fig. 2A. It consists of five components: the 1861 chip, a phono jack for the video output, and three resistors. The circuit shown in Fig. 2B may be used to replace the original crystal used in the Elf microcomputer. This is necessary because, to use the graphics display, the original crystal frequency must be changed to approximately 1.760640 MHz to generate the correct TV horizontal and vertical sync pulses. Crystals of this frequency may be expensive. The Fig. 2B circuit uses a

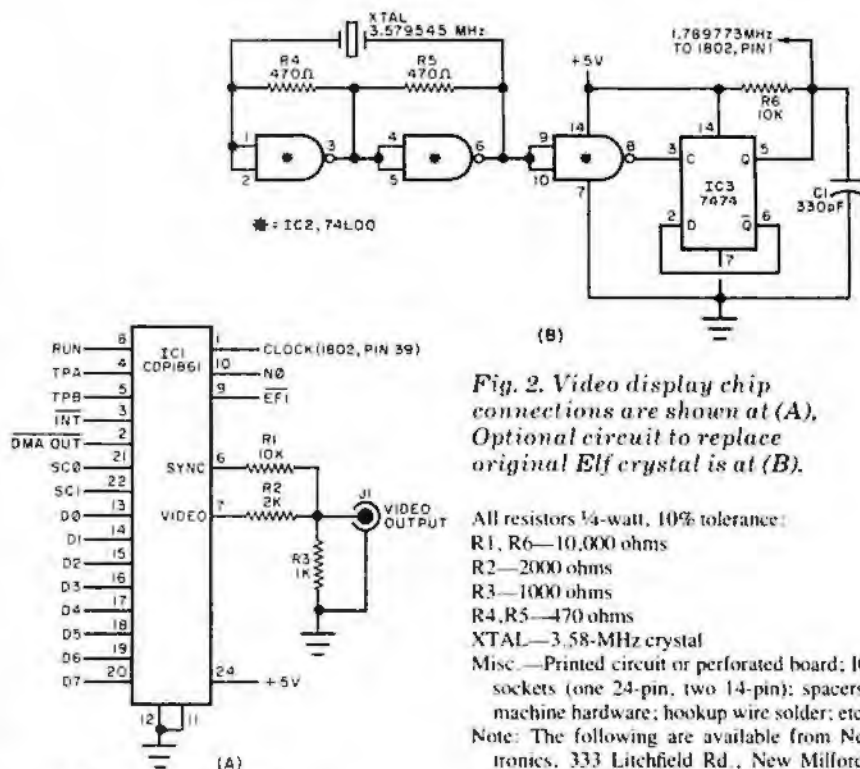


Fig. 2. Video display chip connections are shown at (A). Optional circuit to replace original Elf crystal is at (B).

All resistors 1/4-watt, 10% tolerance:
R1, R6—10,000 ohms
R2—2000 ohms
R3—1000 ohms
R4, R5—470 ohms
XTAL—3.58-MHz crystal
Misc.—Printed circuit or perforated board; IC sockets (one 24-pin, two 14-pin); spacers; machine hardware; hookup wire solder; etc.
Note: The following are available from Neronics, 333 Litchfield Rd., New Milford, CN 06776: kit including all of above Pixie components except those under "Misc." at \$24.95; complete Elf II kit (basic Elf plus Pixie components and hexadecimal keyboard), including pc board, keyboard support IC's and expansion bus at \$99.95, plus \$3.00 shipping. Connecticut residents, add 7% sales tax.

"PIXIE" PARTS LIST

C1—330-pF disc capacitor
IC1—CDP 1861 video IC (RCA)
IC2—74L00 low-power quad 2-input NAND gate IC
IC3—7474 dual-D flip-flop IC
J1—Phono jack

high-order position of the first byte on the line.

The 32 lines of the display can be moved up one line by incrementing the starting refresh address by eight between refresh cycles. Decrementing register 4 (R4) allows the display to be rolled down. Hence, varying the frequency of shifts or rolls varies the animation speed of the displayed image.

Control of the speed is via the Elf's conventional INPUT switches. Setting all switches to zero and depressing the INPUT pushbutton causes a hex 00 to be read into location 13 (stack), in which case, there will be no movement of the displayed image. Loading any nonzero bit through the INPUT switches will animate the image. Any bits loaded are compared to the bits in the low-order byte of register 5 (R5). A shift or roll routine is initiated whenever there is a match between the bits of the low-order byte of R5 and the bits in the byte read into location 13. Register 5 is used to count the refresh cycles and is incremented by one every interrupt cycle.

1D	B0	42	PHI	R0	..17	REFRESH ADDRESS
1E	84	43	GLO	R4	..19	
1F	A0	44	PLO	R0	..21	
		45			..	
20	80	46	GLO	R0	..23	
21	80	47	GLO	R0	..25	
22	80	48	REFRESH	GLO	R0	.. 27
23	E2	49	SEX	R2	.. 29	8 DMA CYCLES
		50			..	
24	E2	51	SEX	R2	..	
25	20	52	DEC	R0	..	8 DMA CYCLES
26	A0	53	PLO	R0	..	
		54			..	
27	E2	55	SEX	R2	..	
28	20	56	DEC	R0	..	8 DMA CYCLES
29	A0	57	PLO	R0	..	
		58			..	
2A	E2	59	SEX	R2	..	8 DMA CYCLES
2B	20	60	DEC	R0	..	
2C	A0	61	PLO	R0	..	
		62			..	
2D	3C22	63	BNI	REFRESH	..	ON EF1 REFRESH
2F	3014	64	BR	RETURN	..	IS OVER.
31	E2	65	MAIN	SEX	R2	.. RX=2
32	69	66	INP	1	..	TELL 1861 TO
		67			..	TURN ON CRT.
		68	..	SPREAD	READS INPUT SWITCHES	TO CONTROL
		69	..	SPEED	OF SHIFTS/ROLLS.	
		70	..	INPUT	SWITCH IS STORED AT	STACK M(R2).
		71	..			
		72	..	INITIAL	VALUE OF STACK IS	ZERO AND THERE IS
		73	..	NO	MOVEMENT OF STAR	SHIP UNTIL A NON ZERO
		74	..	IS	INPUT.	
33	3F38	75	SPREAD	BNI	CKSHIF	.. IF NO INPUT GO
35	3735	76	WTREAD	B4	WTREAD	.. IF TIME TO
37	6C	77	INP	4		.. READ INTO
		78
38	85	79	CKSHIF	GLO	R5	.. GHI R5 VARY
39	F2	80	AND			.. OF STAR
3A	3233	81	BZ	SPREAD		.. SHIFT/ROLL
3C	F800	82	LDI	A.1(BEGSPT)		.. BR ROLL 3061
3E	B9	83	PHI	R9		.. ROLL NO

readily available 3.58-MHz color-TV crystal and frequency divider to generate 1.789773 MHz, which is close enough for the 1861 chip to perform properly.

The 1861 chip uses the same clock as the 1802 μ P chip to trigger internal counters to provide the TV-like composite sync at pin 6. The graphics display is directly refreshed from the memory 60 times each second, accomplished by an interrupt request sent to the 1802 at the same rate.

When the 1802 receives the interrupt request, it temporarily stops the program it is executing and immediately branches to the interrupt routine previously stored in memory. This branch occurs when P is automatically set to 1 and X is set to 2. The interrupt routine program counter is always R1, which must be set to the address of the interrupt routine before the 1861 is activated and starts sending interrupts to the 1802. A pulse from NO is sent to pin 10 of the 1861, permitting this chip to start sending interrupts. A 69 instruction can be used to generate the 1861 activation pulse. The 1861 is always turned off

when the Elf is stopped with the RUN switch down.

In the program shown in Table I, R1 is set to the address of the interrupt routine at M(0011), R2 is set to the address of the work area (or stack) used subsequently for byte storage, R3 is set to the main program starting at M(002D), and setting P=3 causes a branch to M(002D) with R3 as the program counter. The main program permits entry of the bytes at any time via the Elf's toggle switches. This permits you to see what is happening to the CRT screen as memory bytes are changed. The program loops on itself until an interrupt signal is generated by the 1861, activated by the 69 instruction at M(002E).

Exactly 29 machine cycles after the initiation of the interrupt routine, the 1861 requests eight sequential memory bytes by pulling down the DMA-OUT (pin-2) request line for eight bytes (eight machine cycles). This automatically causes eight memory bytes, addressed by R0, to be sequentially fetched and transferred to the 1861 via the data bus. Note that the C4 instructions at M(0015) are special no-op instructions that re-

TABLE II—SPACESHIP PROGRAM

M	Byte Sequence
0040	00 00 00 00 00 00 00 00
0048	00 00 00 00 00 00 00 00
0050	7B DE DB DE 00 00 00 00
0058	4A 50 DA 52 00 00 00 00
0060	42 5E AB D0 00 00 00 00
0068	4A 42 8A 52 00 00 00 00
0070	7B DE 8A 5E 00 00 00 00
0078	00 00 00 00 00 00 00 00
0080	00 00 00 00 00 00 07 E0
0088	00 00 00 00 FF FF FF FF
0090	00 06 00 01 00 00 00 01
0098	00 7F E0 01 00 00 00 02
00A0	7F C0 3F E0 FC FF FF FE
00A8	40 0F 00 10 04 80 00 00
00B0	7F C0 3F E0 04 80 00 00
00B8	00 3F D0 40 04 80 00 00
00C0	00 0F 08 20 04 80 7A 1E
00C8	00 00 07 90 04 80 42 10
00D0	00 00 18 7F FC F0 72 1C
00D8	00 00 30 00 00 10 42 10
00E0	00 00 73 FC 00 10 7B D0
00E8	00 00 30 00 3F F0 00 00
00F0	00 00 18 0F C0 00 00 00
00F8	00 00 07 F0 00 00 00 00

3F	F878	84	LDI	A.0(BEGSFT)	
41	A9	85	PLO	R9	..R9=FIRST LINE
42	F810	86	LDI	16	..TO SHIFT.
44	A6	87	PLO	R6	..SHIFT 16 LINES.
45	99	88	NXTLINE,GHI	R9	
46	8A	89	PHI	RA	..SAVE ADDRESS OF 1st
47	89	90	GLO	R9	..ON LINE IN RA
48	AA	91	PLO	RA	
49	F807	92	LDI	7	..R7=BYTES TO SHIFT-1.
4B	A7	93	PLO	R7	
4C	09	94	LDN	R9	
4D	B8	95	PHI	R8	..SAVE 1ST BYTE ON
4E	76	96	SHRC		..LINE IN R8.1
4F	19	97	NXTBYT,INC	R9	..POINT R9 TO NEXT BYTE.
50	09	98	LDN	R9	..LOAD NEXT BYTE.
51	76	99	SHRC		..SHIFT RIGHT.
52	59	100	STR	R9	..STORE BYTE
53	27	101	DEC	R7	
54	87	102	GLO	R7	..CHECK IF ALL BYTES
55	3A4F	103	BNZ	NXTBYT	..SHIFTED.
57	98	104	GHI	R8	..PUT BIT 0 OF 8TH
58	76	105	SHRC		..BYT ON BIT 7 OF
59	5A	106	STR	RA	..1ST BYT ON LINE.
5A	19	107	INC	R9	..R9=BYTE 0 NXT LINE.
5B	26	108	DEC	R6	
5C	86	109	GLO	R6	..CHECK IF 16 LINES
5D	3A45	110	BNZ	NXTLINE	..SHIFTED.
5F	3033	111	BR	SPREAD	..SKP 38 ROLL AND SHIFT.
61	84	112	ROLL,GLO	R4	..INCREMENT R4 ONE LINE
62	FC08	113	ADI	8	..ROLL SCREEN UP.
64	A4	114	PLO	R4	
65	9A	115	GHI	R4	..CHANGE LINO 116 TO
66	F800	116	LDI	00	..ADCI 0 7C00 IF MORE
68	B4	117	PHI	R4	..THAN 256 BYTES.
69	3233	118	BZ	SPREAD	
6B	84	119	GLO	R4	
6C	B4	120	PHI	R4	
6D	3033	121	BR	SPREAD	
6F	00	122	DC	#00	
		123	..ENTER IMAGE TO BE SHIFTED IN LOCATIONS		
		124	..X'78' - X'F7'.		
		125	END		

The numbers in the program flow chart (right) refer to the line numbers in the program. The program can be set up to shift or roll, or shift and roll. The program is loaded into locations 78 through F7. (Try using the program for the starship shown in Table II of the Pixie article.) Only the data loaded into 78 through F7 is shifted, but the entire area from 00 through FF is rolled.

Loading the program exactly as it is listed here will enable the shift routine only. Loading a 38 (SKP instruction) in location 5F (line 111) will enable both shift and roll routines. Loading 30 61 (BR ROLL) in locations 3C and 3D (line 82) will enable only the roll routine.

After loading and running the program, animation of the display will begin after any nonzero byte is loaded via the INPUT switches and operation of the INPUT pushbutton. By varying the INPUT bit pattern, you can control the speed of the animation.

If you have never seen a stack in "motion" when a program is running, take a look at displayed location 13. Then vary the speed. ◇

TABLE II

	1st BYTE								2nd BYTE							
	1st DIGIT				2nd DIGIT				3rd DIGIT				4th DIGIT			
	7	6	5	4	3	2	1	0	7	6	5	4	3	2	1	0
M(0050)																
M(0058)																
M(0060)																
M(0068)																
M(0070)																

M(0050) 0 1 1 1 0 1 1 0 1 0 1 0 1 1 0

7 B D E

M(0056) 0 1 0 0 0 1 0 0 0 1 0 1 0 0 0 0 0

4 A 5 0

Fig. 3. Diagram showing how to create your own display. This one is for parts of five lines of Spaceship Program.

quire three cycles for each execution. These are used only to provide the delay required between the beginning of the interrupt routine and the first eight-byte DMA request generated by the 1861 display circuits.

Each of the eight display refresh bytes requested by the 1861 is internally converted to a bit serial form and used to provide the luminance (brightness) pulses that come out of the 1861 at pin 7. The actual raster display consists of 262 horizontal lines for each frame, and there are 60 frames per second. Each

display spot is four raster lines high, which means that each eight-byte display row must be repeated four times. With the interrupt routine, R0 is initially set to M(0000), which means that the first DMA request causes the eight bytes from M(0000) to M(0007) to be fetched and displayed. The time of each raster line is exactly 14 machine cycles to permit the transfer of eight bytes (eight cycles) plus the execution of three two-cycle instructions during each raster line time. Following the eight DMA cycles required to refresh the first eight bytes, R0

is restored to its original value so that it remains pointing at the same eight bytes.

The E2 20 A0 instructions at M(0020), M(0023), and M(0026) are used to occupy six machine cycles between the DMA requests and to restore R0 to its initial value before incrementing it by eight during the eight-byte DMA request. The 20 instruction decrements R0.1 back to its initial value if a 256-byte page boundary was crossed during the preceding eight DMA cycles.


After the first group of eight bytes has been displayed for four raster line times, R0 is permitted to advance to the next group of eight bytes to be displayed. This process is continued until 32 groups of eight bytes each (256 total) have been displayed. At this time, the circuits in the 1861 chip cause line EF1=1 (at pin 9) and the interrupt routine terminates.

Other Considerations. The raster refresh involves the display of 32 groups of eight bytes, and each row of eight bytes is repeated on four raster line scans. This means that the display refresh ties up the 1802 μ P for slightly more than 128 raster lines (32×4). Since there are 262 raster lines per frame, the μ P spends about 50% of its time performing the display-refresh function.

Since the 1802 and 1861 clocks must remain synchronized, none of the three-cycle instructions described in the 1802's user's manual should be used in programs that run concurrently with this display. The only exception is the use of the C4 instruction in the interrupt routine.

The sample program given in Table I was designed to run in expanded-memory systems as well as in the basic 256-byte Elf. In the expanded system, just change the bytes at M(0019) and M(001C) so that R0 initially points to any 256-byte segment of the memory you wish to display on the raster. You can write any other main program to run concurrently with this interrupt routine.

The 1861 chip can also be used to display any number of memory bytes from eight to 1024 by rewriting the interrupt routine. For example, change the byte at M(0024) from 20 to 80, and you will see 512 bytes displayed on the CRT screen as 64 spots horizontally by 64 spots vertically. If you have only 256 bytes of memory in your system, you will see the same 256 bytes repeated twice on the screen. When displaying 512 bytes, each spot represents half the

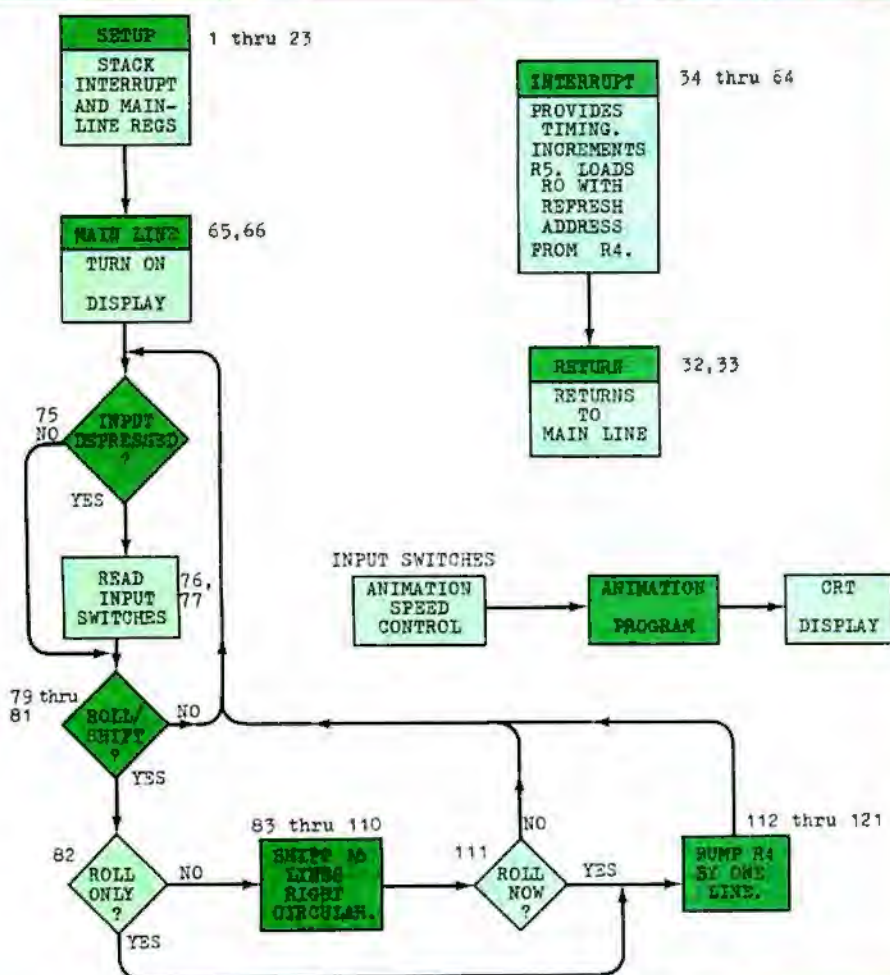

height of those displayed when 256 bytes are displayed.

One of the main advantages of mapping main memory directly into the monitor or TV raster is the ability to manipulate the display using the normal instruction set. In systems that employ an external frame buffer for refresh, specialized instructions are required to change buffer contents. The buffer memory also costs more money. With the refresh buffer approach toward animation, you must store two picture patterns in memory and alternately transfer them to the buffer memory. Using the Pixie graphics display described here, you store the same two-picture patterns in memory but you need only change the initial value of R0 to alternately display them. Not only do you save the cost of a refresh buffer, you can greatly simplify the programming.

Construction. The Pixie circuit can be mounted on the original Elf board by relocating the crystal and two capacitors to the center of the board. Now, the 1861 IC goes on the upper left of the board, the resistors on the bottom of the board, and the output jack on the rear apron of the chassis.

Remove the crystal from the Elf and wire the Fig. 2B frequency divider to pin 1 of the 1802 μ P. Then interconnect the two boards exactly as shown in Fig. 2A and B, including the power lines. Jack J1 can be mounted on a small metal bracket and secured to the add-on board with No. 4 machine hardware. Also, mount R1 and R2 on the add-on board via "flea" clips because they may have to be changed for different-value resistors to suit the modulation requirements of the particular monitor you are using.

Sample Display Program. To test the Pixie, load the program given in Table I, starting at location M(0000). When this program is run, a random spot pattern should be displayed on-screen. At this time, you may have to alter the values of R1 and R2 to produce a tight sync lock and the desired modulation level of the spots. These are only level-adjust resistors and play no role in the actual sync or video production. The displayed pattern represents whatever is stored in the Elf's memory. The top eight rows represent the program given in Table I.


You can familiarize yourself with the new graphics ability of your computer if you visualize a grid of 64 boxes wide by

32 boxes deep, assuming a 256-byte memory. Bear in mind that the operating program given in Table I occupies the top eight lines. Since the program ends at memory location M(003B), load 00 into memory location M(003F) to complete that line.

Now, to display the spacecraft shown in the lead photo, load the programs given in Tables I and II in that order, starting the Table II program at memory location M(0040). Reset and switch to RUN.

If you wish to create your own display, Fig. 3 illustrates how to arrive at the correct hex digits. (In this case, the example used is for a small area of the program in Table II.) Use graph paper to "draw" your picture, shading in the "spots" you want to be white on the CRT screen. Then transfer the line bit pattern into the eight hex bytes per line as shown in Fig. 3.

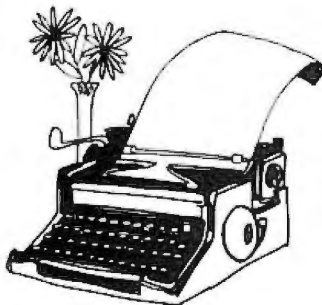Conclusion. The Pixie system described here adds video graphics to your Elf microcomputer at very low cost. So far, we have described how the Pixie system can be used to put simple, stationary images on-screen. Accompanying this article is a program that will put the graphics in motion. ◇



Electronic "Bell" for a TVT-II

Lets you know when you are near the end of a line on a TV typewriter.

BY DENNIS J. DEUTSCH


Here is an add-on circuit for the computer hobbyist that will give his set-up the effect of a bell ringing near the end of a line as it does on a typewriter. The circuit, as shown in the diagram, is for use with the Southwest Technical Products CT-1024 TVT-II terminal.

The CT-1024 produces 32 characters per line, for which access is required to bits 1, 2, 4, 8, and 16 on the CT-1024. These are located at IC35 and IC42.

The circuit as shown is set up to produce the tone on character 27. (Bit 4 is inverted in the 7404 IC so that it is "NOT'ed".) The character number trap consists of an 8-input NAND gate in the 7430 and the single inverter (which can be a single transistor if desired). If you want to stay at character 27, eliminate the inverter and bit 4.

Once the character is counted, the resulting pulse turns on the 74121 one-shot for a short period of time. The timing values of the one-shot can be altered by changing the circuit's time constant.

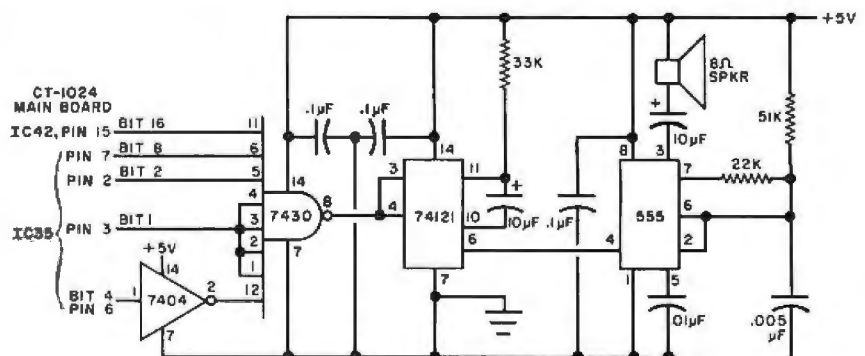The one-shot triggers a 555 timer used as a tone generator to drive a small 8-ohm speaker. To alter the tone, change the value of the capacitor between pin 6 of the 555 and ground. ◇



BUILD THIS TUT-6

YOUR SOFTWARE CONTROL CAN
INCLUDE INTERLACE, SCROLLING,
& A FULL PERFORMANCE CURSOR

UP TO 4096 SHARP CHARACTERS
ON THE SCREEN IN LESS THAN
THREE MEGAHERTZ TV BANDWIDTH

Build the TVT-6: A Low-Cost DIRECT VIDEO DISPLAY

PART I



\$35 microcomputer "add-on" provides:

- User-selectable line lengths
- Scrolling
- Up to 4k on-screen characters with only 3-MHz bandwidth

BY DON LANCASTER

The TVT-6
connected
to a KIM-1.

Thanks to some software tricks, a simple and low-cost add-on circuit, and a new way to speed up a microprocessor, you can now build a video interface for your microcomputer for an investment of only \$20 to \$35. The TVT-6 video system described here permits the choice of virtually any format including 16/32 (16 lines of 32 characters), 16/64, or 32/64. It also features full editing capability and full-performance cursor.

In spite of its simplicity (10 low-cost IC's), the circuit employs a new approach to video processing that permits up to 4000 characters to be displayed on-screen within a 3-MHz bandwidth. Although the TVT-6 was designed for the 6502 microprocessor based KIM-1, software can be used to easily map into the JOLT, EBKA, or Ohio Scientific microcomputers. In addition, the TVT-6 can be adapted to other microprocessors, including the popular 6800, 8080, and Z80. It is easiest to use with 16-address-line systems that operate on a single 5-volt supply and 1- μ s cycle time

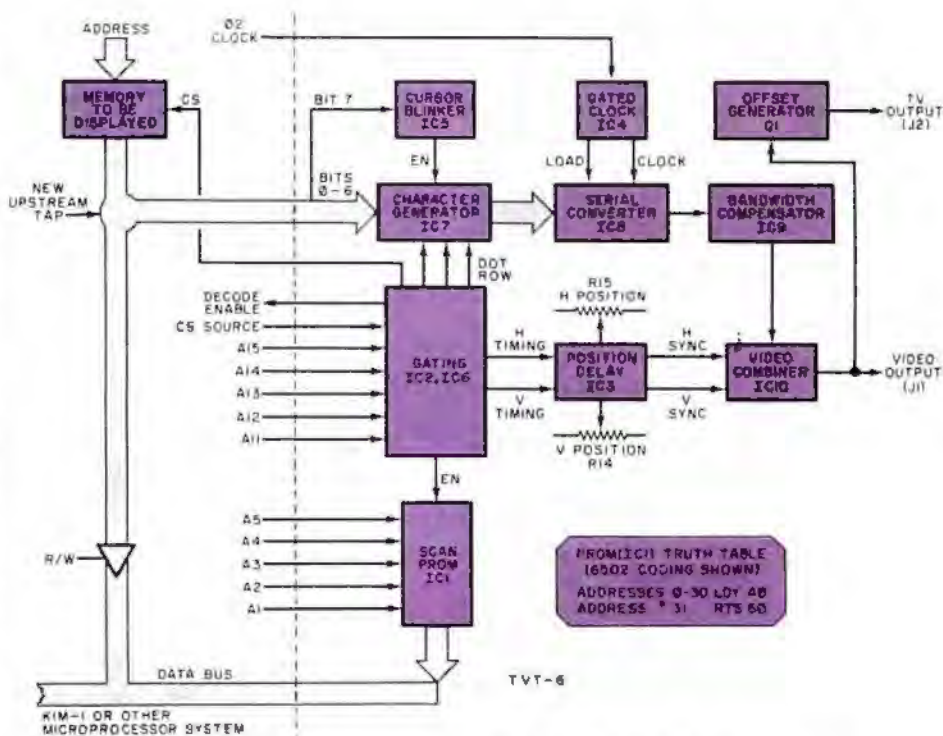


Fig. 1. TVT-6 block diagram and truth table for the PROM.

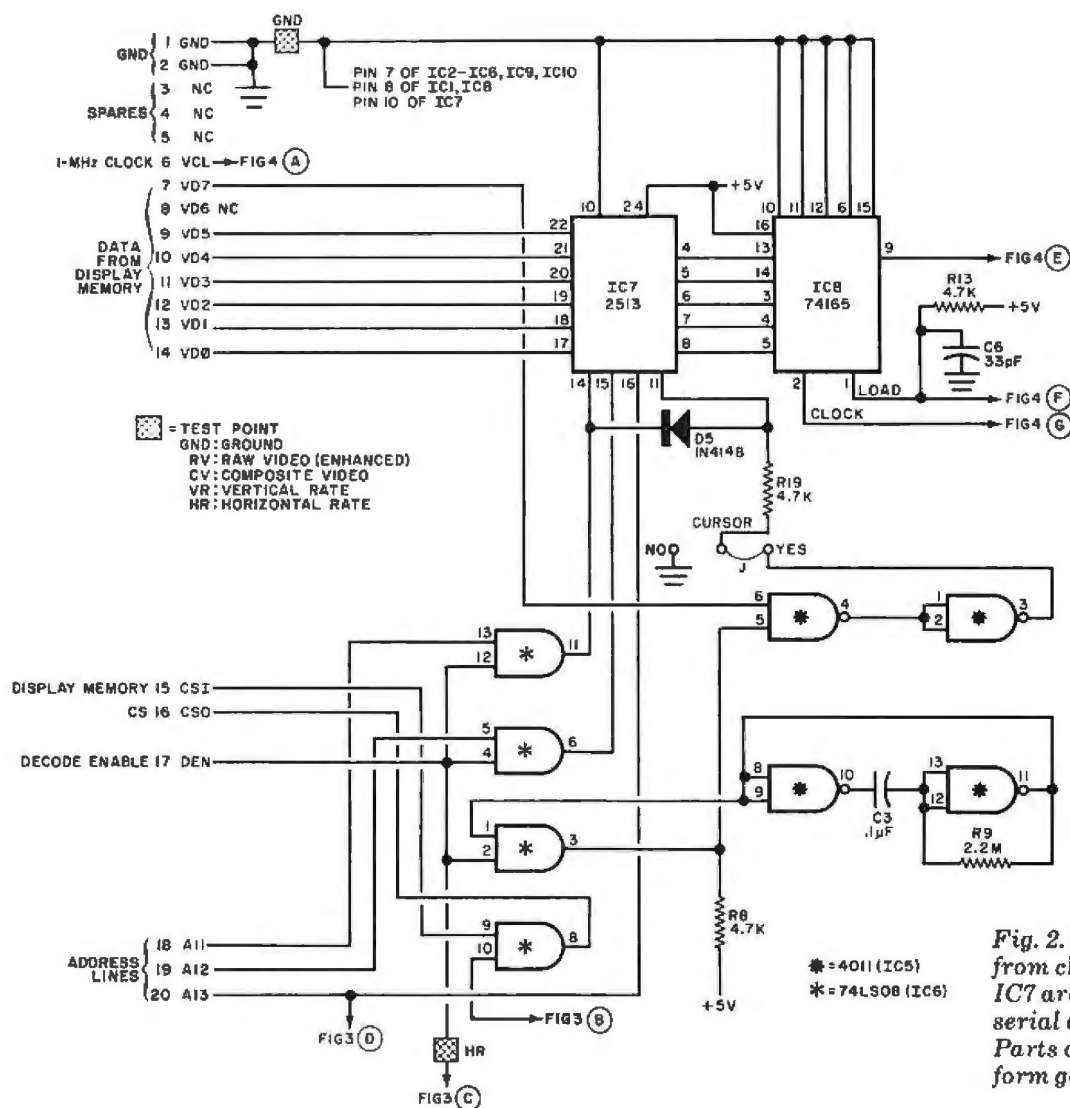


Fig. 2. Parallel outputs from character generator IC7 are converted into serial data in IC8. Parts of IC5 and IC6 form gating circuits.

Other systems will require software and microprogramming translation for their particular machine languages.

In this first of a two-part article, we will cover the hardware and construction details for the TVT-6. Next month, we will cover debugging, some useful software for the system, and provide instructions on how to couple the TVT-6 to other microprocessors.

Circuit Operation. A block diagram of the TVT-6, as used with the KIM-1 system, is shown in Fig. 1. The complete schematic diagram of the video system is shown in Figs. 2 through 4.

As shown in Fig. 1, bits ϕ through 6 from the "upstream tap" on the KIM display memory drive character generator IC7 whose blanking and formatting are helped along by the AND gates in IC6. The cursor bit (bit 7) is stripped off the upstream tap and routed to cursor blinker IC5, which introduces a blinking cursor into the character generator's enable input.

The parallel outputs from IC7 go to

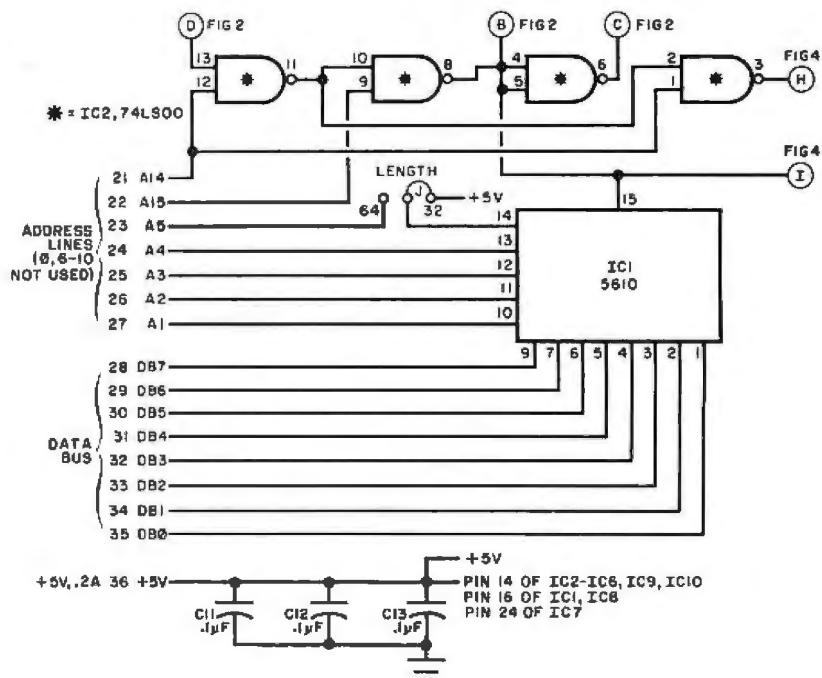


Fig. 3. New SCAN instruction uses PROM IC1, which also has the line length option in its circuit.

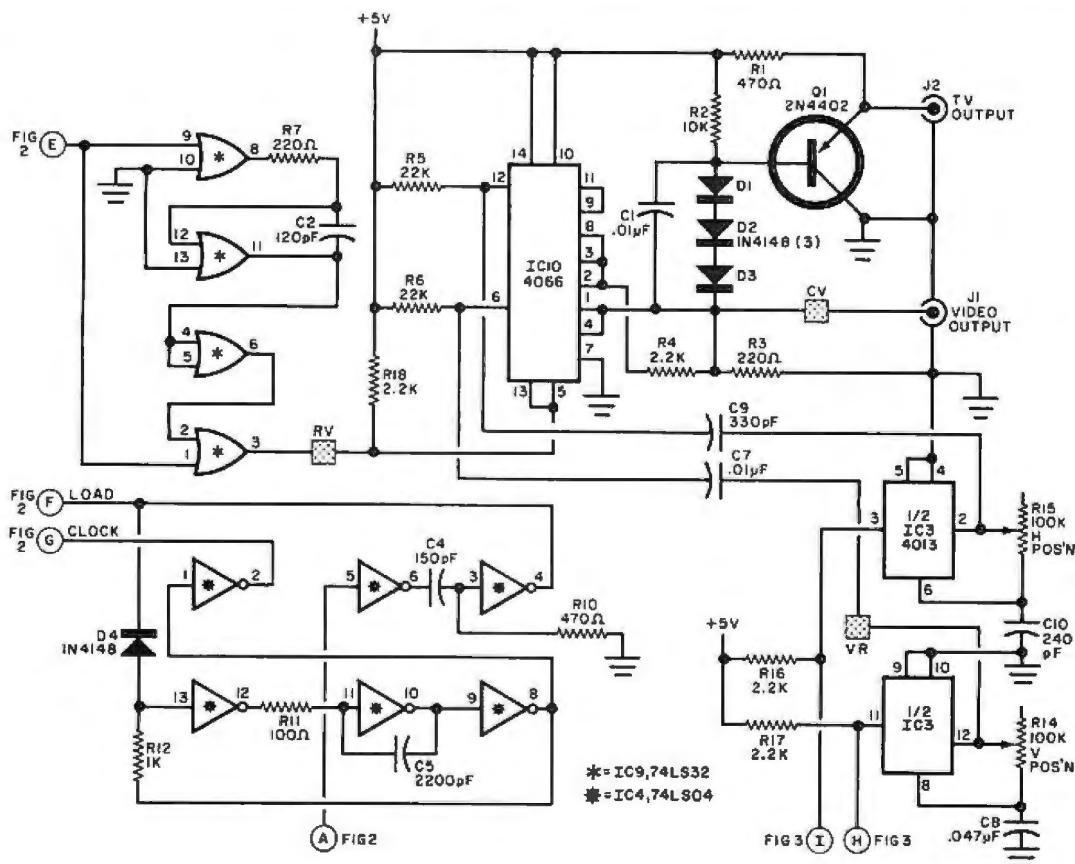


Fig. 4. Video combiner (IC10), offset generator (Q1) and sync delay circuits deliver video to TV. Gated clock (IC4) controls parallel-to-serial converter.

C1, C7—0.01- μ F Mylar capacitor
C2—120-pF polystyrene capacitor
C3, C11, C12, C13—0.1- μ F Mylar capacitor
C4—150-pF polystyrene capacitor
C5—2200-pF polystyrene or Mylar capacitor
C6—33-pF polystyrene capacitor
C8—0.047- μ F Mylar capacitor
C9—330-pF polystyrene capacitor
C10—240-pF polystyrene capacitor
D1 through D5—IN4148 silicon diode
IC1—IM5610 32 \times 8 PROM (or similar)
IC2—74LS00 quad tri-state NAND gate IC
IC3—4013 dual-D flip-flop IC
IC4—74LS04 hex inverter IC
IC5—4011 quad NAND gate IC
IC6—74LS08 quad AND gate IC
IC7—2513 character generator (must be single-supply type, such as General Instruments No. RO-3-2513)

PARTS LIST

IC8—74165 PISO shift register
IC9—74LS32 quad OR gate IC
IC10—4066 quad analog switch IC
J1, J2—Pc-mount phono jack (Molex No. 15-24-2181 or similar)
Q1—2N4402 or MPS6523 (Motorola) transistor
The following resistors are 1/4 watt, 10% tolerance:
R1, R10—470 ohms
R2—10,000 ohms
R3, R7—220 ohms
R4, R16, R17, R18—2200 ohms
R5, R6—22,000 ohms
R8, R13, R19—4700 ohms
R9—2.2 megohms

R11—100 ohms
R12—1000 ohms
R14, R15—100,000-ohm pc-type (upright) potentiometer
Misc.—Sockets for IC's (seven 14-pin, two 16-pin, one 24-pin); 36-contact edge connector with 0.156" centers (Amphenol 225 or similar); solid hook-up wire for jumpers; insulated sleeving; test-point terminals (5); solder; etc.

Note: The following items are available from PAIA Electronics, Box 14359, Oklahoma City, OK 73114: No. PV1-1PC printed circuit board for \$5.95; complete kit of all parts, No. PV1-1K, for \$34.95 (specify blank or KIM-1 programmed IC1); KIM-1 coded cassette, with programs, No. PV1-ICC, for \$5.00. All prices postpaid.

shift register IC8, where they are converted into a serial video signal. The clock and load commands for IC8 come from gated oscillator IC4, which derives its signals from the microcomputer's clock. It is important that the correct clock phase be selected to permit the loading of IC8 to occur when the output of the character generator is valid and settled. This is phase 2 in the KIM-1. (If you are using a different μ P based computer, check this detail.)

The serial video from IC8 goes to the TV Bandwidth Compensator in IC9, which predistorts the video by delaying the video output and OR'ing it against itself. This widens the vertical portions of all characters to generate clean and crisp characters that require minimum bandwidth. The amount of widening is determined by C2 (Fig. 4). The optimum value of C2 is obtained when the generated M or W in the video display just barely closes.

The vertical and horizontal timing signals from IC2 in the gating circuit are delayed by IC3. The display positioning can be varied by potentiometers R14 and R15. The vertical and horizontal sync signals are combined with the enhanced video from IC9 into video combiner IC10. The output from IC10, available at J1, is composite video, with the sync tips at ground, black at 0.4 volt, and white at 1.6 volts. This output can be used to drive conventional video moni-

tors and converted TV receivers. The video output from IC10 is also fed to Q1, which is offset to deliver a +4-volt output for the white level. This output, available at J2, can be connected directly to the first video amplifier of most transformer-powered solid-state TV receivers (see box for details) without requiring biasing, coupling, or translation circuits.

Two options are provided with the TVT-6, both of which are jumper selected. The LENGTH option allows a choice of either 32 or 64 characters/line. The CURSOR option gives the choice of either no cursor or allows the cursor to be displayed under software control.

Construction. The actual-size etching and drilling guide for the printed circuit board used in the TVT-6 is shown in Fig. 5, along with the component-installation diagram. Start assembly by installing and soldering into place the 21 jumpers and test points. (Note that insulated sleeving must be used on two of the long jumpers.) Install the IC sockets, resistors, capacitors, diodes, jacks, and position controls R14 and R15. Do not install the IC's at this time. The correct IC installation sequence and the waveforms to be observed will be discussed in Part 2 next month.

Computer Interface. Detailed in Table I are the requirements of each of the edge connector contacts on the TVT-6 and how to use each contact. Table I also contains the KIM-1 interface connection instructions. The interface consists of adding a new connector and making some add-on connections. One circuit board trace is cut on the KIM-1's pc board to permit an optional change-over switch (or jumper) to be added to the microcomputers. This permits KIM-1 to be used with or without the TVT-6.

General Operation. Since most of today's TVT circuits are used with a microprocessor or microcomputer, it is best to do as much of the display control as possible with the microprocessor and some software. What may not be obvious is that almost all of the timing in the system can also be done using the microprocessor. All this takes is a few dozen words of code.

The four key secrets of operation for the TVT-6 are:

1. Carefully choose how the address lines are defined for TVT operation.
2. Add a new instruction, which we call SCAN, to rapidly address 32 or 64 sequential memory locations.
3. Permanently connect an upstream

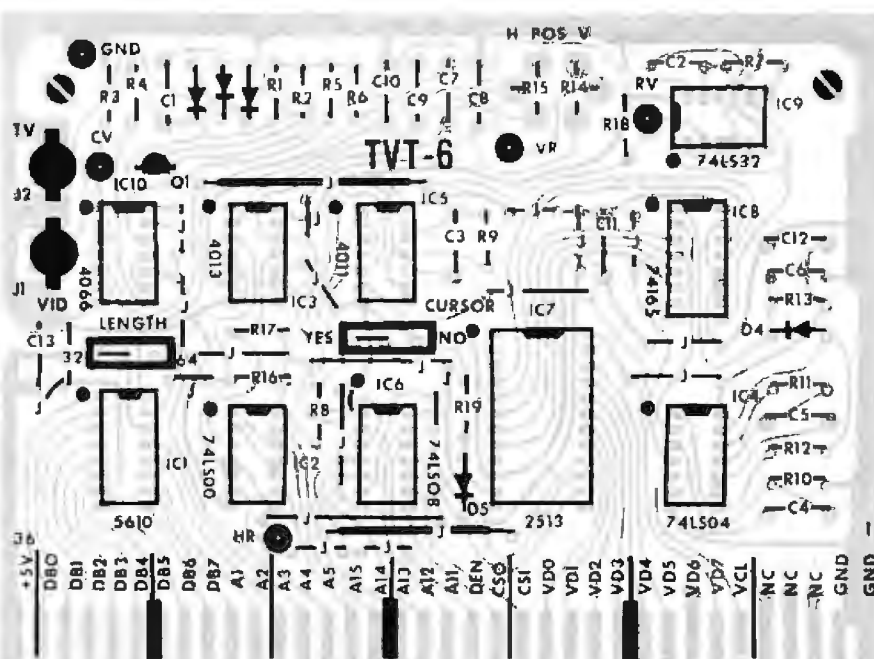
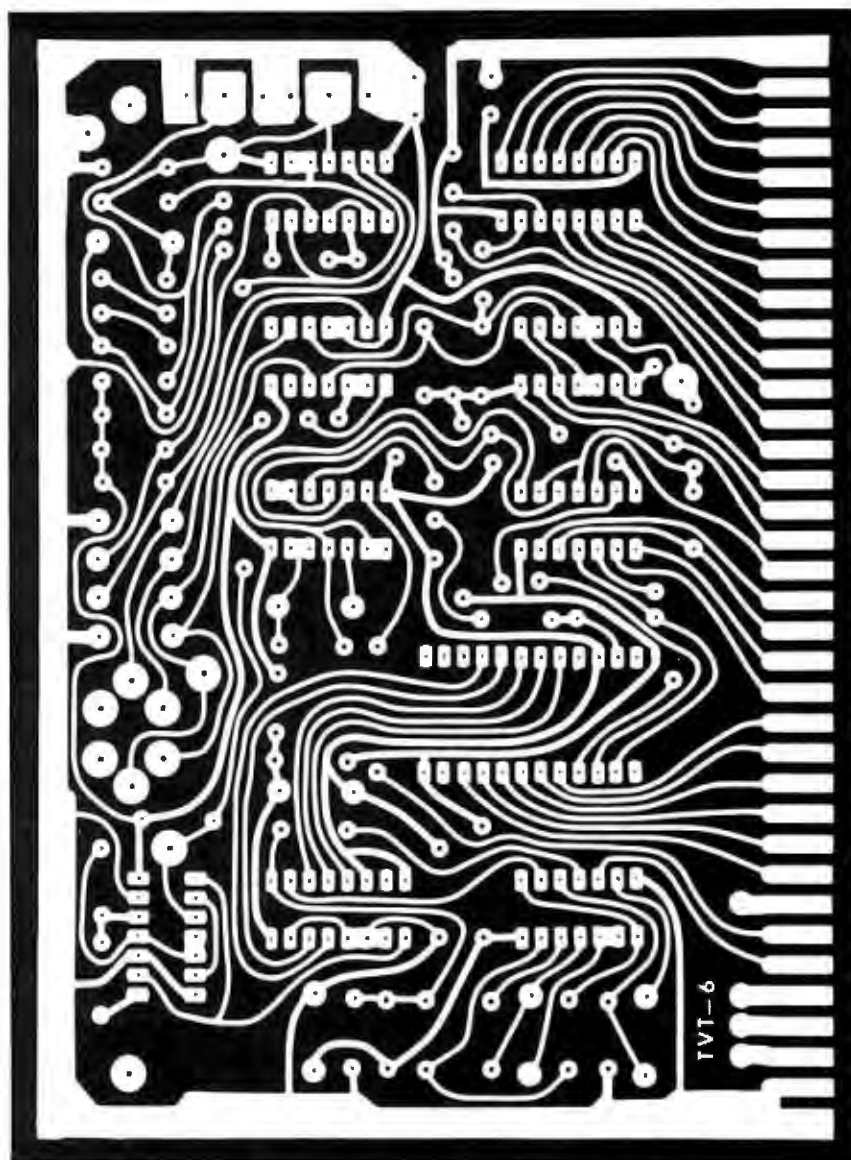


Fig. 5. Actual-size foil pattern (top) and component installation (below). Use sockets for all IC's. Edge connectors go to KIM-1.

TABLE I
TVT-6 PINOUT AND KIM-1 INTERFACE

TVT-6 CONTACT	NAME	REMARKS	A4, A3, A2, A1	R (A13) S (A14) T (A15) F (A5) E (A4) D (A3) C (A2) B (A1)	20 21 22 23 24 25 26 27
1,2	GND	Heavy wire to expansion contact 22 or similar point in KIM-1			
3, 4, 5	NC	Spares			
6	VCL	1-MHz clock from expansion contact U(φ2). (In other systems clock phase must be selected so that load pulse arrives when CG is valid.)			
7,8,9,10, 11,12,13, 14	VD7, VD6, VD5, VD4, VD3, VD2, VD1, VDφ	Data output from memory display; drives character generator. For KIM-1 to display any part of pages 00 through 03, connections must be made as follows: TVT-6 contact: to pin 12 of KIM-1 IC: 7 U5 8 U6 9 U7 10 U8 11 U9 12 U10 13 U11 14 U12	28, 29, 30, 31, 32, 33, 34, 35	DB7, μP data bus; tri-state active high from IC1 during active scan, not used at other times. DB6, Connections to KIM-1 expansion: DB5, KIM-1 contact: to TVT-6 contact: DB4, 8 (BD7) 28 DB3, 9 (DB6) 29 DB2, 10 (DB5) 30 DB1, 11 (BD4) 31 DBφ 12 (DB3) 32 13 (DB2) 33 14 (DB1) 34 15 (DBφ) 35	
15	CSI	Display memory chip select from μP; negative logic OR combined with TVT-6 chip select. From pin 1 of U4 on KIM-1.	36	+5V	Regulated +5-volt (200-mA) power bus; should be heavy wire. From KIM-1 expansion contact 21 or similar point to contact 36 in TVT-6.
16	CSO	Display memory chip select source; enables display memory when either TVT-6 is active or contact 15 is low. Goes to pin 13 of U5 through U12 in KIM-1 when displaying any part of pages 00 through 03. Existing Kφ connection in KIM-1 must be broken.			
17	DEN	Decode enable; goes low when μP is operated in normal mode, high when TVT-6 is doing an active scan. Goes to KIM-1 Applications contact K. Any external ground on applications contact K should be removed.			
18,19,20, 21,22,23, 24, 25, 26, 27	A11, A12, A13, A14, A15, A5	Address inputs from μC, positive true. Addresses Aφ, A6 through A10 not sent to TVT-6. Connections to KIM-1 expansion: KIM-1 contact: to TVT-6 contact: N (A11) 18 P (A12) 19			

Note: KIM-1 conversion consists of breaking one foil trace and adding a new 36-pin socket (Amphenol 127 or similar). Connection to be broken originates as Kφ (pin 1 of U4). Routing of Kφ that goes to memory chip select pin 13 of U5 through U12 should be broken. Other Kφ connections, such as that to pin 1 of U16 should remain intact. Any external ground connections to Application connector contact K (decode-enable) must be removed. All wiring should be made with a wiring pencil.

When KIM-1 is used *without* displaying video, it will behave normally and transparently as long as TVT-6 is plugged in and addresses 8000 through DFFF are not used. To restore KIM-1 operation with TVT-6 out of socket, or to use available addresses for other programs, jumper pin 15 to pin 16 and separately jumper pin 1 to pin 17 in the KIM-1. Note that this jumpering is to be done only when TVT-6 is out of its connector. If you wish, a dpdt changeover switch can be added to perform the jumpering. Switch positions should be changed only when power is off.

memory tap to the character generator and display circuit.

4. Create special software that will allow TVT-6 scanning.

All 16 address lines are used, as assigned as shown in Fig. 6A for a 32-character/line system or as shown in Fig. 6B for a 64-character/line system. Address A15 is the horizontal sync pulse and the key to jumping to the new SCAN instruction. This pulse is followed in descending address order by the vertical sync (A14) and three lines (L4, L2, L1) that produce the "what row of dots do we want?" information for the character generator. The lower address lines are used to select a page of display memory and to select the character that goes into any particular horizontal and vertical location on the display.


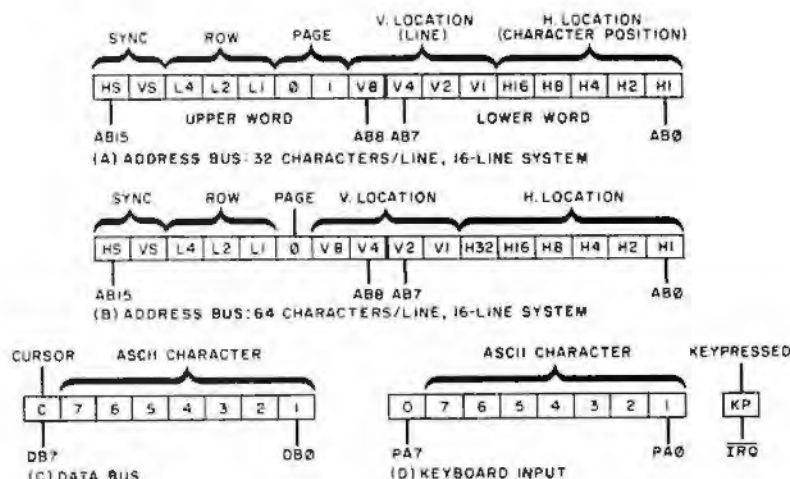


Fig. 6. Bus definitions as used with the TVT-6. All 16 address lines are used as described in text.

DIRECT-VIDEO INPUT CONVERSION

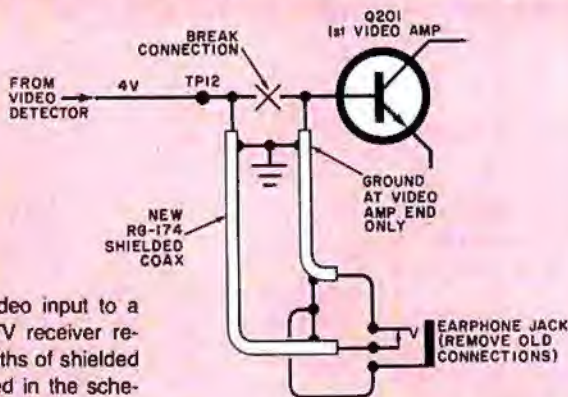

Adding a TVT-6 direct-video input to a small-screen solid-state TV receiver requires only two short lengths of shielded coaxial cable, as illustrated in the schematic. (Important Note: Do not use a hot-chassis TV receiver! Make absolutely certain that the TV receiver you use is transformer powered from the ac line.) The conversion circuit shown here is for the Sears No. 562-50260500 (Sams Photo-fact No. 1565-1). Other TV receivers can be modified in a similar manner.

The earphone jack in the circuit provides automatic changeover from normal receiver performance to video access. Correct bias is provided by TV output of the TVT-6. As an option, you can defeat the sound trap in the Sears TV receiver by lifting one end of capacitor C201.

interrupt and reset vectors on the KIM-1 so that the operating system will work compatibly and properly with the new SCAN instruction.

There are many possible codings for the SCAN program with the limitation that the last address is a return-to-subroutine (RTS) instruction. The obvious choice of NOP or EA runs at only half speed and can't be used. Of the three dozen instructions that operate at full speed, the choice of LDY is the one that does not disturb the accumulator or its flags. This adds flexibility to other programs. The Y register can be viewed as a write-only memory in the SCAN software and we can think of the whole SCAN instruction as a group of double-speed fetch-but-don't-execute instructions. Theoretically, a 64-word PROM would be required for a 64-character line, but this can be overcome by ignoring address A0 and changing the PROM's address every second cycle of the machine.

The data within the machine (see Fig. 6C) uses the lowest seven bits as ASCII character storage. This is arranged by putting the least-significant ASCII character bit in the least-significant data slot, and so on up through the more significant bits. The eighth data bit (DB7) is reserved for a cursor. If DB7 is a zero, a character is displayed, while if it is a one, a cursor box is optionally displayed.

The existing KIM-1 keypad can be used as an ASCII keyboard for many applications, particularly for setup and debugging. If you wish to add an external ASCII keyboard and encoder, connect it to the KIM-1's parallel interface A, following the assignments shown in Fig. 6D. The seven ASCII bits go to the seven low-order data lines, while PA7 is hard wired for a zero. The keypress, or strobe, signal from the keyboard must pull the IRQ (interrupt request line) to ground for 10 μ s to enter a character or machine command.

The truth table for PROM IC1 is shown in Fig. 1. This truth table stores the SCAN instruction, activated by addresses 8000 through DFFF. When IC1 is enabled, it causes the microprocessor's program counter to appear on the address lines for 32 or 64 consecutive scans that advance one count per microsecond. This automatically and sequentially addresses the display memory and produces exactly the data needed for a horizontal scan of TVT characters. The scan instruction runs at least twice as fast as the microprocessor normally moves, which is the key to TVT timing with a microprocessor.

To use the SCAN instruction, jump to a subroutine whose starting address is within the 8000 to DFFF range. For example, if you call JRS 8200, the SCAN instruction will deliver a horizontal sync pulse and initiate operation on the top row of characters, starting with the first character on page 2. After a selected 32

Upstream Tap. The SCAN instruction will sequentially address 32 or 64 memory slots per horizontal scan line at a rate of one-per-clock cycle (1 μ s). These addresses are presented to the entire memory in the computer, including the memory to be displayed. However, during the display times, the SCAN instruc-

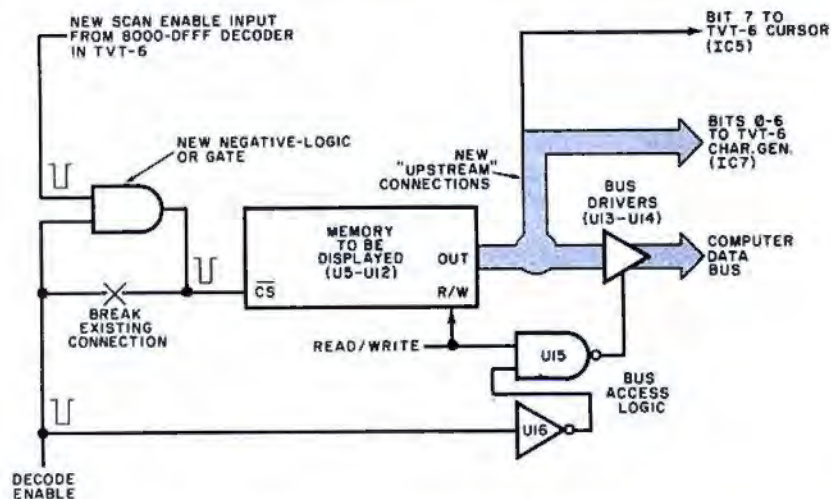


Fig. 7. Adding the upstream tap to the memory to be displayed.

or 64 characters, the SCAN instruction automatically jumps back to the main program.

The SCAN instruction can be viewed as a "portable subroutine" because it readily moves around to automatically output the correct page and character generator's row information, starting with an easily computed JSR address. Addresses above DFFF will not activate the SCAN instruction. This includes the

tion and its PROM have control of the data bus so that the display memory (or anything else) cannot output information to the data bus.

The upstream tap is added as shown in Fig. 7. This tap is always outputting information to the character generator in the TVT-6. The output information is present even (and especially) when the display memory data bus drivers have been inactive. ◇

From: Nagasaki Radio
Nagasaki Japan
OCT 26th 1975

To: Mr. Harry L. Helms, Jr.

QSL
NAGASAKI
JOS
JOR
JOU
JDB
RADIO
JAPAN

Thank you for your QSL report.
Your details are confirmed!

C. Iwasaki, radio operator
of Nagasaki radio

TABLE OF OPERATION HOUR ON HIGH FREQUENCY

CALL SIGN	Power (kW)	FREQ (MHz)	OPERATION HOUR (GMT)
JOS 3	4.128		
JOS 3	4.491.5		
JOR 10	8.521.4		
JOS 3	8.796		
JOR 10	13.002		
JDB 15	13.051		
JOS 3	13.052.5		
JOU 15	13.092		
JOS 3	16.333.2		
JOU 15	16.939.2		
JOR 10	17.093.6		
JDB 15	17.215		
JOS 3	22.396		
JOR 10	22.403		
JOU 15	22.440		
JDB 15	24.575		

JOS, JOR, JOU, JDB (Nagasaki Radio) acknowledges reception with informal QSL which lists call signs, power (kW), frequency (kHz), and operating hours (GMT).

BY HARRY L. HELMS, JR.

END THAT "UTILITY FUTILITY"

DXing CW without knowing Morse code

If you're like a lot of SWL's, you're not getting full use of your shortwave receiver. You DX the international and tropical broadcasting bands for sure, and you probably eavesdrop on the amateurs, broadcast band, and international radiotelephone circuits from time to time. But what about those CW stations—Morse code. Tune outside the broadcasting bands and you'll find scads of those dit-dah stations dotting and dashing away around the clock. Have you ever tried your hand at DXing these stations?

Prime DX lurks in the CW utility bands! Countries such as Iceland, Bermuda, Barbados, and the Canal Zone are missing from many SWL logbooks because they are extremely difficult to hear on the broadcasting bands. But these countries and others are active. They're often heard on the CW utility bands, and they readily verify reports as well!

"But I don't know CW," you may protest. If that's all that has prevented you from DXing the dah-dit stations, *relax*. For the simple fact of the matter is that you don't have to know the code to DX and verify CW stations!

Markers Make it Easy. There's nothing magical about DXing CW stations if you don't know the code. CW stations offer a ready-made DX aid in the *marker transmission*, which is a repeated taped transmission used by a CW station to establish contact or to hold

onto a frequency while waiting for traffic.

Marker transmissions often follow this general format: the tape starts with a series of the letter "V" (VVV VVV VVV, etc.) or a series of CQs (CQ CQ CQ, etc.). This is almost certainly followed by "DE," which is French for "from." Next comes the station callsign, usually repeated three times. Thus, typical marker transmissions read something like this: "VVV VVV VVV DE WXX WXX WXX" or "CQ CQ CQ DE WXX WXX WXX." The marker often contains additional items, such as the Q-code abbreviations "QRU?" ("Do you have anything for me?") or "QSX" (I am listening on

_____). And often you will hear the letters "K," "SK," or "AR" sent at the end of a marker. All three are generally used to denote the end of the text of the marker. Thus you're likely to hear a marker running something like this: "VVV VVV VVV DE WXX WXX WXX QRU? QSX 6 8 12 MHZ AR." Translated, this means that station WXX is not busy at the moment and is asking listening stations if they have any traffic for WXX, and that WXX is listening on the 6, 8, and 12-MHz utility bands for a reply.

How can one translate those dits and dahs into readable letters if one doesn't know CW? The secret lies in the fact

PRIME MARITIME CW DX BANDS

4231-4361 kHz	12689-13170.5 kHz
6345.5-6514 kHz	16917.5-17255 kHz
8459.5-8728.5 kHz	22374-22624.5 kHz

CW MARKER ABBREVIATIONS & CODES

VVV	General opening for a marker; usually sent in a series of three
CQ	General call to any station, often used to start marker
DE	French for "from," precedes station callsign.
QRU?	Do you have any traffic for me?
QRX	I will call on the frequency of _____
QSX	I will be listening on the frequency of _____
QSY	I am changing frequency to _____
K	At end of marker, denotes end of message
AR	Same as K, meaning end of message
SK	Station work completed

COMMONLY HEARD FOREIGN CW STATIONS

4352	NBA	Balboa, Canal Zone
6376	VPN	Nassau, Bahamas
6379	8PO	St. Philip, Barbados
6383	EAD	Madrid, Spain
6386	HKC	Buenaventura, Colombia
6393	ZLO	Waiouru, New Zealand
6439	OXZ	Lyngby, Denmark
6446	OXZ	Lyngby, Denmark
6463	HKB	Barranquilla, Colombia
6464	VIS	Sydney, Australia
6467	JCS	Choshi City, Japan
6470	IAR	Rome, Italy
6487	VRT	Bermuda
6491	PJC	Willemstad, Curacao
6491	JOS	Nagasaki, Japan
6512	TFA	Reykjavik, Iceland
8472	NMR	San Juan, Puerto Rico
8479	JCU	Choshi City, Japan
8481	VIS	Sydney, Australia
8483	DAN	Hamburg, West Germany
8511	DAL	Hamburg, West Germany
8521	VIS	Sydney, Australia
8523	JOR	Nagasaki, Japan
8530	IAR	Rome, Italy
8574	HKC	Buenaventura, Colombia
8598	OXZ	Lyngby, Denmark
8647	JDC	Choshi City, Japan
8666	OXZ	Lyngby, Denmark
8666	HKB	Barranquilla, Colombia
8666	HKC	Buenaventura, Colombia
8670	IAR	Rome, Italy
8682	EAD	Madrid, Spain
8686	JCT	Choshi City, Japan
8690	TFA	Reykjavik, Iceland
8694	PJC	Willemstad, Curacao
8710	VPN	Nassau, Bahamas
8718	8PO	St. Philip, Barbados
8718	VRT	Bermuda
8726	NMR	San Juan, Puerto Rico
12709	8PO	St. Philip, Barbados
12709	VRT	Bermuda
12718	NMR	San Juan, Puerto Rico
12832	DAF	Hamburg, West Germany
12943	ZLO	Waiouru, New Zealand
12952	VIS	Sydney, Australia
13065	EAD	Madrid, Spain
13069	TFA	Reykjavik, Iceland
17170	PJC	Willemstad, Curacao

that a marker is repeated for several minutes at a time, usually at a code speed considerably below that normally used, and the message is the same each time it is repeated. In fact, you may find some markers repeated for hours at a stretch. Thus, you need persistence and patience to bag CW DX, not code proficiency.

Your task will be greatly simplified if you have some form of tape recorder, either reel-to-reel or cassette. If you do, it helps to record several minutes of the marker. If you don't have a tape recorder, you can still log CW stations, but

The Overseas Telecommunications Commission (Australia) has pleasure in confirming your reception of the following transmission:

SERVICE: MARITIME MOBILE
CALL SIGN: VIS 3

EMISSION: A1

TRANSMITTER POWER: 1 KW

AERIAL TYPE: DELTA MATCHED DIPOLE


AERIAL BEARING:

FREQUENCY: 6464 KHz

O.T.C. and Australian national body responsible for telecommunications services between Australia and other countries, and between Australia's external territories and shipping, thanks you for your report on its transmission and conveys best wishes.

Signed for O.T.C.

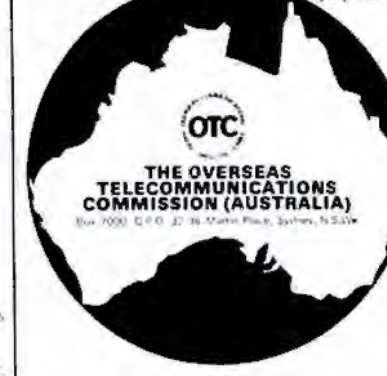Your report of reception heard on 18/8/75



The Overseas Telecommunications Commission (Australia) sends this QSL with service, call sign, emission, transmitter power, antenna type, and frequency as part of the confirmation of one of its transmissions.

you'll have to work quickly and accurately. With practice, you'll find that it will only take a couple of minutes, even without the aid of a tape recorder.

The Morse code is a language of sound, with only two sounds to learn: the dit (a short, staccato sound) and the dah (approximately three times as long as the dit and drawn out). Forget all about dots and dashes—those are relics left over from the days of landline telegraphy—and also forget any visual code table you may have memorized. On radio, CW is sound.

Learn to recognize the "V" or "CQ" series that open markers by their sound in CW. A "V" comes out as "didididah" and "CQ" sounds like "dahdidahdit dah-dahdidah." Memorize these sounds and practice them by repeating them to yourself or by whistling those sounds. Using this technique, you'll be able to recognize the "V" or "CQ" that indicates that you're hearing a marker. Listen carefully to the transmissions that follow the opening. Is it repeated over and over? If

so, turn on your tape recorder, get a pencil and paper, and grab the code table that accompanies this article. We are now going to end your utility futility!

The next thing you are likely to hear after the "V" or "CQ" series are the letters "DE," explained earlier. In CW, they make the sounds "dahdidit dit," and should be memorized along with "V" and "CQ." The call letters of the station are almost invariably next. Concentrate on getting the first letter. As soon as you hear it, look on our code sound table until you find the letter that matches the sound. As an example, suppose that the first sound you hear following "DE" is "didahdah." As soon as you hear it, concentrate on the sound, perhaps by repeating it to yourself—"didahdah, didahdah . . ."—until you locate it on our code table. In this case, you'll find that "didahdah" represents the letter "W." So you'll now have the first letter in the station's call. Repeat this process with the next letter, and the next, until you have the station's complete call sign.

TRT Telecommunications Corporation

Thank you for your reception report of our signals on 8526 KHz

as reported by you on 3/2/75

We appreciate your interest.

Robert F. Kern

Traffic Supervisor

D411 (4-73)

Stamp

**Mr. Harry Nelson, Jr.
115 West LeRoy Street
Fort Mill, S.C. 29715**

TRT Telecommunications Corporation acknowledges reception by confirming the transmitting frequency on the day and date.

This may sound like a long and tedious process, and it may be so at first. But after a little practice you'll be able to copy the complete text of the marker within minutes. If you have trouble with the code sounds, try adjusting your receiver's beat frequency oscillator (BFO) for a different pitch.

Verifications. It's a snap to prove to the CW utility station that you heard them. Simply copy the complete text of the marker transmission and report in the usual manner. Normally it's a no-no under international law to repeat the details of a utility station transmission. Fortunately, markers are an exception. Include the date and time in GMT. Avoid using common reporting codes such as SINPO and SINFO. Plain English will do fine. Make particular note of any hum or frequency shifting of the signal.

Estimate the frequency as best you can. If you are one of those fortunate SWLs with direct-frequency readout receivers, this is no problem. But if you're like most of us and use a general cover-

CW CHART BY SOUND

A didah
B dahdidit
C dahdidahdit
D dahdidit
E dit
F dididahdit
G dahdahdit
H dididit
I didit
J didahdahdah
K dahdidah
L didahdidit
M dahdah
N dahdit
O dahdahdah
P didahdahdit
Q dahdahdidah
R didahdit
S dididit
T dah
U dididah
V didididah
W didahdah
X dahdididah
Y dahdidahdah
Z dahdahdidit
1 didahdahdahdah
2 dididahdahdah
3 didididahdah
4 dididididah
5 didididit
6 dahdididit
7 dahdahdidit
8 dahdahdahdit
9 dahdahdahdahdit
0 dahdahdahdahdah
? dididahdahdit
/ dahdididahdit
• didahdidahdah

WHERE TO SEND CW DX RECEPTION REPORTS

KFS, ITT World Communications, Box 56, Half Moon Bay, Calif. 94019
KHK, RCA Global Communications, 223 S. King St., Honolulu, Hawaii 96804
KLB, ITT World Communications, 3620 Old Hiway 99, Marysville, Wash. 98270
KOK, ITT World Communications, 18500 S. Bloomfield Ave., Cerritos, Cal. 90701
KPH, RCA Global Communications, 135 Market St., San Francisco, Calif. 94105
WAX, TRT Telecommunications, Box 8876, Fort Lauderdale, Florida 33310
WCC, RCA Global Communications, Box 397, North Chatham, Mass. 02650
WLO, Mobile Marine Radio Inc., Box 743, Mobile, Alabama 33601
WMH, Dundalk Marine Terminal, 2700 Broening Highway, Baltimore, Maryland 21222
WNU, TRT Telecommunications, P. O. Drawer E, Pearl River, Louisiana 70452
WNY, RCA Communications Inc., 60 Broad St., New York, NY 10004
WOE, RCA Communications Inc., 8580 Lawrence Rd., Lake Worth, Florida 33460
WPA, RCA Global Communications, Box 1328, Port Arthur, Texas 77640
WSC, RCA Global Communications, Box 34, West Creek, New Jersey 08092
WSL, ITT World Communications, Mackay Marine Div., Amagansett, New York

COMMONLY HEARD AMERICAN CW STATIONS

4247	KPH	San Francisco, Calif.
4274	KFS	Palo Alto, Calif.
4283	KOK	Cerritos, Calif.
4310	WNU	Slidell, Louisiana
4322	WPA	Port Arthur, Texas
4331	WSC	Tuckerton, New Jersey
4346	WMH	Baltimore, Maryland
4349	KLB	Marysville, Wash.
6376	WCC	Chatham, Mass.
6390	WAX	Ojus, Florida
6411	KLB	Marysville, Wash.
6411	WOE	Lantana, Florida
6435	WPA	Port Arthur, Texas
6463	KOK	Cerritos, Calif.
6477	KPH	San Francisco, Calif.
6495	WNU	Slidell, Louisiana
6502	WSC	Tuckerton, New Jersey
6519	WNY	New York, New York
8486	WOE	Lantana, Florida
8502	WMH	Baltimore, Maryland
8514	WSL	Amagansett, New York
8526	WAX	Ojus, Florida
8542	KHK	Honolulu, Hawaii
8558	KFS	Palo Alto, Calif.
8570	WNU	Slidell, Louisiana
8582	KLB	Marysville, Wash.
8586	WCC	Chatham, Mass.
8590	KOK	Cerritos, Calif.
8610	WSC	Tuckerton, New Jersey
8618	KPH	San Francisco, Calif.
8630	WCC	Chatham, Mass.
8642	KPH	San Francisco, Calif.
8658	KLB	Marysville, Wash.
8658	WSL	Amagansett, New York
8686	WMH	Baltimore, Maryland
8714	WLO	Mobile, Alabama
12808	KPH	San Francisco, Calif.
12844	KFS	Palo Alto, Calif.
12925	WCC	Chatham, Mass.
12993	KOK	Cerritos, Calif.
12997	WSL	Amagansett, New York

age receiver not calibrated so accurately, estimate the frequency to the best of your ability. If you get deeply involved with CW DXing, you may find an external frequency standard that puts out markers every 100 kHz will be a good investment. They often run around \$30 more or less.

It is always wise to include a prepared card with your report. Put the station call and location on the card, along with the date and time the station was heard. If you had to estimate the frequency, leave a space blank for the station operator to include the exact frequency. You might like to leave some space for the station operator to make some remarks, along with a line for a signature and station stamp. Frequently, a station will have its own QSL cards or will send a letter, but a prepared card is the best way to ensure a reply.

Included here is a list of the major CW utility bands. They're mainly used by coastal stations. Also presented is a list of commonly heard stations and the frequencies on which they have been active of late. More complete listings of CW stations can be obtained from Handler Enterprises, Box 253, Deerfield, Illinois 60015 and Gilfer Associates, Box 239, Park Ridge, NJ 07656. You might also be interested in joining a radio club that features coverage of CW DX. Three such clubs are American SWL Club, 16182 Ballard Lane, Huntington Beach, Calif., 92649; Newark News Radio Club, Box 539, Newark, New Jersey, 07101; and SPEEDX, Box E, Elsinore, Calif., 92530. Enclose a self-addressed stamped envelope with your requests for information to these clubs, and you might enclose \$1 if you want to examine a sample bulletin.

TAPE RECORDER HYGIENE

*How to maintain tape recorders and tapes
in peak condition.*

BY CRAIG STARK


A PART from inquiries about specific product recommendations, the subject of most concern to readers is how to care for their recorders and tapes.

In addition to routine household dusting, recorders need two kinds of periodic cleaning: physical and magnetic. The tape has yet to be made that does not shed some of its oxide particles with every playing, and unfortunately these tend to accumulate on tape heads and guides, pressure pads, and the capstan/pressure-roller drive system. If not removed, this debris can cause slippage in the drive mechanism. The resulting wow and flutter is heard as inconstancy or "graininess" in pitch. In addition, the oxide accumulations on the heads cause momentary "drop-outs" in the signal and loss of treble response.

Happily, the solution is as near as a bottle of isopropyl or rubbing alcohol and an ordinary cotton-tipped swab. If the tape you use has a brown surface, the

chocolate-colored band that develops on the black pressure roller is an obvious warning that housekeeping is in order. If the tape you use has a black oxide, you will have to look more closely to see the shiny band that appears. In any case, the build-up of flaked-off oxide particles *must* be removed from *all* parts in the head assembly and anywhere the tape contacts the recorder.

Magnetic Considerations. Though unseen, residual magnetism induced in heads, guides, and capstan represents an even greater potential danger to your tape collection, and preventive or therapeutic treatment is indicated at least as often as physical cleaning. Professional studios "degauss" their machines daily (every 8 to 20 hours of operating time is the usual recommended rule of thumb) to guard against this insidious force. A magnetized component anywhere in the tape path will create some hiss and per-

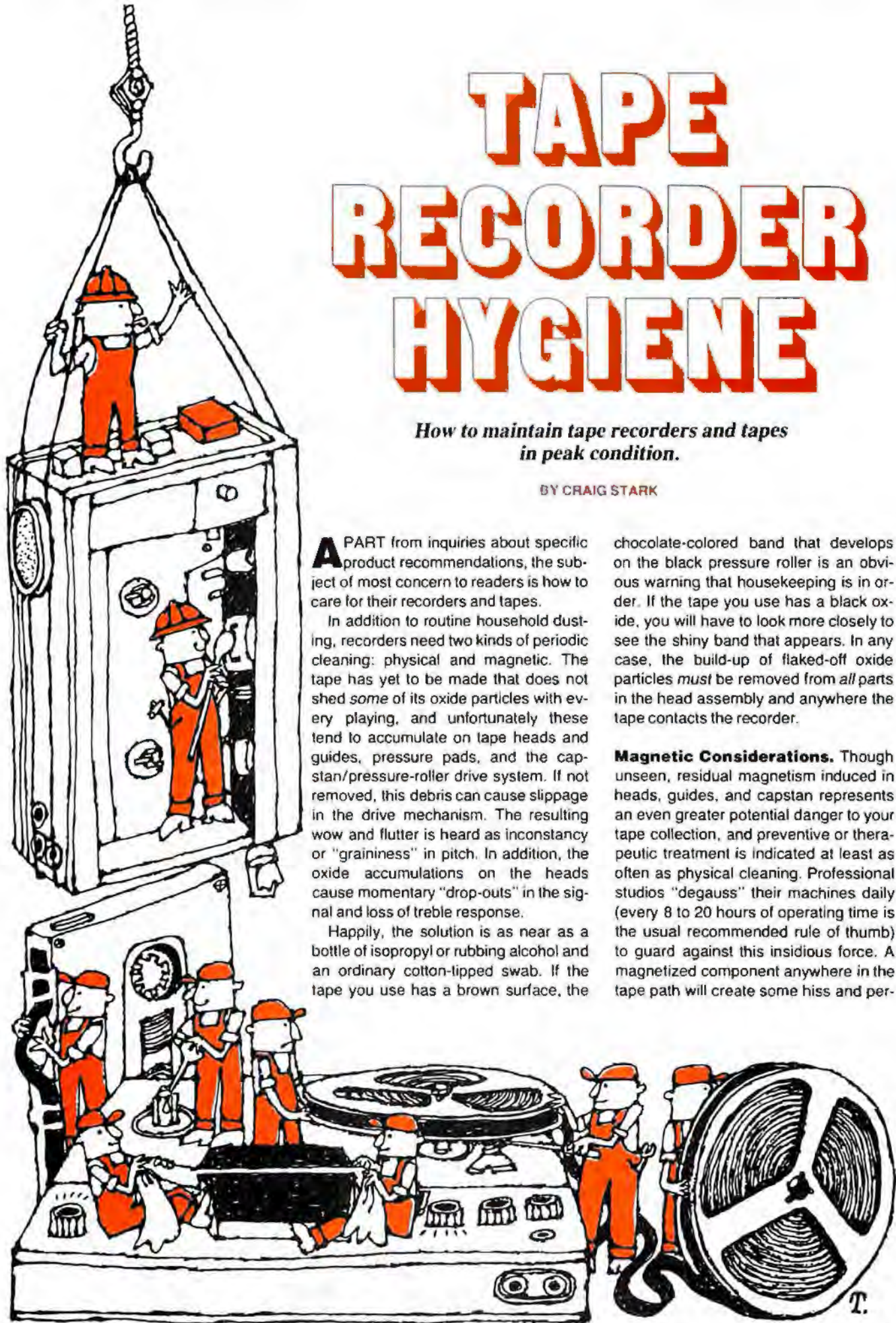

manent loss of high-frequency signal whether you're recording or simply playing back a tape.

Fortunately, head demagnetizers are inexpensive accessories available from all dealers, and using one properly takes less than a minute. Start by turning your recorder off and removing all tapes from the immediate vicinity. Remove the head covers (you should have done this already for the physical cleaning); and, holding the tape-head degausser at arm's length, plug it in, push its "on" button (if it has one), and bring it in close proximity to each of the surfaces that contact the flowing tape. Then, with the demagnetizer still on, withdraw it slowly and smoothly. Turn it off when it is at arm's length from the machine and the job is done. *Note:* to avoid any danger of scratching the tape heads, it is a good idea to put a piece of plastic tape over the tip(s) of the degausser. (Because of differences in physical design, it is not possible to get every tape-head demagnetizer to the heads of every recorder. Check with your dealer to make sure there will be no problem.)

For most audiophiles, lubrication of a recorder is best left to a yearly visit to the service technician. Too much is as great a danger as too little! Obviously, though, bearings and sliding and rotating surfaces must have lubricants. If you want to do the job yourself, follow the manufacturer's instructions carefully.

Caring for Tape. Tape care is no less important. Always keep tapes in their containers when not in use, and put tape reels on edge—not piled atop one another. I recommend the professional practice of leaving tapes in a *played*, not a *fast-wound* condition, for the latter tends not only to create an unevenly wound tape "pack," but also to put internal stresses on the tape layers that may cause damage. For the same reason, it's a good idea to play—not rewind—a tape at least twice a year. Avoid storing tapes next to a radiator, in the immediate vicinity (within 2 to 3 feet) of strong magnetic fields (loudspeakers, motors, or power transformers in hi-fi equipment), or in a car trunk during warm weather. Given proper care, your tapes should outlast their owner!

Accidental erasure, especially of the high frequencies, is something to worry about. I once ruined a \$35 test tape by using a screwdriver, that I didn't know was magnetized, for some head adjustments; and a friend once tearfully played for me a master tape on which his five-year-old had momentarily placed a mag-

net from the kitchen memo board, "to see if it would stick." The magnet didn't, but the once-around blip did.

To assess the potential dangers, I consulted several experts and found they agreed that most fears about accidental damage from magnetic fields—generated by radar, house wiring, home appliances, power transformers, and even loudspeakers—are exaggerated.

The reasons are two formidable-sounding but relatively straightforward factors: "tape coercivity" and "the inverse square law." Coercivity is simply an index of the amount of magnetic energy necessary to erase a tape and is measured in oersteds (Oe). Tapes generally have a coercivity in the 280- to 450-Oe range, but this value is a kind of an average (some oxide particles require more field, some less, for erasure). The consensus among the experts was: a good rule for general tape safety is to keep the absolute peak level of stray fields to less than 10 per cent of the tape coercivity. For ferric-oxide tapes, this amounts to 25 to 30 Oe, and for chromium-dioxide tapes, 45 Oe. One gentleman reported measuring a magnetic field of only 10 Oe at the case of an electric drill, so it surely would be safe to use in the vicinity of most tapes. (In fact, home-appliance motors aren't that different in principle from those used in tape decks.) However, for really critical tapes, it was suggested that external fields should be kept below about 10 and 15 Oe for iron and chrome tapes, respectively, since high frequencies tend to be more easily erased.

The other factor is a function of distance. Even a bulk tape eraser that may generate a powerful 1,000-Oe field measured at a distance of ½ inch measures only one fourth that field at one inch, and one sixteenth at two inches. That's the effect of the inverse square law, and it holds, generally, for magnetic recordings. Thus, even a few inches of separation from potentially damaging fields—magnetic latches on cabinets for example—can prevent signal damage.

You can measure *steady-state* or "permanent" fields (around a speaker cabinet or from magnetized tape heads, guides, and capstans) with an inexpensive (\$6.80) magnetometer from R. B. Annis, 1101 N. Delaware St., Indianapolis, Ind. 46202. Multiply your readings by ten or even a bit more on recorder parts that touch the tape directly. You'll find with speakers that the magnetic "leakage" field varies from model to model and, of course, the point on the cabinet at which it is measured. ◇

Empire's Blueprint For Better Listening

No matter what system you own, a new Empire phono cartridge is certain to improve its performance.

The advantages of Empire are threefold.

One, your records will last longer. Unlike other magnetic cartridges, Empire's moving iron design allows our diamond stylus to float free of its magnets and coils. This imposes much less weight on the record surface and insures longer record life.

Two, you get better separation. The small, hollow iron armature we use allows for a tighter fit in its positioning among the poles. So, even the most minute movement is accurately reproduced to give you the space and depth of the original recording.

Three, Empire uses 4 poles, 4 coils, and 3 magnets (more than any other cartridge) for better balance and hum rejection.

The end result is great listening. Audition one for yourself or write for our free brochure, "How To Get The Most Out Of Your Records." After you compare our performance specifications we think you'll agree that, for the money, you can't do better than Empire.



EMPIRE

Already your system sounds better.

Empire Scientific Corp.
Garden City, New York 11530

An Introduction to Gyrator Theory

*How inductors can be simulated
using resistors, capacitors, and op amps.*

BY BRYAN T. MORRISON

AGYRATOR, believe it or not, is an inductor without any turns of wire. Although the theory behind this interesting circuit has been established for some time, only within the past few years have synthesized inductors been used on a wide scale. Before we examine the gyrator in detail, let's review some basic properties of inductors.

A pure inductance is a circuit element whose opposition to the flow of alternating current (*inductive reactance*) varies directly with frequency. At dc or zero hertz, the ideal inductor has zero ohms of resistance (a perfect conductor) and zero ohms of reactance. Therefore, we can say that it also has zero ohms of impedance—the vector sum of resistance and reactance. However, as we move into the realm of ac, the reactance of an inductor increases according to the formula $X_L = 2\pi fL$; where X_L is measured in ohms; f (frequency) in hertz; and L (inductance) in henries. Its resistance remains zero ohms. At infinite frequency, the inductor has infinite reactance, and will permit no ac to flow.

So far we have been talking about an *ideal* inductor. Actually, every inductor has a certain amount of resistance and capacitance as well as inductance. As shown in Figs. 1A and 1B, an iron-core inductor can be modeled as an inductance in series with a resistance, $R1$; and this combination is in parallel with a capacitance and series resistance, $R2$. An air-core inductor (Figs. 2A and 2B) behaves as an inductance and series resistance $R1$ would. In both cases, L is the inductance of the coil, and $R1$ is the resistance of the wire which comprises the coil. The iron-core inductor contains two additional elements, $R2$ and C , which represent losses within the core. With dc, there are no core losses, and consequently, our model's C permits no current to flow through $R2$. At higher and higher frequencies, core losses increase. Thus, in our model, increased current flows through $R2$ as the capacitor's reactance decreases.

Synthesizing an Inductor. By combining resistors and a capacitor with a

gain stage, we can create a circuit which appears to the "outside world" as a real inductor. To understand how, we will analyze the inductor models (Figs. 1B and 2B) in terms of "port admittance." A *port* is a point through which energy can enter or leave. In the case of an electrical circuit, it can consist of a pair of terminals to which a circuit element is connected. The inductors and their models in Figs. 1 and 2 are ports, and when a voltage source is connected across them, an input voltage (V_{IN}) is applied and an input current (I_{IN}) flows.

Admittance, measured in *mhos*, is the reciprocal of impedance. In other words, admittance is the ratio of current to voltage. If an element's admittance is zero mhos, no current will flow through it no matter how high the voltage is across it. Such an element is a perfect insulator or open circuit. On the other hand, an element with infinite admittance will conduct infinite current, even if a low voltage source is connected across it. It is a perfect conductor or a short circuit. Combining these two terms, port admittance is the ratio of the current flowing into the port (I_{IN}) to the voltage across the port (V_{IN}).

Referring to Fig. 1B, we can see that resistors $R1$ and $R2$ set the limits of port impedance at both very high and very low frequencies. At dc, the admittance of the inductor L is infinite (a short circuit), and only $R1$ limits the current through it. Capacitor C behaves as an open circuit

with zero admittance, so $R2$ is removed from the circuit. At an infinite frequency L is an open circuit and $R1$ is removed from the circuit. However, C is a short circuit and current through it is limited only by $R2$. Between these frequency extremes, L will determine the port's admittance, because it is much larger than C .

The port admittance of the air-core coil at dc is simply the reciprocal of resistance $R1$, since L has infinite admittance. At an infinite frequency, the port admittance is zero, because the inductance acts as an open circuit, and no input current can flow.

Analyzing the Gyrator. Now let's apply these concepts to the gyrator circuits (Figs. 1C and 2C). As in the equivalent circuits, $R1$ represents the ohmic resistance of the coil wire, and C and $R2$ are core losses which increase in step with the applied frequency. However, something new has been added—a gain stage. Any active device can be used, but here we choose an op amp for its simplicity, high gain, almost infinite input impedance, and very low output impedance. The gyrator op amps are strapped for unity-gain, noninverting operation. So, within the frequency limits of the device (assume infinite bandwidth), the voltage at the output is exactly the same as that at the noninverting input.

If we apply a dc voltage across the input terminals of Fig. 1C, capacitor C

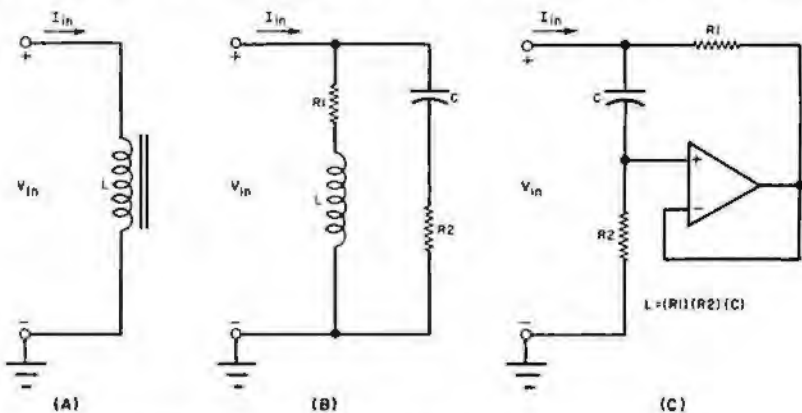


Fig. 1. Iron-core inductor (A) can be modeled as shown in (B) and simulated using the gyrator circuit in (C).

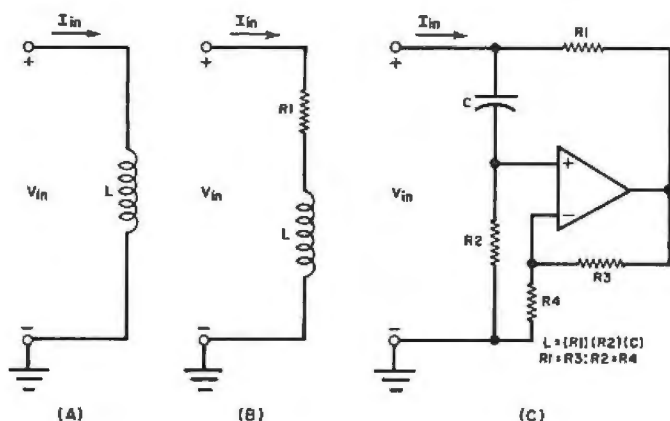


Fig. 2. An air-core coil (A) has an equivalent circuit shown in (B). Op amp gyrator (C) simulates the coil's behavior.

does not conduct, and the voltage at the noninverting input is zero. The output is also at ground potential, and because the op amp has very high output admittance (low output impedance), we can safely say that $R1$ is connected across the port. So, I_{IN} will flow only through $R1$. This agrees with the behaviour of the equivalent circuit of Fig. 1B. The port admittances are maximized at dc, limited only by the values of both $R1$'s (assumed to be equal).

At infinite frequency, C is a short circuit, and therefore the voltage at the op amp's noninverting input (as well as that at the output) is equal to V_{IN} . Since there is no voltage drop across $R1$, it is effectively removed from the circuit. The only admittance path is through $R2$ to

ground, which is the same behavior we noted in the equivalent circuit.

For frequencies between zero and infinity, C and $R2$ act as a high-pass filter, causing less and less voltage drop across $R1$ as frequency increases, and thus less port admittance until $R2$'s limiting effect comes into play. The reactive characteristics of the capacitor have successfully been inverted or gyrated so that the port behaves as an inductor. The equivalent inductance in henries is expressed by the formula $L = (R1)(R2)(C)$ (C), with resistances in ohms and capacitance in farads.

With the addition of two resistors, an air-core inductor can be simulated. Air-core coils have essentially no "core" loss, and therefore have no parallel resistance in their equivalent circuits. Because of this the gyrator (Fig. 2C) uses the additional resistors to set the gain of the op amp. When the values are properly selected, they provide enough gain to compensate for $R2$'s losses at high frequencies. But the amount of gain must be carefully chosen—otherwise the circuit might oscillate! If $R3$ equals $R1$ and $R4$ equals $R2$, the circuit will be stable and exhibit no parallel resistance. In practice, however, little is gained over the circuit of Fig. 1C as long as the ratio $R2/R1$ is at least 90 to 100, because the effects of parallel resistance are negligible in most audio applications commonly encountered.

Practical Design. In synthesizing a useful "inductor," the same basic rules that govern the optimization of wound coils should be followed. For example, series resistance $R1$ should be kept as small as possible and parallel resistance $R2$ as large as possible. This corresponds to a coil wound from the heaviest wire practicable on the least lossy core available. For best performance,

$R1$ should be no lower than the op amp's minimum recommended load resistance, which falls between 100 and 2000 ohms for common op amp types. The largest acceptable value for $R1$ is desirable, so as not to load the op amp too much, thus preventing high distortion and heating effects. To simulate a high-quality toroidally wound coil, $R2$ should be at least 100 times greater than $R1$, but not so large as to become a major contributor to the op amp's input noise. As a rule of thumb, keep $R1$ around 1000 ohms and $R2$ between 10 kilohms and 1 megohm.

Once the values of $R1$ and $R2$ have been chosen, use the formula $C = L / (R1)(R2)$ to find the required capacitance in farads. At least 100 pF should be used to avoid the detuning influences of stray capacitances.

It is important to keep the op amp functioning within acceptable circuit and signal parameters. If for any reason it begins to deviate from the role of a voltage follower, the "inductor" won't work properly. Input signals must lie within the operating bandwidth of the device, and their amplitudes must not cause the output stages to clip. In a gyrator, clipping in the gain stage is analogous to core saturation, which can cause high distortion levels.

However, this is not usually a problem with gyrators. Because they will most often be operated from the same power supplies that other audio stages use, they will not start to clip until the other amplifiers do. Unlike iron-core coils, whose saturation characteristics are functions of core material, size, number of turns, and applied current, the gyrator's saturation point is accurately predictable, and does not occur before the other active stages of the system also saturate or clip.

Using either of the gyrators we have examined will result in high-quality coils with inductances ranging from millihenries to hundreds or thousands of henries. Commonly available parts—including relatively small capacitors—can be employed. Added benefits include high magnetic field immunity and saturation characteristics, and (paradoxically) small amounts of required printed circuit board "real estate." However, there is one limitation. The gyrators we have described are single ended. That is, one side is grounded. To simulate "floating" inductors, neither side of which is connected to ground, more complex circuits using two op amps can be designed. But such gyrators are beyond the scope of this article.

PROPERTIES OF GYRATORS

Advantages

1. Immunity to ambient magnetic fields; no coupling or crosstalk between "inductors."
2. Very small size required for large values of inductance.
3. Inexpensive, use readily available components.
4. Accurately predictable "saturation" levels.
5. Parameters can be fixed by choice of resistors.

Disadvantages

1. Active device generates noise (can be held to low levels if proper devices are selected).
2. More complex circuits are required to simulate "floating" inductors.
3. Inductors with low series resistance and high current handling characteristics are difficult and impractical to simulate, as the circuits require high-power active devices.
4. Simulated inductors are frequency limited by their active devices' usable bandwidths and slew rates (not a problem at audio frequencies in most cases).

"ZAP" NEW LIFE INTO DEAD Ni-Cd BATTERIES

*That dead cell may not be completely gone.
A properly applied high current can often clear a
fault, making the cell useful again.*

BY DOUGLAS C. MYERS

THE NICKEL-CADMIUM cell is a paradox. Capable of being charged many hundreds to many thousands of times, it occasionally fails long before its claimed life cycle comes to an end. Most people simply replace a cell that has failed with a new cell. Considering that most Ni-Cd cell failures are reversible, this is a waste of money.

In this article, we will discuss the most common reason for early Ni-Cd cell failure and how the great majority of all failures can be reversed. The procedure described here will restore just about any dead Ni-Cd cell to provide its entire claimed useful life.

Why Cells Fail. In general, most devices powered by Ni-Cd cells employ more than a single cell. As the battery of

cells is discharged and recharged, the time available between recharges reduces. Almost invariably, this is due to the weakening of a single cell in the battery.

To understand the cause of such a failure—one cell "dead" while the others are still good—refer to Fig. 1, a schematic of a typical Ni-Cd power supply for small battery-powered devices. Without the charging source connected to the circuit, the 200-ohm load "sees" 5 volts and draws 25 mA from the battery of cells. Since each cell must pass the en-

tire 25 mA and each cell's potential is 1.25 volts, Ohm's Law tells us that each cell sees the equivalent load of 50 ohms. Ideally, the four cells deliver identical performance and, hence, share the load equally.

In practice, no four cells in a battery



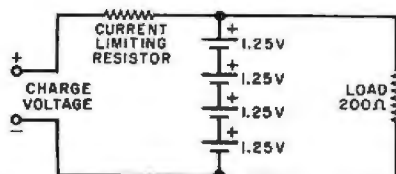


Fig. 1. Schematic of a typical NiCd supply for a small load.

ever exhibit exactly the same output voltage. Assume that one cell is delivering only 1.20 volts, while the other cells are delivering their rated 1.25 volts. Now, the 200-ohm load sees 4.95 volts and draws 24.75 mA. Since all four cells must pass the entire 24.75 mA, each of the strong cells at 1.25 volts sees an equivalent load of 50.5 ohms. This means that the weak cell sees only 48.5 ohms. While this does not seem to be too unequal a distribution, note that the weak cell is working into the heaviest load and, as a result, will discharge more rapidly than the other cells in the battery. Similarly, when the cells are recharged for only a short period of time, the weak cell, which has been working the hardest, is also the one that receives the least charging power.

This unequal loading and recharging is of little consequence in normal operation. The inequality is small for any given charge or discharge cycle, due to the relatively flat output voltage Ni-Cd cells exhibit over most of their range. And a good charge tends to equalize any energy differences between cells. However, during heavy usage, one is tempted to "quick charge" the battery just enough to restore service. A combination of shallow charges and deeper-than-normal discharges tends to exaggerate the energy difference between a weak cell and the other cells in the battery system. Operated continually in this manner, the weak cell inevitably reaches its "knee," the point at which its voltage decreases sharply, long before the other cells reach the same point.

At the knee, the picture changes dramatically. Suddenly, the weakest cell sees an increasingly heavy load, which causes its voltage to drop even faster. This avalanche continues until the cell is completely discharged, even as the other cells continue to force current to flow. The inevitable result is that the weak cell begins to charge in reverse, which eventually causes an internal short.

Once an internal short develops, recharging the cell at the normal rate is futile. The short simply bypasses current around the cell's active materials. (Even though the cell is apparently dead, most of its plate material is still intact.) If the

small amount of material that forms the short could be removed, the cell would be restored to virtually its original capacity once again.

Clearing the Short. Using the circuit shown in Fig. 2, the internal short can be burned away in a few seconds. In operation, energy stored in the capacitor is rapidly discharged through the dead cell to produce the high current necessary to clear the short. Current is then limited by the resistor to a safe charge rate for a small A cell.

Several applications of discharge current are usually necessary to clear a cell. During the "zapping" (restoration) process, it is a good idea to connect a voltmeter across the cell to monitor results. Momentarily close the normally open pushbutton switch several times to successively zap the cell, allowing sufficient time for the capacitor to charge up between zaps, until the voltage begins to rise. Then, with the toggle switch closed, watch as the potential across the cell climbs to 1.25 volts. If the potential

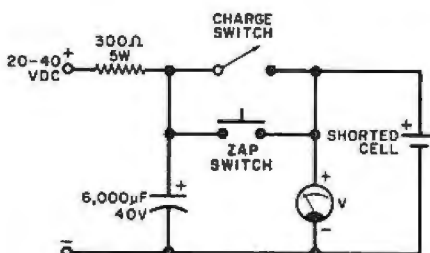


Fig. 2. Shorted cell is cleared by energy stored in capacitor.

stops before full voltage is reached, some residual short still remains and another series of zaps is in order. If you observe no effect whatsoever after several zaps and shorting out the cell and taking an ohmmeter measurement indicates a dead short, the cell is beyond redemption and should be replaced.

Once full cell potential is achieved, remove the charging current and monitor battery voltage. If the cell retains its charge, it can be returned to charge and eventually restored to service. But if the cell slowly discharges with no appreciable load, the residual slight short should be cleared. To do this, short circuit the cell for a few minutes to discharge it, zap again, and recharge it to full capacity.

Not all Ni-Cd cells can be restored by the method described here, but most can. After restoration, a cell's life expectancy will be roughly the same as that of the other cells taken from the same service application. ◇

For maximum
CB performance,
know you're
exactly
"on-channel" with
B&K-PRECISION's
NEW FREQUENCY
COUNTER!



Model 1827 \$120

For the serious CBER, the 1827 and accessory signal tap provide digital readout of transmit frequency, mobile or base on all 40 channels. For best range and signal clarity, your transmitter should be operating exactly on the assigned channels. The only way to accurately check this is with a frequency counter.

The new B&K-PRECISION Model 1827 is a full-feature battery portable frequency counter for only \$120.

- Typically reads to 50MHz with 1Hz resolution
- 6-digit display with switch allowing 8-digit accuracy
- Completely portable, use it in mobile or base
- Optional SA-10 signal tap available for constant output frequency measurements
- Full range of optional accessories available

Available for immediate delivery at your local distributor.

B&K PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Avenue
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Ontario
1011 Ste. Empire Exp., 270 Newtown Rd. Plainville, LI, NY 11303

CIRCLE NO. 7 ON FREE INFORMATION CARD

Heathkit®

SUMMER 1977

- New** High-Performance Frequency Counters with up to 1 GHz Range — See pages 68-69
- New** Budget-Priced Stereo FM-AM Receiver — See page 28
- New** Five-Function Aircraft Clock/Timer — See page 24
- New** Learn-at-home Courses in Electronic Circuits and Amateur Radio—See pages 93, 95

Plus programmable color TV, Digital Clocks and Weather Instruments, Amateur Radio Equipment, Test and Service Instruments, Hi-Fi Components and Speakers, Scanning Monitors, Marine and Auto Accessories, a complete selection of the latest electronics books, and lots more for your knowledge, fun and satisfaction.



1977 Heath Company
See index on page 4

HEATHKIT MAIL ORDER CATALOG

"Heath" and "Heathkit" are registered trademarks of Heath C

Heath Company, Dept. 10-31
Benton Harbor, Michigan 49022

FREE!

Some of the most exciting electronic kits ever to come along are described in this NEW Heathkit Catalog.

NEW! Learn-at-home Electronics Courses

The famous Heathkit learn-at-home electronics courses are now in use by thousands and they've proven to be a really effective and low-cost way to learn about electronics for fun, for knowledge and for profit. Two new courses include the Electronics Circuits course which covers most basic circuits and an Amateur Radio Novice License course that's GUARANTEED to help you get your ticket fast and easy!

NEW! Aircraft Clock Timer

The OI-1154 gives you everything you need for precise flight timing. Two bright red LED displays show GMT or ZULU time, and any one of four other functions: local time; 24-minute timer with minute and second display; 24-hour trip timer; and an alarm time for fuel management and check point notification. It's FAA/PMA approved and meets DO-160 environmental requirements.

GR-2001 Digital "Programmable" Color TV

The color TV that gives you MORE convenience and versatility than EVER! Simply "program" it to change channels at times you select for an entire evening — then just sit back and relax. The GR-2001 automatically changes channels when you want it to, and you can even program it to rotate your outdoor antenna for the best possible reception on each channel.

Complete Electronics Library

The new Heathkit catalog is your low-cost source for electronics books of every description. Our complete selection includes the latest books on microcomputers and microprocessors, digital devices, Amateur and Shortwave radio, television repair, test and service equipment, radio control, automotive, general reference and lots more.

NEW! High-performance frequency counters

Our new "family" of frequency counters gives you the accuracy and flexibility you NEED for frequency measurements all the way to 1 GHz. All feature bright red LED 8-digit readouts, gate and overrange indicators. They also function as events counters, period and period averaging meters. The IM-4110 covers 5 Hz to 110 MHz; the IM-4120 covers 5 Hz to 250 MHz; and the IM-4130 covers 5 Hz to 1 GHz.

NEW! Our "Budget-Priced" Stereo Receiver

The new AR-1219 AF-FM stereo receiver pulls in plenty of stations and gives you the power you want

for easy listening in most any room. 15 watts, minimum RMS, per channel into 8 ohms with less than 0.5% total harmonic distortion from 20-20,000 Hz. It's a quality receiver with smart new styling that's bound to please music lovers on a budget, and it's an easy and fun kitbuilding project, great for first-time builders.

PLUS nearly 400 other superb, easy-to-build, money-saving products. You'll find a complete line of digital electronic clocks and weather instruments, plus useful and unique items for your car, home or office.

There are many more exciting products to read about too! Home convenience items like a practical freezer alarm, a touch-control light switch, intercoms and a unique programmable doorbell. Automotive instruments and accessories, marine equipment, model aircraft Radio Control gear, security systems and more. Plus our world-famous Amateur Radio equipment and test and service instruments.

These are among the nearly 400 quality, fun-to-build kits described in this new Heathkit catalog. Kits for every interest. All with the world-famous Heathkit assembly manual — a step-by-step instruction guide that makes kitbuilding easy and leaves nothing to chance. And all backed by our "We won't let you fail" promise. Find out about the satisfaction, savings and FUN of kitbuilding.

**Send for your
FREE copy today!**

HEATH	
Schlumberger	
Heath Company, Dept. 10-31 Benton Harbor, Michigan 49022	
Please send me my FREE Heathkit Catalog. I am not on your mailing list.	
Name _____	
Address _____	
City _____	State _____
CL-633	Zip _____

Build a PINK NOISE GENERATOR for AUDIO TESTING

Uses a new MOS noise generator IC.

BY DENNIS BOHN

AN INCREASING number of audiophiles are incorporating graphic equalizers into their hi-fi music systems. The new component is most often used as a "super" tone control that offers a degree of frequency response compensation beyond the capabilities of bass and treble controls. However, adjusting 10 to 30 controls to compensate for acoustic deficiencies in the listening room can be challenging. This project—a pink noise generator—makes the job a little easier. It provides a reference signal for performing equalizer adjustments, and uses just one IC and a few passive components.

The IC, National Semiconductor's MM5837, is a digital pseudo-random sequence generator which will produce a broadband white noise signal for audio applications that's converted to pink noise by a passive filter. Unlike traditional semiconductor junction noise sources, the MM5837 provides uniform noise quality and output amplitude. Although it was originally developed with electronic organs and synthesizers in mind, it is equally suited to room equalization applications. A block diagram of the MM5837 is shown in Fig. 1.

White vs. Pink Noise. The output of the MM5837 is broadband white noise. Since pink noise is used in most audio work, it is helpful to understand the difference between the two.

White noise is a composite signal with contributions from all frequencies and a spectral density substantially independent of frequency (equal energy per constant bandwidth). It is characterized by a 3-dB increase in amplitude per octave of frequency change. In comparison, pink noise has a flat amplitude response per octave of frequency (equal energy per octave). Pink noise allows correlation between successive octave equalizer stages by insuring that the same amplitude of input signal is used for each as a reference.

The network required to convert white noise to pink noise is simply a -3-dB/octave low-pass filter; but it presents an interesting problem in circuit design. If capacitive reactance (and thus the response of a simple RC or first-order filter) varies at a rate of -6 dB/octave, how can a slope of less than -6 dB/

octave be obtained? The solution lies in cascading several stages of lag compensation so that the zeros of one stage partially cancel the poles of the next stage. Such a network, shown in Fig. 2, has a -3-dB/octave characteristic ($\pm 1/4$ dB) from 10 to 40,000 Hz.

The complete pink noise generator in Fig. 3 gives a flat spectral distribution (per octave) over the audio band from 20 to 20,000 Hz. An 11.5-V p-p random pulse train appears at pin 3 of the IC, and is attenuated by the filter. The actual output across C5 is about 1 V p-p ac of pink noise riding on an 8.5-V dc level.

Construction. Since the circuit is fairly simple, it can be constructed on a small circuit board using printed circuit, point-to-point wiring, or Wire-Wrap techniques. Resistors in the filter network should have close tolerances. Premium-grade tantalum and polystyrene, ceramic, and film capacitors are recommended. Observe standard precautions in handling the MOS device, and use an IC socket or Molex Soldercons. \diamond

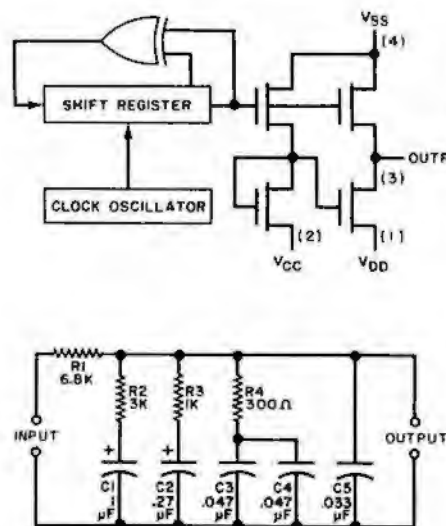


Fig. 1. Block diagram of the MM5837.

Fig. 2. Low-pass filter with -3-dB/octave response.

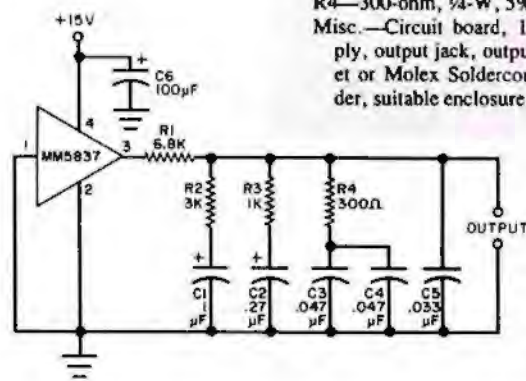


Fig. 3. Schematic diagram of the pink noise generator.

PARTS LIST

- C1—1-µF, 35-V tantalum capacitor
- C2—0.27-µF, 35-V tantalum capacitor
- C3, C4—0.047-µF capacitor
- C5—0.033-µF capacitor
- C6—100-µF, 35-V electrolytic capacitor
- IC4—MM5837 noise generator IC
- R1—6800-ohm, 1/4-W, 5% resistor
- R2—3000-ohm, 1/4-W, 5% resistor
- R3—1000-ohm, 1/4-W, 5% resistor
- R4—300-ohm, 1/4-W, 5% resistor
- Misc.—Circuit board, 15-volt regulated supply, output jack, output connector, IC socket or Molex Soldercons, hookup wire, solder, suitable enclosure, etc.





"Breaker... breaker..."



The World of Electronics

BY FRANK BOLLE

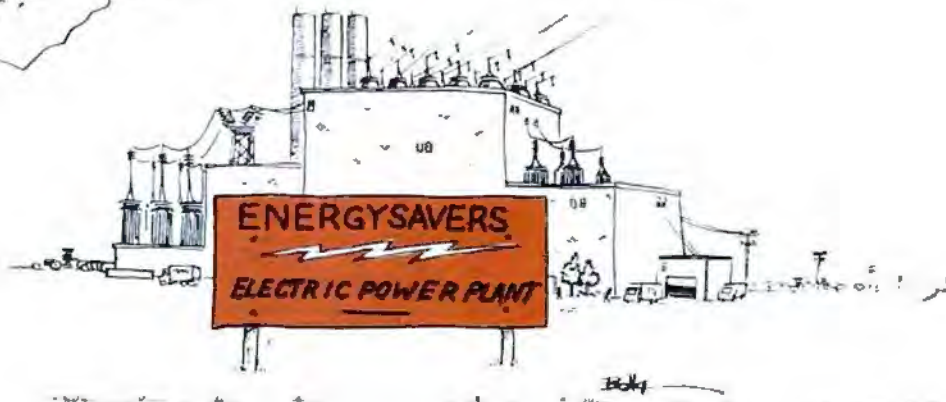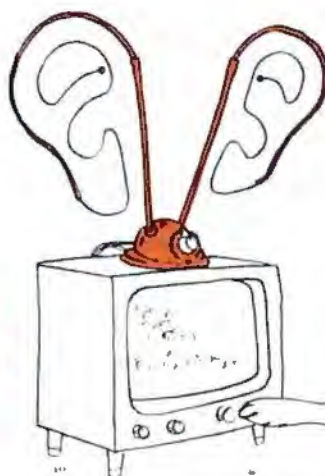

AVERAGE, PEAK, AND RMS VALUES

What is meant by the various ways of specifying ac potentials and currents.

BY HECTOR FRENCH.

WHEN dealing with dc potentials, there is no ambiguity about what kind of voltage is meant. A dc volt is a dc volt. When it comes to ac voltage, however, the picture is very different and often confusing. For example, a potential specified as 100 volts ac has little or no meaning unless it is followed by an identifier like "peak," "rms," "average," or "effective," each of which has a different meaning from the others.

To illustrate what we mean, consider your common 117-volt ac power-line potential. This figure specifies the rms voltage of the power line. The peak potential is actually 164.66 volts, which is 39.8% greater than the rms potential. The average potential, at 11% lower than the rms potential, is 104.52 volts.

The peak voltage is the maximum potential of the entire waveform. This volt-

and capacitor are simply reversed.)

The average voltage is important for two different reasons. First, it is easy to find with simple circuits. Second, it is reliably close to the rms voltage with sine waves. The basic circuit for finding the average ac voltage is illustrated in Fig. 2.

In this case the output is a series of half-waves of the same polarity. (Again, to change the output voltage polarity, simply reverse the diodes.) A meter placed between the output point and ground provides the reading and is usually calibrated with a scale that is compressed just the right amount to give a relatively accurate rms reading with sine-wave signals. This is the type of circuit used in most ac voltmeters ranging from inexpensive portable to expensive laboratory instruments.

put in terms of rms with sine waves. What about nonsinusoidal waveforms? If we take a 117-volt sine wave and allow only one alternation in 10 to come through, the peak potential is still 164.66 volts. Since only a half wave out of every 10 cycles comes through, our average potential would be divided by 10 (104.52/10 = 10.452 volts).

If we allow only one alternation in 10 cycles to come through for a 117-volt ac rms waveform, we cannot simply divide by 10 to find the new rms potential. First, we must square 117, which yields 13,689. Then, we find the average by dividing 13,689 by 10, yielding 1368.9. Finally, we must find the square root of 1368.9, which results in 37 volts rms. This last figure is a long way from the average reading of this one-in-10 waveform, even when the average scale is

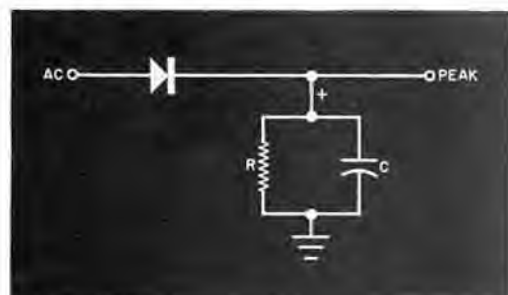


Fig. 1. Simple RC and diode circuit is used to find peak potential.

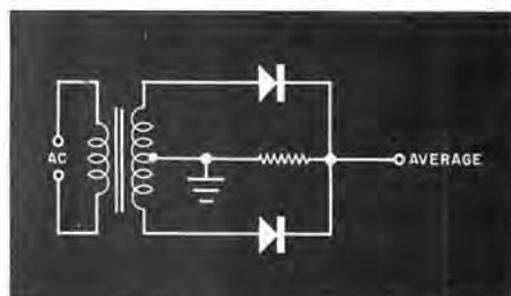


Fig. 2. Series of half waves is measured to find average value.

age is extremely important for designing the insulation of high-voltage ac circuits. An 11,500-volt (rms) line, for example, has a peak potential of $11,500 + 4577 = 16,077$ volts. That difference of more than 4500 volts must be considered when specifying components.

The peak potential is easy to find with the circuit shown in Fig. 1.

The capacitor charges up to the peak voltage during the first positive alternation of the ac input. The charge then slowly drains off through the resistor until the next positive alternation comes along. (For a negative output, the diode

At this point, you are probably wondering where rms voltage comes into the picture. Well, the purpose of the rms measurement is to specify the dc voltage that has the same power capacity as the ac voltage it represents. "Rms" stands for "root mean squared," which is shorthand for saying that to find the rms voltage, you must square the ac waveform, find the average of the squared waveform, and find the square root of that average. About the only simple way of showing an rms detector system is as in Fig. 3.

The average-law circuit gives an out-

compressed to indicate in make-believe rms. Using the compressed scale, the indicated reading would be almost 70% low!

As you can see from the foregoing, when dealing with pure sinusoidal waveforms, you can use a peak-, average-, or rms-indicating circuit to convert from one type of ac voltage to another without introducing errors. But when you are dealing with nonsinusoidal waveforms, watch out. All your readings might be so grossly inaccurate as to be useless for anything other than to indicate the presence or absence of a potential. ◇

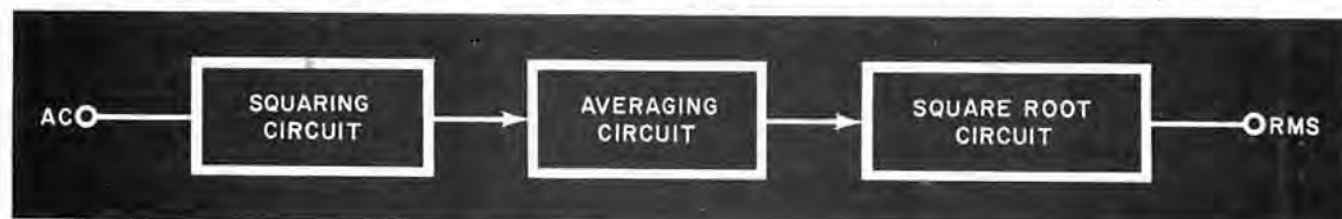


Fig. 3. Simple block diagram of an rms detector circuit.

SOLAR CONTROLLER

Electronic temperature comparator for solar energy systems or attic fans

BY JERALD M. COGSWELL

THE SEARCH for new energy sources has encouraged amateurs as well as professional engineers to experiment with solar energy hardware as used in space heating. A typical solar heating system consists of three functional parts: solar energy collection, heat storage, and heat distribution. Automatic controls are required to operate the fans, blowers, pumps, etc. and coordi-

nate operation of the overall system.

Because the backyard (or rooftop) experimenter may be discouraged by the high cost or unavailability of suitable controls, the Solar Controller described here should come in very handy. It can be built for about \$35 and can be easily adapted to turn on attic fans when needed. It thus reduces the cooling load and prevents costly over-running of fans.

The Solar Controller is a temperature comparator that turns on a blower or pump when the air or fluid in the solar collector is at a sufficiently high temperature to justify a transfer to the storage medium. In the fan application, control is by the temperature difference between the attic and outside air (or between ceiling and floor of a large room).

Circuit Operation. The basic controller circuit is shown in Fig. 1. In IC1, a voltage comparator, the resistances of two temperature-dependent resistors (TDR1 and TDR2) are compared, with TDR1 placed in the storage medium and TDR2 in the solar collector. When TDR1 is warmer than TDR2, its resistance is higher and the higher voltage at the inverting (-) input to IC1 keeps its out-

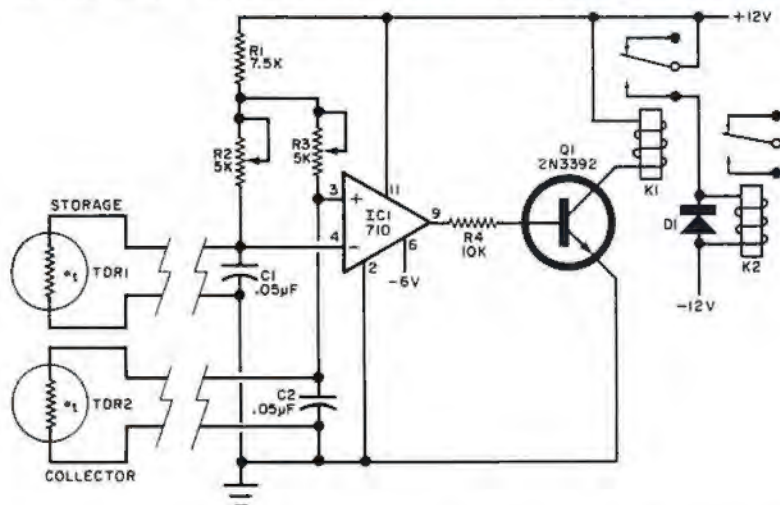


Fig. 1. Comparator IC1 turns on or off depending on resistances of TDR1 and TDR2. When IC1 is on, Q1 and the relays are energized.

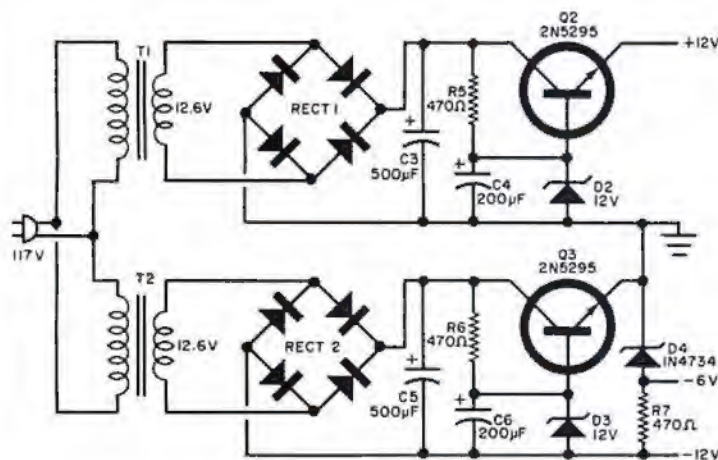


Fig. 2. The power supply for the solar controller is standard design and provides regulated positive and negative outputs.

PARTS LIST

- C1, C2—0.05-µF, ceramic disc capacitor
 - C3, C5—500-µF, 25-V electrolytic capacitor
 - C4, C6—200-µF, 25-V electrolytic capacitor
 - D1—General-purpose silicon rectifier diode
 - D2, D3—12-V, 1-W zener diode (1N4742, or similar)
 - D4—6-V, 1-W zener diode (1N4734 or similar)
 - IC1—710 voltage comparator
 - K1—12-V, 600-ohm coil relay
 - K2—24-V, 10-ampere contacts relay
 - Q1—2N3392 transistor
 - Q2, Q3—2N5295 transistor (or similar)
 - R1—7500-ohm, 1/2-W resistor
 - R2, R3—5000-ohm multi-turn trimmer potentiometer
 - R4—10,000-ohm, 1-W resistor
 - R5, R6, R7—470-ohm, 1/2-W resistor
 - T1, T2—12.6-V, 300-mA transformer (Radio Shack 273-1385 or similar)
 - TDR1, TDR2—TG-1/8, 100-ohm, ±5% Sensor
 - Misc.—Suitable enclosure, perforated or pc board, socket for IC1, twin lead cable for sensors, heat sinks(2), power cord, mounting hardware.
- Note: The Sensors are available from Texas Instruments semiconductor dealers, or from Texas Instruments, 2916 Holmes St., Kansas City, MO 64109 at \$2.40 each.

Portable 60-Hz "CLOCK" OSCILLATOR

Crystal-controlled time base for field use.

BY CHARLES F. SMITH

put in the low state. When *TDR2* gets warmer, the voltage across it gets higher and, when it is about 5 millivolts higher than the voltage across *TDR1*, the output of *IC1* goes high.

When this happens, transistor *Q1* is turned on and activates low-power relay *K1*. The latter, in turn, activates a 24-volt heavy-duty relay, *K2*, which handles the power requirements of the system.

Capacitors *C1* and *C2* prevent transients from affecting the inputs of *IC1*. Trimmer potentiometers *R2* and *R3* are used to preset the voltages on *IC1*. Diode *D1* is a general-purpose silicon rectifier used to protect the contact of *K1*. If desired, *Q1* can be replaced by a power transistor (such as RCA 40594) and one of the relays can be eliminated.

The power supply for the Solar Controller is shown in Fig. 2.

Construction. All components except the power transformer and relays can be mounted on a 3" x 6" piece of perforated board or pc board. Use small solder clips for connections to *TDR1*, *TDR2* and the relay. The entire system can be mounted in any type of enclosure. Use a heat sink for *Q2* and *Q3*.

The temperature sensors can be mounted at a distance from the rest of the circuit provided the resistance of the interconnecting leads does not exceed a few ohms. Use #14 wire or conventional slender twin leads. Solder the leads to the sensors carefully (and quickly) and anchor the soldered ends in silicone or epoxy. Be sure the bodies of the resistors are exposed to insure fast thermal response to temperature changes.

Adjustment. Set trimmer potentiometer *R2* at about its 3/4-resistance point. Then place the body of *TDR1* in a bowl of water that has been heated to the average temperature you expect in the storage medium. Place *TDR2* in another bowl of water that is between 5° and 10°F hotter than the first bowl. You will have to determine the exact temperature difference you want the circuit to detect.

Once both temperature sensitive devices are in their water bowls, and the water temperature difference is what you want, adjust trimmer *R3* until relay *K1* activates. The circuit can be made as sensitive as your needs demand. Note also that although the device appears passive when both probes are at room temperature, a gust of warm breath, or the touch of a finger on *TDR2*; or a drop of cool water on *TDR1*, will cause *K1* to be energized. ◇

MOST digital clocks and sports timers are energized by the ac line—not so much for power as for the 60-Hz frequency that is used as the time base. This means that such digital devices cannot be used in vehicles or boats or

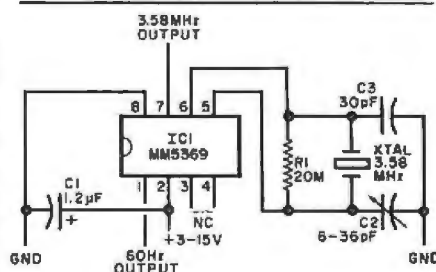


Fig. 1. Schematic of circuit.

PARTS LIST

- C1—1.2-μF, 35-V tantalum capacitor
 - C2—6-36-pF trimmer capacitor
 - C3—30-pF capacitor
 - IC1—MM5369 programmable oscillator/divider, for use with a 3.58-MHz crystal (National)
 - R1—20-megohm 1/4 watt resistor
 - XTAL—3.579545-MHz color-TV crystal
- Note: The following are available from Bill Godbout Electronics, Box 2355, Oakland Airport, CA 94614: etched and drilled pc board (068) at \$2.50; complete kit of parts, including board at \$5.95. California residents, please add 6% sales tax.

for timing outdoor events that are not near an ac power outlet.


The 60-Hz crystal-controlled time base described here (Fig. 1) can be powered by any dc supply between 3 and 15 volts. It has low power consumption, is stable within 2 parts per million and is small enough to fit inside the case of many digital clocks and timers.

How It Works. The integrated circuit used in this time base is an MM5369, a recently introduced 17-stage, mask-programmable oscillator/divider. Although masking options are available for use with almost any crystal frequency, the IC used operates with a low-cost, readily available 3.58-MHz color-TV crystal and delivers 60 Hz at its output pin. Trimmer capacitor *C2* allows for exact frequency adjusting, and a buffered 3.58-MHz output is available. Current drain is approximately 1.2 mA with a 10-volt supply.

Construction. Because of the high frequencies involved, a small pc board (or perforated board) such as that shown in Fig. 2 should be used. Figure 2 also shows component installation. Since the IC is a MOS type, take the usual precautions when installing.

Adjustment. If you have a frequency counter, or a calibrated oscilloscope, check for the presence of 3.579545 MHz at pin 7 of the IC. You can adjust trimmer capacitor *C2* for the correct value. If you do not have a frequency counter, use the Lissajous-figure approach with a scope, with the output of a conventional 6-volt transformer as the horizontal sweep and the output of *IC1* pin 1 for the vertical signal. Adjust *C2* until a very slow-moving square appears on the scope. If you have neither a counter nor a scope and are planning to use the clock with a portable timing device, use some form of accurate time signals such as those from WWV, CHU, etc., to start the timer at a one-minute "beep" and stop it at the next minute "beep." Adjust *C2* to obtain the correct time interval. ◇

Fig. 2. Actual-size etching and drilling guide (far right) and component layout. Components are mounted on nonfoil side.

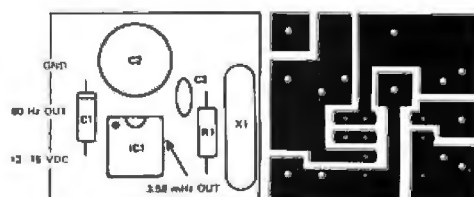


Announcing the **NEW STANDARD** in Stereo Testing!

Get the All-New Model SR12 STEREO TEST RECORD

The most complete...most sophisticated...most versatile
Test Disc available today... **For Just \$6.95!**

Who Needs the New Model SR12?

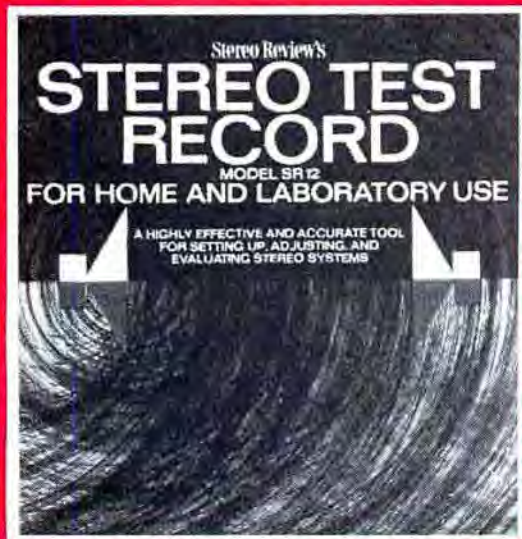If you've read this far, you do. Whether you're an avid audiophile who'll settle for nothing but peak performance from his stereo components... a casual listener who'd like more insight into the challenging world of stereo reproduction... or a professional technician who needs precise standards for lab testing... the new MODEL SR12 will be the most important disc in your entire collection.



Like its predecessor Model 211, MODEL SR12 has been produced by Stereo Review Magazine (formerly HiFi/Stereo Review) as a labor of love — by music lovers... for music lovers who want immediate answers to questions about the performance of their stereo systems and how to get the best possible sound reproduction.

Now greatly expanded and updated with the most modern engineering techniques, MODEL SR12 is the most complete test record of its kind — containing the widest range of checks ever included on one test disc. An ear-opener for every serious listener!

You'll make these important stereo checks BY EAR... (no test instruments of any kind required)

Frequency response—a direct warble-tone check of nineteen sections of the frequency spectrum, from 20 to 20,840 Hz, which will pinpoint any frequency response defects in your system.

Separation—an ingenious test which indicates whether you have adequate separation for good stereo.

Cartridge tracking—the most sophisticated tests ever devised for checking the performance of your cartridge, stylus and tone arm.

Channel balance—two broad-band, random-noise signals which permit you to eliminate any imbalances originating in cartridge, amplifier, speakers or room acoustics.

Hum and rumble—foolproof tests that help you evaluate the actual audible levels of rumble and hum in your system.

Flutter—a sensitive "musical" test to check whether your turntable's flutter is low, moderate, or high.

- Cartridge and Speaker Phasing
- Anti-Skating Adjustment
- "Gun Shot Test" for Stereo Spread
- Multi-purpose Musician's "A"
- Equal-tempered Chromatic Octave
- Guitar-tuning Tones.

Don't waste another minute on less-than-perfect stereo—Order Your Model SR12 Stereo Test Record NOW!

Consider the hundreds—even thousands—you've spent on your set-up and you'll agree \$6.95 is a small price to pay for the most valuable performance tool ever made. So to be sure your order is promptly filled from the supply available, mail the coupon at right with your remittance... today!



CHARGE YOUR ORDER TO YOUR AMERICAN EXPRESS, BANKAMERICARD, MASTER CHARGE OR DINERS CLUB ACCOUNT.



AND, for the ultimate in stereo testing, 7 critical TEST EQUIPMENT checks...

Attention professionals: Stereo Review's new Model SR12 Stereo Test Record is also designed to be used as a highly efficient design and measurement tool. In the following tests, recorded levels, frequencies, etc. have been controlled to laboratory tolerances—affording accurate numerical evaluation when used with oscilloscope, chart recorder, output meter, intermodulation-distortion meter and flutter meter.

- 1,000-Hz square waves to test transient and high-frequency response of phono pickups.
- 500 to 20,000 Hz frequency-response sweep.
- Sine-wave tone-bursts to test transient response of pickup.
- Intermodulation test using simultaneous 400-Hz and 4,000-Hz signals.
- Intermodulation sweep to show distortion caused by excessive resonances in tone arm and cartridge.
- 1,000-Hz reference tones to determine groove velocity.
- 3,000-Hz tone for flutter and speed tests.

Sample waveforms—illustrating both accurate and faulty responses are provided in the Instruction Manual for comparison with the patterns appearing on your own oscilloscope screen.

FREE Instruction Manual Includes Detailed Instructions, Charts, Tables and Diagrams.

Nothing is left to chance... or misinterpretation. Every segment of every band is fully, clearly, graphically explained. You'll know exactly what responses to listen for in each test. Which sounds and patterns indicate accurate performance... which ones spell trouble... as well as the cause of trouble and precise corrective measures to follow and help you pinpoint, analyze and cure your stereo headaches!

Ziff-Davis Service Division, Dept. R, 595 Broadway, New York, N.Y. 10012.

☐ Please send the SR12 Stereo Test Record @ \$6.95, postpaid (\$8.95 outside U.S.A.). PE-77

☐ Enclosed is \$_____. (Residents of Calif., Col., Fla., Ill., Mich., Mo., N.Y. State, D.C. and Tex. add applicable sales tax.)

☐ CHARGE: ☐ BankAmericard ☐ Master Charge ☐ American Express ☐ Diners Club

Account # _____ Exp. Date _____

Master Charge Interbank # _____ (4 numbers over your name)

Signature _____

Print Name _____

Address _____

City _____ State _____ Zip _____

ONE-TOUCH DIODE TESTER

*Identifies good/bad diodes, and tells
which end is anode/cathode.*

BY DAVID MARKEGARD

MOST electronics experimenters seem to have plenty of diodes in their junk boxes—either salvaged from old equipment or purchased at low bulk prices. The problem, usually, is to find out which ones are good, which are bad, and, in the case of the former, which end is which (cathode or anode). Of course, most diodes can be tested using a conventional ohmmeter. However, there are simpler ways, and one is to use the diode checker described here. Simply by touching a diode's leads to its binding posts (in either polarity), you can tell whether or not it is good and identify the anode and cathode.

How It Works. Op amp IC1 forms a simple square-wave oscillator whose output swings from almost full positive to full negative levels with respect to ground.

unknown diode lead connected to BP1 is easily identified.


Construction. The circuit can be assembled on a small piece of perforated board and mounted in small enclosure along with the batteries in holders. The two binding posts and the power on/off switch should be mounted about an inch apart on top of the enclosure. Put the two LED's in rubber grommets near BP1 and identify them properly.

Before installing the LED's, be sure they are of equal brightness. The values of R1, R2, R3, and C1 can be varied if the specified values are not available—as long as the circuit oscillates.

Use. Connect a diode to be tested between the two binding posts. If only one LED glows, the diode is good and the glowing LED will identify the cathode. If

PARTS LIST

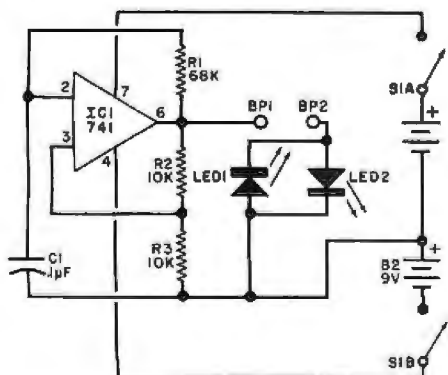B1, B2—9-volt battery
BP1, BP2—Five-way binding post
C1—0.1- μ F capacitor
IC1—741 op amp
LED1, LED2—Red LED (about equal brightness)
R1—68,000-ohm resistor
R2, R3—10,000-ohm resistor
S1—Dpst switch
Misc.—Perforated board, socket for IC1, battery holder, suitable enclosure, grommets for LED's, mounting hardware, etc.



IC1 is square-wave oscillator. Tested diode turns on either LED.

If a good diode is connected between BP1 and BP2 with its cathode toward BP1, LED1 is forward biased and glows. LED2 remains dark because it is reverse biased. If the diode is reversed so that its anode is at BP1, LED2 glows and LED1 is dark. With the LED's properly identified and placed close to BP1, an

both LED's glow, the diode is shorted. If neither LED glows, the diode is open.

Transistor junctions can be tested by connecting the collector to BP1 and the base to BP2. If LED1 glows and is brighter than LED2, the transistor is npn. If LED2 glows, or is brighter than LED1, the transistor is pnp.

SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT
AT LOWEST PRICES.

YOUR REQUEST FOR QUOTA-
TION RETURNED SAME DAY.

FACTORY SEALED CARTONS—
GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

A.D.C.	KLH
A.R.	SHURE
DYNACO	KOSS
SONY	FISHER

PIDNEER

AND MORE THAN 50 OTHERS

BUY THE MODERN WAY

BY MAIL—FROM

ia illinois audio

Department 217S
12 East Delaware
Chicago, Illinois 60611
312-664-0020

CIRCLE NO. 23 ON FREE INFORMATION CARD

FREE catalog

of over
2000
small tools,
measuring
instruments,
and supplies



National Camera
2000 West Union Ave., Dept. 217S
Englewood, Colo., U.S.A. 80110

CIRCLE NO. 30 ON FREE INFORMATION CARD



Chances are, the name on his radio will be Motorola.[®]

The same Motorola that now makes a CB radio for your car.

Like our professional radios, a Motorola CB is exceptionally simple to operate.

It has features like gain control, audio compression, and noise limiting built in, fully automatic.

The result is truly outstanding talk/listen performance. Because the radio is in control. Rather than you.

A digital phase lock loop synthesizer makes tuning precise. Again, automatically.

A professional-quality 3½-inch top-fire speaker produces an audio fidelity that must be heard to be fully appreciated.

A Motorola CB is completely solid state and standardly equipped with a power mic that doesn't have batteries that can fail. That doesn't cost extra.

Of course, there's one feature a Motorola CB offers that's not in the specs. And that's reliability.

Police get it with the name Motorola.

So can you.



Motorola CB

From the voice of experience in 2-way radio.

To find the dealer nearest you, write: Customer Relations Manager, Motorola Inc., Automotive Products Division, 1299 East Algonquin Rd., Schaumburg, Illinois 60196. Motorola is a registered trademark of Motorola Inc.

CIRCLE NO. 29 ON FREE INFORMATION CARD



MAGAZINES AT DISCOUNT!

You SAVE up to 50%

Here's your chance for a real bargain bonanza on your favorite magazines. You may select as many as five of these titles at the special introductory rates shown below—up to 50% off! To order, indicate the magazines you want by inserting their code numbers in the boxes on the attached order card. Or write to: MAGAZINES AT DISCOUNT, A Division of Ziff-Davis Publishing Co., P.O. Box 2703, Boulder, Colorado 80322

CODE NOS.

- (01) **BOATING** You pay only \$7.97
Reg. Rate: 12 Issues for \$12.00
- (02) **CAR & DRIVER** You pay only \$4.99
Reg. Rate: 12 Issues for \$9.98
- (76) **COUNTRY MUSIC** You pay only \$6.95
Reg. Rate: 12 Issues for \$8.95
- (03) **CYCLE** You pay only \$4.99
Reg. Rate: 12 Issues for \$9.98
- (04) **FLYING** You pay only \$7.99
Reg. Rate: 12 Issues for \$12.00
- (29) **MONEY** You pay only \$9.95
Newsstand Rate: 10 Issues for \$12.50
- (34) **PLAYBOY** You pay only \$12.00
Newsstand Rate: 12 Issues for \$19.00
- (06) **POPULAR ELECTRONICS** You pay only \$6.99
Reg. Rate: 12 Issues for \$12.00
- (45) **POPULAR MECHANICS** You pay only \$3.99
Reg. Rate: 12 Issues for \$7.97
- (07) **POPULAR PHOTOGRAPHY** You pay only \$4.99
Reg. Rate: 12 Issues for \$9.98
- (35) **POPULAR SCIENCE** You pay only \$4.50
Newsstand Rate: 12 Issues for \$9.00
- (08) **PSYCHOLOGY TODAY** You pay only \$6.97
Reg. Rate: 12 Issues for \$12.00
- (11) **STEREO REVIEW** You pay only \$3.99
Reg. Rate: 12 Issues for \$7.98
- (39) **TENNIS** You pay only \$4.75
Reg. Rate: 12 Issues for \$9.50
- (40) **TIME** You pay only \$12.50
Newsstand Rate: 25 Issues for \$25.00
- (41) **TV GUIDE** You pay only \$8.35
Lowest Available Sub. Rate for 32 Issues





Solid State

By Lou Garner


IC's FOR TEST INSTRUMENTS

SURPRISING as it may seem, solid-state test instruments were manufactured and used long before the transistor itself was invented. Featuring crystal diode circuitry, the early units were relatively simple instruments—r-f test probes, square-wave clippers, oscilloscope calibrators, dc reference voltage sources, outboard signal generator modulators, etc. Historically, the transistor's first significant commercial use was in hearing aids. Shortly thereafter, however, the recently invented device found its way into pocket AM radio receivers and, almost simultaneously, into portable test instruments. With its small size and low voltage and current requirements, compared to the then standard vacuum tube, the new device was certainly ideal for such applications. Initially, its use was limited to such products as signal tracers, simple meter amplifiers, and limited-range signal generators. Later, as better transistor designs were developed and manufacturing techniques refined, transistors found their way into r-f signal generators, function generators, oscilloscopes, Q-meters, and even microwave gear. As time passed, other solid-state de-

automatic ranging, frequency synthesis, automatic unit conversion, and digital counting and display.


Introduced recently by the National Semiconductor Corporation (2900 Semiconductor Drive, Santa Clara, CA 95051), the LH0091 is one of the latest IC's developed primarily for test instrument applications. Suitable for use in digital voltmeters (DVM's) and digital multimeters (DMM's) as well as in noise, vibration, audio and power meters, the new device is designed to generate a dc output equal to the *true rms value* of any ac or composite ac/dc input signal from 0 Hz (dc) to 2 MHz. With an inherent accuracy of 0.5% of reading, the device can be adjusted using external trimming for accuracies down to 0.5%. In typical applications, it has an input impedance of 5000 ohms and an output impedance of 1 ohm. When operated with a dual ± 15 -volt dc power source, the LH0091

Fig. 1. Simplified schematic (A) and lead connections (B) for LH0091 rms converter IC.

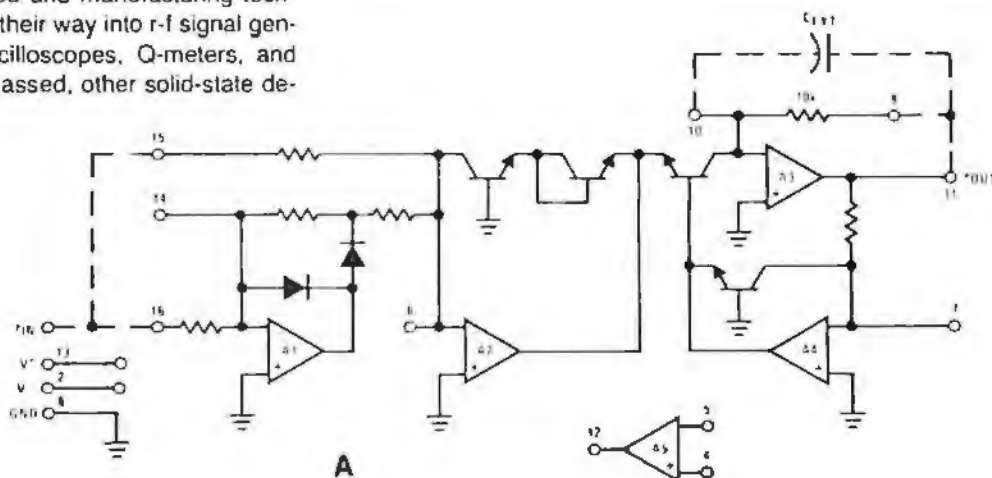

vices were added to test instrument complements, including FET's, SCR's, triacs, diacs, and LED's, culminating in the use of integrated circuits. Today, almost all solid-state test instruments use at least one IC and many a dozen or more. There are, in fact, a number of special-purpose IC's designed specifically for test instrument applications.

For the experimenter and hobbyist, the evolution of integrated circuits and the ready availability of special purpose IC's has made possible the home assembly of inexpensive but sophisticated test instruments which would be both costly and prohibitively large if based on the use of either vacuum tube technology or discrete semiconductor devices. In addition, the development of complex IC's has permitted the efficient use of advanced design concepts and techniques in test equipment design, including phase-locked loops, gyrators,

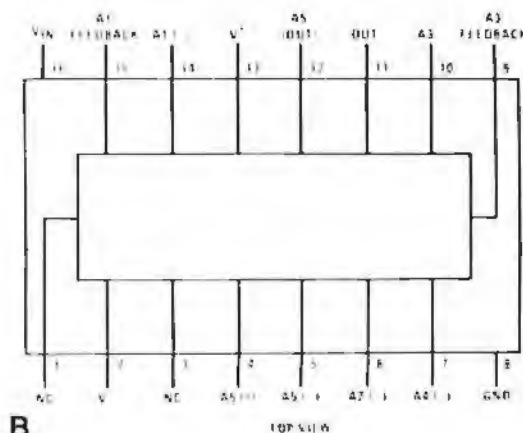

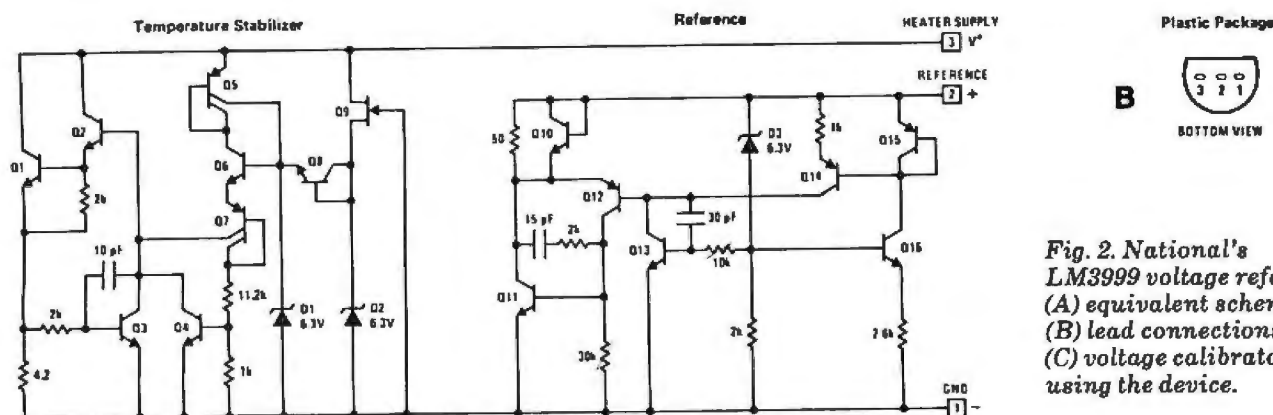


Fig. 2. National's LM3999 voltage reference: (A) equivalent schematic; (B) lead connections; (C) voltage calibrator using the device.


A

will accept input signals of up to ± 15 volts peak. As shown in the unit's simplified schematic diagram, Fig. 1A, the IC includes an uncommitted amplifier, A5, which may be used for filtering, to provide additional gain, or for other applications. Supplied in 16-pin DIP's, with lead connections as identified in Fig. 1B, the LH0091 is available in two versions—one in a metal case, for the standard military temperature range (-55° to $+125^\circ$ C) and the other for commercial operation (-25° to $+85^\circ$ C).

A unique device, the LH0091 is, of course, but one of a substantial number of IC's developed specifically for test instrument applications. Special, as well as general-purpose IC's useful in test equipment designs, are available not only from National Semiconductor but from virtually all other solid-state device manufacturers, including AMI, Exar, Fairchild, Intersil, Motorola, Plessey, RCA, Signetics, Siliconix, and Texas Instruments.


Suitable for power supply and general purpose as well as test instrument applications, another National Semiconductor IC, the LM3999, looks deceptively like an inexpensive transistor, for it is assembled in a three-lead, type TO-92 plastic package. Despite its simple external appearance, however, the unit is a monolithic precision voltage reference which combines a multi-device temperature stabilizing circuit with a zener controlled regulator, as shown in its equivalent schematic diagram, Fig. 2A. Its pin connections are identified in Fig. 2B. In operation, the LM3999 behaves as a highly stable 6.95-volt zener diode with a low dynamic impedance of only 0.5 ohm and an effective current range from 0.5 to 10 mA. Accepting dc inputs from 9 to 36 volts, the separately powered stabilization circuit permits operation from 0° to $+70^\circ$ C with a temperature coefficient of $0.0005\%/^\circ\text{C}$ and a long term stability of 20 ppm. The circuit for a portable voltage calibrator circuit, one of the many possible test equipment applications for the LM3999, is given in Fig. 2C. Here, the LM3999 is used in conjunction with an LM312 operational amplifier. Supplying a precise 10-volt output level for equipment calibration, the instrument requires a warm-up time of ten seconds, but may be used intermittently without degradation of long term stability.

If your instrument project plans include one or more digital meters, you'll want to investigate yet another new National Semiconductor device, the DM7700, a monolithic IC which contains all of the active circuitry, except for display, needed for a $2\frac{1}{2}$ -digit meter. As illustrated by its simplified block diagram, Fig. 3A, the DM7700 comprises amplifier, reference voltage, voltage-to-frequency converter, clock, time-base, counter and latch circuits. Analog-to-digital conversion is

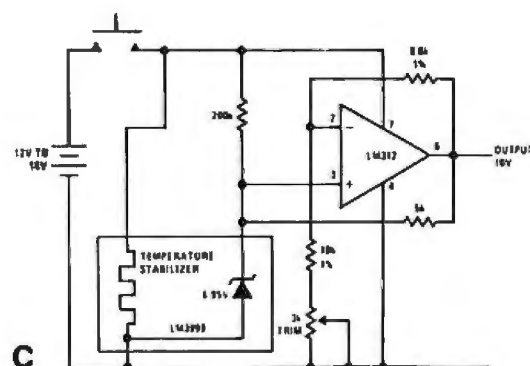


accomplished through the use of a dual voltage-to-frequency technique. One voltage-to-frequency converter generates a signal proportional to the input voltage while the other provides a sample window and determines the clock frequency for counting the output of the first. Requiring $+5$ - and -15 -volt dc sources for operation, the IC features a temperature compensated reference and both autopolarity and over-range output indicators. With an input impedance of 500,000 ohms, the device offers a full-scale analog range of ± 1.99 volts, a conversion time of 1 second, and an accuracy of $\pm 1.0\%$. Two versions of the IC are offered by the manufacturer, differing only in their temperature ratings. The standard DM7700 is specified for operation from -20° to $+95^\circ$ C, the less expensive DM8700 for operation from 0° to $+50^\circ$ C. Both versions are supplied in standard 24-pin double-width DIP's, with pin connections as identified in Fig. 3B, and both can provide adequate current drive for standard LED numeric displays. A typical application circuit for the DM7700 (or DM8700) is given in Fig. 3C. Except for the IC, the NSN-33 LED readout, and the dc power supply, the only components needed for operation are three capacitors, three fixed resistors, and two potentiometers.

After the multimeter and the oscilloscope, many technicians feel that the basic signal tracer is the next most valuable of bench service instruments. Essentially a self-contained audio amplifier with integral loudspeaker, the signal tracer can be used with appropriate accessory probes for checking radio and TV receivers, CB transceivers, intercoms, PA systems, tape recorders, record players, hearing aids, and stereo installations. The medium power audio amplifier IC's offered by many semiconductor manufacturers are ideal for assembling signal tracers. A typical circuit is shown in Fig. 4. Abstracted from a Fairchild Semiconductor (464 Ellis St., Mountain View, CA 94042) data sheet, the design features a type TBA800 monolithic audio amplifier IC. Assembled in a 12-pin power

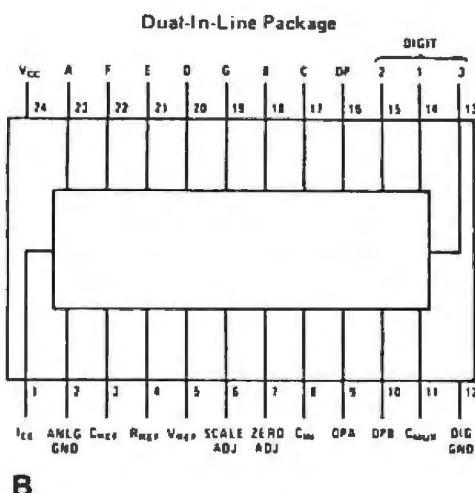

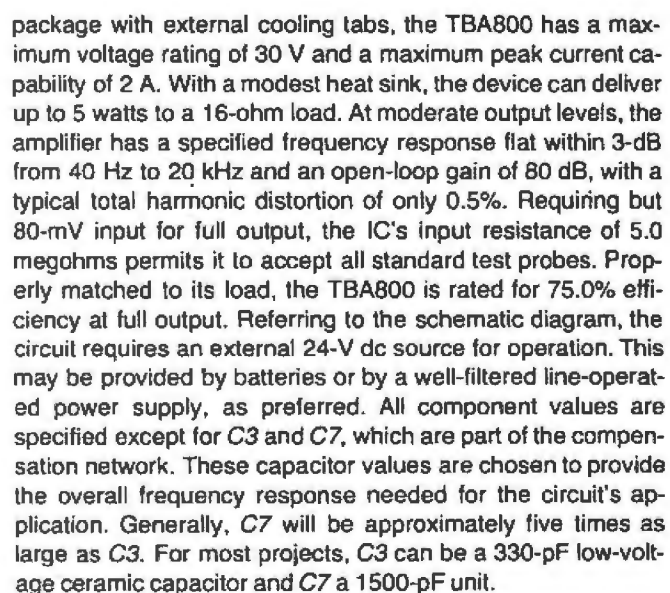Pin connection diagram for the DS2770C IC. The diagram shows connections for VCC, VEE, ANALOG GROUND, VREF, SCALE ADJ, ANALOG GND, RREF, CREF, ZERO ADJ, CREF, DPA, DPB, COUT, COUT, DIG GND, and a system of supplies. The IC pins are labeled 1 through 16. The output pins 15 and 16 are labeled D1 and D2 respectively.



Although special-purpose IC's are ideal for instrument designs ranging from digital meters to multi-output function gen-

erators, operational amplifiers, as a broad class, are probably the most versatile of all IC's for general test equipment applications. Op amps may be used, typically, in sine-wave oscillators, pulse generators, oscilloscope preamps, active filters for signal analysis, bridge amplifiers, frequency meters, and staircase generators. Two representative examples of the many possible op amp test equipment circuits are given in Figs. 5 and 6. Both circuits were abstracted from application notes published by Intersil, Inc. (10900 N. Tantau Ave., Cu-

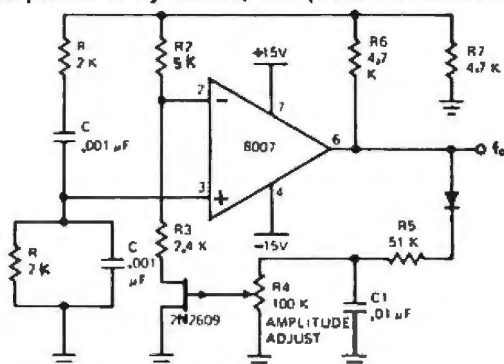


Fig. 5. Op amp Wein bridge oscillator described in an Intersil application note.

pertino, CA 95014), both feature FET-input op amps, and both are designed for operation on standard ± 15 -volt dual dc power sources.

Capable of delivering an output signal of 20 volts peak-to-peak, the Wein Bridge oscillator circuit shown in Fig. 5 may be used either alone as a test-tone source or as part of a complete audio-signal generator design. A type 8007 op amp serves as the basic oscillator, with a 2N2609 JFET used as a feedback element to provide amplitude control. In operation, the circuit's output frequency is determined by the values of the resistors and capacitors in the bridge feedback network and may be calculated from

$$f_0 = 1/2\pi RC,$$

where the frequency, f_0 , is in Hz, R is in megohms and C in μ F. Multiple output frequencies may be provided by using a number of different RC values, selected by means of a suitable multiposition switch. Continuous frequency coverage within a broad range can be obtained by replacing the two fixed resistors in the feedback network with a matched-pair gang potentiometer. The two techniques can be combined, of course, with switch selectable capacitors establishing different ranges and continuous coverage within each range provided by the ganged potentiometers.

Suitable for use in a variety of test equipment designs from counters to characteristics curve analyzers, the staircase generator circuit illustrated in Fig. 6 develops a cyclic stepped output signal waveform. Its active device complement includes a type 8043 dual op amp, a pair of low-leakage diodes, a type 1H5042 CMOS analog switch, and a type 311 voltage comparator. In operation, a high-frequency clock (square-wave) signal is applied to the first op amp, half of an 8043. Amplified, this signal drives the second op amp, which, in turn, charges a 0.02- μ F capacitor in small steps through a pair of low-leakage diodes. The capacitor's instantaneous voltage level is continuously compared to an externally applied dc reference by the 311 voltage comparator. When the capacitor voltage reaches the preestablished level, the comparator applies a signal to close the analog switch, discharging the capacitor to end the cycle and reset the circuit. The relative time width of

each step is determined by the initial clock frequency while the number of steps per cycle and hence the cyclic rate is established by the dc reference voltage applied to the 311 comparator.

Looking to the future, the next major evolutionary step in test instrument design probably will be the increased use of microprocessors and memory circuits. The use of these devices will permit the development of a whole family of automatic test instruments . . . units capable of performing a broad series of tests and, perhaps, of even changing the test procedures on the basis of initial results. More sophisticated future instruments may even provide aural outputs, telling the service technician where a circuit defect is located and which component or device should be replaced.

Reader's Circuit. Faced with frequent power interruptions in his area and having electrical equipment which required special start-up procedures if the ac power was removed for more than a few seconds, reader John M. King (1194 Idylberry Road, San Rafael, CA 94903) devised the protective control circuit shown in Fig. 7. The control is designed to maintain power-line contact with the protected equipment for short intervals in the event of a power failure, but to disconnect the equipment if the failure period exceeds a preset limit.

As shown in the schematic diagram, line power is applied to the external equipment connected to the dual outlet (SO1) through the contacts of relay K1 which, in turn, is controlled by a solid-state sensing circuit. Step-down transformer T1 in conjunction with bridge rectifier RECT1 and filter capacitor C1 form a dc power supply for the control circuit. Equipment operation is initiated when pushbutton S1 is depressed, turning on SCR1 and energizing K1. With SCR1 conducting, a dc charge is maintained on C2 by current flow through blocking diode D1. Should a momentary power failure occur, SCR1 will continue to conduct until C1 is discharged below the SCR's maintenance voltage, holding K1 closed and permitting the immediate reapplication of power to the external equipment. Thereafter, the SCR will switch to a high impedance state,


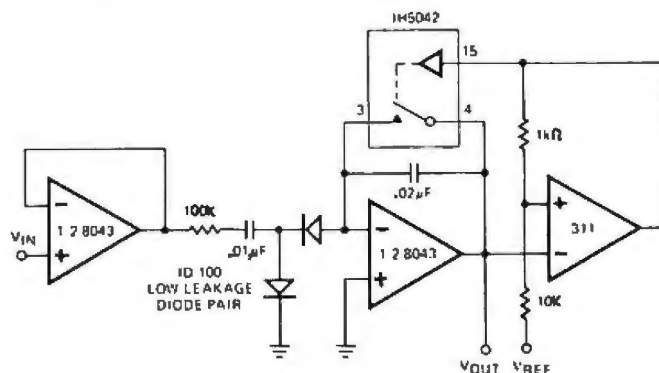


Fig. 6. Another Intersil circuit shown here is an op amp staircase generator.

opening the relay. However, a small gate voltage will be maintained on the SCR for a short while by the accumulated charge on C2. Thus, if ac line power is restored before C2 is discharged below the level needed to "fire" the SCR, circuit operation will be initiated automatically. If the power failure interval is longer than the time required for C1 and C2 to discharge, operation must be restarted manually by depressing S1, permitting the operator to carry out any necessary start-up procedures required by the protected equipment.

John used Motorola semiconductor devices in his design,

Fig. 7. This circuit maintains power-line contact during short power outages but will disconnect the equipment if failure exceeds a preset limit.

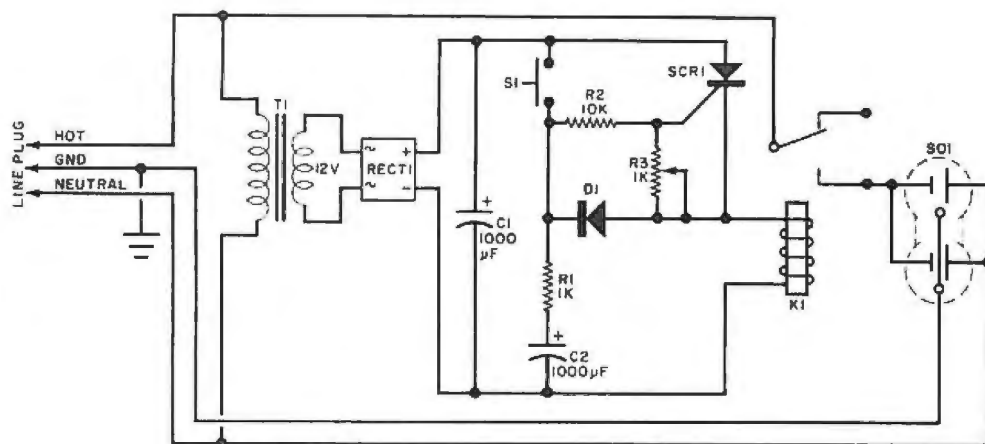

with the bridge rectifier a HEP type R0801, SCR1 a HEP type R1216, and diode D1 a HEP R0050. The step-down transformer may be any standard type with a 12-volt, 500-mA secondary. Resistors R1 and R2 are half-watt types. Capacitors C1 and C2 are 16-volt electrolytics. A 12-volt dc relay with a 95-ohm coil and contacts rated at 10 A is used for K1, while the control switch, S1, is a spst, momentary contact, NO pushbutton or lever type. Finally, the receptacle (SO1) is a familiar 3-wire dual wall outlet.


With neither layout nor lead dress critical, the circuit can be duplicated using any preferred construction technique but, for maximum safety, the wiring should be housed in a sturdy (and grounded) metal case or box. According to John, the time delay before manual resetting is required can be adjusted (by means of R3) between 1 and 12 seconds, which is more than adequate for most momentary power interruptions. If, for some reason, a longer delay is required, this may be achieved by increasing the values of C2, R2 and R3. Delays of up to a minute or two should be feasible with standard components.

Device/Product News. RCA's Solid State Division (Box 3200, Somerville, NJ 08876) has added a new series of devices to its growing family of BiMOS (Bipolar/MOS) operational amplifiers, which feature MOSFET inputs and COS/MOS outputs. The new CA3160 series are frequency-compensated versions of the earlier CA3130 series op amps, and feature gate-protected p-channel MOSFET's in the input stage to provide input impedances of 1.5×10^{12} ohms (typical), very low input currents (5 pA typical at 15 V), and exceptional speed performance. In each, the output stage employs a complementary-symmetry MOS transistor pair capable of swinging the output voltage to within 10 mV of either supply voltage terminal, permitting direct interface with either CMOS or bipolar 7400 TTL series devices. Other features include wide bandwidth (15 MHz), high slew rate (10 V/µs unity-gain follower), and strobing capability to reduce standby power consumption. Suitable for applications in sample-and-hold amplifiers, long duration timers, wideband amplifiers, voltage followers, voltage regulators, Wein Bridge oscillators, VCO's, and photo-diode sensor amplifiers, the devices are offered in both standard and dual-inline formed 8-lead TO-5 packages.

In addition to its special purpose test instrument IC's, National Semiconductor has announced a new family of positive regulators with several fixed output voltages in three temperature ranges. Identified as the LM140LA series, the new devices have a 2.0% output voltage specification, 0.04%/volt line regulation, a 0.01%/mA load regulation, and can deliver up to 100 mA with adequate heat sinking. Offered in metal

TO-39 and plastic TO-92 packages, the new regulators are available with outputs ranging from 5.0 to 24.0 volts. All of the devices are protected by internal current limiting and thermal shutdown circuitry.

International Rectifier's Semiconductor Division (233 Kansas St., El Segundo, CA 90245) has recently introduced a pair of 900-volt npn transistors with power dissipation ratings of 50 watts. Designated types IR 708 and 709, the new units are suited for applications in video deflection circuits, high-voltage switching power supplies, power controls, and switching regulators. Both offer continuous collector current ratings of 3 A with fall times of 1.5 µs, and both are supplied in standard TO-3 metal cases. ◇

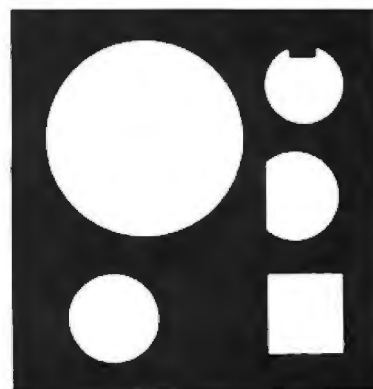

Put more punch in your work.


With a Greenlee Chassis Punch you can punch clean, true holes in seconds. Round, square, key or D. In 16-ga. metal, hard rubber, plastic or epoxy. Available at radio and electronics parts dealers. Write for catalog E-730. Greenlee Tool Co, Rockford, Ill. 61101.

GREENLEE TOOL CO

a subsidiary of

Ex-Cell-O Corporation

CIRCLE NO. 21 ON FREE INFORMATION CARD

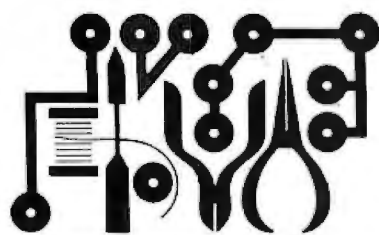

Experimenter's Corner

By Forrest M. Mims

THE 556 DUAL TIMER

IF THERE'S anything better than the popular 555 timer, it's the 556 dual timer. The 556 is two 555's on a single chip packaged in a 14-pin DIP. The pin outline of this versatile chip is shown in Fig. 1. Either or both halves of the 556 can be used for all the standard 555 applications. This month, we'll look at several that use two 555's and are therefore ideally suited for the 556.

generator. The tone continues until the one-shot's timing cycle is complete. The result is a tone burst which you can use for signaling, alarms, electronic music, and other effects.

You can experiment with the various timing and frequency-controlling components (R_1 , C_1 , R_2 , R_3 and C_4) to produce different sound effects. Remember that you're looking for a tone which con-

timing capacitor. The 556 dual timer makes it easy to double the time delay of a single 555 by connecting the output of the first chip to the input of the second. After the first timer completes its timing cycle, it triggers the second timer.

A timer using this principle is shown in Fig. 3 where R_2 and C_1 determine the time delay of the first timer and R_3 and C_4 determine the delay of the second timer. The output of the first timer is coupled to the input of the second by C_5 .

Operation of the circuit is straightforward, and you should easily be able to generate time delays of more than twenty minutes. Though Fig. 3 shows potentiometers for R_2 and R_3 , you can use fixed resistors if you prefer. The potentiometers, of course, are handy for altering the delay of each half of the timer.

You can also use a range of values for C_1 and C_4 . Naturally, large-value capacitors will give long time delays; but if you only need a delay of a few minutes or so, you can use less costly units.

Finally, though the main purpose of this circuit, which I've borrowed from Signetics, is to extend the time delay of a single 555, you might want to take advantage of the first timer's output, too. Lots of interesting sequencer applications are possible since each timer can be adjusted for a different timing period.

Extra-Long Time-Delay Circuit. A neat way to increase the time delay of a single 555 by a factor of ten is to connect a low-cost TTL decade counter like the 7490 to the basic timer circuit. This trick can provide time delays of up to a few hours—even more if you use a high-quality timing capacitor.

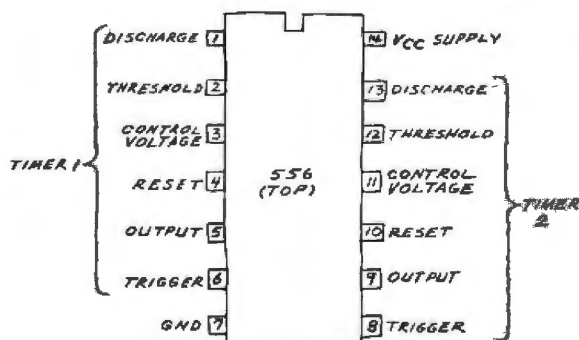


Fig. 1. Pin outline of the 556 timer.

Tone-Burst Generator. Figure 2 shows a circuit for a tone-burst generator using a single 556 dual timer. The first half of the 556 is connected as a monostable multivibrator (one-shot) whose timing period is controlled by R_1 and C_1 . The second half of the 556 is connected as an astable (free-running) multivibrator which produces an audio tone with a frequency governed by R_2 , R_3 and C_4 .

Normally the speaker is quiet; but when pushbutton switch S_1 is pressed, the one-shot begins its timing cycle while simultaneously activating the tone

tinues after S_1 is released, so adjust R_1 until this occurs.

Dual-Action Timer Circuit. The maximum time delay of a single 555 timer is limited to ten or fifteen minutes unless you use an expensive low-leakage

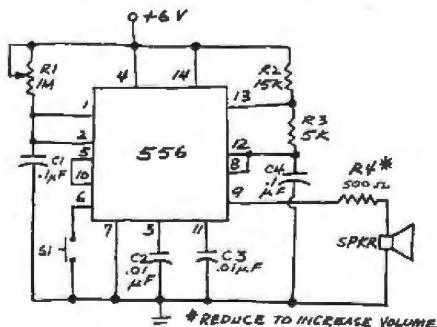


Fig. 2. Tone-burst generator.

Fig. 3. Dual-action timer circuit using the 556 IC.

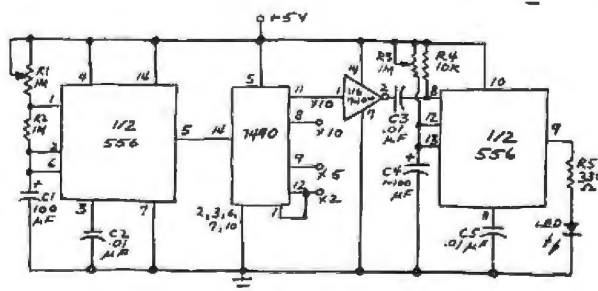
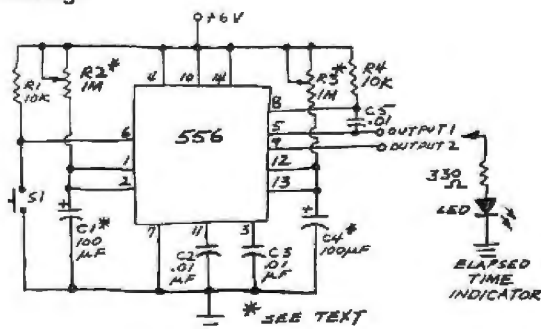


Fig. 4. Extra-long time delay circuit.

Operation of this circuit is made possible by the divide-by-ten operation of the 7490. The 7490 simply counts input pulses from the 555 until ten have been received. It then produces an output pulse of its own.

It's possible to connect the divide-by-ten output of the 7490 directly to an elapsed-time indicator such as an LED or audio oscillator. A better approach, however, is to connect a second 555 hooked up as a one-shot to the 7490. The one-shot is easy to adjust, and it will turn on the elapsed-time indicator for a fixed length of time. This is a handy feature if you want to use a bell or buzzer as an elapsed time indicator since the second 555 will trigger a quick burst of sound instead of a continuous noise.

Figure 4 shows how everything is connected together. A single 556 takes the place of the two 555 timers. One of the inverters in a 7404 hex inverter complements the output signal from the 7490 to provide the proper triggering potential. If you don't have a 7404 handy, use one of the gates in a 7400 quad NAND gate. Connect the two inputs of one gate together to form the inverter's input. (For example, connect pins 1 and 2 of the 7400 to pin 11 of the 7490. Connect pin 3 of the 7400 to pin 8 of the 556. Connect pins 14 and 7 of the 7400 to the positive and ground connections, respectively.)

The extra long timer circuit has several features you'll want to tinker with. First, note that potentiometer *R1* sets the delay time while potentiometer *R3* sets the on time of the elapsed time indicator. I used an LED for the elapsed-time indicator in the prototype circuit, but you can use a relay if you prefer (Radio Shack 275-004 or equivalent).

Second, note that the 7490 has four outputs. Both pins 11 and 8 will provide a time delay ten times that of the first 555 (one pulse out for every ten pulses in). Pin 9 will provide a time delay five times that from the 555. And pin 12 will provide twice the delay available from the 555.

Finally, if you want *really* long delays, you might consider connecting one or more additional 7490 decade counters in series with the first. Just connect pin 11 of the first 7490 to pin 14 of the second 7490. Pin 11 of the second 7490 goes to still another 7490 or to the inverter. Incidentally, note that this circuit is a repetitive, free-running timer. In other words, it begins a new timing cycle immediately upon completion of the first. Keep this in mind if you decide to tinker with super-long time delays.

FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

SEND TODAY!

McIntosh Laboratory, Inc.
East Side Station P.O. Box 96
Binghamton, N.Y. 13904
Dept. PE

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

If you are in a hurry for your catalog please send the coupon to McIntosh.
For non rush service send the *Reader Service Card* to the magazine.

CIRCLE NO. 26 ON FREE INFORMATION CARD

BUILD YOUR OWN

BIG SCREEN COLOR TV!

YOU ASKED FOR IT!

THE NEW LIFESCREEN II



The SELF-CONTAINED internal projection TV that will utilize any transistor portable TV (12" to 18") ... requires only 2 x 4 feet of floor space ... fits neatly against any wall ... and lends its beauty to the decor of any room.

COMPONENT LIST

- 1 set of LIFESCREEN II Plans
- 1 Portable transistor Color TV (12" to 18")
- 1 LIFESCREEN Lens
- 2 LIFESCREEN Front Surface Mirrors, one 8"x10" and one 14"x20"
- 1 EXTRON LS 50 Screen, 32"x40" (50" Diag.)

WE HAVE RECEIVED THOUSANDS OF INQUIRIES!

YOU REQUESTED PLANS FOR A BIG SCREEN TV THAT WOULD:
utilize any portable TV as an image source - require a minimum of floor space
- be a beautiful piece of furniture.

NOW - EXTRON IS HAPPY TO ANNOUNCE

THE NEW LIFESCREEN II

The LIFESCREEN was designed for the Do-It-Yourself enthusiast who wishes to have the enjoyment and excitement of a professional Big Screen TV - but refuses to pay the \$1500 to \$4000 that most manufacturers charge for this luxury.

FACTS

The special LIFESCREEN, Lens and Front Surface mirror supplied by Extron are the same type used by major Big Screen TV manufacturers (Sony, Muntz, etc.). THESE PROFESSIONAL COMPONENTS SHOULD NOT BE CONFUSED WITH THE CHEAP PLASTIC MAGNIFYING IMITATIONS NOW FLOODING THE MARKET BECAUSE OF THE POPULARITY OF BIG SCREEN TV. The EXTRON TV Screen - the same used by the major Big Screen TV manufacturers - is 16 TIMES BRIGHTER than a flat matte surface and 8 TIMES BRIGHTER than most flat beaded mirror screens. Its parabolic shape rejects extraneous light, concentrating a highly efficient and directionally selective television image that is exceptionally sharp and colorful.

COMPLETE LIFESCREEN II PACKAGE

\$299

THE EVERYTHING GUARANTEE
EXTRON GUARANTEES EVERYTHING: THE PROFESSIONAL QUALITY, ACCURACY OF DESCRIPTION, AVAILABILITY AND PROMPT DELIVERY OF COMPONENTS DESCRIBED IN THIS AD. If, after building your LIFESCREEN PROJECTION SYSTEM, you are not satisfied for any reason, return all components to EXTRON, 8831 Sunset Boulevard, West Hollywood, California for instant refund of the purchase price.

\$269

The INDEPENDENT projection system that can be used with ANY SIZE screen up to 80" Diagonal - one of the many reasons for its tremendous success.

COMPONENT LIST

- 1 set of LIFESCREEN I Plans
- 1 Sharp 13" Model 13A21 Color TV or Sony 15" Model KV-1541R Color TV
- 1 LIFESCREEN Lens
- 1 LIFESCREEN Front Surface Mirror, 8" x 10"
- 1 EXTRON LS 50 Screen 32"x40" (50" Diagonal)

LARGER SCREENS can be ordered through EXTRON (67" or 80" Diag.)

- ☐ PLEASE RUSH ME ONE COMPLETE SET OF LIFESCREEN I PLANS \$19.00
- ☐ PLEASE RUSH ME ONE COMPLETE SET OF LIFESCREEN II PLANS \$19.00

PLEASE ALSO SEND ME THE ITEMS CHECKED BELOW

- ☐ LIFESCREEN LENS \$150.00
- ☐ LIFESCREEN FRONT SURFACE MIRROR, 8" x 10" \$30.00
- ☐ LIFESCREEN FRONT SURFACE MIRROR, 14" x 20" \$50.00
- ☐ EXTRON LS 50 SCREEN 32" x 40" (50" Diagonal) \$90.00

- ☐ COMPLETE LIFESCREEN I PACKAGE \$1269.00
- ☐ COMPLETE LIFESCREEN II PACKAGE \$1299.00

All Prices F.O.B. factory - Cal. residents add 6.75% sales tax

TOTAL: \$

EXTRON LIFESCREEN PROJECTION SYSTEM
8831 Sunset Boulevard,
West Hollywood, California 90069

Name _____
Address _____
City _____ State _____ Zip _____

CARD NAME _____
CARD NUMBER _____
EXPIR. DATE _____

INFO PAK 50c

Hobby Scene

TVI AND CB TRANSCEIVERS

Q. I have a TVI problem whenever I use my CB transceiver. My neighbors get very upset and tell me to turn off the radio. Is there anything I can do without going off the air? —Dwayne Edwards, Canton, NY.

By John McVeigh

STATIC CRASHES


Q. Please advise how to eliminate unbearable noise that my school's heating system produces on my Halli-crafters SX62A shortwave receiver. A line filter was tried to no avail. The most deafening noise is heard for two or three seconds between 5 and 18 MHz.—Gerard Richard, Sherbrooke, Quebec, Canada.

A. It sounds like a thermostat or thermostat-controlled power relay is arcing and generating r-f crashes. If you can "sniff out" the source with a small field-strength meter or even a portable radio (the static should also affect the AM broadcast band), try placing a suitable bypass capacitor across the arcing thermostat or relay contacts. A 0.1- μ F, 1000-V ac disc ceramic capacitor should squelch the r-f. If you can't locate the source, try the "Ear Saver" circuit shown in the Hobby Scene column on p. 34 of the January 1977 issue.

RESISTOR QUIZ

Q. Here's a problem which was posed by one of my professors. You have an infinite lattice of 1-ohm resistors as shown in the diagram. What's the effective resistance between points A and B?—Bryan Baker, Houston, TX.

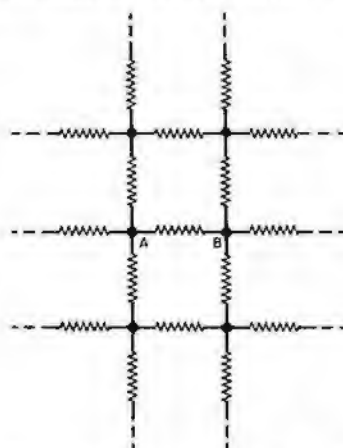A. Offhand, I think the effective resistance is zero ohms. There is an infinite number of resistors in parallel, and




even though the further away from A and B the more series resistors you have in each parallel combination, it looks like the resistance will go to zero. The only other solution I could possibly see is a finite limit in the parallel combinations. But my tendency is to say zero ohms. Actually, the effective resistance of an ever-increasing number of parallel resistors will approach zero ohms, but will never reach it—just like the graph of a hyperbola or an exponentially decaying function. If any reader comes up with different solution, feel free to send it in!

TRIGGERING THYRISTORS

Q. I would like to control 120-volt ac devices with TTL logic without using relays. Is there a way to do this using triacs or SCR's? They would only have to handle 1 or 2 amperes.—Dominick Testa, Skokie, IL.

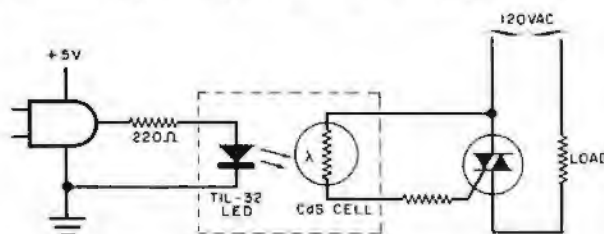A. The easiest way to trigger an SCR or triac from a TTL output is to use an optoisolator. It is essentially a LED, a cur-

rent limiting resistor, and a photocell. Of course, you can make your own optoisolator by enclosing the LED and CdS cell in a light-tight box. Connect the optoisolator as shown in the figure. An external current limiting resistor may be needed to keep the thyristor's gate current to a safe value. This depends on the lit resistance of the CdS cell. Using a 10,000-ohm, 1/4- or 1/2-watt series resistor will limit gate current to 17 mA peak.



A. If your CB transceiver is a fairly recent vintage, type accepted, and used properly, it should not be generating TVI. Often, the interference is the result of overload within the TV receiver in the presence of a strong 27-MHz signal. The way to identify overloading is to determine the extent of the interference at the TV receiver. If TVI occurs on all channels, receiver overloading is the culprit. Visual interference can range from fine cross-hatching to a completely dark screen. When the sound portion of the program is also subject to interference, overloading is taking place.

The cure for this problem is to prevent the CB signal from reaching the TV. This can usually be done by attaching a high-pass filter such as the Drake TV-300-HP (for twinlead) or TV-75-HP (for RG-59-U coax) at the antenna terminals on the back of the receiver. In some cases, the filter will have to be installed at the tuner input inside the receiver's enclosure. When the CB signal is really strong, the use of the high-pass filter might have to be supplemented by more effectively shielding the receiver. Fine copper or brass screening or flashing carefully installed (beware of accidental shorts!) can be installed on the inside of the TV enclosure and grounded.

When visual interference occurs only on TV channels harmonically related to the 27-MHz Citizens Band (principally Channel 2 at 54 MHz and Channel 5 at 81 MHz), the transceiver is radiating undesired signals. This can occur when the transceiver circuitry is improperly adjusted or operated. Over-modulation from "power mikes" is a common cause of harmonic radiation. Don't overmodulate the transceiver and don't use a power amplifier. If the harmonic suppression of the transceiver must be improved, insert a low-pass filter in the coax transmission line close to the transceiver. Be sure you use a filter with a cut-off frequency around 40 MHz and attenuation of at least 60 dB at TV frequencies (Drake TV-42-LP or equivalent).

Have a problem or question on circuitry, components, parts availability, etc? Send it to the Hobby Scene Editor, POPULAR ELECTRONICS, One Park Ave., New York, N.Y. 10016. Though all letters can't be answered individually, those with wide interest will be published.



Product Test Reports

COBRA MODEL 29XLR MOBILE 40-CHANNEL CB TRANSCEIVER

Digital readout AM rig provides strong transmission punch.



DYNASCAN's Cobra Model 29XLR is a handsome 40-channel AM CB mobile transceiver that uses digital frequency synthesis and a red LED numeric display for channel identification. It incorporates such features as: display dimmer control, illuminated S/r/relative-power meter, LED transmit/modulation indicator, microphone and r-f gain controls, and switchable noise blanker (NB) and automatic noise limiter (anl). In addition, the transceiver has audio, squelch, and Delta tune controls; PA facilities; external-speaker jacks; automatic modulation control (amc); detachable dynamic microphone; bottom-facing speaker; line filter; and reverse-polarity protection. Operation is from a nominal 13.8-volt dc source with negative or positive ground.

The transceiver measures 9½"W × 7¼"D × 2¼"H (24 × 18.5 × 5.6 cm). Suggested list price is \$229.95.

Technical Details. The receiver employs double conversion, with frequency control provided by a phase-locked-loop (PLL) frequency synthesis system. A 10,695-kHz first i-f is obtained by heterodyning the CB signal with the PLL's voltage-controlled oscillator (vco) signal in the range of 37,660 to 38,100 kHz. The second conversion is to a 455-kHz i-f with a 10,240-kHz crystal oscillator, from which a 10-kHz standard reference for the PLL system is also derived through dividers. The 10-kHz vco comparison

signal is set up by combining the output of the vco with a 36,570-kHz crystal signal at a "down" converter (mixer). The difference frequencies are extracted and go to an IC divider that is controlled by the channel-selector switch.

Inductively coupled circuits at the input of the r-f amplifier and output of the second mixer, along with a bandpass-coupled circuit between the mixers, aid in good image and unwanted-signal rejection. This is augmented by a 10,695-kHz ceramic filter after the first mixer. The 455-kHz selectivity is also obtained with a ceramic filter.

Two i-f stages are followed by a diode detector and agc, the switchable anl, squelch system, and an IC audio section. The noise blanker employs an IC r-f amplifier/detector and three pulse amplifiers for gating the output of the second mixer. Electronic voltage regulation is supplied for all critical circuits.

The transmitter combines the output of the vco with a 10,695-kHz crystal oscillator signal, using the difference frequencies, at a dual-gate MOSFET transmitter mixer that is followed by bandpass coupling and the usual r-f stages. The multi-section output network includes a TVI trap. The SWR bridge is a trough-line type. The collectors of the driver and power amplifier stages are modulated by the receiver's audio output stage, providing the customary high- and low-level class-B modulation. Amc is obtained with a bootstrap setup

around an IC microphone amplifier. Transmit/receive transfer is conducted electronically.

It is interesting to note that the 29XLR utilizes ferrite beads at strategic points in place of wire-wound r-f chokes. These beads slip over a lead of the circuit to be isolated or stabilized. The beads save space, hold down circuit resistance, minimize resonance effects, and are highly effective in comparison to the wire-wound chokes.

Test Results. Receiver sensitivity of the Cobra 29XLR measured 0.5 μ V (with 30% modulation at 1000 Hz). Image and i-f signal rejection measured 80 dB minimum, while spurious response rejection of signals near the CB range was 45 dB. Adjacent-channel rejection and desensitization were nominally 60 dB. The overall 6-dB audio response was 240 to 2400 Hz. The maximum sine-wave output power measured 2.75 watts at 3% THD at 1000 Hz into 8 ohms at the onset of clipping. It measured 3 watts in the PA mode.

The agc held the audio output to within 10 dB with a 26-dB r-f input change at 0.5 to 10 μ V and to 13 dB with an 80-dB input change at 1 to 10,000 μ V. A nominal 50- μ V signal registered S9 on the signal meter. The threshold range of the squelch circuit was 0.3 to 10,000 μ V.

The transmitter put out a 4-watt carrier with operation from a 13.8-volt dc source. The modulation capabilities ran up to 100%. With the microphone input level raised 25 dB above the level required for 50% modulation, the THD was 7% at 1000 Hz, and the modulation held to just within the legal limit. The THD with a 400-Hz test tone was noticeably greater in both waveform observation and measurement, the latter varying between 10% and 20%, depending on the level of the amc.

We obtained high average modulation with voice inputs without overmodulation or adverse splatter. With voice input or 1000-Hz tone, the splatter at \pm 5000 Hz from the carrier frequency was at least 60 dB down. Using a 2500-Hz tone input, it was 50 to 55 dB down. The overall 6-dB audio response of the transmitter was 400 to 2300 Hz. R-f frequency tolerance on any channel was within \pm 3 Hz of -110 Hz.

User Comment. This is a smartly styled mobile transceiver, set in a black case with brushed silver-colored front panel and chrome-trimmed knobs. The control knobs are located in a row along the lower half of the front panel.

Our one complaint about the control sequence arrangement is that the DYNA MIKE (microphone gain) control is located at the far left of the panel, where we automatically reach for the more-often used VOLUME control.

The channel selector control knob has a bar grip that makes it easy to manipulate. Other switching functions are handled by miniature toggle switches located in a line across the top of the front panel between the meter and numeric display. Two of these switches have three positions that do not have much lever swing, which sometimes makes it difficult to stop at the center position. A two-position switch, H.F./OFF, switches in and out a "hash" filter that is a fixed-setting tone control that drops the upper frequency response to minimize high-pitched noises.

The edgewise meter is easier to read than most other similar meters we have encountered. It is illuminated whenever the transceiver is turned on except when

in the PA function. Hence, instead of having the numeric readout display the letters PA, as is generally the case, the meter's light extinguishes to indicate that the transceiver is in the PA mode.

We determined that, when the transmitter is working into a nonreactive 50-ohm load (representing a 1:1 SWR), the actual r-f output was accurately indicated at any point on the meter's SWR scale. (This does not necessarily hold true for other loads or high SWR's.)

Use of the noise blanker allowed readability of weak signals in the presence of high impulse noise from our impulse-noise generator. It was similarly effective on ignition noise in a vehicle, where it almost entirely eliminated the noise (with a slight loss in signal level). The ant also performed well.

Although the speaker in this transceiver is bottom facing, its sound reproduction is clean and crisp without the usual muddyness associated with bottom-facing speakers. It provided good readabil-

ity in our on-the-road tests. It should be noted that the microphone must be plugged into its connector to permit the speaker to function.

On-the-air, we obtained a hefty punch from the amc system, which prevented overmodulation even when the microphone gain was fully advanced. We experimented with the DYNA MIKE control to determine its best setting. The cleanest sounding signal was obtained with the mike gain reduced to the point where the MOD indicator blinked only occasionally. At this point, we still obtained a high average modulation level without sacrificing intelligibility.

The excellent performance of the Cobra 29XLR transceiver far outweighs the minor criticisms noted here. It provides high sensitivity and fine selectivity, has a good transmitted signal without adverse splatter, and possesses effective noise-handling capabilities.

CIRCLE NO. 104 ON FREE INFORMATION CARD

WAHL MODELS 7700 AND 7800 CORDLESS SOLDERING IRONS

Battery-powered irons with recharging stands.



Iso-Tip Quick-Charge Model 7700.

When electrically powered cordless soldering irons first appeared, we lauded them because they gave us freedom from the ac line. Especially useful in the field, they also proved to be very practical on our workbench. We did, however, observe one shortcoming—we could not use the cordless iron for major project and kit building that required hundreds of connections to be soldered.

It was not that a fully charged iron provided just 100 to 150 soldered joints, but that it required up to 14 hours to recharge to full capacity. Now, however, there are "fast-charge" cordless soldering irons, as examined here.

The two fast-charge soldering irons from Wahl are the Iso-Tip "Quick Charge" Model 7700 that requires about four hours to recharge and the Iso-Tip 60 Model 7800 that comes up to full charge in about 60 minutes. Both irons come with their own recharger stand. The Model 7700 retails for \$24.95, the Model 7800 for \$34.95. Available as an option is the Model 6500 (\$10.95) printed circuit board drilling attachment that fits all Wahl cordless soldering irons.

General Description. The two soldering irons feature a couple of improvements that were not part of the original Wahl cordless soldering iron we tested five years ago. The first is that the header has been redesigned to hold tips firmly in place by friction instead of with the tiny Allen-type setscrews used on the original iron. This makes installation and removal of tips a simple plug-in/pull-out operation. Of course, the tip can still be semi-permanently fixed to the header by loosening the header screws, inserting the tip, and retightening the screws.

The second improvement is in the

power-on pushbutton switch. The button is rotatable so that its index can be set to either of two positions. To use the iron, the index must be set to the USE position before it can be depressed. Only in this position can the button be depressed far enough to close the switch contacts and allow power to be applied to the tip. Whenever the iron is not in use, the button is rotated until the index is pointing to the LOCK legend molded into the iron's housing. When the button is in the LOCK position, the iron cannot be accidentally turned on, which is a good safety feature on a bench or in a crowded toolbox.

The major improvement in the new irons is the fast-charging feature. The Model 7700 iron's average four-hour recharging cycle is roughly a third of that required by the original Wahl iron. For just \$10 more, the Model 7800 cuts the recharging time of the original iron to less than a tenth. Needless to say, with either iron, you can make many times more solder joints in a workday than was possible before. Hence, you can tackle a fairly large project or kit-building job without resorting to a line-powered iron.

Special nickel-cadmium cells are used in the new irons. These cells, plus the newly designed charger stands, are responsible for the new fast-charge rates. In addition, the Model 7800 is equipped with a thermostat that automatically re-

duces the full fast-charge rate to a safe "trickle" once the cells have come up to full charge. When the cells are fully charged, and as long as the iron is still in its stand, a LED near the power switch comes on to indicate the full-charge status. A RESET switch on the left side of the iron must be pushed down to allow the iron to charge at the fast rate again.

Both irons are equipped with screw-in lamps that illuminate the work area near the tip when the power button is pressed. Also, both come with two tips, one a standard chisel and the other a fine configuration for IC soldering.

The new irons are equivalent to 50-watt line-powered soldering irons. The tips come up to soldering temperature within about five seconds after the power button is pressed, and each iron is rated to deliver approximately 160 twisted-tail solder connections, using 22-gauge wire, from full charge.

User Comment. The first test we performed on these new soldering irons was to fully charge them from the completely discharged states in which they arrived. The Model 7700 took almost exactly four hours to come up to full charge, the Model 7800 about 50 minutes. Both irons became warm to the touch, especially the Model 7800, which was quite warm when the full-charge LED came on.

Our next test was to determine approximately how many solder joints each iron would deliver from full charge. To do this, we did not replace the irons in their respective stands between solder operations as recommended by Wahl. We performed this test three times each for twisted-tail, solder-lug, and pc-board connections with both the chisel and fine points installed, recharging fully after each run. We obtained averages of 187 joints for 22-gauge twisted-tail wire connections, 131 for solder-lug connections, and 217 pc-board connections with the fine tip installed. Using the more massive chisel tip, the counts averaged 152, 114, and 180 connections, respectively. The averages were about the same for both irons.

As we were performing our solder-joint count test, we kept track of the times required for recharging to full capacity. Though the charging times did vary from charge to charge, they were well within 10% of the four-hour and 60-minute ratings specified by Wahl.

Our next test was to tackle two rather large construction projects, one a 4-k computer memory board and the other a computer I/O interface board, both of



Iso-Tip 60 Model 7800.

which required several hundred connections to be made. We found that intermittent operation of the Model 7800 iron, replacing it in its charging stand whenever it was not being used to solder a connection, allowed us to complete the entire memory board in two four-hour stints, which is about the amount of time one would normally spend on a project even with a line-powered iron. The Model 7700 iron provided enough soldering power in intermittent operation to allow

us to assemble completely the I/O port in three one-hour stints. Needless to say, we were favorably impressed by the performance we obtained from both irons, particularly the Model 7800.

In our final test, we used the irons to operate the optional pc-board drilling attachment. The attachment itself accepts a single size (No. 56) drill bit, which is good for just about all component-lead and IC-pin holes. The attachment snaps onto the tip-header end of the irons and snaps into place on the newer irons or is held in place by a small screw on the older Wahl irons. During our tests, the high-speed drill effortlessly drilled holes through paper-phenolic, polyester, and epoxy-fiberglass boards, both clad and unclad, with great accuracy and at a high-volume rate. We did not attempt to run down the power packs in the irons with the drilling attachment because, after drilling several hundred holes in each case, the irons were still going strong.

Using the irons in both field service work and on our bench, we found no faults in their performance. They are nicely contoured and light enough in weight to eliminate user fatigue. The built-in lamps accurately illuminate the work area and are very convenient when working in chassis with deep recesses. Also, the tips came up to operating temperature almost immediately.

In all, we consider either Wahl quick-charge cordless soldering iron an excellent tool for any hobbyist's workbench, the choice dictated by the amount of continuous soldering time generally needed. We also highly recommend the drilling attachment.

CIRCLE NO. 105 ON FREE INFORMATION CARD



The Model 6500 pc drilling attachment fits all Wahl cordless irons.



CB Scene

By Ray Newhall, KWI6010

THE ANATOMY OF CBRS

ALL OF US who have traveled the green stamp with wheels on our CB rigs (driven on turnpikes with mobile CB radios in our cars) know that CB makes driving safer, provides additional security in case of vehicle breakdown, and is fun to use. It keeps the driver awake and busy on the road and it makes the trip seem shorter. But does its usefulness to highway users account for the CB fever that has spread throughout America? Why have ten million people shelled-out \$100, \$200, or \$300 each for CB rigs during 1976? What prompted nearly a million new CB license applications to flood FCC offices during the single month of January 1977?

The sociologists who keep watch on the habits of the public are eyeing the CB syndrome and believe it is more than a fad which will soon pass on. They consider that it may signal an entirely new shift in sociological behavior. One Columbia University psychologist recently remarked to an FCC assemblage that the growth of CB may be one of the most healthy sociological events since the demise of the telephone party-line. For the first time in forty years there are extensive personal "one-to-one" communications occurring between people who are total strangers.

Oddly enough, this new form of personal communication we call CB has characteristics which are distinctly different from our more traditional communication forms. It is not "face-to-face" and projects an aspect of anonymity. Opinions exchanged through this media are apt to be more candid and open in nature because there is no fear of "peer disapproval" or reprisal. It is a medium in which the young and the old can communicate on common grounds and with similar interests; a far cry from the tragically common communication failures which occur between parents and their teenaged children.

Most CB'ers have given a great deal of thought to the selection of their CB handles. Handles serve a far greater purpose than to provide temporary iden-

tification between strangers on "the party line." They also serve a somewhat paradoxical purpose of revealing much of a CB'ers personality while concealing his true identity. I know several people who are making collections of the most unusual handles they hear. Some of the oddest ones are those "pairs" of handles used by a CB'er and his XYL or other members of his family.

The CB "lingo" is also unique. Although it is colorful and mystic to newcomers, it is concise and descriptive to those familiar with it, serving a true communication need. Its use gives CB'ers the feeling of belonging to a group, just as Hams are joined by their knowledge of Morse code. In fact, it is sometimes implied that one who doesn't bother to learn the CB language is not too welcome on the band.

The CB Radio Service as we see it today is a unique and useful "game" for young and old alike, and it serves the need of a mobile community. However, it is far from the type of personal radio service the FCC had in mind when the Citizen's Band was first authorized. CB was originally conceived as a two-way radio service for use by families and small businesses. Until recent years, there were only a few channels for communications between different station licensees. As the CBRS has developed today, it is not too effective for its original purpose in heavily populated areas. Yet, the need for such a service still remains!

GMRS, The Other CB Service. The CBRS (formerly the Class D service) is not the only personal radio service available to the general public. The General Mobile Radio Service (GMRS), formerly called Class A, was the first CB radio service. It was authorized in the early 1950s. Eight pairs of uhf frequencies were allocated above 460 MHz. The Class B service authorized low-power mobile two-way radio in the same frequency spectrum. Neither of these two CB services was used extensively because, until recently, we have not had

the radio technology to mass produce suitable transceivers at a price the personal user could afford. In fact, the Class B service was abandoned because it had not found any practical personal application.

However, the GMRS service is still available and has now become a high-quality, practical CB service for personal-use radio communications, although equipment cost is substantially higher than Class D gear. The new 460-MHz police communications equipment operates on assigned frequencies very close to the 462/467-MHz GMRS frequencies, and this equipment can be used. It is now feasible to mass-produce solid-state equipment to operate on uhf. On GMRS you may operate up to 50 watts input power and raise your antenna up to 200 feet in height. Line-of-sight FM transmission is most normally used. Repeaters and auto-patches are currently permitted, just as the Hams now use them on the 2-meter band.

In the Chicago, Cleveland and Dallas areas, to name but a few, GMRS "CBers" have banded together to set up community repeaters. They use 15-watt mobile units or 2½-watt hand-held transceivers to reach the repeaters for reliable rebroadcast to other stations as far as 25 to 40 miles away. In this way, they can contact their families or offices through the repeater, or they can dial direct landline calls to business associates by use of a touch-tone pad on the back of their mikes. Tone-encoded squelch circuits are said to work so well that these FM transceivers will be activated only by those calls intended specifically for them.

As a matter of fact, this columnist just mailed a Form 400 for a GMRS license to the FCC this morning. I have a standard CBRS AM unit in my car for use on the road, but it is not too practical to call my home (located in a densely populated Eastern Seaboard area) unless I'm rather close by. I operate a small consulting service and I intend to use GMRS radio to keep in touch with my customers from my car while I am within 25 miles of my home.

GMRS is not for everyone, but it does meet the needs of those who want high-grade personal and business communications. The cost is from two to five times as much as the current prices of CBRS equipment; more if you hang on all these accessories. But for many people it serves a practical purpose and in many cases may eliminate the need for telephone answering service or even a secretary. ◇



Computer Bits

ASSEMBLERS

By Hal Chamberlin

ACCORDING to a recent magazine survey, one of the most popular applications of personal computers is software development, or simply writing programs. As anyone who has been bitten by the programming bug undoubtedly knows, each new program is always bigger and fancier than the last. Beyond a certain point in program complexity, however, the use of an assembler program is almost mandatory to eliminate most of the drudgery associated with hand coding in octal or hex. This is particularly true when one wishes to make a "small improvement" to a hand-assembled program which otherwise requires it to be rewritten.

Functions of an Assembler. Using an assembler in machine language program development has three important advantages over hand coding. First, an assembler allows the programmer to use operation mnemonics such as "LDA" for the "load register A" operation rather than the octal code 072 (8080 microprocessor). When looking at a program you wrote several weeks ago or one written by somebody else, the LDA is much more meaningful than the 072, which in turn makes the program easier to understand.

The second and most important advantage is that the addresses of sections of code and data items can be given *symbolic names* and referred to by name. Again, a name like TAXTAB used to refer to a table of tax rate data is more meaningful than its address which might be 005:120. The most important benefit of symbolic names comes when a program is changed for some reason. With a hand-coded program, some of the addresses used in the program would probably have to change as sections of the program and data are shuffled around to make room for additions. Then, every reference to addresses that were changed would also have to be changed. The result is that, in a large program, a considerable number of changes may be necessary for what

would otherwise be a minor addition. With symbolic names, the assembler can do all of the address shuffling when the program is reassembled and the programmer need be concerned only with the additions. The concept is analogous to solving an equation in general using symbols and algebra and then substituting actual values into the *solution* rather than solving the equation for each set of values needed.

A third advantage is that the use of an assembler tends to develop good program documentation habits which adds to the value of a program. All assemblers allow the latter part of each statement to be used for comments. A well-written program has an English explanation of what the machine instructions are accomplishing as comments on nearly every statement. A neat assembly listing of a program is also much easier to reproduce and read than hand scrawls on coding sheets. Conversely, buying a machine language program without documentation in the form of commented assembly listings is like buying electronic equipment without a schematic.

Using the assembler program itself is generally quite simple. First the assembly language program which is called a *source program* is converted into machine readable form. Such a form may be ASCII characters on paper tape, audio or digital cassette records, floppy disk sector records, or even ASCII data in memory depending on the system and assembler used. Usually some kind of program editor is used to aid in entering and editing the source program. Next the assembler is loaded and ex-

ecuted. During execution, the assembler will scan the source program and produce a *listing* file containing a copy of the source program along with the octal machine codes and an *object* file containing only the machine codes.

The assembler may also flag some statements as having errors. Common errors that an assembler can catch include using non-existent instruction mnemonics and undefined symbols. The latter is the case when a reference is made to a symbolic address but an actual address is never assigned to the symbol. These and other errors detected by the assembler are usually caused by typing mistakes. After editing the source program to eliminate errors and reassembly, the object program is ready to be loaded into memory and executed.

Types of Assemblers. Although all assemblers perform basically the same function, there is considerable variety in the implementation and use details. Perhaps the most distinguishing characteristic is the number of scans or *passes* over the source code done by the assembler.

A classical assembler makes two passes over the source program. During the first pass, all symbol definitions are searched out and placed in a *symbol table* maintained by the assembler. During the second pass, the mnemonics are translated into their octal equivalents and the listing file and object file are generated. The two passes are needed because a reference to a symbolic address may occur in the program ahead of the definition of the symbol. This is called forward referencing. If the assembler is to know what octal address to substitute for the symbol, it will have to see the definition first.

Several attempts have been made at one-pass assemblers and a couple of these are available on hobbyist systems. The advantage of a one-pass assembler is increased assembly speed since the source file, which may be many thousands of characters in length, needs to be read only once. Often however the one-pass assembler imposes

```
.MACRO
*   MACRO DEFINITION FOR A DOUBLE PRECISION ADD FROM MEMORY
*   MACRO-INSTRUCTION
*   ADDS THE CONTENTS OF $ADDR AND $ADDR+1 TO REGISTERS B AND
*   C WITH THE RESULT IN H AND C, CONDITION FLAG UNAFFECTED

$BL:  DPAD $ADDR          DOUBLE PRECISION ADD PROTOTYPE

      PUSH H              SAVE H AND L
      LHLD $ADDR          GET TWO BYTES TO ADD IN H AND L
      DAD H               ADD THEM TO B AND C
      MOV B,H             COPY RESULT INTO B AND C
      MOV C,L
      POP H               RESTORE H AND L
      MEND
```

Fig. 1. Example of macro definition.

restrictions on program organization and the free placement of symbols. This is due to the "look ahead" problem mentioned earlier. Sometimes a one-pass assembler is "faked" by a two-pass one. In this case the source file is read for the first pass and then saved in memory for the second pass which is invisible to the user. The difficulty with this approach is that a large amount of memory is needed to assemble a reasonably large program.

Occasionally a "three-pass" assembler is seen. These are really two-pass assemblers with the second pass split in two to accommodate a Teletype with built-in paper tape. These machines cannot punch the object file at the same time as printing the listing file so a separate pass is required for each function.

A *conversational* assembler is another variation. Basically a combination of a simple text editor and a conventional assembler, the conversational assembler is very convenient for experimentation and testing of short programs and subroutines. Operation of a conversational assembler is much like most BASIC language systems. The program is typed in line-by-line and edited using line num-

bers and simple editing commands. When a RUN command is given, the program is quickly assembled directly into memory and executed. Program size is limited since the source program ASCII text, symbol table, and object program as well as the conversational assembler program itself must all fit into memory at once.

Advanced Assembler Features.

As assembly language programming experience increases, some of the more sophisticated assembler features available will be appreciated. Although these features have been rare in hobbyist oriented systems, the assemblers being supplied with recently announced floppy disk systems generally have most of them.

One such feature is *macro-instruction* capability. A macro-instruction (often abbreviated as "macro") is one that may generate many machine language instructions when assembled. When writing a program, macro-instructions may

same dummy argument in the LHLD instruction as in the prototype. The .MEND signals the assembler that the macro definition is complete. The definition is then saved by the assembler in a special table in memory reserved for that purpose.

Figure 2 shows the use of this macro-instruction in a program (octal). In this example all of the instructions generated when the macro was expanded are shown on the listing with a preceding minus sign. Generally the assembler will have a command that would suppress printing of these expansion instructions if desired. With a good library of macro definitions, assembly language programming may become almost as easy as programming in a higher level language.

Another advanced feature is called "relocatable object code" capability. An assembler having this feature supplies additional information in the object file so that it may be later loaded into memory *anywhere* desired completely auto-

EXAMPLE PROGRAM SEGMENT ILLUSTRATING USE OF DPAD MACRO

001:100 116	MOV C,M	LOAD ORIGINAL RAW VALUE (16 BITS)
001:101 043	INX H	
001:102 106	MOV B,M	
001:103	DPAD CORR	ADD IN CORRECTION FACTOR
001:103 345	PUSH H	SAVE H AND L
001:104 052 200 001	LHLD CORR	GET TWO BYTES TO ADD IN H AND L
001:107 011	DAD B	ADD THEM TO B AND C
001:110 104	MOV B,H	COPY RESULT INTO B AND C
001:111 115	MOV C,L	
001:112 341	POP H	RESTORE H AND L
001:113 160	MOV M,B	UPDATE WITH CORRECTED VALUE
001:114 053	DCX H	
001:115 161	MOV M,C	

Fig. 2. Example of use of a macro-instruction.

be used just as if the microprocessor actually had them as real instructions in its repertoire.

Macros can be defined by the programmer at the beginning of his program according to his needs. Although exact details of macro definitions and usage differ among various assemblers, a typical macro definition is shown in Fig. 1. The .MACRO on the first line alerts the assembler that a macro definition follows rather than ordinary program instructions. The next line gives the macro *prototype* which defines how the macro-instruction would look in a source program. The symbols preceded by dollar marks are sometimes called "dummy arguments" because, when the macro-instruction is actually expanded by the assembler, they are effectively replaced by the actual symbols used in the macro-instruction. Following the prototype are the actual machine instructions that would be generated when the macro-instruction is used. Note the use of the

macro-instruction in the LHLD instruction as in the prototype. The .MEND signals the assembler that the macro definition is complete. The definition is then saved by the assembler in a special table in memory reserved for that purpose. Figure 2 shows the use of this macro-instruction in a program (octal). In this example all of the instructions generated when the macro was expanded are shown on the listing with a preceding minus sign. Generally the assembler will have a command that would suppress printing of these expansion instructions if desired. With a good library of macro definitions, assembly language programming may become almost as easy as programming in a higher level language. Another advanced feature is called "relocatable object code" capability. An assembler having this feature supplies additional information in the object file so that it may be later loaded into memory *anywhere* desired completely auto-

With this little bit of background, the reader should be able to evaluate more fully the assembly language program development facilities of a particular system. ◇

SPEAKER KITS.



Money-saving, multi-element stereo speaker kits. Build them yourself to save up to half the retail cost of comparable ready-built systems. And get great sound in the bargain.

Send us your name and address and we'll mail you our free 44-page catalog of speaker kits, raw speakers, crossovers, enclosures and tips on design and construction. It's practically a manual on speaker building.



Dept. PE-8 5500 35th NE Seattle, WA 98105

HOBBYIST COMPUTER CLUBS

COMPILED BY Popular Electronics

(Additions to list published April 1977)

CALIFORNIA

Association for Educational Data Systems
c/o Dr. Jane D. Gawronski
Dept. of Education
5401 Linda Vista Rd.
San Diego, CA 92111
Inland Computer Society
c/o Tom Munnecke
P.O. Box 55052
Riverside, CA 92517
Southern California Computer Society
P.O. Box 54751
Los Angeles, CA 90054

ILLINOIS

SCCS 5063
c/o Roy Emerson
14904 S. Calis Ave.
Posen, IL 60469
St. Louis Area Computer Club
c/o Lou Elkins
Box 1143, St. Louis, MO 63188

MASSACHUSETTS

Boston Computer Society
c/o Donald Bradley
123 Commonwealth Ave.
Boston, MA 02116
Greater Boston Computer Users Group
c/o Steven Hain
40 Wiltshire Dr. (Door 2)
Sharon, MA 02067

MINNESOTA

Minnesota Computer Society
P.O. Box 35317
Minneapolis, MN 55435

MISSOURI

St. Louis Area Computer Club
c/o Lou Elkins
Box 1143, St. Louis, MO 63188

NEBRASKA

Mid-America Computer Hobbyists
c/o L.L. Tom Smith
2708 Calhoun St.
Bellevue, NB 68005

NEVADA

SCCS
Quentin C. West
15 Ballerina
Henderson, NV 89015

NEW JERSEY

SCCS
c/o William Staats
Box 947, McGuire AFB, NJ 08641

NEW MEXICO

US Robotics Society
Box 26484, Albuquerque, NM

NEW YORK

Stony Brook Homebrew Computer Club
c/o Dr. Ludwig Braun
College of Eng. and Applied Science
State University of New York
Stony Brook, NY 11794

OHIO

Dayton Microcomputer Association
Dayton Museum of Natural History
2629 Ridge Avenue
Dayton, OH 45414

North Central Ohio Computer Club
c/o Bill Hicks
618 Teakwood Court
Galion, OH

OKLAHOMA

Tulsa Computer Society
P.O. Box 1133
Tulsa, OK 74101

PENNSYLVANIA

Northeast Computer Association
834 Lawler Street
Philadelphia, PA
St. Thomas District HS Computer Club
1025 Braddock Avenue
Braddock, PA 15104
Wilkes College Computer Club
c/o Eric Jansen, Math Dept.
Wilkes College
Wilkes-Barre, PA 18703

TEXAS

Panhandle Computer Society
c/o Tex Everett
2923 S. Spring
Amarillo, TX 79103
Theater Computer Users Group
Theater Sources Inc.
4712 Northway Dr.
Dallas, TX 75206

VIRGINIA

Roanoke Valley Computer Club
c/o Lee Yosafat
2026 Wynnere Dr. S.W.
Roanoke, VA

WISCONSIN

Durant Club
c/o James White
901 S. 12th Street
Watertown, WI 53094

CANADA

Montreal Micro-68 Computer Club
Case Postale al Succor Sale
Montreal, Canada H4Y 1A2
Ottawa Computer Group
P.O. Box 13218
Kanata, Ontario, K2K 1X4
Societe d'Informatique Amateur du Quebec
IRISCO du Quebec Inc.
376 du Roi, Suite 304
Quebec, Canada PQ 2W6

ENGLAND

Amateur Computer Club
7 Dordells
Basildon, Essex, England

JAPAN

Japan Microcomputer Club
First Ohkura Building 4F 2-1
Nihoubashi, Chuo-ku,
Tokyo, Japan

MEXICO

Carlos de Leon
Avenue Chapultepec 318-603
Mexico 7, DF, Mexico

If your club was not listed in the previous, or this coverage, please inform "Computer Bits," POPULAR ELECTRONICS, One Park Ave., New York, N.Y. 10016.

FOR YOUR OWN
**PERSONAL
COMPUTING
POWER**

Only \$169.95



with
**MOTOROLA'S EDUCATOR II
MICROCOMPUTER HEP KIT**

- Motorola M6800 Technology
- Test-as-you-build in easy steps — normally one evening assembly
- Completely self-contained with all parts, cabinet and instructional manual

Learn MPU theory and programming as you build, and then get ready to expand your computing power with these new accessory kits that will be coming soon—

- Video Display Card
- Keyboard Kit
- Module Card Rack and Power Supply
- Memory Modules
- Application Programs on Cassettes

Also available...

**MOTOROLA HEP EDUCATOR II
POWER SUPPLY KIT**



\$29.95

- 5 V @ 1.0 Amps
- Designed specifically for Educator II Microcomputer Kit
- Complete Kit — all parts, cabinet and construction manual

Send today for more information about Educator II

Please print label clearly.

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____




MOTOROLA
Semiconductor Products Inc.

HEP/MRO OPERATIONS
705 West 22nd Street — Tempe, AZ. 85282

Tips & Techniques

BLOWN-FUSE INDICATOR

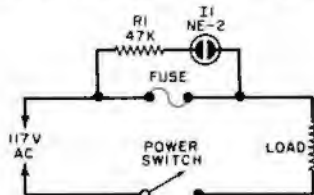This simple circuit will enable you to tell at a glance whether you have blown a fuse—without removing the fuse from its holder. As long as the fuse is good, no



current will flow through $R1$ and $I1$, an NE-2 neon bulb. If the fuse blows, the ac takes the alternate path through $R1$ and $I1$. A 47,000-ohm, $\frac{1}{2}$ -watt resistor is used to limit current through $I1$ to a safe value. Mount $I1$ in any convenient (but visible) location.—*Ross Thompson, Lis-towell, Ontario, Can.*

INEXPENSIVE ELECTRIC EYE

Here's an electric eye that can be built from junkbox parts. It consists of a CdS photocell, a 7486 exclusive-OR gate IC, an npn switching transistor (2N3055 or similar) and a small electric bell. When no object interrupts the light path from a lamp to photocell $LDR1$, both inputs to the ex-OR gate are low. Thus the gate's output is low and the transistor is cut off. Interrupting the light beam causes the

DESOLDERING BRAID


An inexpensive source of desoldering "wick" is the outer conductor of RG-58 and RG-59 coaxial cable. Cut your scrap into 8- to 10-inch (20.4- to 25.4-cm) lengths. Hold the braid and inner conductor firmly with pliers, and pull off the outer insulating jacket with your free hand. Then, push the two ends of the braid together to loosen it, and pull out the inner conductor and surrounding insulation.—*Arnold Irvine, Coopersburg, PA.*

TEST JACK ADAPTER

Have you ever bought a new meter or other piece of test equipment only to discover that none of your standard $\frac{3}{4}$ -inch spaced test plugs will fit the jacks on it? If you can't or don't want to modify your new piece of gear by slotting the test jack mounting holes, consider this simple adapter you can make to rectify the situation. All you need are a pair of banana jacks, a pair of noninsulated banana jacks, and a $1\frac{1}{4}$ -inch (3.81-cm) square piece of $\frac{1}{8}$ -inch (3.2-mm) thick plexiglass or bakelite. Round the corners of the plastic and drill two holes at opposite corners for the jacks, spaced $\frac{3}{4}$ -inch (1.9-cm) apart. Then carefully measure the spacing between the test jacks on the new equipment and drill holes for the plugs in the plastic square to match this spacing. Assemble and wire the plugs and jacks and you're all set.—*Donald R. Hicke, San Diego, CA.*

PC DRILLING GUIDE

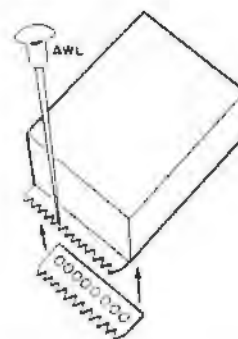Here's a handy guide for drilling IC pin holes on a pc board. Epoxy a length of discarded Molex Soldercon holder strip to a block of wood as shown. Attach a few strips of double-faced adhesive tape (Scotch No. 666 or equivalent) to the




bottom of the block to prevent slippage. Hold the block on the pc board with one hand and make indentations with an awl at each "valley" along the holder strip. Then remove the block. You will find a line of depressions that can easily be drilled through the board, exactly 0.1" (2.54 mm) apart.—*Robert J. Murrell, Verona, PA.*

IC SOLDERING AID

To prevent heat or static damage to an integrated circuit while soldering, push the pins of the device through a few sheets of aluminum foil measuring 2" x 2" (5.1 x 5.1 cm). Then mount the IC on the circuit board. The foil will dissipate heat and electrically tie all the pins together. When the IC is in place, tear away the foil. Check carefully for stray pieces of foil before powering the board. The foil will generally come away in a few pieces without leaving tiny scraps.—*Aart M. Olsen, Newark, DE.*

BIKE LIGHT SAVER

I installed a Soubitez alternator to power the head and tail lights on my bicycle. Unfortunately, I found that the bulbs were burning out rather quickly when I was travelling at speeds greater than 15 mph. The problem was solved by installing two zener diodes back-to-back as shown in the figure. Before the modification, the alternator output was 6 volts rms at speeds greater than 6 mph. After the change, the voltage applied to the bulbs dropped to about 4.9 volts rms. Bulb life was considerably extended without significant reduction of light output. In the diagram, left, the miniature headlight ($I1$) is rated at 6 volts and 300 mA. The taillight ($I2$) is rated at 6 volts and 100 mA. The two zener diodes ($D1$ and $D2$) are rated at 6 volts and 3 watts. Higher-powered zeners can be used.—*D.F. O'Connell, Palo Alto, CA.*

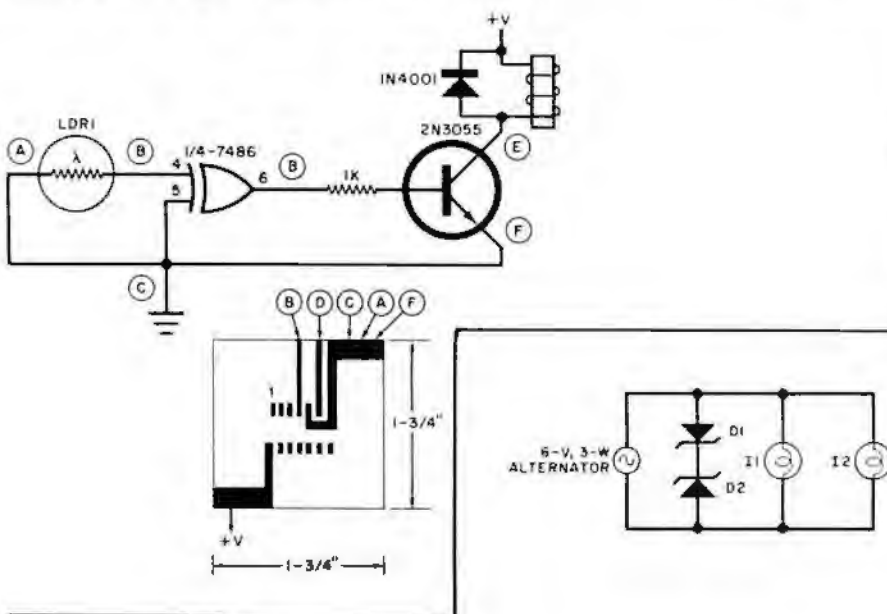

Operation Assist

If you need information on outdated or rare equipment, a schematic, parts list, etc., another reader might be able to assist. Simply send a request to Operation Assist, POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They appreciate it. Only those items regarding equipment not available from normal manufacturers are listed.

American Scientific Development TV-20 tube tester. Schematic, operating manual, chart. Will buy or copy. Terry Nixon, RR 1, Box 182, Potosi, MO 63664.

Sprague TO-3 capacitor checker. Need 15-watt 50-ohm power rheostat. Ray Parsons Jr., Portsmouth Ave., Stratham, NH 03885.

Kris "Match Maker," serial 3302003. Schematic and/or specifications such as frequency, impedance, etc. Bob Danner, 80 Billington Rd., East Aurora, NY 14052.

AGS IC-RS-82 eight-track recorder/player. Schematic. Henry D. Mikkelsen, VA Hospital, Manon, IL 62959.

Gran Sonic GS-2 stereo receiver. Schematic, also need power transformer, marked SAT-260 OCM. John D. Gill, Rte. 5, Box 370, Blountville, TN 37617.

RCA WO-918 oscilloscope. Operating manual. Donald R. Anthony, 821 Lantana St., Corpus Christi, TX 78408.

Allied Knight 83Y102 Star Roamer radio. Schematic. Will buy or copy. Gerald Fox, Fox Electronics, Box 890, Rte. 3, New Holland, PA 17557.

RCA WP-23A regulated power supply. Schematic, operating instructions, or service manual. Ronald Gillen, Box 383, Huston, WI 53034.

Cartrivision video tape recorder. Source of tapes and spare parts. Donald Weber, 1333 N. Camino Alto, Apt. 245, Vallejo, CA 94590.

Bell & Howell 34 oscilloscope (DeVry Inst. of Tech.). Operating manual, schematic. R. Wood, 465 San Antonio, Palo Alto, CA 94306.

Hickok 640 oscilloscope. Schematic and/or service manual. Robert Zusman, 200 East Indian Spring Dr., Silver Spring, MD 20901.

Lloyd TM-988 AM/FM receiver. Schematic, operating manual and/or parts list. Peter B. Trippett, 581 Glen Rd., Sparta, NJ 07871.

Friden paper-tape readers, typewriters, Justowriters. Schematics, operating instructions. J.I. Taylor, Box 289, Salem, MA 01970.

General Radiotelephone MC-5 CB transceiver. Schematic, manual. Elliott Electronics, RR 2, Box 61, Ettingham, IL 62401.

Tektronix 564 scope. Need 3B3 time base, 3A6 vertical plug-in. Ramesh B. Panik, P.O. Box 17356, Bombay 400 058, India.

Fisher 400 receiver. Schematic and/or information on power transformer. **Magnavox** 9—295HH console. Schematic, power capabilities of 15" woofers that come with console. Thom Filippetti, Rte. 1, Box 39-Z, Connie Lane, Shingle Springs, CA 95682.

Radio City 488 multimeter, circa 1942. Schematic and any other information. Joe H. Hibbs, 971-87 Borden Rd., San Marcos, CA 92069.

Jackson Instrument 641-A signal generator. Schematic, alignment procedure. J.M. Nightingale, 1675 Comox St., Vancouver, B.C. Canada V6G 1P4.

Devtronics SR-55 calculator. Owner's manual, source of case and keytops. Ivan Dzombak, 621 Spring St., Latrobe, PA 15650.

Kear TR-505 uhf repeater. Schematic, owners manual or any info. V.C. Reed Jr., 1104 Abbot Ln., Park Forest South, IL 60466.

Solid State Devices Trigsweep, circa late 1960's. Instruction manual, pc artwork, parts list. John A. Harlan, 9720 Prospect Ave., Chicago, IL 60643.

Superior Instruments 707 or 707-A VOM multimeter. Schematic, instruction manual, parts list. Buy or copy. Arthur Knefler, 84 Bennett Ave., Neptune City, NJ 07753.

Rutherford B16R pulse generator, serial 171. Service manual and/or schematic. Vilson Silveira, 7708 Regent Ave. N., Brooklyn Park, MN 55443.

Marlux 407 reel-to-reel recorder. Schematic, service manual, or any info. T.K. Flanagan, U.S. Bluefish (SSN 675) FPO NY 09501.

RCA Berkshire, circa 1948. Literature and data, also speaker Fabns. 3626 Morse Dr., San Jose, CA 95127.

Transcorder TR300 reel-to-reel recorder. Need erase and record head. Erase head has 230-mH inductance, 1.5-V dc erase, dc bias. Play-record head has 380-mH inductance, 0.2 V bias. Curt Palmer, 990 Waverline Rd., North Vancouver, B.C., Canada V7R 1S5.

Heathkit 0-8 oscilloscope. Schematic and/or construction manual. Fred W. Buschmann, 3736 Pine Rd., Huntington Valley, PA 19006.

Heathkit 0-12 oscilloscope. Need power transformer. Kenneth Huffines, 356 O'Brian Dr., Stone Mountain, GA 30088.

Crosley 96 radio. Circa late 30's. Schematic, power transformer. Richard R. Nolette, RFO #1, River Rd., Kennebunkport, ME 04046.

Mercury Electronics 1101 tube tester. Manuals, any information. James B. Martin, 1708 Dave Dr., McAlester, OK 74501.

Atwater Kent 35 radio, serial 772713. Date of production, value. Kenneth J. Roberts, Box 367, Belling, AR 72923.

Transcom RCT 203 audio data terminal with strip printer. Schematic and/or manual. Will pay for copying. J. Bryan Loolbourrow, Box 1237, Mountainside, NJ 07092.

Century VT-10 VTVM. Schematic, operating manual, probe. **Eico** 232 VTVM. Schematic, operating manual, probe. **Supreme** 542 multimeter. Schematic, operating manual. Allen C. Fryou, 3735 Fairmont Dr., New Orleans, LA 70122.

Sharpe HA-10A or other Sharpe headphones. Source. Dr. James P. Gaston, 45 East End Ave., Apt. 5A, New York, NY 10028.

Precision 100 VOM. **Simpson** 311 VTVM. Schematics. Alan Neville, Rte. #2, Box 283, Forest City, NC 28043.

Hallicrafter S-38-E. Schematic, alignment manual, or any info. Steve L. Porter, 429 Balsam, Rogers City, MI 49779.

Conar 250 oscilloscope. **Motorola** FMTRU80D(A)1C2C mobile 2-motor transceiver. Schematics, operating manuals, any other info. David Eubank, Box 113, Greenup, IL 62428.

Skycrafter "VHF Superphone" AMT-9 transmitter, AMR-4 receiver. Schematics and any other info. Al Gwinn, 3321 Beverly Dr., Dallas, TX 75205.

Radio Shack 26-138 color organ kit. Schematics, parts list, or instruction manual. Gary Girzon, 4665 St. Kevin #3, Montreal, P.Q. Canada H3W 1N8.

A.C. Cossor 1434 preamplifier. Source of 120-V battery. **A.C. Cossor** 1049 MKII oscilloscope. Original camera, CRT. Claude Houde, 7427 Boyer St., Montreal, P.Q. H2R 2R9.

Olson AM-240 50-watt amplifier. Output transformers, 8-ohm output impedance. W.B. Wells, 172 Topsfield Rd., Pittsburgh, PA 15241.

Erie Pacific 720 frequency counter. Service manual, schematic, parts list, source for Elesta EZ10A and Burroughs 5031 tubes for counter. Gordon Wheatley, 9 Lynngrove Ave., Toronto, Ontario, Canada M8X 1M3.

Collins 32V2 transmitter. Instruction manual. Marvin E. Weber, Box 1261, Alamogordo, NM 88310.

Realistic 212 preamplifier, 210 ultra-linear amplifier. Any info. R.A. Rouge, Box 92, Hollywood, CA 90028.

U.S. Govt. RAD-2 Navy shortwave receiver (National type NC-120), Navy CNA-46187. Service manual and/or schematic. David L. Larson, 13011 S. First, Harlingen, TX 78550.

Precision EV10A VTVM. Schematic, manual. Willis J. Ball, 320 Bloxam Ave., London, Ontario, Canada N6J 3K6.

Crosley Showbox, circa early 1900's. Schematic, any rebuilding or service info. Kenneth Huffines, 356 O'Brian Dr., Stone Mountain, GA 30088.

National SW-3 receiver. Need series 10-20 coils, bandspread if possible. Martin Edelheit, 245-21 77 Crescent, Belton, NY 11426.



CITIZENS BAND HANDBOOK

The all-new 1977 edition, by the editors of POPULAR ELECTRONICS, has all the authoritative information you need in CB two-way radios to make an intelligent buying decision.

It features a

COMPLETE BUYING GUIDE

for the new 40-channel CB two-way radios, antennas and accessories—fully described with technical specifications, features, latest prices and photos. Other articles include the latest FCC Rules and Regulations changes in down-to-earth language • How to install a CB mobile system—and save money • How to operate and communicate with your first CB rig • Will sunspots affect CB range • CB language translation chart • How emergency CB associations can save your life • Manufacturers' specifications—"decoded" so that you will be able to read a "spec sheet" with ease • and much more information packed into one volume, all written by the experts.

1977 CITIZENS BAND HANDBOOK GOES ON SALE NATIONALLY JULY, 1977

RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.50

This offer is available to readers of POPULAR ELECTRONICS only. Regular price is \$1.95; mail order \$2.50. Save money and enjoy the convenience of having the 1977 CITIZENS BAND HANDBOOK mailed to you from first off-the-press copies when published. Complete the Reservation Form and return it promptly with your remittance.

PRE-PUBLICATION RESERVATION FORM

CITIZENS BAND HANDBOOK, PE-777
Consumer Service Division
595 Broadway, New York, NY 10012

Enclosed is \$1.50 (plus de U.S.A. \$2.00) for the 1977 CITIZENS BAND HANDBOOK to be mailed to me in July, 1977 when published.

Residents of CA, CO, FL, IL, MI, MO, NY, STATE, DC and TX add applicable sales tax.

Print Name _____

Address _____

City _____

State _____ Zip _____

Signal Corps BC-458-A transmitter. Schematic and/or operating manual. Dan Williams, Rte. 58, El Cerrito, CA 94530.

Heathkit W-3AM amplifier, with or without matching WA-P2 preamplifier. Source: David Hayes, 35 Cotton St., Gardner, MA, Canada A1V 1E3.

WW II Equipment. Model RDO (Navy issue) receiver (circa 1945); Model AN/SPR-2 receiver; Model AN/APA-6A oscilloscope. Schematics and general manuals. John Andrews III, 11011 Waycroft Way, Rockville, MD 20852.

Stephens "TruPhonic" midrange speaker systems. Circuitry and parts information. Frank J. Burris, 35640 Avenue F, Yucaipa, CA 92399.

Bunker Ramo Model 203-B-MON teleregister video display. Schematics and/or service manual. F. Ascolillo, Park Lane, North Windham, ME 04062.

Microsystems International DTMF receiver card. Schematics and manuals or any available information on touch-tone receiver cards. James Chochos, Jr., A-E 6107, San Luis Obispo, CA 93409.

Philco Model 41-606, Code 122 radio-phonograph combination. Schematic, parts list, tubes and parts source. R. Galligan, Box 326, Niantic, CT 06357.

Leak point-one stereo preamplifier and stereo-fifty power amplifier. **Altac Lansing** Model 445A stereo preamplifier. Schematics needed. Bill Rathen, 19 Broadway, Bayonne, NJ 07002.

Simpson Model 330 tube checker. Schematics, operations manual and current tube sheet. Duane Schuh, 824 La Porte Dr., La Canada, CA 91011.

Meisner Analyst Operating and service manual. John Graham, Box 186, Wurtsboro, NY 12790.

Superior Instruments Model 77 VTVM Schematic and/or service manual. Mr. Test, P.O. Box 9064, Newark, NJ 07104.

Eldico Model MT 2 2-meter AM transmitter. Schematics and operations manual. Francis H. Bailey, 641 Hill P.O., Dudley, MA 01570.

Keppo Labs Model 150 rack-mount variable power supply. Schematic, parts list and wiring diagram. Also, **Crystal Re-**

search Products Model 203 crystal checker. Schematic and any available information. Craig K. Sellen, Box 293, Carbondale, PA 18407.

Micronta Model 22-012 tube tester. Need tube chart. Charles A. Mizera, 3226 N. Kostner Ave., Chicago, IL 60641.

Clough-Brengle Model 111 frequency modulator. Operations manual or any available information. G.J. Kulp, 1115 L-lac Lane, West Lawn, PA 19609.

Heathkit Model 1G-62 color bar and dot generator. Schematic and/or service manual. Earl D. Kent, 810 E. 1st St., Emmett, ID 83617.

Panasonic Model RF-1006M AM/FM/MB radio. Schematic and operations manual. Bruce Stanley, 350 Beechwood O.T.S., Granburg, TX 76048.

B&K Model 1075 television analyst; Model A107 Dyna-Sweep circuit analyzer; Model 445 CRT tester. Service and operation manuals. Paul S. Panikowski, 5006 Edgewood Rd., College Park, MD 20740.

Cartridge Television Inc. Model MCA-0001 video camera. Schematic and service manual. Michael A. Lizzio, Apt. 8C, Clover Path, Spring Hill Apts., Maple Shade, NJ 08052.

Reflector, 18-in. parabolic. Need source. Albert Bhutapher, 5008 W. Pullerton Ave., Chicago, IL 60639.

Jackson Model TVG-2 TV/FM sweep alignment generator. Schematic and operation manual. Eden Rubin, 227-12 57th Ave., Bayside, NY 11364.

Measurement Control Devices Model 300 oscilloscope. Schematic and manual. Michael E. Headberg, 7760 NW 171 St., Hialeah, FL 33015.

Automatic Radio "Tom Boy" AM radio (circa late 1930's-early 40's). Parts list and/or schematic. C. Walker, 131 Bernard St., San Francisco, CA 94109.

Precise Model 305R triggered scope. Schematic, parts list and instruction manual. William H. Bragg, 1424 Collage, Des Moines, IA 50314.

Transcom Electronics Model SBT3 SSB transceiver. Alignment instructions, schematic and any other available information. Ari Procopio, QSL Bureau, P.O. Box 22 Labre, Sao Paulo SP 1000, Brazil.

Solid State Model ST-1000 TV camera. Any available information. Leigh Klotz, Jr., 119 Harmony St., McComb, MS 39648.

Honeywell Model TCM-31-C memory. Need PAC card layout. Joe Schram, Box 1818 Washington, DC 20013.

Hallcrafters Model 538E shortwave receiver and Precision Model E-200 signal generator. Need schematics. S. Bergen Wilson, 1403 Lyttleton St., Camden, SC 29020.

Hammarlund Model FM50A outroom and Knightkit Cal. No. 83Y146 oscilloscope. Schematics and manuals. James F. Reuter, 2595 Marlborough, Detroit, MI 48215.

Radio Compass Type R101/ARN6 receiver control box. Handbook and RX mounting rack needed. Lionel L. Sharp, 19 Kelso St., Chermade, Queensland, Australia 4032.

American Concertone Model 505 reel-to-reel tape recorder. Schematic and service information. Duncan Crawford, 206 Cedarwood, Flushing, MI 48433.

Rockland Model 5500 frequency synthesizer. Schematic needed. Thomas Barrett, 39 Lake Drive, Monroe, LA 71201.

Superior Instrument Model 800 allimeter. Schematic and operating manual. Robert E. Heltz, 317 Woodward Ave., Buffalo, NY 14214.

Navy Surplus oscilloscope type TS-34A/AP. Schematic and service manual. James W. Booker, 2808 W. Boyce Ave., Fort Worth, TX 76133.

Magnavox Model FM-16 AM/FM radio. Schematic. Robert J. Hewitt, 318 N. Greenbay Rd., Waukegan, IL 60085.

Burroughs 9350-2 (Friden #7311) computer terminal keyboard/printer. Control unit schematics and maintenance manual. Gary Alderman, 8815 Portsmouth Dr., Laurel, MD 20811.

Grundig Model M72 PX musical instrument. Schematic or tube list. Greg Banersee, 311 Monroe St., Valders, WI 54245.

Advance Electronics Model OS 15 oscilloscope. Schematic and any available information. Anil Rodrigues, Gilpin Ave., #1, Wilmington, DE 19806.

Webster wire recorder. Recording wire needed. A. Markowitz, 9 Henneberry Ln., Goff, IL 60029.

EMC Model 600 oscilloscope and Model 400 signal generator. Schematics and instruction manuals. J. Massing, 208 Dickens Dr., Toledo, OH 43607.

Dumont Type 241 oscillograph and **Hickok** Model RFO-5 oscillograph. Schematics and/or parts lists. A. Elliot, 221 N. 4th St., Tonawanda, PA 18848.

Elco Model 221 VTVM. Meter needed. Hervey C. Cain, Box 66, Coal Hill, AR 72832.

Zenith Model 85532 2-band table radio. Operating manual, schematic, parts and alignment information. A. Hawk, 21 Rivercrest, Hanover, NH 03755.

RCA Model WT-100A electron-tube micromho-meter. Operation manual, schematic and tube chart. Danny Tovar, 4700 Rockmoor Ln., Fort Worth, TX 76118.

Hallcrafters Model CN-1 FM converter. Schematic needed. H.A. Wicker, 5 Deenview Ln., Asheville, NC 28804.

Concert Company Model 8003 "Emulator." Schematic and parts list for servicing. Bud Petersen, 801 Polynesian Dr., Long Beach, CA 90805.

Canadian Marconi Model C-2 frequency indicator (circa 1943). Schematic and operating instructions. M. Armstrong, 243 Howard, Sherbrooke, P.Q., Canada.

McMurdo Model 900 Silver Vornax. Schematic and operating manual. Don White, 109 Burns Street, Essexville, Michigan 48732.

Miranda "Nocturne" stereo tape recorder. Schematic or any available information. Walter Baker, 162 N. Queens Ave., N. Massapequa, NY 11758.

Microsystems International touch-tone receiver. Manual and/or schematic. J. Chochos, Box A-E 6107, San Luis Obispo, CA 93409.

McIntosh Model C-8 or C-8P. Looking for unit. B. Gerber, 8221 Streamwood Dr., Ba Ho., MD 21208.

Hallcrafters Model SX-100 receiver. Operator's manual, schematic or other information. Dale C. Vawter, 117 Altana St., San Rafael, CA 94901.

Racorn Model 2174-610 selective voltmeter. R. Reed, 2054 Bradley, Ypsilanti, MI 48197.

Hartman "Hurricane" vhf-FM marine transceiver, 5-channel. Circuit diagram and manual. Paul Smith, 65 West St., New London, CT 06320.

Dumont Type 322 dual-beam oscillograph. Service or schematic. David Passeur, 6327 Everglades Dr., Alexandria, VA 22312.

Military radio receiver Model R-440 (XN-1) manufactured by RCA. Operating manual, service manual, schematics or any available information. Peter Z. Simpson, 18 University Dr., Natick, MA 01760.

Knight Model KG-2000 oscilloscope. Service and calibration data, power transformer data, and/or source. Ron Hunter, 308 Mertens Ave., Racine, WI 53405.

APELCO Model AE-31MA radiotelephone, **AMECO** Model CMA multiband converter and **B&K** Model 500 "Dyna-Quk" tube tester. Service manuals or any available information. Herb. Mitschan, 1688 Baywood Dr., Petaluma, CA 94952.

Philco Model 41-250 radio. Schematic, parts list and parts source. Charles M. Pache, Box 208, Marysville, KS 66508.

Philco Model 19 MK II wireless set with Model 3A MK II control unit. Built for Russian tanks during W.W. II. Need any available information. Cliff Holm, 1900 Grant Dr., Regina, Sask., Canada.

Johnson "Viking Ranger I" transmitter and **Drake** Model 2B receiver. Operation and service manuals. Paul Barbuto, Box 385, Genesee, ID 83832.

DeVry Tech. Model 1-15 5-inch oscilloscope. Builder's manual and calibration instructions. Andy Van Loenen 4684 Wakefield N.E., Comstock Park, MI 49321.

Muse sequencer oscillator, **Western Electric** Model TP25-1 amplifier and 3-M Model 78-9020 microphone. Schematics and parts source. James D. Craig, 511 Cedar St., Allentown, PA 18102.

Crosley Model Super 11 radio. Schematic and any available information. David P. Lesser, 82 Rolling Green, Amherst, MA 01002.

Teletype Corp. Model 15Y typing unit. Schematic and instruction manual. Martin H. Bunshaft, 29A Forest Acres Dr., Bradford, MA 01830.

THE PAIA 8700 COMPUTER/CONTROLLER

An exceptional price on an
applications oriented 6503 based
micro-processor system



\$149.95

THE IDEAL, LOW COST SOLUTION TO IMPLEMENTING
THOSE WILD COMPUTER BASED CONTROL SYSTEMS
YOU'VE BEEN DREAMING OF!

PAIA software currently available or under development includes: Music synthesizer interface; Home applications package including: multi-zone fire/burglar alarm, real time clock, energy saving heat/air conditioning control, computer generated "door-bell"; Model railroad controller and more.....

8700 COMPUTER/CONTROLLER KIT \$149.95
(requires 5v. @ 1.2A.; 12v. @ 150 ma.)

Shipped direct from PAIA (add \$3.00 postage)

Also available at FULL LINE computer stores

DETAILS IN OUR FREE CATALOG

**PAIA • DEPT. 7-P • 1020 W. Wilshire Blvd. •
Oklahoma City, OK 73116**



Electronics Library

ELECTRONIC TROUBLESHOOTING WITH SIMPLIFIED CIRCUIT ANALYSIS

by Leo Rozman

The author aims to familiarize the reader with a wide variety of circuits, how they operate, and how to localize trouble using symptom analysis, signal injection and/or tracing. Using simple circuits (mostly solid-state) as examples, the author covers troubleshooting via dc and ac measurements, the effects of passive components, identifying circuits, controls and adjustments, and symptom analysis. The stress is on practical, time-saving techniques in repairing radio and TV receivers.

Published by Parker Publishing Co., West Nyack, NY 10994. 240 pages. \$12.95 soft cover.

MODERN ELECTRONICS MATH

by Jerrold R. Clifford and Martin Clifford

Immediate application is the keyword here, with electronics first brought into the picture on page 21, in a problem on adding series resistance. Arithmetic, algebra and trigonometry are thoroughly explored, with a multitude of examples taken from electronics. In the section on square root, the reader is shown how to calculate current, given power and resistance. In the chapter on trigonometry, phase angle and impedance calculations are introduced, among many other areas. A chapter on logarithms gets into decibels, power gain, etc. Four chapters are aimed at computer math: binary numbers, octal and hex numbers, other number systems, and Boolean algebra.

Published by Tab Books, Blue Ridge Summit, PA 17214. 684 pages. \$9.95 soft cover, \$12.95 hard cover.

THE RADIO AMATEUR'S HANDBOOK (54TH ED.)

by the ARRL Headquarters Staff

The 1977 edition of the radio amateur's "bible" has been revised to reflect changes in both technology and amateur radio. An introductory chapter explains the basic characteristics of the amateur radio service, and is followed by chapters dealing with radio theory. The handbook is well illustrated and contains many graphs, formulae, and representative circuits. An expanded chapter on radio propagation, a section on radio and boating, and a frequency chart covering vlf to uhf are included. Among the new projects appearing in the handbook are an 80-to-10-Meter solid-state

JULY 1977

transceiver with digital readout, a 2-kW 8877 linear amplifier, a 50-MHz frequency counter, and improved RFI filters. New amplifiers and a mobile antenna for 220 MHz are featured. An antenna coupler employing fixed capacitors and a homemade variable inductor helps beat the parts procurement problem.

Published by the American Radio Relay League, Inc., 225 Main Street, Newington, CT 06111. 704 pages. \$12.50 hard cover (\$13.50 in Canada, \$14.50 elsewhere), \$7.50 soft cover (\$8.50 in Canada, \$9.50 elsewhere).

ELECTRONICS ONE-SEVEN, VOLS. 1 AND 2

These two volumes (one on electronics, one on electricity) are revised second editions of elementary self-teaching texts that first came out ten years ago. Each features one topic or concept per page, with at least one illustration on every page. Coverage is thorough, and very little math is used. Each volume is made up of seven parts. The electronics volume covers electronic signals, electronic building blocks, electron tubes, semiconductors, power supplies, oscillators, and auxiliary circuits. The electricity text covers "producing electricity," dc circuits, ac circuits, LCR circuits, test equipment, power sources, and electric motors.

Published by Hayden Book Co., 50 Essex St., Rochelle Park, NJ 07662. Electronics: 1,000 pages. \$21.95. Electricity: 992 pages, \$20.85. Hard cover.

TV TYPEWRITER COOKBOOK

by Don Lancaster

As the "subtitle" indicates, this is a "complete guide to low-cost television display of alphanumeric and graphic data for microprocessor systems, computer hobbyists, ham RTTY, TV titling, word processing, and video games." The author, who has also written other electronic "cookbooks," covers TV typewriters in depth: IC's for TVT use, memory, timing, cursor and update circuits, keyboards and encoders, serial and TV interfaces, hard copy, and color graphics. Dozens of schematics provide information for building one's own TVT, or serve as background material for the hobbyist interested in knowing what's inside the kit or wired TVT he's bought.

Published by Howard W. Sams & Co., 4300 W. 62 St., Indianapolis, IN 46206. 256 pages. \$9.95 soft cover.

ELECTRONIC SYSTEMS THEORY AND APPLICATIONS

by Henry Zanger

This text expounds how to use available IC's rather than how to design circuits, so the stress is on the system. There are chapters on system analysis, transducers, components, communications systems, instrumentation, control systems, and reliability and maintainability. The hardware ranges from op

The "Click and Pop" machine

only by

SAE



Ever since the invention of the recorded disc annoying "clicks" and "pops" caused by scratches, static and imperfections have consistently disturbed the listening pleasure of music lovers.

Now, SAE introduces the unique model 5000, an Impulse Noise Reduction System which eliminates those unwanted sounds with no adverse effect on the quality of the recorded material.

This breakthrough in electronic circuitry is so demonstrably effective that the SAE 5000 is destined to become an essential part of any sound system.

The SAE 5000 is compact and sleek, built to SAE's exacting standards, and ready to enhance the performance of any system, from the standard receiver/turntable combination, to the most sophisticated audiophile components.

SAE is proud to add the 5000 to their broad line of *Components for the Connoisseur*.

SAE

Scientific Audio Electronics, Inc.
P.O. Box 60271, Terminal Annex
Los Angeles, Cal. 90060

Please send more information on the 5000.

Name _____

Address _____

City _____

State _____ Zip _____

PE-777

CIRCLE NO 43 ON FREE INFORMATION CARD

Put Professional Knowledge and a
COLLEGE DEGREE
 in your Electronics Career through
**HOME
 STUDY**

**Earn Your
 DEGREE**

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin E-77*.

Grantham College of Engineering
 2000 Stoner Avenue
 P. O. Box 25992
 Los Angeles, CA 90025

Worldwide Career Training thru Home Study
 CIRCLE NO. 20 ON FREE INFORMATION CARD

**FREE
 EICO
 CATALOG**

**358 Ways To Save On
 Instruments, CB,
 Burglar Alarms,
 Automotive & Hobby
 Electronics!**

The more you know about electronics, the more you'll appreciate EICO. Every EICO product is designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"BUILD-IT-YOURSELF" and save up to 50% with our famous electronic kits.

For the latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO—283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative
 electronics since 1945.



CIRCLE NO. 13 ON FREE INFORMATION CARD

amps to plotters, the math from Laplace transforms to transfer function analysis, in this technical look at a wide range of systems.

Published by Prentice-Hall, Englewood Cliffs, NJ 07632. 352 pages. \$15.95 hard cover.

COLOR TELEVISION TROUBLESHOOTING

by Edward Bannon

Reflecting the rapid advances of electronic technology, this book presents the current status of color TV servicing. It is intended as a teaching tool for instructors, technicians, and technical-school or trade-school students. A fundamental knowledge of radio and TV theory is assumed. Troubleshooting is discussed as it relates to color reproduction problems in the black-and-white sections; bandpass amplifier; color-sync procedures; chroma demodulators; chroma and color matrices; systematic color circuits; color picture tube circuitry; modular procedures; and digital color TV circuitry.

Published by Reston Publishing Co., P.O. Box 547, Reston, VA 22090. 264 pages. \$14.95 hard cover.

DIGITAL/LOGIC ELECTRONICS HANDBOOK

by William L. Hunter

This handbook starts out with chapters on numbering systems (binary, octal, hex), basic arithmetic operations, and the laws of logic (Boolean algebra, Venn diagrams, truth tables) applied to digital circuits. The logic chapter also gets into DeMorgan's Theorem for simplifying Boolean equations. The next two chapters explore logic circuits such as flip-flops, counters, adders, converters and multiplexers, and basic digital circuits including multivibrators, gates, and the Schmitt trigger. Logic symbols are examined thoroughly, as is the 54/74 family of TTL IC's. The last chapter, on logic applications, looks at a digital-readout timer by Sprague, and four digital Heath Kits (multimeter, clock, calculator, thermometer).

Published by Tab Books, Blue Ridge Summit, PA 17214. 308 pages. \$6.95 soft cover, \$9.95 hard cover.

A DICTIONARY OF MICROCOMPUTING

by Philip E. Burton

If you are just getting into microcomputing or are just thinking about it, this is one book you might want to get at the start. It translates and defines the meanings of such things as ACIA, DMA, DOS, assembler, emulator, handshaking, iteration time, and a host of other terms and phrases used in computing. For example, it will make clear the difference between software, firmware, and hardware; JUMP and LOOP instructions; bit and byte; etc. Diagrams, drawings, and tables are provided to illustrate the text. The Appendix contains the complete listing of the full ASCII code; tables

of binary and hexadecimal numbers; and hexadecimal addition and multiplication tables.

Published by Garland Publishing, Inc., 545 Madison Ave., New York, NY 10022. Hard cover. 171 pages. \$12.50.

SEMICONDUCTOR REFERENCE HANDBOOK

Data on Radio Shack's line of Archer brand semiconductors is compiled in this new reference handbook that contains cross-reference data on more than 36,000 semiconductor devices. The handbook also has sections on the care and handling of transistors, soldering precautions, case styles and dimensions, testing of transistors, and a glossary of terms, symbols, and abbreviations used in electronics. The handbook is available from Radio Shack stores.

Published by Radio Shack, Forth Worth, TX 76102. Soft cover, 128 pages. \$1.95.

HOW TO DESIGN & USE MULTIVIBRATORS

by Courtney Hall

Various types of multivibrators are examined in this book at the introductory level. Astable, bistable, and monostable multivibrators as well as Schmitt trigger and half-shot circuits are discussed. Other chapters explain the design and applications of multivibrator circuits. The book also presents techniques for tailoring circuits to meet specific demands. A few of the projects covered are pulse generators, electronic counters, lamp flashers, tachometers, phase meters, voice-operated relays, and time-delay circuits.

Published by Howard W. Sams & Co., 4300 W. 62nd Street, Indianapolis, IN 46206. 96 pages. \$3.95 soft cover.

RECORDING AND LISTENING GUIDES

Master Hi-Fi Installation (151 pages), by Gordon J. King, describes in a straightforward manner the functions of the main components of a hi-fi system. It details the differences between mono, stereo, and quadraphonic sound and the effects of room acoustics. The guide is designed to help the reader select the right components for his audio system. *Master Stereo Cassette Recording* (112 pages), by I.R. Sinclair, covers just about everything you need to know to record and replay, and to maintain and improve your recording equipment for professional results. Coverage also includes noise-reduction equipment and special techniques and equipment for considerably boosting the quality of recordings. *Master Electronics In Music* (120 pages), by T.D. Towers, is a guide to the proper use and maintenance of such popular electronic instruments as electric guitars, electronic organs, amplifying systems for musical instruments, and other electronic musical equipment.

Distributed by Hayden Book Co., Inc., 50 Essex St., Rochelle Park, NJ 07662. Soft cover. \$5.45 per volume.

POPULAR ELECTRONICS

ELECTRONICS MARKET PLACE

REGULAR CLASSIFIED: COMMERCIAL RATE: For firms or individuals offering commercial products or services. \$2.25 per word. Minimum order \$33.75.
EXPAND-AD CLASSIFIED RATE: \$3.35 per word. Minimum order \$50.25. Frequency discount, 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.35 per word. No minimum! **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$260.00. 2" by 1 column, \$520.00. 3" by 1 column, \$780.00. Advertiser to supply film positives. For frequency rates, please inquire.
GENERAL INFORMATION: Payment must accompany copy except when ads are placed by accredited advertising agencies. First word in all ads set in caps. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Ads are not acknowledged. They will appear in first issue to go to press after closing date. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st). Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016, Attention: Hal Cymes

FOR SALE

FREE! Bargain Catalog—L.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts. Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

GOVERNMENT and industrial surplus receivers, transmitters, sniperscopes, electronic parts. Picture Catalog 25 cents. Meshina, Nahant, Mass. 01908.

LOWEST Prices Electronic Parts. Confidential Catalog Free. KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

ELECTRONIC PARTS, semiconductors, kits. FREE FLYER Large catalog \$1.00 deposit. BIGELOW ELECTRONICS, Bluffton, Ohio 45817.

RADIO—T.V. Tubes—36 cents each. Send for free catalog Cornell, 4213 University, San Diego, Calif. 92105.

AMATEUR SCIENTISTS. Electronics Experimenters, Science Fair Students. Construction plans—Complete, including drawings, schematics, parts list with prices and sources. Robot Man — Psychodelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter...over 60 items. Send 50 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

METERS—Surplus, new, used, panel or portable. Send for list. Manchett, Box 5577, Riverside, CA 92507.

MECHANICAL, ELECTRONIC Devices catalog 10 cents. Greatest Values — Lowest Prices. Fertik's, 5249 "D", Philadelphia, Pa. 19120.

POLICE/Fire scanners, large stock scanner crystals, antennas. Also CBs. Harvey Park Radio, Box 19224, Denver, CO 80219.

TELETYPE EQUIPMENT for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224 Tel: (212) 372-0349.

ELECTRONIC Ignition Capacitor-Discharge, pointless. Auburn Sparkplugs. Wheel Stabilizers. Information 20 cents. Anderson Engineering, Epsom, N.H. 03234.

WHOLESALE C.B., Scanners, Antennas, Catalog 25 cents. Crystals Special cut, \$4.95. Monitor \$3.95. Send make, model, frequency. G Enterprises, Box 461P Clearfield, UT 84015

COMPUTER HOBBYISTS—classified advertising newsletter, \$3.75/year. Free Sample. ON LINE, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

SOUND SYNTHESIZER KITS—Surl \$12.95, Wind \$12.95, Wind Chimes \$17.95, Electronic Songbird \$6.95, Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

BUGGED??? New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

YOU WILL SAVE BIG MONEY! Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (redeemable). ETCOA Electronics, Box 741, Monreal, H3C 2V2, U.S. Inquiries.

HEAR POLICE/FIRE Dispatchers! Catalog shows exclusive directories of "confidential" channels, scanners. Send postage stamp. Communications, Box 56-PE, Commack, N.Y. 11725.

UNSCRAMBLERS. Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4" square \$29.95, fully guaranteed. Dealer inquiries welcomed. PDQ Electronics, Box 841, North Little Rock, Arkansas 72115

RECONDITIONED Test Equipment. \$0.50 for catalog. Walter's Test Equipment, 2697 Nickel, San Pablo, CA 94806

CB RADIOS, monitors, crystals, CD ignitions. Southland, Box 3591-B, Baytown, Texas 77520.

SURPRISES GALORE! Projects, ham radio, music synthesizers, etc. IC's, pots, hardware, crystals, keyboards, resistors, etc. Send 13 cents stamp for catalogue. UTEP, Box 26231B, Salt Lake City, Utah 84125.

NAME BRAND Digital/Analog Test Equipment. Discount prices. Free catalog. Salen Electronics, Box 82, Skokie, Ill. 60076.



**ORGAN KITS
KEYBOARDS**
THE ULTIMATE IN DESIGN
AND SOUND
Demo Record & Brochure \$1.00

Wurlitzer reproductions
DEVTRONIX ORGAN PRODUCTS, Dept. C
5872 Amapola Dr. • San Jose, CA 95129



**SIX DIGIT 12/24 HR.
CLOCK KIT**
\$22.95
MODEL DC-5

The best looking, most complete kit on the market! Features include: time set pushbutton, jumbo 4" readouts, Polaroid lens filter, pie cord transformer, super quality PC boards and durable extruded aluminum case available in five different colors. All parts are included. There are no extra needed! Super instructions reduce assembly time to 1-2 hours. Fully guaranteed. Colors available: gold, silver, bronze, blue and black (specify).

\$22.95
\$24.95
\$25.95

Clock Kit, DC-5
Alarm Clock Version, DC-8
12-24 Hr Clock with 10-Minute ID Timer, DC-10

**VIDEO TERMINAL
KIT \$149.95**

A compact 5 x 10-inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are: single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines read in and from memory, computer and keyboard-operated cursor and page control, parity error display and control, power-on initialization, full 64-character ASCII display, block-type write-through cursor, keyboard computer control backspaces, forward spaces, line feeds, rev line feeds, home, return cursor. Also clear page, clear to end of line, select page 1 or 2, read from or to memory. The card requires 5 volts at approx. 600 ma and outputs standard 75 ohm composite video.

TH3216 Kit \$149.95
TH3216, Assembled and Tested \$239.95
VD-1, Video to RF Modulator Kit \$ 6.95

MINI-KITS

**FM WIRELESS
MIKE KIT**
FM-1 \$2.95
Transmit and receive 100' to 1000' ft. with any FM radio. Requires no soldering. Includes all parts and instructions. Complete kit, TH-1 \$4.95

**LED
BLINKY KIT**
LED-1 \$2.95
A simple, yet fascinating project. Includes all parts and instructions. Complete kit, BL-1 \$2.95

**LED
BLINKY KIT**
LED-1 \$2.95
A simple, yet fascinating project. Includes all parts and instructions. Complete kit, BL-1 \$2.95

SUPER-SNOOP AMPLIFIER
A super sensitive amplifier with a built-in pre-amplifier. Includes all parts and instructions. Complete kit, SN-9 \$4.95

MUSIC LIGHTS KIT
See music, come alive! 3 different lights flash with music or voice. One light for three, one for the other two. Includes all parts and instructions. Complete kit, ML-1 \$7.95

SIREN KIT
Produces siren and alarm sounds. Includes all parts and instructions. Complete kit, SN-3 \$2.99

CODE OSCILLATOR KIT
Produces 1-10 MHz square wave. Includes all parts and instructions. Complete kit, CO-1 \$2.50

POWER SUPPLY KIT
Produces 1-10 VDC, 1-100 mA. Includes all parts and instructions. Complete kit, PS-1T \$6.95

DECADE COUNTER PARTS KIT
Includes 1000 10 MHz counter, 2225 10 MHz counter, 10 MHz counter, 10 MHz counter, 10 MHz counter, 10 MHz counter, 10 MHz counter, 10 MHz counter. Complete kit, DCU-1 \$3.50

CAR CLOCK KIT
6-Digit 12/24 HR.

- High Accuracy (1 Min. Month)
- Big 4" high readout
- Special circuit suppresses all spikes and transients
- Same case as DC-5 above
- Display blanks with ignition

Complete Kit, DC-7 \$25.95

CALENDAR ALARM CLOCK KIT
6-Digit 12/24 Hour

Has every feature one could ever ask for. Kit includes all parts except case. Build it into wall station or even can! Uses the incredible 7001 chip. Features:
 • 6-digit 5" high
 • Calendar shows mo, day
 • 24-Hour alarm with snooze
 • 12- or 24-Hr Format
 • Battery backup with on-chip time base
 Complete kit, less case, DC-9 \$34.95

**CAR
CLOCK
KIT \$27.95**

- 12-24-Hour 12-Volt AC or DC
- High Accuracy (1 minute month)
- Jumbo 4" LED readouts
- Easy no-polarity hookup
- Display blanks with ignition
- Case mounting bracket included
- Super instructions

Complete Kit, DC-11 \$27.95



**600 mHz
Prescaler**
\$59.95



Fully assembled and tested. Extend the range of your counter to 10 times higher in frequency. Works with any counter. High sensitivity input with built-in on-chip pre-amp.
 PS-1B 10 \$59.95

741 OP-AMP
Factory pre-mixed. 10 for \$2.00



MA-1003A CAR CLOCK MODULE \$23.95
MA-1002A ALARM CLOCK MODULE \$12.95
 Includes transformer and switches. Auto powers pre-mixed for use with 741.

LINEAR

555 .50
556 .75
567 1.75
1458 .65
LED DRIVER
75491 .50
75492 .50

REGULATOR

309K .99
309H .99
340K-12 .99
7805 .75
7812 .75
7815 .75
7818 .75

TRANSISTORS

NPN 2N3904 type 10/\$1.00
PNP 2N3906 type 10/\$1.00
NPN Power Tab 40W 3/\$1.00
PNP Power Tab 40W 3/\$1.00
FET MPF-102 type 3/\$2.00
JUN 2N2646 type 3/\$2.00
2N3055 NPN Power .75

ramsey electronics

P.O. BOX 4072 ROCHESTER, N.Y. 14610

(716) 271-8487

Telephone
Orders
Welcome

Free
Satisfaction
Guaranteed

Master Charge
Visa

Satisfaction guaranteed or money refunded. C.O.D. orders add \$1.00. Orders under \$10.00 add \$ 75. N.Y. residents add 7% sales tax.

PLANNING TO MOVE?

Let us know 8 weeks in advance so that you won't miss a single issue of **POPULAR ELECTRONICS**.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly.

Write to: P.O. Box 2774, Boulder, CO 80322 giving the following information:

☐ Change address only ☐ Extend my subscription

ENTER NEW SUBSCRIPTION

☐ 1 year \$12.00 ☐ Payment enclosed (1 extra BONUS issue)
Allow 30-60 days for delivery. ☐ Bill me later

AFFIX OLD LABEL

If you have no label handy, print OLD address here.

Name _____ please print

Address _____

City _____ Zip _____

State _____

NEW ADDRESS HERE 0208

Name _____ please print

Address _____ Apt. _____

City _____

State _____ Zip _____

Additional postage on foreign orders: add \$3 a year for Canada, \$5 a year for all other countries outside the U.S. and its possessions. Cash only on foreign orders, payable in U.S. currency

BUILD YOUR OWN SPEAKERS AND SAVE UP TO 50%

Send for our free fact-packed 44 page catalog manual and learn how to assemble your own multi-element stereo speakers from scratch or from kits. Our catalog includes chapters on design, construction, crossovers, enclosures, mountings, woofers, tweeters and horns. Write us today!

SPEAKERLAB
Dept. PE-A, 5500 35th N.E.
Seattle, Washington 98105



SURPLUS 'SMART' TERMINALS, components, serious music synthesizer kits, plans, parts, and more. Send SASE for FREE INFO Package. CFR Associates, POBF, Newton, N.H. 03858.

NON SEMI SURPLUS. Monthly picture flyer. Quality. Low prices. Send 25 cents. U.S. only. Startronics, Box 683, McMinnville, OR 97120.

BUILD AND SAVE. TELEPHONES, TELEVISION, DETECTIVE, BROADCAST Electronics. We sell construction plans with an Engineering Service. Speakerphones, Answering Machines, Carphones, Phonovision, Dialers, Color TV Converters, VTR, Games, \$25 TV Camera, Electron Microscope, Special Effects Generator, Time Base Corrector, Chroma Key, Engineering Courses in Telephone, Integrated Circuits, Detective Electronics. **PLUS MUCH MORE**. NEW Super Hobby Catalog PLUS year's subscription to Electronic News Letter, \$1.00. Don Britton Enterprises, 8200 Wilshire Blvd., Los Angeles, Calif. 90048.

NAME BRAND Digital/Analog Test Equipment. Discount prices. Free catalog. Salen Electronics, Box 82, Skokie, Illinois 60076.

SURPLUS COMPONENTS. Communication and test equipment. Illustrated catalog 25 cents. E. French, P.O. Box 248, Aurora, Illinois 60505.

ANYONE CAN SOLDER WITH — DO-IT-YOURSELFERS!

Let Kester solder aid you in your home repairs or hobbies. A radio, TV, model train, jewelry, plumbing, etc. Save money — repair it yourself. Send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".

KESTER SOLDER / 4201 Wrightwood Ave. Chicago, Ill. 60639

TELEPHONES UNLIMITED, Equipment, Supplies, All types, Regular, Keyed, Modular. Catalog 50 cents. Box 1147E, San Diego, California 92112.

FREE CATALOG. Solar Cells, Nicads, Kits, Calculators, Digital Watch Modules, Ultrasonics, Strobos, LEDs, Transistors, IC's, Unique Components. Chaney's, Box 27038, Denver, Colorado 80227.

POWERFUL, ADJUSTABLE, REGULATED, THREE OUTPUT POWER SUPPLY and 900 easily removable parts in complete CARTRIVISION television recorder electronic assembly with documentation. Perfect for MICROPROCESSOR, IC, transistor, television, CB radio applications. \$21.45. Free brochure. MADISON ELECTRONICS, INCORPORATED, 369, D55, Madison, Alabama 35758. SATISFACTION GUARANTEED.

CB RADIOS—Police Scanners. Wholesale only!! Send letterhead for lowest prices anywhere. Four Wheeler, 10PE, New Scotland, Albany, N.Y. 12208.

LEDs, red with mounting clip 20 cents each, 10 for \$1.80 prime parts. 75 cents postage and handling. CA res. add 6% tax. Hooker Electronics, P.O. Box 388, Hanford, CA 93230.

PROMS PROGRAMMED

No. bits	256	1024	2048	4096
TTL	\$ 7 up	\$ 8 up	\$ 11 up	\$ 19 up
Schottky	10 up	11 up	19 up	25 up
MOS	—	—	33 up	45 up

Price depends on mfr. type. Send \$1.00 packet fee now, bits desired. Receive specs on all our PROMS, program sheets, PROM postage credit. Pencil in program sheets, remit balance of price. We will send new guaranteed programmed PROM. Send packet fee (check or money order only) to: RBH Enterprises, Box 12344, Wichita, KS 67277

RADAR DETECTOR KIT. Build a long range radar detector with over one mile range. Kit comes with complete documentation and drilled, etched and plated PC board. Only \$4.95. Thousands sold nationally. Satisfaction guaranteed. Same day shipment. J.B. Saunders Company, 3050 Belmont, Boulder, Colorado 80501.

SEEKING JAPANESE TRANSISTORS for CB Repair? Request list. Fuji-Save Enterprise, Dept. P, Box 40325, Cincinnati, OH 45240.


PROFESSIONAL UNSCRABLERS — several models that fit any scanner. Free information. Capri Electronics, 8753T Windom, St. Louis, MO 63114.

BREATHE Better Air With Negative Ion Generator \$275.00. (KIT \$185.00.) Golden Enterprises, Box 1282PE, Glendale, Arizona 85311.

INTERNATIONAL ELECTRONICS UNLIMITED

SPECIAL SUMMER SALE (GOOD THRU AUGUST)

DIGITAL	SHIFT REGISTERS	LINEAR	LED
7400 \$.09	2511 \$1.49	301 mDIP \$.23	RED LED .190" \$.10
7410 .13	2527 1.95	311 mDIP	WHITE LED
7438 .17	2532 2.29	or 14 pin .69	(RED EMIT.)
7453 .14		340T 6V 1.09	RL2-03.160" .14
74181 1.95		723 DIP .49	DL 702 RED C.C. .30" LHD .99
74123 .49	CALCULATOR CHIP	741 mDIP .25	
74153 .69	5738 1.95	1458 mDIP .53	
74154 .99		75453 mDIP .27	
74C00 .13			

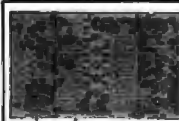

UNIVERSAL BREADBOARD

Accommodates 8, 14, 16, 4, 28 & 40 pin IC's. 2 triple rows of 27 holes for DIP IC's. Additional space for transistors, resistors & capacitors. Very versatile & simple to use. 1/16" phenolic with silver plated copper circuits. 3 3/16" x 5 1/16" **\$.89**

KEYBOARD

20 KEYS
2 SLIDE SW
3 x 3" **\$.69**

2102 \$1.29
1024X1 STATIC RAM 16 PIN

LED S

DL10A	RID CA .27" LHD	\$1.89
DL 707	RID CA .30" RHD	1.49
DL 507	RID CA .30" RHD	1.49
FND 359	RID CC .375" RHD	.89
DL 702	RID CC .30" LHD	1.39
NSN 74R	RID CC .30" RHD	1.49
DL 500	RID CC .30" RHD	1.49
MAN5	GREEN CA .27" LHD	1.39
MAN8	YELLOW CA .27" LHD	1.39
MAN82	YELLOW CA .3" LHD	1.89
MAN66	RID CA .5" LHD	2.19
DL747	RID CA .5" LHD	2.39

SPECIAL DEVICES

172	AP-IE Strip Detector DIP	2.99
546	AM Radio Receiver Subsystem DIP	.75
1310	FM Stereo Demodulator DIP	1.90
1496	Balanced Modulator-Demodulator	.99
1800	Stereo Multiplexer DIP	2.49
ULN2209	PM Gain Block 34db (typ) mDIP	1.19
ULN2209	PM Gain Block 48db (typ) mDIP	1.35
2513	Character Generator 16bits DIP-24	16.29
3046	Transistor Array DIP-14	.73

SHIFT REGISTERS

		EACH
2502	1024 bit MULT DYN 16 pin	\$3.75
2504	1024 bit MULT DYN 8 pin	3.75
2511	Tri-State Dual 50-100-200 bit	
	STATIC 14 pin	2.95
2518	Hex 32-bit STATIC 16 pin	2.95
2519	Hex 40-bit STATIC 16 pin	2.95
2527	Dual 256 bit STATIC 8 pin	2.95
2532	Quad 80 bit STATIC 16 pin	3.95
5013	1024 bit accum. Dynamic 8 pin	1.75
5016	508/512 bit Dynamic 8 pin	1.59

74S200

256 BIT RAM TRI-STATE
\$3.25
10% OFF WITH \$25 ORDER
15% OFF WITH \$100 ORDER
THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED



Carbon film - 5%

1/4 or 1/2 watt

455 resistors, 44 values

supplied in a 15 drawer,

60 compartment storage

cabinet — table or wall

mount. Ready to use

RESISTOR KIT

1/4 WATT 01255

1/2 WATT 01505

\$24.95

ADDL SHIPPING CHGS

\$2.00

RESISTOR ASSORTMENT

R (OHMS)

R	QTY.	R	QTY.	R	QTY.	R	QTY.
1.5	5	68	5	2.2K	20	33K	20
3.3	5	220	10	2.7K	10	39K	10
6.8	5	270	5	3.3K	10	47K	10
10	10	330	10	3.9K	10	68K	10
15	5	470	20	4.7K	20	100K	20
22	5	680	10	6.8K	10	150K	10
33	5	1.0K	20	22K	10	220K	10
47	10	1.5K	10	27K	10	270K	5

FREE CATALOG AVAILABLE ON REQUEST

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), or money order. Phone Orders — Both AM and M/C card or C.O.D.

Add \$1.00 to cover shipping and handling if order is less than \$10.00
California residents add sales tax. Include shipping expense for orders shipped out of U.S. and Canada approx. 10% of order.

INTERNATIONAL ELECTRONICS UNLIMITED
VILLAGE SQUARE, P.O. BOX 449
CARMEL VALLEY, CA 93924 USA
PHONE (408) 654-3171

IC SOCKETS

8 pin \$.17 24 pin .42
16 pin .20 28 pin .59
18 pin .22 40 pin .69
16 pin .24

WIRE WRAP - gold plate

14 pin .49

LINEAR CIRCUITS

100	\$.71	173	4.42	723	.43
101	.29	276	.64	733	.69
102	.53	300	1.50	739	1.87
104	.80	180-8	1.25	741	.12
105	.71	181	1.75	747	.71
107	.26	182	1.25	748	.35
108	.89				
109A	1.15	151	2.95	7458	.62
110	1.07	500	2.95	7459	2.48
111	.93	555	4.45	7524	.71
112	1.13	556A	1.19	7525	.90
1201	1.29	560	3.39	8038	4.25
1202	1.39	562	3.39	7454	1.25
122	1.78	565	1.95	75150	1.75
124	1.52	566	1.95	75451	.55
129	1.58	567	1.95	75452	.55
1401	1.69	709	.26	75453	.71
1401	1.69	710	.25	75454	.71
152	2.93	711	.26	75452	.80

Data included with order on request.
Add \$.30 ea. if item is priced below \$1.00

UNSCRAMBLE CODED MESSAGES from Police, Fire and Medical Channels. Same day service. Satisfaction guaranteed. Don Nobles Electronics, Inc., Rt. 7, Box 2658, Hot Springs, Arkansas 71901. (501) 623-6027.

UNSCRAMBLERS/DESCRAMBLERS: If you have tried the "cheapie" Squawk-Box unscramblers and have had nothing but aequal and frustration, then breathe new life into your scanner with our CODE-BREAKER. Tunes all scramble frequencies and operates with all scanners and monitors. Factory built and guaranteed. \$34.95. Catalog of many other descramblers and unusual electronic items. 25 cents. COD orders Tel. (501) 273-5340. KRISTAL KITS, Box 445, Bentonville, Ark. 72712.

TELEPHONE technology. Recent Schematics, ads, manuals. 5,000 pages: \$9.95 Guaranteed. Automated, Box 1027, Issaquah, WA 98027.

ANYTHING ELECTRONIC — we've got it. Catalog \$1.00. Razoo, Box 1224, Cupertino, Calif.

SLEEP UNDISTURBED! Mask unwanted sound with soothing "pink noise". \$57.50. Golden Enterprises, Box 1282-PE, Glendale, Arizona 85311.

PENNY FORMULAS. Private collection. 1,000 easily prepared product formulas only \$10. Distributor, R7B88, Milton, Florida 32570.

C2708, 8K EPROM: \$35.00; C1702A: \$7.50. PROGRAMMING: C2708 — \$20.00; C1702A — \$5.00. HEX OR OCTAL LISTING. ELECTRONIC DISCOUNT SALES, 138 N. 81st Street, Mesa, Arizona 85207

DEAD BATTERY? Lights left on. Easily installed alarm alerts driver with pulsing tone. \$12.95 postpaid. CFL Enterprises, P.O. Box 415, Export, PA 15632.

MICROCOMPUTER HARD COPY. Attachment converts any electric typewriter. Free Brochure. Stout Microcomputer, Box 1573, Fremont, CA 94538.

FREE CATALOG of Goodies — Clock kits, power supplies, DVM kits, LED's, semis, all at lowest prices. DIAMOND-BACK, Box 194P, Spring Valley, IL 61362.

TANK — TV GAME, Complete construction PLANS — \$10.00; P.C. BOARD — \$55.00; KITS — \$195.00; FREE information. ADVANCED ELECTRONICS, P.O. Box 133, Corvallis, OR 97330.

PRINTED CIRCUITS. Print photo resist with aerosol \$15.25. Quartz developer \$5.60. Four packs dry etchant \$5.58. Print in plating solution \$6.50. 8x10 auto lock exposure frame \$11.50. Ultraviolet lamp \$18. Shipping prepaid. CIRCOLEX, Box 168, Harp, N.Y. 13403.

GAMES for HP-35: Lunar Lander, Rascalack, Blackjack, Tank, Submarine, Nim; \$6. McCabe Engineering, 8107 Winsford Ave., L.A., CA 90045.

CUT & STRIPPED 30 AWG Wire \$9.10 per 1000. Price list free. Electro Products, 6110 S. Pilgrim St., Seattle, Washington 98118.

ELECTROLYTIC CAPACITORS top quality, reasonable prices, prompt delivery and free brochure. Ecom Parts Div., 3417 W. 8th St., L.A., CA 90005.

WIRE — Stranded and solid conductor — Wire — Wrap — Ribbon cable and connectors — MORE. Send 13 cents stamp for complete list. Ram Electronics, Box 338-P, Brookhaven, N.Y. 11719.

CARBON FILM RESISTORS 1/4W, 1/2W - 1.7 cents each. FREE sample / specifications. Other components. COMPONENTS CENTER, Box 134P, New York, N.Y. 10038.

FREQUENCY ALLOCATION CHART 2KHz-200Ghz. Send \$2.00. Collins Chart Co., Box 1067, Coronado, CA 92118.

TTL 7400N			TTL LOW POWER SCHOTTKY			CMOS							
SN7400N	.13	SN74125N	.40	SN74LS00N	.23	SN74LS138N	1.25	CD4000BE	.09	CD4035BE	.99	CD4507BE	.52
SN7401N	.14	SN74126N	.40	SN74LS01N	.23	SN74LS139N	1.35	CD4001BE	.18	CD4040BE	.99	CD4510BE	1.05
SN7402N	.14	SN74128N	.59	SN74LS02N	.23	SN74LS145N	1.19	CD4002BE	.13	CD4041BE	.67	CD4511BE	1.25
SN7403N	.14	SN74132N	.69	SN74LS03N	.23	SN74LS151N	.99	CD4006BE	.99	CD4042BE	.63	CD4512BE	1.15
SN7404N	.17	SN74136N	.59	SN74LS04N	.28	SN74LS153N	.99	CD4007BE	.17	CD4043BE	.45	CD4514BE	2.50
SN7405N	.17	SN74141N	.88	SN74LS05N	.28	SN74LS155N	1.45	CD4008BE	.80	CD4044BE	.45	CD4515BE	2.50
SN7406N	.25	SN74142N	3.70	SN74LS06N	.23	SN74LS156N	1.45	CD4009BE	.37	CD4046BE	2.45	CD4516BE	1.10
SN7407N	.25	SN74143N	3.98	SN74LS07N	.23	SN74LS157N	.99	CD4010BE	.37	CD4047BE	2.45	CD4518BE	.90
SN7408N	.17	SN74144N	3.88	SN74LS10N	.23	SN74LS158N	1.10	CD4011BE	.18	CD4049BE	.37	CD4519BE	.79
SN7409N	.17	SN74145N	.69	SN74LS11N	.23	SN74LS160N	1.50	CD4012BE	.17	CD4050BE	.37	CD4520BE	.79
SN7410N	.14	SN74147N	1.58	SN74LS12N	.25	SN74LS161N	1.50	CD4013BE	.37	CD4051BE	1.15	CD4522BE	1.98
SN7411N	.20	SN74148N	1.19	SN74LS13N	.65	SN74LS162N	1.50	CD4014BE	.89	CD4052BE	1.15	CD4526BE	1.50
SN7412N	.21	SN74149N	.95	SN74LS14N	1.35	SN74LS163N	1.50	CD4015BE	.89	CD4053BE	1.19	CD4527BE	1.50
SN7413N	.39	SN74151N	.61	SN74LS15N	.23	SN74LS164N	1.60	CD4016BE	.37	CD4055BE	1.29	CD4528BE	1.20
SN7414N	.84	SN74153N	.61	SN74LS20N	.30	SN74LS168N	2.25	CD4017BE	.94	CD4060BE	1.40	CD4531BE	1.25
SN7415N	.24	SN74154N	.95	SN74LS21N	.23	SN74LS169N	2.25	CD4018BE	.99	CD4066BE	.59	CD4539BE	1.20
SN7416N	.29	SN74155N	.70	SN74LS22N	.23	SN74LS170N	2.70	CD4019BE	.42	CD4068BE	.24	CD4555BE	.75
SN7420N	.14	SN74156N	.64	SN74LS26N	.37	SN74LS174N	1.25	CD4020BE	1.04	CD4069BE	.24	CD4556BE	.75
SN7421N	.20	SN74157N	.59	SN74LS27N	.27	SN74LS175N	1.25	CD4021BE	.99	CD4070BE	.24	CD4558BE	1.80
SN7422N	.20	SN74159N	2.50	SN74LS28N	.30	SN74LS181N	3.30	CD4022BE	.89	CD4071BE	.24	74C85/40085PC	1.20
SN7423N	.25	SN74160N	.85	SN74LS30N	.23	SN74LS190N	1.80	CD4023BE	.18	CD4072BE	.29	74C160/40160PC	1.50
SN7425N	.25	SN74161N	.85	SN74LS32N	.33	SN74LS191N	1.80	CD4024BE	.67	CD4073BE	.29	74C161/40161PC	1.50
SN7426N	.22	SN74162N	.85	SN74LS33N	.37	SN74LS192N	1.80	CD4025BE	.17	CD4075BE	.29	74C162/40162PC	1.50
SN7427N	.25	SN74163N	.85	SN74LS37N	.37	SN74LS193N	1.80	CD4026BE	1.39	CD4076BE	1.05	74C163/40163PC	1.50
SN7428N	.28	SN74164N	.98	SN74LS38N	.37	SN74LS194N	1.30	CD4027BE	.39	CD4078BE	.24	74C174/40174PC	1.40
SN7430N	.14	SN74165N	.97	SN74LS40N	.37	SN74LS195N	1.30	CD4028BE	.75	CD4081BE	.24	74C175/40175PC	1.40
SN7432N	.23	SN74166N	1.09	SN74LS43N	.37	SN74LS196N	1.40	CD4029BE	.79	CD4082BE	.24	74C192/40192PC	1.50
SN7433N	.39	SN74167N	2.75	SN74LS47N	1.10	SN74LS197N	1.40	CD4030BE	.37	CD4085BE	.75	74C193/40193PC	1.50
SN7437N	.21	SN74170N	1.69	SN74LS48N	1.10	SN74LS221N	1.30	CD4033BE	1.60	CD4086BE	.75	74C195/40195PC	1.40
SN7438N	.20	SN74172N	8.75	SN74LS49N	1.10	SN74LS240N	2.50	CD4034BE	2.95	CD4502BE	1.15		
SN7440N	.14	SN74173N	1.24	SN74LS51N	.23	SN74LS241N	2.40						
SN7442N	.37	SN74174N	.94	SN74LS54N	.23	SN74LS242N	2.40						
SN7443N	.68	SN74175N	.84	SN74LS55N	.23	SN74LS243N	2.40						
SN7444N	.85	SN74176N	.77	SN74LS56N	1.75	SN74LS244N	2.50						
SN7445N	.65	SN74177N	.76	SN74LS73N	.45	SN74LS247N	1.30						
SN7446N	.70	SN74178N	1.19	SN74LS74N	.45	SN74LS248N	1.30						
SN7447N	.67	SN74179N	1.49	SN74LS75N	.65	SN74LS249N	1.30						
SN7448N	.69	SN74180N	.67	SN74LS76N	.45	SN74LS251N	1.50						
SN7450N	.14	SN74181N	1.94	SN74LS78N	.45	SN74LS253N	1.50						
SN7451N	.14	SN74182N	1.94	SN74LS80N	1.39	SN74LS257N	1.50						
SN7453N	.14	SN74183N	1.75	SN74LS85N	1.60	SN74LS258N	1.40						
SN7454N	.14	SN74185N	1.74	SN74LS86N	.48	SN74LS261N	2.95						
SN7456N	.14	SN74186N	6.95	SN74LS90N	.89	SN74LS266N	.55						
SN7470N	.26	SN74188N	2.96	SN74LS91N	1.15	SN74LS279N	.75						
SN7472N	.25	SN74190N	1.04	SN74LS92N	.85	SN74LS283N	1.35						
SN7473N	.29	SN74191N	1.04	SN74LS93BN	.85	SN74LS290N	1.30						
SN7474N	.29	SN74192N	.84	SN74LS95AN	1.50	SN74LS293N	1.30						
SN7475N	.46	SN74193N	.84	SN74LS96N	1.65	SN74LS295AN	1.75						
SN7476N	.30	SN74194N	.89	SN74LS107N	.45	SN74LS298AN	1.75						
SN7480N	.35	SN74195N	.54	SN74LS109N	.50	SN74LS324AN	2.25						
SN7481AN	.95	SN74196N	.87	SN74LS112N	.45	SN74LS352AN	1.45						
SN7482N	.55	SN74197N	.73	SN74LS113N	.45	SN74LS353AN	1.70						
SN7483AN	.65	SN74198N	1.64	SN74LS114N	.45	SN74LS365AN	.69						
SN7484AN	1.50	SN74199N	1.64	SN74LS114N	1.14	SN74LS366AN	.69						
SN7485N	.84	SN74221N	1.14	SN74LS123N	.99	SN74LS367AN	.69						
SN7486N	.30	SN74246N	1.95	SN74LS124N	1.95	SN74LS368AN	.69						
SN7488N	1.85	SN74247N	1.70	SN74LS125N	.75	SN74LS375AN	.75						
SN7490AN	.43	SN74248N	1.75	SN74LS126N	.75	SN74LS386AN	.59						
SN7491AN	.59	SN74249N	1.75	SN74LS132N	1.19	SN74LS395AN	1.95						
SN7492AN	.44	SN74251N	1.05	SN74LS136N	.50	SN74LS670AN	2.75						
MOS AND BI-POLAR MEMORIES													
P/N		Description		Price									
C1702A		(1 Microsecond) 256 x 8 EPROM		8.95									
C1702A		(1.5 Microsecond) 256 x 8 EPROM		5.95									
C2708		1K x 8 EPROM (450 NS)		49.00									
8080A		8 Bit MOS CPU (2 microsecond)		14.95									
2102-1P		1K Static Ram 1024 x 1 (450 NS)		2.50									
3342PC		Quad 64 Bit Static Shift Register		4.50									
3347PC		Quad 80 Bit Static Shift Register		4.50									
3341APC		4 x 64 MOS FIFO 1 MHz Shift Register		4.50									
TMS0117NC		Decimal Arithmetic Processor		10.00									
LCM1001		Microprocessor Learning Module		149.95									
TMS4024NC		64 x 9 FIFO		8.95									
TMS4050NL		4K Dynamic RAM Plastic 300NS (18 Pin)		6.95									
TMS4060NL		4K Dynamic RAM Plastic 300NS (22 Pin)		6.95									
AY5-1013P		8 Bit UART		14.95									
SEMI 4804A		4K STATIC RAM 1024 x 4 (450 NS) single 5V supply		6.85									
93415PC		1K RAM 40 NS Open Collector		11.00									
93425PC		1K RAM 40 NS Tri-State		13.00									
AM2901DC		4 Bit Bi-Polar Microprocessor slice		31.50									
AM2902PC		Carry Look Ahead Circuit		3.19									
AM2905PC		Quad 2 Input Bus Transceiver		8.10									
AM2907PC		Quad Bus Transceiver with Tri-State Receiver and Parity		7.00									
AM2908PC		4 Bit Cascadable Microprogram Sequencer		7.15									
AM2918PC		Quad Deregister with Standard and Tri-State Outputs		4.32									
F8 Kit		8 Bit Microprocessor Evaluation Kit with Software		185.00									

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15
16	17	18
19	20	21
22	23	24
25	26	27
28	29	30
31	32	33
34	35	36

Please refer to heading on first page of this section for complete data concerning terms, frequency discounts, closing dates, etc. **WORD COUNT** 15 WORD MINIMUM. Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zip Code not counted. Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols such as 35mm, CDD, PQ, AC, etc., count as one word. Hyphenated words count as two words. Telephone numbers count as one word.

Words

\$2.25 (Commercial Rate)
\$1.35 (Reader Rate)
\$3.35 (Expand-Ad Rate)

☐ Payment of \$ _____ enclosed for _____ insertions.

☐ AmEx ☐ BAC

☐ MC ☐ Diners

CHARGE for _____ insertions
You will be billed monthly.

Account # _____ Expiration Date _____

Master Charge Interbank # (4 digits above name)

SIGNATURE MUST BE PROVIDED BELOW

PRINT NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____ PE-777

INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHCSC, Free Booklet. NILES BRYANT SCHOOL, 3631 Stockton, Dept. A, Sacramento, Calif. 95820.

SCORE high on F.C.C. Exams... Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar. Third and Second Test, \$14.50; First Class Test, \$15.00. All tests, \$26.50. R.E.I., Inc., Box 806, Sarasota, Fla. 33577.

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D's. Free revealing details. Counseling, Box 317-PE7, Tustin, California 92680.

SELF-STUDY CB RADIO REPAIR COURSE. THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write: CB RADIO REPAIR COURSE, Dept. PE07, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-2D, Olympia, Washington 98507.

GRANTHAM'S FCC LICENSE STUDY GUIDE — 377 pages, 1465 questions with answers/discussions — covering third, second, first radiotelephone examinations. \$13.45 postpaid. GSE, P.O. Box 25992, Los Angeles, California 90025.

INTENSIVE 5 week course for Broadcast Engineers. FCC First Class license. Student rooms at the school. Radio Engineering Inc., 81 N. Pineapple Ave., Sarasota, FL 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

LEARN BASIC Digital Troubleshooting by correspondence. Course includes text and demonstration modules. Educational Technologies, Box 224, Reynoldsburg, Ohio 43068.

HIGHLY EFFECTIVE Degree Program in Electronics Engineering. Advance rapidly! Our 31st Year. Free literature. Cook's Institute, Box 20345, Jackson, Miss. 39208.

BURGLAR/FIRE ALARM EXPERTS NEEDED for cars, homes, industry. Learn high profit systems installation at home spare time. Simple, quick, complete. Free information by mail. No salesmen. Security Systems Management School (homestudy), Dept. 7373-077, Little Falls, N.J. 07424.

GET YOUR COMMERCIAL FCC License. New exams by author of successful published workbooks of FCC Practice Tests. 500 Questions Second Class, \$11.95; 200 First Class, \$7.95; 100 Radar, \$4.95; postpaid. Save, all three \$19.95. Complete mathematical solutions. Free counselling service. Victor Veley, P.O. Box 14, La Verne, Calif. 91750.

1977 TESTS-ANSWERS for FCC First Class License. Plus "Self-Study Ability Test." Proven! \$9.95. Moneyback Guarantee. "FREE" BROCHURE. Command, Box 26348-P, San Francisco 94126.

FCC License Preparation, Communications Electronics, Electronic Technology with Lab., Television Servicing. Free Catalog. Genn Tech., 5540 Hollywood Blvd., L.A., CA 90028.

For
faster
service

USE
ZIP
CODE

on
all
mail

GODBOUT
BILL GODBOUT ELECTRONICS
BOX 2355 OAKLAND AIRPORT CA 94614

TERMS: Add \$6 orders under \$10. Allow up to \$1 for shipping; excess refunded. We require street address for COD. BankAmericard/Mastercharge (\$15 min) call 415-562-0636, 24h CA res add tax.

NEW 4K EconoROM \$265
with editor, assembler, and monitor routines for the 8080

Improved listing, bigger and better -SP and PSW are now implemented for greater user facility. Very low power, quality board, sockets for all ICs, and so on. Find out what moved Jay Bell, editor of Print-Out, to write:

"Without a doubt, this board is the best buy I have made for my Altair 8800 out of the \$5000 I've spent."

PRINT OUT, September 1974

CPU Power Supply \$45

Gives 5V @ 4A with crowbar overvoltage protection, +12V @ 1A, +12V @ 1A, and an adjustable 5-10V bias supply. Although intended for small computer systems, this is also a handy little bench supply for digital experiments.

CCc 8K EconoRAM II" \$163.84

Under 1¢ per bit. Configured as two independent 4K blocks for maximum flexibility. Full buffering, tri-state outputs drive the S-100 bus or any bidirectional bus; low power Schottky support ICs plus selected RAMs give low power operation, zips along at 450 ns or better (use 1 wait state with 2 801). Low profile sockets included for all ICs. Plated through, double-sided epoxy glass board.

UUu 10 Slot Motherboard \$85

Includes 10 edge connectors, use as IMAT add-on or for stand alone system. Active, regulated terminations minimize crosstalk, overshoot, and other bus problems. Epoxy glass board, quality parts, S-100 compatible, heavy power traces.

RRR 18 Slot Motherboard \$118

Same features as above, but with 18 slots & edge connectors.

KKk Terminator Board \$29.50

Add active terminations to your bus, and clean up the noise, crosstalk, ringing, and overshoot that can foul up data and crash programs. Plug into 1 slot of an S-100 compatible motherboard, and you are ready to go.

DEALER INQUIRIES INVITED

CAVE

BULLET ELECTRONICS
(214)823-3240
P.O. BOX 19442P
DALLAS, TEXAS 75219

THE MK-05 MINI MOBILE is a compact 6 digit DC clock with a quartz crystal timebase and alarm capability. The readout is a magnified .125" LED calculator readout. Kit comes complete with all components, PC board and instructions. 12 hour format only. Do not be fooled by our low price, this is a quality timepiece with voltage and noise suppression. 2 1/2 x 2 1/4 x 1 1/2 \$12.95

Own the most unique electronic clock on the market! The MG-01 MINI GRANDFATHER has a swinging pendulum, matching tick-tock sound, and a pleasant bell-like chime that is adjustable in pitch, volume and sustain. The chime sounds and counts the hours (ie: 3 times for 3 o'clock). Kit comes complete with 2 plated and drilled PC boards (8.5"x4.5"), 7 CMOS integrated circuits and a 40 pin clock IC. Also included are switches, speaker, bright 4 digit .5" LED display with colon and all necessary electronic components. \$39.95 Kit (less case)

Beautiful solid wood case over 8" tall custom cut for the MG 01 with ruby front filter and drilled rear panel. Available in WALNUT or ASH (please specify!) \$18.95 finished, shipped unassembled

OUR CUSTOMERS WRITE ABOUT OUR CDI KIT:

"...great kit!"

"...unbelievable value... good design!"

"...fantastic kit and service. Send three more."

The CDI kit is all these things and more. Get in on a one time deal. Complete electronics \$39.95

Requires heatsink (not included) also works for voltage source for high intensity strobe

MK-03 AIRCRAFT/CLOCK TIMER KIT.

You don't have to be a pilot to need the MK 03. If you want a mobile clock that offers: six .4" LED readouts, 24 hour real time readout, 24 elapsed time readout, alarm, snooze, display blanking. Time and clock share same set of readouts but are totally independent of each other. Timer has reset and freeze feature. Many other options are available. Solid less case and switches because of the various mountings and options available. \$26.95/complete electronics and boards less switches and case.

ULTRASONIC SENDER-RECEIVER KIT

A special buy on a high quality ultrasonic transducer allows us to offer this kit at a super price — but hurry, quantities are limited! You can build intrusion alarms, motion detectors, remote controls, echo ranging or liquid level measurement equipment. We supply the basic transmitter and receiver electronics including a drilled and plated PC board. The units work at 23KHz with a range of 20 ft. and can be positioned opposite each other or side-by-side and bounced off a solid surface. The output will sink up to 300ma to drive a relay, alarm circuit, etc. ORDER US-01 \$19.95

AUTOMATIC TIME-OUT CIRCUIT for ultrasonic or mechanical switch alarm. Provides a five second entry delay. Sounds alarm for one minute, then re arms itself. Requires 6-15VDC \$3.95

TERMS: NO COD's * Send check or M.O. * Add 5% postage Tx. Residents add 5% sales tax * Foreign add 10% (20% airmail) Orders under \$10. add 60¢ handling * Repair service available Accepting phone orders on Master Charge and BankAmericard.

DIGI-KEY CORPORATION

Quality Electronic Components

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES
PRICE BREAKTHROUGH ON 74LS'

74LS00	28	74LS00	28	74LS00	57	74LS157	25	74LS248	79
74LS01	28	74LS01	33	74LS02	57	74LS158	25	74LS249	79
74LS02	28	74LS03	33	74LS03	57	74LS159	102	74LS250	84
74LS03	28	74LS04	33	74LS04	57	74LS160	102	74LS251	84
74LS04	28	74LS05	33	74LS05	57	74LS161	102	74LS252	84
74LS05	28	74LS06	33	74LS06	57	74LS162	102	74LS253	84
74LS06	28	74LS07	33	74LS07	57	74LS163	102	74LS254	84
74LS07	28	74LS08	33	74LS08	57	74LS164	102	74LS255	84
74LS08	28	74LS09	33	74LS09	57	74LS165	102	74LS256	84
74LS09	28	74LS10	33	74LS10	57	74LS166	102	74LS257	84
74LS10	28	74LS11	33	74LS11	57	74LS167	102	74LS258	84
74LS11	28	74LS12	33	74LS12	57	74LS168	102	74LS259	84
74LS12	28	74LS13	33	74LS13	57	74LS169	102	74LS260	84
74LS13	28	74LS14	33	74LS14	57	74LS170	102	74LS261	84
74LS14	28	74LS15	33	74LS15	57	74LS171	102	74LS262	84
74LS15	28	74LS16	33	74LS16	57	74LS172	102	74LS263	84
74LS16	28	74LS17	33	74LS17	57	74LS173	102	74LS264	84
74LS17	28	74LS18	33	74LS18	57	74LS174	102	74LS265	84
74LS18	28	74LS19	33	74LS19	57	74LS175	102	74LS266	84
74LS19	28	74LS20	33	74LS20	57	74LS176	102	74LS267	84
74LS20	28	74LS21	33	74LS21	57	74LS177	102	74LS268	84
74LS21	28	74LS22	33	74LS22	57	74LS178	102	74LS269	84
74LS22	28	74LS23	33	74LS23	57	74LS179	102	74LS270	84
74LS23	28	74LS24	33	74LS24	57	74LS180	102	74LS271	84
74LS24	28	74LS25	33	74LS25	57	74LS181	102	74LS272	84
74LS25	28	74LS26	33	74LS26	57	74LS182	102	74LS273	84
74LS26	28	74LS27	33	74LS27	57	74LS183	102	74LS274	84
74LS27	28	74LS28	33	74LS28	57	74LS184	102	74LS275	84
74LS28	28	74LS29	33	74LS29	57	74LS185	102	74LS276	84
74LS29	28	74LS30	33	74LS30	57	74LS186	102	74LS277	84
74LS30	28	74LS31	33	74LS31	57	74LS187	102	74LS278	84
74LS31	28	74LS32	33	74LS32	57	74LS188	102	74LS279	84
74LS32	28	74LS33	33	74LS33	57	74LS189	102	74LS280	84
74LS33	28	74LS34	33	74LS34	57	74LS190	102	74LS281	84
74LS34	28	74LS35	33	74LS35	57	74LS191	102	74LS282	84
74LS35	28	74LS36	33	74LS36	57	74LS192	102	74LS283	84
74LS36	28	74LS37	33	74LS37	57	74LS193	102	74LS284	84
74LS37	28	74LS38	33	74LS38	57	74LS194	102	74LS285	84
74LS38	28	74LS39	33	74LS39	57	74LS195	102	74LS286	84
74LS39	28	74LS40	33	74LS40	57	74LS196	102	74LS287	84
74LS40	28	74LS41	33	74LS41	57	74LS197	102	74LS288	84
74LS41	28	74LS42	33	74LS42	57	74LS198	102	74LS289	84
74LS42	28	74LS43	33	74LS43	57	74LS199	102	74LS290	84
74LS43	28	74LS44	33	74LS44	57	74LS200	102	74LS291	84
74LS44	28	74LS45	33	74LS45	57	74LS201	102	74LS292	84
74LS45	28	74LS46	33	74LS46	57	74LS202	102	74LS293	84
74LS46	28	74LS47	33	74LS47	57	74LS203	102	74LS294	84
74LS47	28	74LS48	33	74LS48	57	74LS204	102	74LS295	84
74LS48	28	74LS49	33	74LS49	57	74LS205	102	74LS296	84
74LS49	28	74LS50	33	74LS50	57	74LS206	102	74LS297	84
74LS50	28	74LS51	33	74LS51	57	74LS207	102	74LS298	84
74LS51	28	74LS52	33	74LS52	57	74LS208	102	74LS299	84
74LS52	28	74LS53	33	74LS53	57	74LS209	102	74LS300	84
74LS53	28	74LS54	33	74LS54	57	74LS210	102		
74LS54	28	74LS55	33	74LS55	57				
74LS55	28	74LS56	33	74LS56	57				
74LS56	28	74LS57	33	74LS57	57				
74LS57	28	74LS58	33	74LS58	57				
74LS58	28	74LS59	33	74LS59	57				
74LS59	28	74LS60	33	74LS60	57				
74LS60	28	74LS61	33	74LS61	57				
74LS61	28	74LS62	33	74LS62	57				
74LS62	28	74LS63	33	74LS63	57				
74LS63	28	74LS64	33	74LS64	57				
74LS64	28	74LS65	33	74LS65	57				
74LS65	28	74LS66	33	74LS66	57				
74LS66	28	74LS67	33	74LS67	57				
74LS67	28	74LS68	33	74LS68	57				
74LS68	28	74LS69	33	74LS69	57				
74LS69	28	74LS70	33	74LS70	57				
74LS70	28	74LS71	33	74LS71	57				
74LS71	28	74LS72	33	74LS72	57				
74LS72	28	74LS73	33	74LS73	57				
74LS73	28	74LS74	33	74LS74	57				
74LS74	28	74LS75	33	74LS75	57				
74LS75	28	74LS76	33	74LS76	57				
74LS76	28	74LS77	33	74LS77	57				
74LS77	28	74LS78	33	74LS78	57				
74LS78	28	74LS79	33	74LS79	57				
74LS79	28	74LS80	33	74LS80	57				
74LS80	28	74LS81	33	74LS81	57				
74LS81	28	74LS82	33	74LS82	57				
74LS82	28	74LS83	33	74LS83	57				
74LS83	28	74LS84	33	74LS84	57				
74LS84	28	74LS85	33	74LS85	57				
74LS85	28	74LS86	33	74LS86	57				
74LS86	28	74LS87	33	74LS87	57				
74LS87	28	74LS88	33	74LS88	57				
74LS88	28	74LS89	33	74LS89	57				
74LS89	28	74LS90	33	74LS90	57				
74LS90	28	74LS91	33	74LS91	57				
74LS91	28	74LS92	33	74LS92	57				
74LS92	28	74LS93	33	74LS93	57				
74LS93	28	74LS94	33	74LS94	57				
74LS94	28	74LS95	33	74LS95	57				
74LS95	28	74LS96	33	74LS96	57				
74LS96	28	74LS97	33	74LS97	57				
74LS97	28	74LS98	33	74LS98	57				
74LS98	28	74LS99	33	74LS99	57				
74LS99	28								

INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400	21	7476	32	74181	215	4012	23	4520	114
7401	21	7480	70	74182	70	4013	23	4521	114
7402	21	7482	70	74184	219	4014	23	4522	114
7403	21	7483	70	74185	219	4015	96	4523	1.68
7404	21	7485	89	74188	350	4016	40	4524	1.68
7405	21	7486	28	74189	350	4017	23	4525	1.68
7406	21	7489	219	74190	23	4018	105	71002	24.95
7407	21	7490	44	74191	123	4019	23	CA3004	1.99
7408	21	7491	70	74192	58	4020	114	UM2111N	1.80
7409	21	7492	44	74193	88	4021	23	UM3099N	1.80
7410	21	7493	44	74194	88	4022	96	UM3407-5	1.25
7411	21	7494	44	74195	58	4023	23	UM3407-6	1.25
7412	21	7495	70	74196	58	4024	84	UM3407-8	1.25
7413	21	7496	44	74197	88	4025	23	UM3407-9	1.25
7414	89	74100	128	74198	149	4026	68	UM3407-115	1.25
7415	25	74121	30	74199	149	4027	40	UM3407-18	1.25
7416	25	74123	33	74200	109	4028	23	UM3407-34	1.25
7420	21	74101	35	74279	55	4029	114	UM3909N	1.80
7421	25	74122	44	74365	67	4030	23	UM3909N	1.80
7422	35	74123	61	74366	67	4031	53	MC14569	1.99
7423	35	74124	40	74367	67	4032	53	MC14569	1.99
7424	35	74126	40	74368	67	4033	114	MC3309	1.13
7427	33	74130	70	8093	40	4040	114	NE53A7	3.24
7428	28	74141	88	8094	40	4041	79	NE54D	2.04
7429	28	74142	70	8095	67	4042	79	NE55A	2.04
7430	25	74147	1.63	8096	67	4043	30	NE55A	2.04
7433	30	74148	130	8097	67	4044	70	NE56B	3.83
7437	25	74150	116	8098	67	4046	86	NE5618	3.83
7440	21	74151	116	8099	116	4047	79	NE5618	3.83
7442	53	74153	65	75450	88	4050	40	NE565A	1.28
7444	53	74154	103	75451	61	4051	26	NE566A	1.28
7445	63	74155	70	75452	61	4052	26	NE567V	1.38
7446	70	74156	70	75453	61	4053	26	UM209V	1.80
7447	70	74157	70	75454	61	4054	58	UM4700A	44
7448	70	74160	88	75451	81	4056	79	UM4710A	44
7449	70	74161	88	75452	81	4057	23	UM4711A	50
7450	21	74162	88	75453	199	4057	73	UM4712A	50
7451	21	74163	88	75454	119	4073	23	UM4714V	44
7452	21	74164	96	87225	219	4075	29	UM4747C	44
7454	21	74165	115	87226	115	4076	23	UM4802C	1.25
7459	21	74166	126	4001	22	4067	23	UM78025CU	1.25
7460	21	74170	264	4002	23	4502	79	UM7809CU	1.25
7470	30	74173	142	4006	123	4510	114	UM7809CU	1.25
7471	30	74174	142	4007	123	4511	114	UM7810CU	1.25
7473	30	74175	93	4008	79	4514	280	UM7815CU	1.25
7474	30	74176	79	4009	44	4516	280	UM7818CU	1.25
7475	89	74180	70	4010	44	4518	14	UM7824CU	1.25

HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure, Pickering, Stanton, Empire, Grado and ADC. Send for free catalog. LYLE CARTRIDGES, Dept. P, Box 69, Kensington Station, Brooklyn, New York 11218.

MUSIC GENERATOR—Real-time automatic composition and production of music. See Radio-Electronics, June, 1977 or write: Inner Space Electronics, Box 308, Berkeley, CA 94701.

TUBES

RADIO & T.V. Tubes—36 cents each. Send for free Catalog. Cornett, 4213 University, San Diego, Calif. 92105.

TUBES receiving, factory boxed, low prices, free price list. Transistoric, Inc., 1365 39th Street, Brooklyn, N.Y. 11218A, Telephone: 212-633-2800.

TUBES: "Oldies", Latest. Supplies, components, schematics. Catalog Free (stamp appreciated). Steinmetz, 7519-PE Maplewood, Hammond, Ind. 46324.

BURGLAR ALARMS

DIALING UNIT automatically calls police. \$29.95. Free security equipment catalog. S&S Systems, 5619-C St. John, Kansas City, MO 64123. (816) 463-4612

MUSICAL INSTRUMENTS

UP TO 60% DISCOUNT. Name brand instruments catalog. Freeport Music, 114 G. Mahan St., W. Babylon, N.Y. 11704.

SERVICES

SWL's, CB's, HAM's. WDX will register your listening post and issue a certificate with call sign-type identification. Details for return post-age from Monitor, P.O. Box 3333, Cherry Hill, N.J. 08034.

GOVERNMENT SURPLUS


MANUALS for Govt Surplus radios, test sets, scopes. List 50 cents (coin). Books, 7218 Roanne Drive, Washington, D.C. 20021.

GOVERNMENT SURPLUS. Buy in your Area. How, where. Send \$2.00. Surplus, 30177-PE Headquarters Building, Washington, D.C. 20014.

JEEPS, TRUCKS, Typically from \$52.40 ... Automobiles, Boats, Motorcycles, Airplanes, Oscilloscopes, Tools, Clothing, Sports, Camping, Photographic, Electronics Equipment ... 200,000 Bid Bargains Nationwide Direct from Government ... Low as 2 cents on Dollar! Surplus Catalog and Sales Directory \$1.00 (refundable). National Surplus Center, 240 Eastcase-PEL, Joliet, Illinois 60432.

WANTED

GOLD, Silver, Platinum, Mercury wanted. Highest prices paid by refinery. Ores assayed. Free circular. Mercury Terminal, Norwood, MA 02062.




Olson

ELECTRONIC PARTS AND ACCESSORIES

249 PH-331 REG. **2.99**

Stereophones

- Comfortable, Lightweight
- 25-18k Hz. Response
- With 6-Ft. Cord & 1/4" Stereo Plug



NICKEL CADMIUM "AA" Pen-Lite Cells

• Rechargeable
For radios, calculators, etc. 1.2 Volt.

\$1 Ea.

BA-341


	Reg.	Sale
60 Min. Cassette, Pkg. of 3, TA-879	1.49	.87
2V. RED L.E.D., Pkg. of 5, PL-233	1.99	.59
40 Min. 8-Track Tape, TA-907	.69	.39
Elect. Cap. Kit, 50 Ass't., CD-407	5.00	1.70
Black Light Bulb, XM-291	1.00	.49
CB Converter for Car, CD-417	14.99	9.99
Resistors 1/2 watt, Pkg. 100, RR-077	1.79	.79
Volume Controls, 12 Ass'td. VC-274	1.00	.49
Empire 999 Mag. Phono Cart. PC-188	9.99	6.99
3-6V DC Hobby Motors, 5 Ass'td. MD-333	2.00	.59
Solder Terminal Strips, 40 Ass'td. XM-501	1.38	.50
Double Face Foam Tape 1/4" x 52", TA-903	1.00	.80
1/4 RPM Timing Motor, 117 VAC, MO-277	.49	.30
Tape Mailers, 3" Pkg. 5, TA-936	.79	.39
Ceramic Disc Cap., 100 Ass'td. CC-210	1.29	.80
Knob Kit, 25 Pcs. Ass'td., KN-030	1.80	.69
8-Track Tape Deck Chassis, RA-383	17.00	12.99
7 Seg. L.E.D. Display Conn. K., XM-414	2.00	1.00
Calculator Keys, 20 Ass'td. XM-538	.75	.39
6V-.5A. Transformer TF-047	1.09	.49
2SB474 TO'66 Output Trans., TR-147	3.79	1.19

Olson

electronics

260 S. FORGE ST.
DEPT. IZ AKRON, OHIO 44327

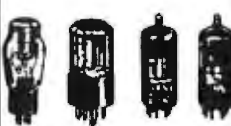NAME _____
ADDRESS _____
CITY _____ STATE _____
ZIP _____ ☐ Send Olson Cat.
ENCLOSE POSTAGE AND SALES TAX



EDLIE TUBE BONANZA

BUY BRAND NEW MANUFACTURER'S BOXED TUBES (Raytheon, Dumont, IEC Mullard, etc.) AT 70% OFF LIST!

MONEY BACK GUARANTEE

Terms: Minimum order \$10.00. Include postage. Either full payment with order or 30% deposit, balance C.O.D. F.O.B. Levittown, N.Y.


70% OFF LIST!			
1AD2	1.67	6AR5	.92
1B3	1.67	6AU4	2.97
1BC2	1.59	6AU5	2.54
1K3	1.67	6AU6	1.34
1S2A	1.04	6AU8	2.25
1U4	1.67	6AV6	1.16
1V2	1.02	6AW8	1.88
1X2B	1.64	6AX4	1.59
2AH2	1.67	6AY3	1.59
2AV2	1.32	6AZ8	3.37
2D21	1.95	6BA6	1.41
2GK5	1.65	6BA11	2.06
2HA5	1.43	6BC5	1.41
3AT2	1.65	6BE6	1.55
3BS2	1.79	6BH6	1.59
3CN3	1.74	6BH11	2.13
3CU3	2.06	6BK6	1.74
3CY3	1.85	6BK4	3.14
3DJ3	1.79	6BK7	2.10
3GK5	1.62	6BL8	1.16
3HA5	1.61	6BM8	1.56
3HQ5	2.39	6BN6	2.07
3JC6	2.16	6BN8	1.73
3V4	2.30	6BN11	3.09
4AU6	1.67	6BQ5	1.65
4B26	1.49	6BQ7A	2.19
4C86	1.16	6BR8A	2.24
4DT6	1.64	6BY11	2.48
4EH7	1.52	6BX6	1.56
4EJ7	1.52	6BZ6	1.32
4HS8	1.58	6C4	1.65
4JC6	2.15	6C5	3.28
4JDE	1.98	6CA4	1.70
4KE8	2.60	6CA7	2.34
4LJ8	1.91	6CB6	1.40
5AQ5	1.61	6CD6	2.98
5AR4	2.15	6CG3	1.65
5C6B	1.71	6CG7	1.28
5EW6	1.71	6CG8	1.82
5GH8	1.98	6CJ3	1.58
5GJ7	1.25	6CL3	1.70
5GS7	1.43	6CL6	2.18
5GX7	1.76	6CL8	2.04
5HZ6	1.26	6CM6	1.77
5JK6	1.77	6CM7	1.80
5JL6	2.10	6CS6	1.76
5KE8	2.60	6CU5	1.73
5LJ8	1.85	6CW4	4.17
5U4GB	1.31	6CW5	1.43
5Y3GT	1.38	6D6	2.39
5Y4GT	2.10	6DA6	2.10
6A8	4.70	6DJ8	2.50
6AB4	1.61	6DK6	1.55
6AC7	3.87	6DL4	2.39
6AC10	1.82	6DO6	2.25
6AD10	3.86	6DT6	1.40
6AF4	2.31	6DW4	1.58
6AF9	2.39	6DX8	1.17
6AG7	4.53	6E5	3.90
6AH6	2.40	6EA8	1.65
6AJ8	2.10	6EB8	2.52
6AL3	1.28	6EH7	1.61
6AL5	1.37	6EJ7	1.50
6AM8	2.31	6EM7	2.37
6AN8	1.91	6EU7	1.70
6AQ5	1.43	6EW6	1.50
6AQ8	1.49	6EW7	2.51

6F6GT	4.09	6JW8	1.41	7KY6	2.16
6FG6	1.43	6K6GT	1.71	7Y7	3.60
6FG7	2.40	6K7GT	2.40	8A8	1.13
6FM7	1.94	6K8	3.60	8AC9	2.43
6FQ7	1.28	6KA8	2.04	8AR11	3.12
6GE5	1.64	6KD6	3.54	8BA11	2.36
6GF7	2.24	6KE8	2.66	8BM11	3.39
6GH8	1.32	6KM6	3.54	8BQ11	2.49
6GJ7	1.25	6KT8	2.28	8BU11	2.42
6GK5	1.95	6KV6	2.81	8CB11	3.24
6GK6	1.47	6KZ8	1.71	8CG7	1.28
6GM6	1.76	6L6GB	2.57	8CW5	1.43
6GM8	3.30	6L6	4.50	8JL8	1.43
6GS7	1.52	6L7	4.50	8JY8	1.95
6GU7	1.76	6LB6	3.38	8L78	1.68
6GW8	1.47	6LE8	2.39	9A08	2.31
6GX6	1.46	6LF6	3.36	9G8	1.32
6GX7	1.92	6LH6	3.23	9KX6	2.16
6H6	3.33	6LH8	1.85	10CW5	1.43
6HA5	1.61	6LJ8	1.84	10DX8	1.17
6HB7	1.62	6LM8	2.04	10GF7	2.18
6HE5	2.01	6LN8	1.11	10GK6	1.91
6HF5	3.96	6LR6	3.23	10GN8	2.01
6HF8	2.28	6LT8	1.71	10J78	2.16
6HQ5	2.13	6LU8	2.01	10JY8	1.56
6HS5	3.09	6LX8	1.11	10KX8	2.15
6HS6	2.66	6M11	3.30	11AF9	2.39
6HS8	2.00	6MB8	1.95	11AR11	2.60
6HY5	3.72	6MD8	2.46	11BM8	2.09
6HZ6	1.34	6MG8	1.41	11BT11	3.17
6J5GT	1.77	6SA7	3.74	11FY7	1.67
6J7	4.35	6SG7	3.95	11KV8	2.31
6J10	2.66	6SJ7GT	2.33	11LQ8	2.27
6J86	2.54	6SK7GT	2.40	11MS8	1.71
6JC6A	1.88	6SL7GT	2.40	12AB5	1.43
6JDE	1.94	6SN7GT	1.59	12AT7	1.43
6JEEGA	3.51	6SO7GT	2.42	12AUE	1.52
6JF6	1.90	6T8A	2.01	12AU7	1.29
6JH6	1.50	6T10	2.36	12AY6	1.08
6JH8	2.64	6U8A	1.64	12AZ7	1.32
6JMG6A	2.28	6U10	1.70	12BA6	1.86
6JN6	2.13	6V6	4.01	12BE6	1.22
6JS6C	3.12	6V6GT	1.92	12BF11	2.49
6JT6	2.54	6X4	1.52	12BH7	1.67
6JTB	2.01	6X5GT	1.55		
6JVB	2.99	6X8	1.92		
6JUB	1.86	6X9	1.88		
6JV8	1.89	7F8	9.00		

WRITE FOR FREE VALUE PACKED CATALOG

EDLIE ELECTRONICS, INC.

2700-PP HEMPSTEAD TPKE., LEVITTOWN, N. Y. 11756



DD1456-DIGITAL COLOR CONVERGENCE GENERATOR BY SCIENCE WORK SHOP. The miracle of Large Scale Integration (LSI) which made the low cost pocket calculator possible has now been applied to test equipment. A single monolithic P-channel MOS integrated circuit generates a composite video signal, complete with all sync and blanking pulses. Binary countdown from a single master clock oscillator (rather than 2 separate, unsynchronized oscillators) provides solid phase-lock of all horizontal, vertical and color signals. There are NO COUNTING ADJUSTMENTS! Using digital matrix switching techniques, 4 slide switches select any one of 16 patterns. A unique oscillator/modulator stage provides both R.F. and VIDEO output for trouble shooting circuits by signal injection. Although primarily intended for servicing Color TV sets, these compact (1 1/4" x 2 1/4" x 4") generators are excellent for amateur TV, computer terminals, closed circuit TV, video tape equipment, TV broadcast subsystems and cable TV wire. TV station type spec. No counter adjustments. Crystal controlled chroma osc. Epoxy-glass PC Boards. 2 year warranty video & RF output 3 color patterns. Model DB-12 (16 patterns) wired only \$64.95. Model DB12K in kit form \$49.95. Model DB11 (13 patterns) wired only \$49.96. Model DB11K (13 Patterns) in Kit Form \$39.95. 2 YEAR WARRANTY ON BOTH TYPES.

102

CIRCLE NO 34 ON FREE INFORMATION CARD

CIRCLE NO 14 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

7400 TTL					5400 SERIES					MOTOROLA CIRCUITS					JAPANESE CIRCUITS							
7400	21	7442	108	74121	95	5400	100	5475	150	MC725P	150	MC1741CG	98	AN136	290	HA1312	405	STK056	1135	TA7201P	640	
7401	21	7448	115	74122	49	5404	125	5486	190	MC740L	155	MC1804P	98	AN203	375	HA1322	520	STK415	1150	TA7203P	700	
7402	21	7450	26	74123	05	5410	100	5493	200	MC790P	150	MC1810P	98	AN208	475	HA1339	520	TA7045M	350	TA7204P	650	
7404	21	7451	27	74125	60	5426	125	54100	180	MC832P	48	MC2033L	45	AN211	330	LA1201	425	TA7054P	305	TA7205P	650	
7405	24	7453	27	74126	81	5473	150	54LS04	100	MC1004L	125	MC3004L	132	AN214	490	LA1366	500	TA7055P	550	TA78005M	250	
7406	45	7454	41	74132	300					MC1008L	125	MC3006P	144	AN217	330	LA1364	470	TA7060P	185	TA78005P	195	
7407	45	7456	22	74134	115					MC1010L	125	MC3007P	132	AN229	635	LA3301	485	TA7149P	400	TA78012M	250	
7408	25	7472	38	74150	110					MC1011L	125	MC3021L	215	AN232	575	LA4030	485	TA7063P	225	TA78015M	250	
7409	25	7473	45	74151	126	4001AE	29	4022AE	120	MC1036L	1250	MC3021P	215	AN239	650	LA4031P	485	TA7074P	490	TA78015P	195	
7410	20	7474	45	74153	135	4002AE	29	4023AE	99	MC1037L	1250	MC3060L	265	AN241	320	LA4031P	485	TA7075P	490	TC9100P	1200	
7411	30	7475	80	74154	125	4007AE	29	4034AE	150	MC1357P	105	MC3062L	300	AN245	650	TA8401	350	TA7076P	455	UPC100P	1200	
7413	85	7482	175	74155	121	4009AE	58	4040AE	35	MC1406CP	395	MC4024P	220	AN274	395	LD3080	400	TA7089P	290	UPC20C	500	
7416	43	7483	115	74157	300	4010AE	58	4026AE	149	MC1468L	290	MC14501CP	31	AN277B	340	LD3120	310	TA7102	515	UPC41C	395	
7417	43	7485	112	74161	145	4011AE	29	4042AE	160	MC1469L	250	MC14502CP	118	AN288	480	LD3141	240	TA7106P	325	UPC48C	395	
7420	21	7486	45	74164	165	4012AE	29	4029AE	290	MC1510G	800	MC14507CP	82	AN328	405	M5112	540	TA7120P	220	UPC554C	390	
7422	150	7489	249	74165	165	4013AE	52	4030AE	65	MC1514L	450	MC14510CP	240	BA511	390	M5155P	285	TA7120P-C	230	UPC563H2	800	
7425	43	7490	69	74166	170	4015AE	125	4037AE	450	MC1550G	150	MC14511CP	276	BA521	390	M5155	285	TA7122AP	230	UPC568H	225	
7427	37	7491	120	74174	95	4016AE	65	4040AE	240	MC1558	437	MC14512CP	192	HA1158	630	STK011	1050	TA7124P	185	UPC575C	410	
7428	33	7492	82	74175	195	4018AE	110	4044AE	150	MC1595L	625	MC14519CP	94	HA1159	660	STK015	1050	TA7148P	410	UPC100H2	515	
7430	26	7493	82	74180	105	4019AE	65	4046AE	275	MC1596G	325	MC14528CP	174	HA1202	310	STK025	1250	TA7153P	455	UPC1020H	550	
7432	31	7494	91	74181	355	4020AE	175	4049AE	75	MC1722CG	125	MC4044P	480	HA1306W	520	STK032	1420	TA7200P	625	UPC1025	950	
7437	47	7495	91	74191	150	4021AE	150	4050AE	75													
7438	40	7496	91	74195	100																	
7440	21	74100	125	74197	100																	
7441	110	74107	49	74298	130																	

74L SERIES TTL					MISC CIRCUITS					VOLTAGE REGULATORS					IC's ON THE MOVE							
74L00	33	74LS04	45	74LS113	98	BC184L	60	LM309K	195	SN15844N	55	LM340K-5	195	BBD BUCKET BRIGADE DEVICE		MM3001	1950	MM3002	1170	MM3003	945	
74L10	33	74LS10	39	74LS138	189	CA3001	75	LM351AN	70	SN15845	55	LM340K-6	195	HALL IC	DN834	125	DN837	150				
74L30	33	74LS20	39	74LS174	250	CA3005	80	LM741CP	40	SN158097N	60	LM340K-12	195	DN835	135	DN838(NEW)						
74L42	150	74LS51	39	74LS386	550	CA3018	160	MFC9020	15	SN727410N	85	LM340K-15	195	SN76001	175	SN76002	195					
74L86	69	74LS74	65	74LS153	225	CA3018A	160	MR955A	105	SN72741C	45	LM340K-18	195	PLLO2A	MIDLAND PHASE LOCK LOOP							
74LS00	39	74LS112	65	74LS387	195	CA3026	215	MSC5967P1	50	SN72748P	45	LM340K-24	195									
					CA3035	245	N5555	55	UA703C	95	LM340T-5	175		MICROPROCESSOR CHIPS								
					CA3039	135	N5898B	50	UA709C	40	LM340T-6	175		1404A	325	2102	250	MM5013	325			
					CA3058	190	N555V	45	USF7733393	240	LM340T-8	175		CI702A	1995	C2708	9500	8008	1995			
					CK707P	45	PA771131	45	995879	650	LM340T-12	175		2101	695	CA702A	1995	8080A	2995			
					CS134J	115	PL994551	45	996078	1250	LM340T-16	175		MC4200 P-11	4096x1	256x16	Ram					
					CS135J	120	RC14370B	35	996979	900	LM340T-18	175		CS101-3	1024 Bit	(Dynamic)	Static C-Mos Ram					
					CS138	125	SC9962P	70	936550	110	LM340T-24	175		MC14514	4 Bit	Latch	4 to 16 Line Decoder					
					IC3(GE)	150	SC9966P	125	93130DC	120				CALL OR WRITE FOR FURTHER INFORMATION.								
					LM301AN	35	SN15830N	50	93128DC	275				SPEC'S AVAILABLE								
										NEGATIVE REGULATORS AVAILABLE												

ELECTROLYTIC CAPACITORS			CARBON RESISTORS Minimum 5 Pcs Per Value			HOBBY SPECIALS			PACE/PATHCOM PART #'S				
			QUANTITY			YOU TEST EM SAVE BIG MONEY							
2 2MF50	AXIAL LEADS	15	PRICING	5-25	30-95	100-495	Power Pac	100 Asst (includes Case T03, T056	\$2 99	130079	4 00	IP20-0123 2 75	
3 3MF10	AXIAL LEADS	15	1/4w5	06	05	04	Transistor	100 Asst (includes Case T05,		1300821	65	IP20-0131 2 50	
3 3MF10	NO POLARITY	15	1/2w5	08	07	06	Diode Pac	T039 T018, D07, 0041)	\$1 99	13-0122	1 75	IP20-0141 3 00	
10MF25	AXIAL LEADS	15	STANDARD RESISTANCE VALUES				I/C Pac	100 Asst (includes 14 & 16 Pim)	\$3 50	83-0007	2 50	IP20-0142 3 00	
10MF50	AXIAL LEADS	15	OHMS				Resistor Pac	50 Asst (Associated values)	\$1 50	83-0007	2 50	IP20-0139 4 3	
10MF150	AXIAL LEADS	20	10	270	820	4 7K	Mos Fet Pac	10 Asst (many top #'s Case T072)	\$0 99	83-0008	2 50	IP20-0154 6 00	
25MF35	AXIAL LEADS	15	22	300	910	5 1K	SCR Pac	100 Asst (similar to C103 Series) Case to 92.	\$4 00	83-0015	3 00	IP20-0155 2 50	
30MF25	AXIAL LEADS	15	47	330	1 0K	6 8K	VR 10-100V, 1 400MA 1GT 200MA				IP20-0005	3 00	IP20-0181 4 00
47MF25	RADIAL LEADS	15	51	470	1 5K	7 5K					IP20-0016	40	IP20-0177 2 75
47MF50	RADIAL LEADS	20	100	510	2 2K	8 2K					IP20-0034	85	IP20-0176 2 85
100MF16	RADIAL LEADS	15	150	560	2 7K	10K					IP20-0037	85	IP20-0181 72
100MF25	RADIAL LEADS	20	220	680	3 3K	15K					IP20-0045	2 00	
500MF50	AXIAL LEADS	60									IP20-0073	2 50	IP20-0093 2 50
1000MF53	AXIAL LEADS	60									IP20-0073	2 50	
										ZENER DIODES			
										1/2 & 1 Watt 10%, 30 each UP TO 33V.			
										GREATER THAN 33V CALL FOR PRICING			

JAPANESE TRANSISTORS • CB. AUDIO. INDUSTRIAL										POPULAR JEDEC SEMICONDUCTORS											
2SA52	60	2SC206	100	2SC774	175	2SC1173	95	2SD77	100	1N34	25	2N818	60	2N2218	25	2N2906A	30	2N3646	14	2N4220A	45
2SA316	55	2SC240	110	2SC775	275	2SC1175	85	2SD81	325	1N60	25	2N830	25	2N2218A	30	2N2907	25	2N3730	250	2N4234	95
2SA473	75	2SC291	65	2SC776	300	2SC1029	55	2SD88	150	1N270	40	2N855	30	2N2910A	30	2N3731	375	2N4400	18		
2SA483	195	2SC292	300	2SC777	400	2SC1213	75	2SD118	325	1N914	10	2N860	90	2N2219A	30	2N3733	150	2N4401	18		
2SA485	80	2SC320	75	2SC778	400	2SC1228A	125	2SD130	125			2N862	95	2N2221	25	2N2914	120	2N3771	175	2N4402	18
2SA490	70	2SC352	75	2SC781	300	2SC1231	40	2SD141	225	2N173	175	2N867	95	2N2222A	30	2N2915A	365	2N3772	190	2N4403	20
2SA505	70	2SC353	75	2SC783	100	2SC1239	400	2SD151	225	2N174	350	2N1136	175	2N2223	25	2N2916A	50	2N3773	300	2N4404	18
2SA564	50	2SC371	70	2SC784	70	2SC1243	150	2SD170	200	2N177A	90	2N1142	225	2N2223A	30	2N3053	30	2N3819	40	2N4410	18
2SA582	65	2SC372	70	2SC785	100	2SC1293	85	2SD180	275	2N327A	115	2N1300	100	2N2223	100	2N3054	70	2N3823	70	2N4418	75
2SA643	85	2SC394	70	2SC789	100	2SC1306	475	2SD201	195	2N334	120	2N1301	110	2N2270	40	2N3055	75	2N3858	20	2N5081	30
2SA647	275	2SC458	70	2SC793	250	2SC1307	575	2SD218	475	2N338	90	2N1302	125	2N2323	100	2N3227	100	2N3866	85	2N5084	50
2SA673	85	2SC480	70	2SC796	315	2SC1308	475	2SD235	100	2N386A	105	2N1303	70	2N2324	135	2N3247	340	2N3903	18	2N5130	20
2SA679	375	2SC478	80	2SC797	250	2SC1317	60	2SD300	250	2N388B	150	2N1304	125	2N2325	200	2N3250	50	2N3904	18	2N5133	15
2SA682	85	2SC481	185	2SC798	310	2SC1318	70	2SD313	110	2N404	75	2N1305	75	2N2326	285	2N3275	650	2N3905	18	2N5138	15
2SA689	130	2SC482	175	2SC799	425	2SC1325	495	2SD315	75	2N443	250	2N1306	135	2N2327	400	2N3393	20	2N3906	18	2N5192	375
2SA689A	145	2SC481	250	2SC802	375	2SC1327	70	2SD316	250	2N456	130	2N1307	75	2N2328	425	2N3394	17	2N3925	375	2N5294	50
2SA705	55	2SC495	110	2SC803	400	2SC1338	175	2SD317	125	2N501A	300	2N1308	150	2N2329	475	2N3414	17	2N3954	350	2N5296	50
2SA815	85	2SC497	160	2SC816	75	2SC1346	80	2SD318	95	2N508A	45	2N1309	90	2N2336	25	2N3415	18	2N3954A	375	2N5308	20
2SA816	85	2SC502	150	2SC828	75	2SC1347	80	2SD325	125	2N555	75	2N1552	325	2N2369	25	2N3418	19	2N3955	245	2N5354	20
		2SC515	80	2SC829	75	2SC1354	150	2SD341	95	2N677	800	2N1557	115	2N2712	18	2N3442	185	2N4038	75	2N5400	40
2SB22	65	2SC517	425	2SC830	160	2SC1377	550	2SD350	325	2N706	25	2N1560	280	2N2884	40	2N3553	150	2N4037	80	2N5401	50
2SB54	70	2SC535	75	2SC838	70	2SC1383	75	2SD352	80	2N708B	75	2N1805	35	2N2903	330	2N3583	20	2N4093	85	2N5457	35
2SB56	70	2SC536	65	2SC839	85	2SC1384	85	2SD380	570	9N711	90	2N1813	30	2N2904	25	2N3585	20	2N4124	18	2N5458	30
2SB77	70	2SC537	70	2SC922	55	2SC1409	125	2SD389	75	2N711B	110	2N1817	10	2N2904A	25	2N3588	20	2N4126	20	CIQ37	25
2SB128	225	2SC563	250	2SC929	70	2SC1410	125	2SD390	75	2N716	25	2N1907	40	2N2905	25	2N3642	20	2N4141	20	CIQ61	20
2SB152	450	2SC607	125	2SC930	85	2SC1447	125			2N718A	30	2N2080	165	2N2905A	30	2N3843	20	2N4142	20	CIQ61B	50
										2N720A	50	2N2102	40	2N2906	25	2N3845	20	2N4143	20		

2SA52	60	2SC206	100	2SC774	175	2SC1173	95	2SD77	100										
2SA316	75	2SC240	110	2SC775	275	2SC1175	85	2SD81	135										
2SA473	75	2SC291	60	2SC776	300	2SC1209	55	2SD118	325										
2SA483	195	2SC292	300	2SC777	400	2SC1213	75	2SD130	125										
2SA489	80	2SC320	74	2SC778	400	2SC1226	125	2SD141	225										
2SA490	70	2SC352	75	2SC781	300	2SC1237	45	2SD151	225										
2SA505	70	2SC353	75	2SC783	100	2SC1239	400	2SD170	200										
2SA564	50	2SC371	70	2SC784	70	2SC1243	150	2SD180	275										
2SA643	85	2SC394	70	2SC789	100	2SC1306	475	2SD201	195										
2SA647	275	2SC458	70	2SC793	250	2SC1307	575	2SD218	475										
2SA673	85	2SC480	70	2SC794	100	2SC1308	475	2SD220	475										
2SA674	100	2SC481	70	2SC795	100	2SC1309	475	2SD221	475										
2SA675	125	2SC731	300	2SC796	100	2SC1310	475	2SD222	475										
2SA676	125	2SC731	300	2SC797	375	2SC1311	475	2SD223	475										
2SA681	210	2SC732	300	2SC798	375	2SC1312	475	2SD224	475										
2SA682	125	2SC733	300	2SC799	375	2SC1313	475	2SD225	475										
2SA683	125	2SC733	300	2SC800	375	2SC1314	475	2SD226	475										
2SA684	125	2SC733	300	2SC801	375	2SC1315	475	2SD227	475										
2SA758	125	2SC733	300	2SC875	375	2SC1389	475	2SD301	475										

TREASURE FINDERS

SERIOUS COIN SHOOTERS — Semtech's solid-state METL-SENSOR pin-points ALL metal objects, yet defines the target before you dig. **FOR FREE** literature write Semtech Corporation, 652 Mitchell Rd., Newbury Park, Calif. 91320.

TAPE AND RECORDERS

RENT 4-Track open reel tapes—free brochure. Stereo-Parti, P.O. Box 7, Fulton, CA 95401.

WE WILL BEAT any price sheet in America. Featuring TDK, MAXELL, and others. Tape World International, 220 Spring St., Butler, PA 16001.

8-TRACK and CASSETTE BELTS — money back guarantee. Long wearing. Free Catalog — \$3 minimum order. PRB Corp., Box 176, Whitewater, Wisconsin 53190.

LP's, TAPES, Current, Outlets, Imports, Catalogs \$1; Beatles LP-Tape Sale. NERT, Box 268-PE, Lawrence, Mass 01842.

HOME ENTERTAINMENT FILMS

MIDSUMMER FILM SALE — All vs. Inoki (The Boxer vs. the Wrestler or Karate vs. Ali) Super 8 B&W SPECIAL \$6.95 ea. PPD. Wrestling featuring wrestlers like Jim Londos & Joe Savoldi — set of 2, \$8.95 ea. PPD (5 bouts to a reel — \$2.00 off per reel) — Buy singly or as a set! Add to or start a World Series Official Film collection: Your choice of 200' Super 8 B&W \$8.95 ea or Color \$16.95 ea — 1969-1975 — each a separate reel. Indicate exact year. Send for Columbia catalog, \$0.65; Universal 8 catalog, \$0.75; Sport-lite forms \$0.35. SPORTLITE, Elect-7, Box 24-500, Speedway, Indiana 46224.

PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes-Verlag, Box 110680-Z, D-1000 Berlin 11, Germany.

WARTS. Vengo® Cream is painless, safe, easy, gentle. Buy Vengo® at better pharmacies.

P.O. Box 4430C Santa Clara, CA 95054
(408) 988-1640



Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

740000	17	74LS200N	41	LM339AN	4	740001	21	740002	21
740001	17	74LS200N	41	LM339AN	4	740002	21	740003	21
740002	17	74LS200N	41	LM339AN	4	740003	21	740004	21
740098	17	74LS200N	41	LM339AN	4	740099	21	740100	21
740099	17	74LS200N	41	LM339AN	4	740100	21		

740100	21	740101	21	740102	21	740103	21	740104	21
740101	21	740102	21	740103	21	740104	21	740105	21
740102	21	740103	21	740104	21	740105	21	740106	21
740230	21	740231	21	740232	21	740233	21	740234	21
740231	21	740232	21	740233	21	740234			

Radio Hut

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under \$15.00 add 75 cents. Foreign orders add 10% for postage.

For your convenience, call your BankAmericard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.



P.O. Box 64783P
Dallas, Texas 75206



Memorex computer boards
with IC's, diodes, transistor,
etc. 5 Boards containing
100 - 200 IC's
ONLY \$ 4.25

BRIDGE RECTIFIERS

6 Amp	50V	1.10
10 Amp	50V	1.25
25 Amp	50V	1.39

RESISTORS

Over 50,000,000
in stock

*330 ohm	22K ohm
470 ohm	27K ohm
*680 ohm	33K ohm
1K ohm	39K ohm
1.2K ohm	43K ohm
2.2K ohm	47K ohm
3.3K ohm	82K ohm
4.7K ohm	100K ohm
6.8K ohm	150K ohm
10K ohm	220K ohm
20K ohm	

*1.8 W only

*1.2 W only

All resistors are P.C. Lead but are
not pull offs
100 min. order for each value

NO MIX

100/99

MK 5005

4 digit counter/latch
decoder; 7 segment
output only. 24 pin
dip with specs.

\$ 8.00 EACH

UNSCRAMBLER KIT for all Scanners

- Tunes easily
- Full instructions included
- Easy to install
- 3 1/2" x 3 1/2" x 1 1/2"

Only \$19.95

PLASMA DISPLAY KIT

Kit Includes: 12 digit display .4" Character
Power supply for display
above Complete specs for
hookup.

Line cord Not Included. **ONLY \$ 3.95**



SPECIAL DEVICES

82S23	2.19
2513	10.00
MK4102-1	.99

PROJECT CASES

Small	Med	Large
\$1.50	\$2.00	\$2.75
D 2 1/2"	D 2"	D 2 1/2"
W 4 3/4"	W 4 7/8"	W 7"
H 1 7/8"	H 3 1/2"	H 4"

All cases have a slotted front, white
with black veneer finish

REGULATORS

7805	7818
7806	7824
7808	7905
7812	7912
7815	7915
Your Choice \$.95	

READOUTS



FND70 .4"C.C.	.59
FND800 .8"C.C.	1.69
TI 6 digit array C.C.	3/1.00
MAN 8 .3"CA Yellow	.89
LT767 .7"C.C. 4 digit stick	\$ 3.95

WATERGATE SPECIAL

Telephone Relay automatically starts and
stops tape recorder. No batteries required.
Kit complete with drilled P.C. Board.

Parts and Case **ONLY \$ 10.95**

CLOCK KIT

Kit includes

- LT701 clock module
- Power Supply
- Punched Case
- 12 or 24 hour operation

Complete
except for line cord

LT701E 12 hour clock
LT701G 24 hour clock
ONLY \$ 14.95



VARIABLE POWER SUPPLY KIT NO. 1

- *Continuously variable from 5V to 20V
- *Excellent regulation up to 500 mil.
- *4400 Mfd of filtering
- *Drilled fiberglass PC Board
- *One hour assembly
- *Kit includes all components
- *Case Included

ONLY \$ 10.95



VARIABLE POWER SUPPLY KIT NO. 2

Same as above but with 1 amp output, also with case.
ONLY \$ 13.95

BATTERY CLIPS

Standard 9V battery clip with
4-1/2" tinned leads. 25/\$1.00

TTL

7400	17	7473	21
7401	17	7474	35
7402	17	7475	55
7403	17	7476	35
74H04	25	7480	45
7404	17	7483	78
7406	25	7485	89
7408	17	7486	35
7409	17	7490	71
7410	17	7491	71
7411	25	7492	71
7413	45	7493	67
7420	17	7494	90
7421	17	7495	71
7423	35	7496	85
7425	27	74100	96
7426	25	74121	31
7427	17	74123	81
7430	25	74125	44
7432	30	74141	71
7437	35	74145	97
7438	35	74151	71
7440	17	74153	81
7442	60	74154	97
7443	60	74181	91
7444	85	74183	105
7446	85	74184	105
7447	81	74174	91
7448	81	74175	140
7450	20	74180	78
7451	17	74181	225
7453	17	74181	120
7454	17	74182	120
7470	35	74193	95
7472	21	74196	65

TRANSISTORS - DIODES

*MJE110	1.10
MJ1001	1.10
N2	6.10
N2 1/2	6.10
*N2 1/2	4.10
*N2 1/2	15.10
N1406	6.10
N4200	6.10
N4441 SCR	1.10
N4004	15.10
N400	10.10
N4140 (N414) 20/1.00	
N201 VHF Pre amp 80	
D40C1 Power Dart - 8/1.00	

*House numbered
and P.C. Lead

PC BOARDS

4 digit PCB for FND800 or 807	2.50
6 digit PCB for FND800 or 807	3.50
4 digit PCB for DL 707	1.50
6 digit PCB for DL 707	2.00
4 digit PCB for FND503 or 510	2.00
6 digit PCB for FND503 or 510	3.00
4 digit PCB for DL 747	2.50
6 digit PCB for DL 747	3.00
4 digit PCB for DL 727 or 728	2.00
6 digit PCB for DL 727 or 728	3.00
4 digit PCB for FND359 or 70	1.75

NOTE: All PC Boards are multiplexed
for adding additional digits.

HARDWARE

New, includes 2-56, 4-40, 6-32 and 8-32
screws and nuts. A very usable selection.

1/2 pound \$1.50
1 pound \$2.60

L S

74LS00	.25
74LS02	.25
74LS04	.30
74LS08	.25
74LS10	.25
74LS11	.32
74LS20	.31
74LS21	.33
74LS22	.33
74LS27	.30
74LS30	.31
74LS32	.33
74LS37	.40
74LS38	.35
74LS74	.49
74LS90	.85
74LS132	.90
74LS138	.89
74LS139	.89
74LS155	.90
74LS157	1.00
74LS162	1.39
74LS163	1.39
74LS175	1.09
74LS193	1.09
74LS258	1.09
74LS367	.70
74LS368	.70

CMOS SALE

4020	.85	4046	.90
CD4000	.16	CD4040	1.00
CD4001	.16	CD4041	.69
CD4002	.16	CD4042	.59
CD4007	.16	CD4043	.60
CD4009	.45	CD4044	.59
CD4010	.45	CD4047	.59
CD4011	.16	CD4049	.35
CD4012	.16	CD4050	.35
CD4013	.29	CD4051	.90
CD4014	.75	CD4053	.90
CD4015	.75	CD4056	1.00
CD4016	.29	CD4058	.90
CD4017	.80	CD4060	1.00
CD4018	.80	CD4066	.69
CD4019	.39	CD4069	.30
CD4021	.90	CD4071	.16
CD4022	.90	CD4076	.99
CD4024	.70	74C04	.29
CD4025	.19	74C107	.29
CD4027	.39	CD4116	.39
CD4028	.75	CD4507	.40
CD4029	.99	CD4512	.50
CD4030	.16	CD4516	.85
CD4034	2.30	CD4518	.85
CD4035	.99	CD4520	.85

LINEARS

LM301	.30
LM309	.30
LM309A	.95
LM311	.85
LM3	.85
LM380 (8 pin)	.75
LM3900	.30
LM710	.25
LM711	.25
LM723	.40
LM741	.25
LM748	.75
NE553	1.95
NE555	.40
NE556	.95
NE565	.95
NE566	.95
NE567	1.10
1458	.49
RCA3043	.75
75491	.30
75492	.30

60 Hz L(•)(•)K

Crystal Time Base Kit - Kit
enables a MOS clock circuit to
operate from a DC power source. Ideal
for car, camper, van, boat, etc.

60Hz output with an accuracy of
.005% (typ.) Low power consumption
2.5 ma (typ.). Small size will
fit most any enclosure. Single MOS
IC oscillator/divider chip 5-15 volts
DC operation.

ONLY \$ 5.95
2 for \$10.00

RADIO HUT GUARANTEE

If you are not satisfied with any of
our products **NO MATTER WHAT
THE REASON** we offer you a full
money back guarantee if the product
or products are returned within
14 days after you receive them.

ORDER BY PHONE. Charge your
order to BankAmericard or
Master Charge.

USE OUR TOLL FREE WATTS

1-800-527-2304

World's Lowest IC Prices

* SPECIAL PRICES *

MEMORIES		74100	2.95	74174	2.95	CNOS	
RAMs		74118	1.95	74175	2.05	4001	.15
745200	2.95	74123	.45	74181	2.95	4002	.15
2102	1.50	74141	.85	74197	2.50	4003	.90
2102-1	1.70	74145	.75	74257	1.50	4007	.15
74100		74150	.80			4008	.70
74101		74151	.80			4012	.15
74102		74152	.80			4013	.15
74103		74153	.80			4018	.30
74104		74154	.80			4019	.70
74105		74155	.80			4020	.30
74106		74156	.80			4021	.35
74107		74157	.80			4022	.15
74108		74158	.80			4023	.20
74109		74159	.80			4024	.35
74110		74160	.75			4025	.30
74111		74161	.75			4026	.30
74112		74162	.75			4027	.30
74294		74344	.75			4209	.30

FREE INFORMATION:

Learning more about a product that's advertised or mentioned in an article in this month's issue is as simple as one, two, three. And absolutely free.

1 Print or type your name and address on the attached card. Use only one card per person.

2 Circle the number(s) on the card that correspond to the number(s) at the bottom of the advertisement or article for which you want more information. (Key numbers for advertised products also appear in the Advertisers' Index.)

3 Simply mail the card, and the literature will be mailed to you free of charge from the manufacturer.

FREE INFORMATION:

This address is for our product Free Information Service only. Editorial inquiries should be directed to POPULAR ELECTRONICS, One Park Avenue, New York, N.Y. 10016.

POPULAR ELECTRONICS

USE ONLY ONE CARD PER PERSON

PE7773

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

(Zip Code must be included to insure delivery.) (Void after Sept. 30, 1977)

Do you feel that electronic home study courses are:

- Reliable a. ☐ Yes b. ☐ No
Difficult c. ☐ Yes d. ☐ No
Expensive e. ☐ Yes f. ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

POPULAR ELECTRONICS

USE ONLY ONE CARD PER PERSON

PE7772

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

(Zip Code must be included to insure delivery.) (Void after Sept. 30, 1977)

Do you feel that electronic home study courses are:

- Reliable a. ☐ Yes b. ☐ No
Difficult c. ☐ Yes d. ☐ No
Expensive e. ☐ Yes f. ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

POPULAR ELECTRONICS

USE ONLY ONE CARD PER PERSON

PE7771

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

(Zip Code must be included to insure delivery.) (Void after Sept. 30, 1977)

Do you feel that electronic home study courses are:

- Reliable a. ☐ Yes b. ☐ No
Difficult c. ☐ Yes d. ☐ No
Expensive e. ☐ Yes f. ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

First Class
Permit No. 217
Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905
Clinton, Iowa 52732

First Class
Permit No. 217
Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905
Clinton, Iowa 52732

First Class
Permit No. 217
Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905
Clinton, Iowa 52732

Stereo Review's Model SR12 STEREO TEST RECORD



The most complete...
most sophisticated...
most versatile Test Disc
available today...

For Just \$6⁹⁵!

Who needs the New Model SR12? You do. Whether you're an avid audiophile, a casual listener, or a professional technician... the new MODEL SR12 will be the most important disc in your entire collection. MODEL SR12 has been produced by Stereo Review Magazine for music lovers who want immediate answers to questions about the performance of their stereo systems and how to get the best possible sound reproduction. It is the most complete test record of its kind—containing the widest range of checks ever included on one test disc.

Make these important stereo checks BY EAR... (no test instruments required)

• Frequency response • Separation • Cartridge tracking • Channel balance • Hum and rumble • Flutter • Cartridge and Speaker Phasing • Anti-Skating Adjustment • "Gun Shot Test" for Stereo Spread • Multi-purpose Musician's "A" • Equal-tempered Chromatic Octave • Guitar-tuning Tones

Attention professionals: For the ultimate in stereo testing, 7 critical TEST EQUIPMENT checks...

- 1,000-Hz square waves to test transient and high-frequency response of phono pickups
 - 500 to 20,000 Hz frequency-response sweep
 - Sine-wave tone-bursts to test transient response of pickup
 - Intermodulation test using simultaneous 400-Hz and 4,000-Hz signals
 - Intermodulation sweep to show distortion caused by excessive resonances in tone arm and cartridge
 - 1,000-Hz reference tones to determine groove velocity
 - 2,000-Hz tone for flutter and speed tests
- Sample waveforms—illustrating both accurate and faulty responses are provided in the Instruction Manual for comparison with the patterns appearing on your own oscilloscope screen.

FREE Instruction Manual Includes Detailed Instructions, Charts, Tables and Diagrams

HERE'S HOW TO ORDER

CASH: Mail your order along with your name, address and remittance in the amount of \$6.95. Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax.

CHARGE: To your American Express, BankAmericard, Master Charge or Diners Club account! Mail your order, name, address, credit card # and expiration date (Master Charge customers include 4-digit Interbank # above your name). Be sure your signature is on your order. You will be billed at \$6.95.

OUTSIDE U.S.A. RECORD IS \$8.95.

ORDER FROM: STEREO TEST RECORD, CONSUMER SERVICE DIVISION, 595 BROADWAY, NEW YORK, N. Y. 10012.

Poly Pak's EXCLUSIVE SURE-FIRE BARREL KITS®

Way to Fight Inflation! Each kit carries a money-back guarantee!

Buy
10
BARREL KITS
AND CHOOSE THE
11TH
Free!

Test 'em yourself 'n save! Includes 100% material, too!

INFLATION!

Each kit carries a money-back guarantee!

BARREL KIT #230 SHIELDED CABLE 50-ft. \$1.98 For Mike, stereo, 1-coad, plug shield, 22 ga. vinyl jacket. Wt. 1 lb. 7E3577	BARREL KIT #230 HALF INCH READOUTS 7E3629 15 for \$1.98 From factory to you. Includes: Fairchild FND-500 & 501's	BARREL KIT #225 SOUND TRIGGERS 3 for \$1.98 "Hand clap" switches, crystal mike amplifier, triggers SCR. Cat. No. 7E3625	BARREL KIT #231 IC SOCKETS 8 for \$1.98 Mir. underlaid Four 14-pin, Four 18-pin. Solder, call, in-profile. Cat. No. 7E3621	MIXED READOUTS 15 for \$1.98 Barrels of untested 17", 3", 6" Trigs. Like FND-507, 400, 603, MAN-3's. Wt. a buy! Cat. No. 7E3619	BARREL KIT #205 MINI BLOCK CAPACITORS 50 for \$1.98 Unbelievable! Worth \$50. High precision submini caps for all applications. Cat. No. 7E3628	BARREL KIT #203 CALCULATOR KEYBOARDS 10 for \$1.98 It's true! 20-key, 4 function keyboards at ridiculous give-away. Wt. 12 oz. Cat. No. 7E3624
BARREL KIT #210 GLOW-IN- DARK PANELS 3 for \$1.98 4" x 1" panels that glow blue-green with 110VAC. Use for night lights, indicators, etc. Cat. No. 7E3550	100 for \$1.98 PLUGS, SOCKETS Distributor's untested! Includes: AC, DC, RF, audio, 4-7 pin, all kinds. Wt. 1 lb. Cat. No. 7E3527	BARREL KIT #201 6V INDICATORS 15 for \$1.98 Test lamp manufacturer dumps inventory! Worth 60¢ ea. Like strain-on-wheat. Cat. No. 7E3526	BARREL KIT #200 9 DIGIT READOUT MODULES 5 for \$1.98 With calculator driver chips beneath epoxy. Cat. No. 7E3515	BARREL KIT #199 TRANSISTORS & DARLINGTONS 50 for \$1.98 Motorola dumps 1,000,000 TO-220 in barrels. NPN & PNP. Cat. No. 7E3543	BARREL KIT #191 CARBON FILM RESISTORS 800* for \$1.98 1/2 round, approx. 1.5, 1.4 watt. Ass't values. Unmarked. Cat. No. 7E3448	BARREL KIT #188 400 Parts \$1.98 Includes: transistors, caps, transformers, rectifiers, diodes, etc. for p.c. work. Refractory, dumped into barrels by factory. 100% Cat. No. 7E3401
BARREL KIT #187 AUDIO IC'S 30 for \$1.98 National & Sprague, 2 to 4 watters, LM-350, LM-377, 227's, etc. DIPs, some with heat sinks. Untested Cat. No. 7E3392	BARREL KIT #185 PC BOARDS 400 parts \$1.98 parts: 80 transistors, 50 1/2 watters, 200 capacitors, diodes, etc. Cat. No. 7E3388	BARREL KIT #184 1/4-WATT METAL FILM 150 for \$1.98 100% metal film resistors. Long leads. 7E3412	BARREL KIT #182 JUMBO RED LEDS 15 for \$1.98 100% material, used in calculator from factory dumps. 3V 10 mil. For 100's of projects, red lens. Cat. No. 7E3369	BARREL KIT #183 MINI TRIM POT'S 30 for \$1.98 Ass't. values 100 to 1 meg. What a buy. Single sure. 1/4 W. Wt. 6 oz. 7E3345	BARREL KIT #181 POP! PLASTIC TRANSISTORS 25 for \$1.98 353004's with a watter 2N3005's of 100% material. TO-92, Performed. Cat. No. 7E3343	BARREL KIT #160 V. REGULATORS 10 for \$1.98 Hobby No. 7E3330 LM300KC TO-3 V.R.'s barreled. Bot by the pound.
BARREL KIT #159 MODULAR SWITCHES 25 for \$1.98 Centralab switches TV-makers excess. Dpdt, 6pdt, etc. Brand new. Cat. No. 7E3360	BARREL KIT #158 MAGNIFIED MAN-3'S 20 for \$1.98 MAN-3's, 7-watt readout, built-on magnifier, factory distributed line. 100% material. Cat. No. 7E3355	BARREL KIT #155 MOLDED CAPACITORS 75 for \$1.98 Ass't. values, red, green, yellow, blue plastic cases, axial leads, 1 lb. 7E3311	BARREL KIT #154 CLOCK CHIPS 20 for \$1.98 We gathered up assortment of clock chips, alarm, calendar, beepers, who knows, all mixed. Cat. No. 7E3309	BARREL KIT #145 MINI TRANSFORMER 15 for \$1.98 Output, interstage, output. Only 1/2 W. Wt. 2 lb. 7E3294	BARREL KIT #144 RCA PHONO PUS 40 for \$1.98 1,000,000 RCA phono plugs for use in separate. You know what they are... 100% material. 7E3293	BARREL KIT #138 PANEL SWITCHES 30 for \$1.98 Did you hear of OAK? Another great maker barreled all types of potting, electronic, slides, etc. 7E3268
BARREL KIT #135 MICRO MINI LAMPS 20 for \$1.98 Imaginal Micro size 1/4 x 1/4, with wire leads, 3 to 5 VDC, 10 mil. 7E3259	BARREL KIT #132 MINI DIP IC'S 100 for \$1.98 Large mfr dumped 100's of 14, 16, 18 pin barrels. Includes 741, LM-300-8, 702, 567, 555, 555A—but who knows? Wt. 1 lb. 7E3249	BARREL KIT #127 AXIAL ELECTROS 40 for \$1.98 Ass't. capacitors and voltages. Cat. No. 7E3227	BARREL KIT #126 UPRIGHT ELECTROS 40 for \$1.98 1 mil to 30 mil in mixture of voltages. 100% material in good. 7E3226	BARREL KIT #121 MINI SCRS 50 for \$1.98 UNBELIEVABLE! TO-92 plastic SCRS in barrels... 100% material. Includes all voltages up thru 200 pvt. 7E3235	BARREL KIT #117 OPTICAL FIBERS 20 mil. 200-FT. \$1.98 Fiber optic factory bank... 100% material. High quality, most commonly used size (20-mil). CLEAR. 7E3204	BARREL KIT #115 MOLEX SOCKETS 100 for \$1.98 100% good. Cat. No. 7E3146
BARREL KIT #112 MICRO MINI LEDS 40 for \$1.98 All the tiny LEDs, axial, upright of Monsanto, Litron, variety of colors. Yield 80% or better. 7E3128	BARREL KIT #109 TERMINAL STRIPS 100 for \$1.98 Wide ass't. of terminal strip connectors, from 1 contact up. Strip manufacturers barrel dump is your gain. Wt. 1 lb. Cat. No. 7E3136	BARREL KIT #108 TO-5 PLASTIC TRANSISTORS 40 for \$1.98 Includes: PNP, NPN, 2N-2638, 2N161, 2N5000 series, etc. Untested. Cat. No. 7E3101	BARREL KIT #104 SLIDE VOLUME CONTROLS 10 for \$1.98 Cat. No. 7E1007	BARREL KIT #101 RESISTOR SPECIAL 200 for \$1.98 Includes: 1/2, 1, 2, 5, 10, 20, 50, 100, 200, 500, 1000, 100% good. 7E3054	BARREL KIT #99 PHOTO ELECTRIC CELLS 10 for \$1.98 Ass't. GE types, CDS types. Mixed by factory. Big job for use in separate. 100% good. Cat. No. 7E1052	BARREL KIT #93 HALF WATTERS 200 for \$1.98 Resistor factory tried to tool us by making 100's, color-coded resistors in barrel. But value is there. & on 7E3048. Untested.
BARREL #91 SILVER MICAS 100 for \$1.98 Axial, red case, variety of physical sizes & values. Cat. No. 7E1018	BARREL KIT #88 LITRONICS LED READOUTS 10 for \$1.98 Hobby... 100% good. Cat. No. 7E2861	BARREL KIT #87 NATIONAL IC BONANZA 100 for \$1.98 Types: 7400, 7410, 7411, 7412, 8825, 882				

7400N TTL

SN7400N	18	SN7400N	25	SN7400N	100
SN7401N	16	SN7401N	22	SN7401N	99
SN7402N	31	SN7402N	45	SN7401N	99
SN7403N	16	SN7403N	39	SN7401N	99
SN7404N	18	SN7404N	37	SN7401N	99
SN7405N	24	SN7405N	32	SN7401N	99
SN7406N	20	SN7406N	30	SN7401N	99
SN7407N	20	SN7407N	32	SN7401N	99
SN7408N	20	SN7408N	32	SN7401N	99
SN7409N	20	SN7409N	32	SN7401N	99
SN7410N	20	SN7410N	32	SN7401N	99
SN7411N	20	SN7411N	32	SN7401N	99
SN7412N	33	SN7412N	39	SN7401N	99
SN7413N	45	SN7413N	49	SN7401N	99
SN7414N	40	SN7414N	44	SN7401N	99
SN7415N	35	SN7415N	39	SN7401N	99
SN7416N	35	SN7416N	39	SN7401N	99
SN7417N	35	SN7417N	39	SN7401N	99
SN7418N	35	SN7418N	39	SN7401N	99
SN7419N	35	SN7419N	39	SN7401N	99
SN7420N	35	SN7420N	39	SN7401N	99
SN7421N	35	SN7421N	39	SN7401N	99
SN7422N	35	SN7422N	39	SN7401N	99
SN7423N	35	SN7423N	39	SN7401N	99
SN7424N	35	SN7424N	39	SN7401N	99
SN7425N	35	SN7425N	39	SN7401N	99
SN7426N	35	SN7426N	39	SN7401N	99
SN7427N	35	SN7427N	39	SN7401N	99
SN7428N	35	SN7428N	39	SN7401N	99
SN7429N	35	SN7429N	39	SN7401N	99
SN7430N	35	SN7430N	39	SN7401N	99
SN7431N	35	SN7431N	39	SN7401N	99
SN7432N	35	SN7432N	39	SN7401N	99
SN7433N	35	SN7433N	39	SN7401N	99
SN7434N	35	SN7434N	39	SN7401N	99
SN7435N	35	SN7435N	39	SN7401N	99
SN7436N	35	SN7436N	39	SN7401N	99
SN7437N	35	SN7437N	39	SN7401N	99
SN7438N	35	SN7438N	39	SN7401N	99
SN7439N	35	SN7439N	39	SN7401N	99
SN7440N	35	SN7440N	39	SN7401N	99
SN7441N	35	SN7441N	39	SN7401N	99
SN7442N	35	SN7442N	39	SN7401N	99
SN7443N	35	SN7443N	39	SN7401N	99
SN7444N	35	SN7444N	39	SN7401N	99
SN7445N	35	SN7445N	39	SN7401N	99
SN7446N	35	SN7446N	39	SN7401N	99
SN7447N	35	SN7447N	39	SN7401N	99
SN7448N	35	SN7448N	39	SN7401N	99
SN7449N	35	SN7449N	39	SN7401N	99
SN7450N	35	SN7450N	39	SN7401N	99
SN7451N	35	SN7451N	39	SN7401N	99
SN7452N	35	SN7452N	39	SN7401N	99
SN7453N	35	SN7453N	39	SN7401N	99
SN7454N	35	SN7454N	39	SN7401N	99

MANY OTHERS AVAILABLE ON REQUEST
20% Discount for 1000 Combined 7400's

CMOS

CD4000	25	CD4000	25	CD4000	25
CD4001	25	CD4001	25	CD4001	25
CD4002	25	CD4002	25	CD4002	25
CD4003	25	CD4003	25	CD4003	25
CD4004	25	CD4004	25	CD4004	25
CD4005	25	CD4005	25	CD4005	25
CD4006	25	CD4006	25	CD4006	25
CD4007	25	CD4007	25	CD4007	25
CD4008	25	CD4008	25	CD4008	25
CD4009	25	CD4009	25	CD4009	25
CD4010	25	CD4010	25	CD4010	25
CD4011	25	CD4011	25	CD4011	25
CD4012	25	CD4012	25	CD4012	25
CD4013	25	CD4013	25	CD4013	25
CD4014	25	CD4014	25	CD4014	25
CD4015	25	CD4015	25	CD4015	25
CD4016	25	CD4016	25	CD4016	25
CD4017	25	CD4017	25	CD4017	25
CD4018	25	CD4018	25	CD4018	25
CD4019	25	CD4019	25	CD4019	25
CD4020	25	CD4020	25	CD4020	25
CD4021	25	CD4021	25	CD4021	25
CD4022	25	CD4022	25	CD4022	25
CD4023	25	CD4023	25	CD4023	25
CD4024	25	CD4024	25	CD4024	25
CD4025	25	CD4025	25	CD4025	25
CD4026	25	CD4026	25	CD4026	25
CD4027	25	CD4027	25	CD4027	25
CD4028	25	CD4028	25	CD4028	25
CD4029	25	CD4029	25	CD4029	25
CD4030	25	CD4030	25	CD4030	25

LINEAR

LM309	30	LM309	30	LM309	30
LM309A	30	LM309A	30	LM309A	30
LM309B	30	LM309B	30	LM309B	30
LM309C	30	LM309C	30	LM309C	30
LM309D	30	LM309D	30	LM309D	30
LM309E	30	LM309E	30	LM309E	30
LM309F	30	LM309F	30	LM309F	30
LM309G	30	LM309G	30	LM309G	30
LM309H	30	LM309H	30	LM309H	30
LM309I	30	LM309I	30	LM309I	30
LM309J	30	LM309J	30	LM309J	30
LM309K	30	LM309K	30	LM309K	30
LM309L	30	LM309L	30	LM309L	30
LM309M	30	LM309M	30	LM309M	30
LM309N	30	LM309N	30	LM309N	30
LM309O	30	LM309O	30	LM309O	30
LM309P	30	LM309P	30	LM309P	30
LM309Q	30	LM309Q	30	LM309Q	30
LM309R	30	LM309R	30	LM309R	30
LM309S	30	LM309S	30	LM309S	30
LM309T	30	LM309T	30	LM309T	30
LM309U	30	LM309U	30	LM309U	30
LM309V	30	LM309V	30	LM309V	30
LM309W	30	LM309W	30	LM309W	30
LM309X	30	LM309X	30	LM309X	30
LM309Y	30	LM309Y	30	LM309Y	30
LM309Z	30	LM309Z	30	LM309Z	30

74LS00 TTL

74LS00	25	74LS00	25	74LS00	25
74LS01	25	74LS01	25	74LS01	25
74LS02	25	74LS02	25	74LS02	25
74LS03	25	74LS03	25	74LS03	25
74LS04	25	74LS04	25	74LS04	25
74LS05	25	74LS05	25	74LS05	25
74LS06	25	74LS06	25	74LS06	25
74LS07	25	74LS07	25	74LS07	25
74LS08	25	74LS08	25	74LS08	25
74LS09	25	74LS09	25	74LS09	25
74LS10	25	74LS10	25	74LS10	25
74LS11	25	74LS11	25	74LS11	25
74LS12	25	74LS12	25	74LS12	25
74LS13	25	74LS13	25	74LS13	25
74LS14	25	74LS14	25	74LS14	25
74LS15	25	74LS15	25	74LS15	25
74LS16	25	74LS16	25	74LS16	25
74LS17	25	74LS17	25	74LS17	25
74LS18	25	74LS18	25	74LS18	25
74LS19	25	74LS19	25	74LS19	25
74LS20	25	74LS20	25	74LS20	25
74LS21	25	74LS21	25	74LS21	25
74LS22	25	74LS22	25	74LS22	25
74LS23	25	74LS23	25	74LS23	25
74LS24	25	74LS24	25	74LS24	25
74LS25	25	74LS25	25	74LS25	25
74LS26	25	74LS26	25	74LS26	25
74LS27	25	74LS27	25	74LS27	25
74LS28	25	74LS28	25	74LS28	25
74LS29	25	74LS29	25	74LS29	25
74LS30	25	74LS30	25	74LS30	25
74LS31	25	74LS31	25	74LS31	25
74LS32	25	74LS32	25	74LS32	25
74LS33	25	74LS33	25	74LS33	25
74LS34	25	74LS34	25	74LS34	25
74LS35	25	74LS35	25	74LS35	25
74LS36	25	74LS36	25	74LS36	25
74LS37	25	74LS37	25	74LS37	25
74LS38	25	74LS38	25	74LS38	25
74LS39	25	74LS39	25	74LS39	25
74LS40	25	74LS40	25	74LS40	25

CLOCK CHIPS

UM5309	8 Digi	UM5309	8 Digi	UM5309	8 Digi
UM5310	8 Digi	UM5310	8 Digi	UM5310	8 Digi
UM5311	8 Digi	UM5311	8 Digi	UM5311	8 Digi
UM5312	8 Digi	UM5312	8 Digi	UM5312	8 Digi
UM5313	8 Digi	UM5313	8 Digi	UM5313	8 Digi
UM5314	8 Digi	UM5314	8 Digi	UM5314	8 Digi
UM5315	8 Digi	UM5315	8 Digi	UM5315	8 Digi
UM5316	8 Digi	UM5316	8 Digi	UM5316	8 Digi
UM5317	8 Digi	UM5317	8 Digi	UM5317	8 Digi
UM5318	8 Digi	UM5318	8 Digi	UM5318	8 Digi
UM5319	8 Digi	UM5319	8 Digi	UM5319	8 Digi
UM5320	8 Digi	UM5320	8 Digi	UM5320	8 Digi
UM5321	8 Digi	UM5321	8 Digi	UM5321	8 Digi
UM5322	8 Digi	UM5322	8 Digi	UM5322	8 Digi
UM5323	8 Digi	UM5323	8 Digi	UM5323	8 Digi
UM5324	8 Digi	UM5324	8 Digi	UM5324	8 Digi
UM5325	8 Digi	UM5325	8 Digi	UM5325	8 Digi
UM5326	8 Digi	UM5326	8 Digi	UM5326	8 Digi
UM5327	8 Digi	UM5327	8 Digi	UM5327	8 Digi
UM5328	8 Digi	UM5328	8 Digi	UM5328	8 Digi
UM5329	8 Digi	UM5329	8 Digi	UM5329	8 Digi
UM5330	8 Digi	UM5330	8 Digi	UM5330	8 Digi
UM5331	8 Digi	UM5331	8 Digi	UM5331	8 Digi
UM5332	8 Digi	UM5332	8 Digi	UM5332	8 Digi
UM5333	8 Digi	UM5333	8 Digi	UM5333	8 Digi
UM5334	8 Digi	UM5334	8 Digi	UM5334	8 Digi
UM5335	8 Digi	UM5335	8 Digi	UM5335	8 Digi
UM5336	8 Digi	UM5336	8 Digi	UM5336	8 Digi
UM5337	8 Digi	UM5337	8 Digi	UM5337	8 Digi
UM5338	8 Digi	UM5338	8 Digi	UM5338	8 Digi
UM5339	8 Digi	UM5339	8 Digi	UM5339	8 Digi
UM5340	8 Digi	UM5340	8 Digi	UM5340	8 Digi

DATA HANDBOOKS


7400	Pin out & Description of 7400 Series IC's	\$2.95
CMOS	Pin out & Description of 4000 Series IC's	\$2.95
Linear	Pin out & Description of Linear IC's	\$2.95
ALL THREE HANDBOOKS		\$8.95

Timeband by FARRCHILD


— Watches —

Men's & Ladies


- Solid State
- Displays hour, minute, second, month & day
- Snap-out battery replacement
- Free set of replacement batteries
- Choose LED or LCD styles
- One year factory warranty



1201 Black Bracelet LED \$19.95



1201 White w/strap \$29.95
1202 Yellow w/strap \$34.95



1201 White w/bracelet \$29.95
1202 Yellow w/bracelet \$34.95

CHANNEL F

Freeze Action • Speed Option • Automatic time and scorekeeping • Battery-free AC operation • Dual controls with 8-way action • Built-in Pro Hockey and Tennis games • Easy hook-up on any B/W or Color TV • Factory warranty

\$159.95

Channel F — additional cartridges — \$19.95 ea.

- #8112 - Desert Fox/Shooting Gallery
- #8114 - Spillfire (1 or 2 players)
- #8111 - Tac-Toe/Toe-Shooting Gallery/Doodle-Quadra-Doodle
- #8113 - Blackjack (1 or 2 players)
- #8115 - Space War

DISCRETE LEDS

TYPE	POLARITY	HT	TYPE	POLARITY	HT
MAN 1	Common Anode	200	MAN 1600	Common Cathode	200
MAN 2	Common Anode	200	MAN 1610	Common Cathode	200
MAN 3	Common Anode	200	MAN 1620	Common Cathode	200
MAN 4	Common Anode	200	MAN 1630	Common Cathode	200
MAN 5	Common Anode	200	MAN 1640	Common Cathode	200
MAN 6	Common Anode	200	MAN 1650	Common Cathode	200
MAN 7	Common Anode	200	MAN 1660	Common Cathode	200
MAN 8	Common Anode	200	MAN 1670	Common Cathode	200
MAN 9	Common Anode	200	MAN 1680	Common Cathode	200
MAN 10					

REAL ESTATE

BIG...FREE...CATALOG! Over 2,500 top values coast to coast! UNITED FARM AGENCY, 612-EP, West 47th, Kansas City, MO 64112.

RUBBER STAMPS

RUBBER STAMPS, BUSINESS CARDS. Many new products. Catalog, Jackson's, Dept. K, Brownsville Rd., Mt. Vernon, Ill. 62864.

DO-IT-YOURSELF

MODULAR TELEPHONES now available. Sets and components, compatible with Western Electric concept. Catalog 50 cents. Box 1147W, San Diego, California 92112.

MODE 8 — 8 channels TTL on ANY scope plus triggered memory logic probe. Kit \$52.50; plans \$5.00. BASIX, 1067 Seneca, Bethlehem, PA 18015.

TAPE-SLIDE SYNCHRONIZER, lap-dissolve, multiprojector audiovisual plans \$8.50. Free Catalog. Millers, 1896 Maywood, South Euclid, OH 44121.

BUILD ELECTRONICS DEVICES in your home. Get started in your spare time. Big Profits — Experience not necessary. Write for free literature telling how. Electronics Develop Lab., Dept. D, Box 1535, Pinellas Park, Fla. 33565.

PLANS AND KITS

POCKET COLOR/BAR GENERATOR kit, 16 patterns, \$49.95. Plans, \$4.95 Workshop, Box 393PC, Bethpage, New York 11714.

FIVE OCTAVE Touch Sensitive Electronic PIANO Kit. Components \$245 airmail U.S.A., Canada. Ciel Products, 31 Mountfield Road, Bramhall, Cheshire, England.

CONVERTER KIT: Two meters to AM Broadcast, \$8.95 ppd. Send stamp for flyer. Electronics Hobbies, 3421 Hawthorne Rd., Gainesville, FL 32601.


FORTY CHANNEL CONVERSION KIT fits all 23 channel AM rigs. 40 Plus, 11301 Melody 308, Northglenn, Colorado 80234.

AMAZING ELECTRONIC PRODUCTS

LASERS SUPER POWERED. RIFLE PISTOL. POCKET SEE IN DARK. PYRO TECHNICAL DE BUGGING. UNCRAMBLERS. GUN TESTS. STUNWAND TV DISRUPTOR. ENERGY PRODUCING. SCIENTIFIC DETECTION. ELECTRIFYING. CHEMICAL. ULTRASONIC. CD XERO AUTO AND MECH DEVICES. HUNDREDS MORE — ALL NEW PLUS INTO UNLIMITED PARTS SERVICE

INFORMATION unlimited
Catalog \$1
Box 626 Lord Jeffery PZ • Amherst, N.H. 03031

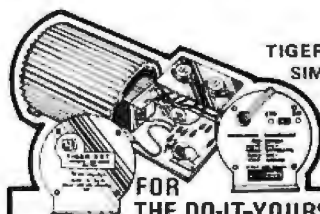MIXERS — Preamps — Speakers. Top Quality Kits — Plans — Parts. Send 25 cents for catalog. Audio Design & Engineering Co., P.O. Box 154, Lee, Mass. 01238. (413) 243-1333.



TIGER SST
SIMPLI-KIT

FOR THE DO-IT-YOURSELF
NOW! a high quality CD Electronic Ignition System in kit form.

Contains all components and solder to build complete Solid-State Electronic CD Ignition System for your car. Assembly requires less than 3 hours.

- Increases MPG 15%
- Increases horsepower 15%
- Eliminates 4 of 5 tune-ups
- Instant starting, any weather
- Plugs and Points last 50,000 miles
- Dual system switch

Fits only 12 volt neg. ground Only \$21.95 postpaid

Star Corporation

P.O. Box 1727 Grand Junction, Colorado 81501

FREE KIT Catalog contains Test and Experimenters Equipment. Dage Scientific Instruments, Box 1054P, Livermore, CA 94550.

WERSI KITS

Organs, Pianos, Strings
Rhythms, PA Systems
104-page catalog \$2
WERSI electronics, Inc.
Dept. A2, Box 5318,
Lancaster, PA 17601

EMPLOYMENT OPPORTUNITIES

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240E, Northport, New York 11768.

OVERSEAS JOBS — FANTASTIC PAY! All Occupations. Computerized Reports — \$2.00. TRANSWORLD, International Airport, Box 90802-N, Los Angeles, Calif. 90009.

ROCKY MOUNTAIN JOBS!! Colorado — Idaho — Montana — Wyoming!! Free details. Intermountain-S7, 300 Dundee, Boise, Idaho 83708.

MISCELLANEOUS

WINEMAKERS. Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

1977 COMMUNICATIONS HANDBOOK

Everything you want to know—need to know—about CB, Ham Radio, SW Listening, Police-Fire Monitoring, Marine Radio. Features, specifications, latest prices and photographs of equipment on the market are at your fingertips. Order your copy from Communications Handbook, Consumer Service Division, 595 Broadway, New York, N.Y. 10012. Enclose \$2.50 (\$1.95 plus 55c for postage and handling). Outside U.S.A. \$3.00, postpaid. Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax. Postage and handling charges non-taxable.

AUTO BURGLAR ALARM KIT

KIT #ALR-1
\$9.95

#ALR-1WT
WIRED &
TESTED
\$19.95

EASY TO ASSEMBLE AND EASY TO INSTALL. ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR PDS & GROUNDING SWITCHES OR SENSORS WILL PULSE HORN RELAY AT 1/2 RATE OR DRIVE BUREN KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY. RESISTS FALSE ALARMS. A PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.

JUMBO DIGIT CLOCK KIT
A complete Kit (less Cabinet) featuring six 5" digits, MM5314 IC, 12-24 Hr. Integ. 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts. (Ideal Fit in Cabinet II) Kit # 5314-5
WITH PC Board \$19.95 ea 2/38.

CABINET I
3"H, 6"W, 5"D
CABINET II
2"H, 5"W, 4"D

NEW LSI TECHNOLOGY FREQUENCY COUNTER KIT 8 LARGE .4" RED LED DIGITS

ONLY 8 IC's! • XTAL TIME BASE
A truly "State of the Art" counter using quality components throughout.
KIT INCLUDES: DETAILED INSTRUCTIONS, XTAL, TOP QUALITY FIBERGLASS DOUBLE SIDED PC BOARD, IC'S WITH SOCKETS AND ALL PARTS LESS POWER SUPPLY AND CABINET.
50 MHZ COUNTER KIT #FC-50 \$89.95
5 VOLT REGULATED 1 AMP POWER SUPPLY KIT #PS-02 \$9.95
350 MHZ PRESCALER KIT #PSL-350 \$23.95
650 MHZ PRESCALER KIT #PSL-650 \$29.95
CABINET & MOUNTING HARDWARE #CAB-III \$19.95
[CABINET WILL HOUSE #FC-50, #PS-02, AND A PRESCALER]

DELIVERIES TO START IN MAY, 1977

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME

Orders Under \$15 Add \$1.00 Handling
Fla. Res. Please Add 4% Sales Tax

OPTOELECTRONICS, INC.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921 2056

WE PAY ALL SHIPPING IN CONTINENTAL USA — OTHERS ADD 5% [10% FOR AIRMAIL]

CIRCLE NO 35 ON FREE INFORMATION CARD

MOBILE LED CLOCK

12 OR 24-HOUR OPERATION MODEL #2001
12 VOLT AC or DC POWERED
SIX LARGE 4" DIGITS

• MOUNTING BRACKET INCLUDED
KIT #2001
COMPLETE KIT (Less 9V Battery) 29.95 ea 2 OR MORE \$27.95 ea
ASSEMBLED UNITS
ORDER #2001 WT. WIRED & TESTED (LESS 9V BATTERY) \$39.95 3 OR MORE \$37.95 ea
WORLD FOR 12 HR. OP. IF NOT SPECIFIED OTHERWISE

2102Z PRIME .450 MS LOW POWER
1-24 \$1.95
25-99 \$1.75
100-199 \$1.50
200-499 \$1.45
Over 500 \$1.00

OP AMPS
3/8100
301 TO-5
708 TO-5
708 TO-5
741 DIP
741 M-DIP
741 TO-5
741 TO-5

PROM
1702 E Prom \$8.95
5203 E Prom \$8.95

DIODES
IN 4002 1A, 100 PIV 12/61 00
IN 4005 1A, 600 PIV 11/61 00
IN 4007 1A, 1000 PIV 10/61 00
RECTIFIER 2.5A, 1000 PIV 4/61 00
IN 914 SIL. SIGNAL 20/61 00
IN 4148 SIL. SIGNAL 20/61 00
DYAC 28V. 4/61 00

JUMBO DIGIT CONVERSION KIT \$9.95 ea.
Convert small digit LED clock to large 5" displays. Kit includes 6" 5" LED's, Multiplex PC Board & easy hook-up info.
Kit # JD 1CC for common Cathode
Kit # JD 1CA for common Anode

DISCRETE LED'S
JUMBO RED
10 FOR \$1.00
100 FOR \$9.50

DIGITAL CLOCK IC'S
MM 5312 \$ 4.95
MM 5313 3.95
MM 5375AB 3.95
CT 7001 7.95
CT 7002 13.95
MM 5368 2.50

PC TRIM POTS
25K 6 \$1.00
47K 6 \$1.00
5K 7K 6 \$1.00
SPECTROL 10K 10 TURN 95c
10K 10 TURN 4/63 00

PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.
Black, White or Clear Cover

60 HZ.

XTAL TIME BASE
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC.
1"x2" PC Board
Power Req: 5-15V (2.5 MA. TYP.)
Easy 3 wire hookup
Accuracy ± 2PPM
WTB-1 (Adjustable)
Complete Kit \$4.95 ea
Wir & Cal \$9.95

VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

• VARIABLE FROM 4 to 14V
• SHORT CIRCUIT PROOF
• 723 IC REGULATOR
• 2N3055 PASS TRANSISTOR
• CURRENT LIMITING AT 1 amp
KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (LESS TRANSFORMER) KIT #PS-01 \$8.95
TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 15V with #PS-01. \$3.50

RED OR GREY PLEXIGLAS 3"x6"x1/8" FOR DIGITAL BEZELS

95¢ ea 4/63

Fairchild Super Digit FND-359

4" Char. Ht. 7 segment LED RED Com. Cath. Direct pin replacement for popular FND-70.
95¢ ea. 10/\$8.50
100/\$79.00

MOLEX PINS

Form Inexpensive Sockets
100 for \$1.25
Real of 1000 - \$9.50

25 AMP BRIDGE

\$1.95 ea.
3/\$5.00
100 PIV

NYLON WIRE TIES

8" TIE-WRAP 100/\$1.95
4" TIE-WRAP 100/\$1.75

IC SOCKETS

PINS 1-24 25 100
8 1 25 1 22 6 20
14 25 22 20
18 28 25 23
18 31 28 26
24 50 45 40
28 60 55 50
40 75 70 66


SOLVE YOUR TEST CONNECTION PROBLEMS WITH EZ-HOOK

E-Z Hooks have been designed and field tested throughout the industry to save time and money in commercial electronic production and servicing. The spring-loaded hook attaches firmly, yet so gently it will not damage component — frees hands while testing. Durable construction and fully insulated to a single contact point assuring true readings. Meets exacting laboratory and space age computer technology requirements. AVAILABLE IN 10 RETMA COLORS: Red, black, blue, green, orange, yellow, white, violet, brown or gray.


Jumper with X-100W Mini Hooks			
Order No.	Length	Price	
204-12W*	12"	\$1.60	
204-24W*	24"	1.60	



Jumper with X-100W Mini Hook to Stacking Banana Plug			
Order No.	Length	Price	
201W*	32"	\$1.40	

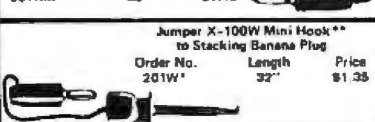


Jumper with X-100W Mini Hooks			
Order No.	Length	Price	
204X-12*	12"	\$1.70	
204X-24*	24"	1.70	

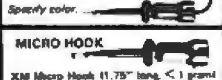

MICRO HOOK			
Order No.	Length	Price	
204X-12*	12"	\$1.70	
204X-24*	24"	1.70	



EXTRA LONG MINI HOOK			
Order No.	Length	Price	
204XL-1-12	12"	\$2.80	
204XL-1-24	24"	2.80	

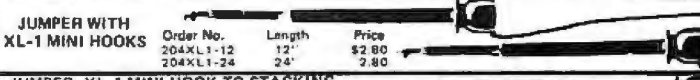

JUMPER WITH XL-1 MINI HOOKS			
Order No.	Length	Price	
204XL-1-12	12"	\$2.80	
204XL-1-24	24"	2.80	



E-Z-HOOK


ORDER YOUR XM-S MICRO HOOK SET TODAY! (Includes 1 ea. red, black, blue, green, orange, yellow, white, brown, violet and gray Micro Hook). At this low price you can afford more than one set.
COMPLETE SET (10) MICRO HOOKS — \$7.95



SOCKETS & BUS STRIPS

Plug-in, wire, test, modify or expand without patch cords or solder. Snap together to form breadboard needed.

PN/Description	Terminals	Price
QT69S Socket	118	\$12.50
QT56B Bus	20	2.60
QT47S Socket	94	10.00
QT47B Bus	18	2.25
QT35S Socket	70	8.50
QT35B Bus	12	2.00
QT18S Socket	36	4.75
QT12S Socket	24	3.75
QT8S Socket	16	3.25
QT7S Socket	14	3.00

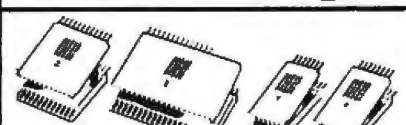

PROTO-CLIP

For power-on/hands off signal tracing. Bring IC leads up from PC board surface for fast troubleshooting.

PC14	14-pin	\$ 4.50
PC16	16-pin	4.75
PC24	24-pin	8.50
PC40	40-pin	13.75

CARBON FILM RESISTORS (5%)

Only in Multiples of 100 pcs per value (ohms)
1/4W ... \$1.89 per 100
1/2W ... \$1.79 per 100

10	100	1.0K	10K	100K	1.0M
11	110	1.1K	11K	110K	1.1M
12	120	1.2K	12K	120K	1.2M
13	130	1.3K	13K	130K	1.3M
14	140	1.4K	14K	140K	1.4M
15	150	1.5K	15K	150K	1.5M
16	160	1.6K	16K	160K	1.6M
17	170	1.7K	17K	170K	1.7M
18	180	1.8K	18K	180K	1.8M
19	190	1.9K	19K	190K	1.9M
20	200	2.0K	20K	200K	2.0M
21	210	2.1K	21K	210K	2.1M
22	220	2.2K	22K	220K	2.2M
23	230	2.3K	23K	230K	2.3M
24	240	2.4K	24K	240K	2.4M
25	250	2.5K	25K	250K	2.5M
26	260	2.6K	26K	260K	2.6M
27	270	2.7K	27K	270K	2.7M
28	280	2.8K	28K	280K	2.8M
29	290	2.9K	29K	290K	2.9M
30	300	3.0K	30K	300K	3.0M
31	310	3.1K	31K	310K	3.1M
32	320	3.2K	32K	320K	3.2M
33	330	3.3K	33K	330K	3.3M
34	340	3.4K	34K	340K	3.4M
35	350	3.5K	35K	350K	3.5M
36	360	3.6K	36K	360K	3.6M
37	370	3.7K	37K	370K	3.7M
38	380	3.8K	38K	380K	3.8M
39	390	3.9K	39K	390K	3.9M
40	400	4.0K	40K	400K	4.0M
41	410	4.1K	41K	410K	4.1M
42	420	4.2K	42K	420K	4.2M
43	430	4.3K	43K	430K	4.3M
44	440	4.4K	44K	440K	4.4M
45	450	4.5K	45K	450K	4.5M
46	460	4.6K	46K	460K	4.6M
47	470	4.7K	47K	470K	4.7M
48	480	4.8K	48K	480K	4.8M
49	490	4.9K	49K	490K	4.9M
50	500	5.0K	50K	500K	5.0M
51	510	5.1K	51K	510K	5.1M
52	520	5.2K	52K	520K	5.2M
53	530	5.3K	53K	530K	5.3M
54	540	5.4K	54K	540K	5.4M
55	550	5.5K	55K	550K	5.5M
56	560	5.6K	56K	560K	5.6M
57	570	5.7K	57K	570K	5.7M
58	580	5.8K	58K	580K	5.8M
59	590	5.9K	59K	590K	5.9M
60	600	6.0K	60K	600K	6.0M
61	610	6.1K	61K	610K	6.1M
62	620	6.2K	62K	620K	6.2M
63	630	6.3K	63K	630K	6.3M
64	640	6.4K	64K	640K	6.4M
65	650	6.5K	65K	650K	6.5M
66	660	6.6K	66K	660K	6.6M
67	670	6.7K	67K	670K	6.7M
68	680	6.8K	68K	680K	6.8M
69	690	6.9K	69K	690K	6.9M
70	700	7.0K	70K	700K	7.0M
71	710	7.1K	71K	710K	7.1M
72	720	7.2K	72K	720K	7.2M
73	730	7.3K	73K	730K	7.3M
74	740	7.4K	74K	740K	7.4M
75	750	7.5K	75K	750K	7.5M
76	760	7.6K	76K	760K	7.6M
77	770	7.7K	77K	770K	7.7M
78	780	7.8K	78K	780K	7.8M
79	790	7.9K	79K	790K	7.9M
80	800	8.0K	80K	800K	8.0M
81	810	8.1K	81K	810K	8.1M
82	820	8.2K	82K	820K	8.2M
83	830	8.3K	83K	830K	8.3M
84	840	8.4K	84K	840K	8.4M
85	850	8.5K	85K	850K	8.5M
86	860	8.6K	86K	860K	8.6M
87	870	8.7K	87K	870K	8.7M
88	880	8.8K	88K	880K	8.8M
89	890	8.9K	89K	890K	8.9M
90	900	9.0K	90K	900K	9.0M
91	910	9.1K	91K	910K	9.1M
92	920	9.2K	92K	920K	9.2M
93	930	9.3K	93K	930K	9.3M
94	940	9.4K	94K	940K	9.4M
95	950	9.5K	95K	950K	9.5M
96	960	9.6K	96K	960K	9.6M
97	970	9.7K	97K	970K	9.7M
98	980	9.8K	98K	980K	9.8M
99	990	9.9K	99K	990K	9.9M
100	1000	10.0K	100K	1000K	10.0M

RESISTOR KITS

5% CARBON FILM RESISTORS



COMPLETE WITH STORAGE BIN

1/4 WATT KIT

42 Different Values

(68Ω to 4.7 MΩ)

20 Each Value

1/2 WATT KIT

42 Different Values

(68Ω to 4.7 MΩ)

20 Each Value

1/4W — \$24.90 PER KIT

1/2W — \$25.90 PER KIT

RESISTOR ASSORTMENTS

Each assortment contains 5 pcs each of 10 different values

Values included are shown in (Ohms)

1/4W 5% (50 pcs total) ... \$1.75 / 1/2W 5% (50 pcs total) ... \$1.85

Ass. 1: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56 ohm

Ass. 2: 68, 82, 100, 120, 150, 180, 220, 270, 330, 390 ohm

Ass. 3: 470, 560, 680, 820 ohm, 1K, 1.2K, 1.5K, 1.8K, 2.2K, 2.7K

Ass. 4: 3.3K, 3.9K, 4.7K, 5.6K, 6.8K, 8.2K, 10K, 12K, 15K, 18K

Ass. 5: 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K

Ass. 6: 1M, 1.2M, 1.5M, 1.8M, 2.2M, 2.7M, 3.3M, 3.9M, 4.7M, 5.6M, 6.8M, 8.2M, 10M, 12M, 15M, 18M, 22M, 27M, 33M, 39M, 47M, 56M, 68M, 82M, 100M, 120M, 150M, 180M, 220M, 270M, 330M, 390M, 470M, 560M, 680M, 820M, 1000M

Ass. 7: 1M, 1.2M, 1.5M, 1.8M, 2.2M, 2.7M, 3.3M, 3.9M, 4.7M, 5.6M, 6.8M, 8.2M, 10M, 12M, 15M, 18M, 22M, 27M, 33M, 39M, 47M, 56M, 68M, 82M, 100M, 120M, 150M, 180M, 220M, 270M, 330M, 390M, 470M, 560M, 680M, 820M, 1000M

Ass. 8: (All seven assortments above)

1/4W 5% 350 pcs total \$10.95 1/2W 5% 350 pcs total \$11.55

PROTO-BOARD UNITS

The Solderless Breadboarding System That Saves You Hours On Every Project

Like our QT system, Proto-Board units let you assemble, test and modify circuits literally as fast as you can think. Rugged, heavy duty construction for use in engineering laboratories, in educational institutions, on production lines, etc.

PROTO-BOARD 8 KIT—Complete List Price \$15.95
One preassembled QT-47S socket, two preassembled QT-47B bus strips, four 5-way binding posts and all hardware.

PROTO-BOARD 100 KIT—Complete List Price \$19.95
Two preassembled QT-38S sockets, one preassembled QT-38B bus strip, two 5-way binding posts and all hardware.

PROTO-BOARD 101—Complete List Price \$28.95
Fully assembled breadboard contains two QT-38S sockets and four QT-38B bus strips mounted on metal ground/base plate with non-marring feet. Excellent for audio and small digital projects.

PROTO-BOARD 102—Complete List Price \$39.95
Fully assembled breadboard contains two QT-47S sockets, three QT-47B bus strips and one QT-38B bus strip. Excellent for intermediate digital needs.

PROTO-BOARD 103—Complete List Price \$59.95
Fully assembled breadboard contains three QT-59S sockets, four QT-59B bus strips, plus four 5-way binding posts. Build calculators, interfaces, networks, etc.

PROTO-BOARD 104—Complete List Price \$79.95
Fully assembled breadboard contains four QT-59S sockets, seven QT-59B bus strips and four 5-way binding posts. Build a CPU, encoder, complex display, etc.

PROTO-BOARD 203—Complete List Price \$75.00
Proto-Board flexibility plus built-in 1% regulated 5 VDC, 1A supply, 2250 All the features of the PB-203 plus additional power supply flexibility: provides 1% regulated 5 VDC supply, regulated separate +16 VDC and -15 VDC 0.5A supplies, each with internally and independently adjustable output voltage; ripple and noise of + and -15V supplies, 10 mV at 0.25A.

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

PROTO-BOARD 203A—Complete List Price \$120.00

S. D. SALES CO.

P.O. BOX 28810 - D
DALLAS, TEXAS 75228

JUMBO LED CAR CLOCK

\$16.95 KIT



**50,000 Satisfied Clock
Kit Customers Can't Be Wrong!**

ALARM OPTION - \$1.50
AC XFMR - \$1.50

The Hottest Selling Kit We Ever Produced!

You requested it! Our first D.C. operated clock kit. Professionally engineered from scratch. Not a makeshift kluge as sold by others.

- Features:
- A. Bowmar Jumbo .5 inch LED array.
 - B. MOSTEK - 50250 - Super Clock Chip
 - C. On board precision crystal time base.
 - D. 12 or 24 hour Real Time Format.
 - E. Perfect for cars, boats, vans, etc.
 - F. P.C. Board and all parts (less case) included.

Specials!

3.579545
MHZ Time
Base Crystal
\$1.25

28 PIN IC
Sockets
3/\$1.00
11,000 MFD
50WVDC
Computer
Grade
Cap - \$3.

60HZ Crystal Time Base \$5.95

2/\$10.

1702A 2K EPROM

We tell it like it is! We could have said these were factory new, but here is the straight scoop. We bought a load of new computer gear that contained a quantity of 1701 A's in sockets. We carefully removed the parts, verified their quality, and are offering them on one heck of a deal. First come, first served. Satisfaction Guaranteed! U. V. Erasable. (2.3 US access time.) NEW PRICE!

\$2.95 each

UP YOUR COMPUTER!

21L02-1 1K LOW POWER 500 NS STATIC RAM
Time is of the essence!

And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02-1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off!

8 for \$12.95

FEATURES:

- A. 60HZ output with accuracy comparable to a digital watch.
 - B. Directly interfaces with all MOS clock chips.
 - C. Super low power consumption (1.5MA typ.)
 - D. Uses latest MOS 17 stage divider IC.
 - E. Eliminates forever the problem of AC line glitches.
 - F. Perfect for cars, boats, campers, or even for portable clocks at ham field days.
 - G. Small size; can be used in existing enclosures.
- Kit includes Crystal, Driver IC, PC board, plus all necessary parts and specs. At last count - over 20,000 sold!

S.D. Sales Exclusive!

\$12.95 S. D. Sales Exclusive! \$12.95

MOS 6 DIGIT UP-DOWN COUNTER

40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYPE), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare output, BCD and seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking, 1MHZ. count input frequency. Very limited quantity!

IC's from XEROX

7400 - 1c
7402 - 3c
7404 - 9c
7406 - 11c
7407 - 11c
7410 - 9c
7415 - 13c
7420 - 9c

7430 - 9c
7440 - 9c
74123 - 32c
74123 - 32c
74151 - 22c
74155 - 22c
7474 - 16c
7475 - 24c
7488 - 16c

7493 - 26c
74121 - 22c
74123 - 32c
74151 - 22c
74155 - 22c
74193 - 35c
8233 - 35c
Intel - 1302 - 45c

1402A-Shift Regulator-50c
MM0025CN - 85c

IC'S REMOVED FROM
PC BOARDS
ALL TESTED:
FULL SPEC.

1000 MFD

Filter Caps
Rated 35 WVDC Up-
right style with PC
leads. Most popular val-
ue for hobbyists. Com-
pare at up to \$1.19 ea.
from franchise type a
electronic parts stores.

4/\$1.00

SLIDE SWITCH Assortment

Our best seller. Includes
miniature and standard
sizes; single and multi-
position units. All new,
first name brand. Try
one package and you'll
reorder more! Special!

12/\$1.00

POWER RESISTOR

15 OHM
25W
BY
CLAROSTAT

75¢ ea.

RESISTOR ASSORTMENT

1/4W 5% & 10% PC
leads. A good mix of
values.

200/\$2.

P.C. LEAD DIODES

1N4148/1N914
100/\$2.00
1N4002 - 1A
100 PIV

40/\$1.

Transistor Grab Bag no. 1

Just received a good
mixed lot of National
TO92 plastic transis-
tors, PNP & NPN, even
a few FET's. 40 to 50%
Yield. Untested. Asst.

500/\$3.

DISC CAP ASSORTMENT

PC leads. At least
10 different val-
ues. Includes:
.001, .01, .06
plus other stan-
dard values.

60/\$1.00

\$9.95 KIT

P.C. Board - \$3.00
AC XFMR - \$1.50
Do not confuse with Non-Alarm
kits sold by our competition!
Eliminate the hassle -
avoid the 5314!

SIX DIGIT ALARM CLOCK KIT

WE MADE A FANTASTIC KIT EVEN BETTER. REDESIGNED TO TAKE ADVANTAGE OF THE LATEST ADVANCES IN I.C. CLOCK TECHNOLOGY. FEATURES: LITRONIX DUAL 1/2" DIS-PLAYS, MOSTEK 50250 SUPER CLOCK CHIP, SINGLE I.C. SEGMENT DRIVER, SCR DIGIT DRIVERS. GREATLY SIMPLIFIED CONSTRUCTION. MORE RELIABLE AND EASIER TO BUILD. KIT INCLUDES ALL NECESSARY PARTS (except case). P.C.B. OR XFMR OPTIONAL. NEW! WITH JUMBO LED READOUTS!

MOTOROLA SCR
2N4443. 8 AMP 400 PIV.
P.C. Leads. \$3/\$1.00

FAIRCHILD - TBA 641
4W. Audio power Amp. Just
out! In special heat sink DIP.
One super audio IC.
\$1.50 with data


AC LINE FILTER
Rated 3 AMPS - 115/230V
50 to 400 HZ.

Noise Proof Your Computer
\$3.00 each

GRAB BAG NUMBER 2
Mixed Motorola TO-18 case met-
al transistors. About 60% yield.
PNP & NPN. Untested. A good
assortment! 100 for \$3.00

PRICES SHOWN SUBJECT
TO CHANGE WITHOUT
NOTICE.

Price Cut! ~~\$15.95~~
\$12.

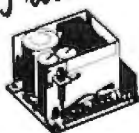

COMPUTER POWER SUPPLY

A very fortunate purchase. One of the best industrial quality REG-ULATED supplies we have seen. High performance, small size. Input is 120VAC 60HZ. Has the following regulated outputs:
-5VDC@800MA, -15VDC@1.25AMP, -25VDC@180MA. Sold at
a fraction of original cost. Do yourself a favor and order NOW.

AMD - 1702A

Factory Prime Units - Brand New - 1.5 Micro-seconds Access Time. - \$4.95 each
10 FOR \$40. HUGE FACTORY DIRECT PURCHASE!

TERMS:

MONEY BACK GUARANTEE.
NO COD's. TEXAS RESIDENTS
ADD 5% SALES TAX. ADD
5% OF ORDER FOR POSTAGE
& HANDLING. ORDERS
UNDER \$10.00 ADD 75c.
FOREIGN ORDERS: U. S.
FUNDS ONLY!

Call your BankAmericard or
Master Charge order in on our
continental United States toll
free Watts:

1-800-527-3460

Texas Residents Call Collect:

214/271-0022

CHEAP DC SUPPLY
Actually an AC adapter for calculators.
5VDC-no load, 6VDC@200MA,
4VDC@375MA

\$2. ea.

S.D. SALES CO.
P.O. BOX 28810 - D
DALLAS, TEXAS 75228

Orders over \$15. - Choose \$1. FREE MERCHANDISE!

AMAZING & HARD-TO-FIND SCIENCE BUYS! ALTERNATE ENERGY SPACE AGE • HOBBIES

SUPER POWER FOR ANY AM RADIO



Antenna assist has pulled in stations up to 1000 miles off! No wires, clips, grounding. Solid state—no elec. batts., tubes.
No. 72,005AV \$19.95 Ppd.
ULTRA SELECT-A-TENNA (OVER 1000* MILES)
No. 72,147AV\$24.95
SUBJ. TO LOCAL COND.

SAVE 50%! 8 x 20 MONOCULAR



Top quality Spy Scope, a \$30 value, now \$14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box.
No. 1568AV ..\$14.95 Ppd.

GIANT MAGNET. LITTLE PRICE!



Tie a line to our over-150 lb.-lift ceramic magnet and haul up treasure from the sea. 4 ceramic magnets, in series, between steel plates. A 1-lb. "giant!"

No. 42,318AV (1 x 1 1/4 x 4 1/4)\$11.95 Ppd.

NASA-CHOSEN FOR APOLLO/SOYUZ



The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses, 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!

No. 1556AV(9 1/2 x 5 1/2); 47.5 oz) \$99.95 Ppd.

MEASURE WIND SPEED ANYWHERE



Hold handy (16 oz.) low cost Anemometer into the wind, quickly read wind speed on its big dial—from 5 to 70 mph. Acc. to ±3% of full scale (2.1 mph); no batts., adjustments, recalibration req! (7 1/2" HIGH)
No. 42,428AV ..\$19.95 Ppd.

WORLD'S LARGEST SOLAR CELL...



...the most powerful silicon, cheapest dollar per watt! 4" dia. giant can put out 1 full watt, over 2 amps of current at .45v. Rated 100mW/Cm² light intens. at .45v.

No. 42,314AV...(TAB LEADS).....\$29.95 Ppd.
No. 42,270AV...(1 AMP 1/2W 3" DIA.).....\$17.95 Ppd.



DELUX HI-TEMP SOLAR FURNACE

Oversized Fresnel lens enables unit you screw together to attain temperatures over 2000°F at prime focus! Use to temper small parts; fire enamel on jewelry, more! 6 parts easily assembled w/instrs.

No. 80,257AV(8 1/2 lb, 34" hi)\$59.95 Ppd

ELECTRONIC COUNT-DOWN STOPWATCH



Hand-held 5-oz digital stopwatch counts up, down, sounds alarm—w/full range LED display (9 hrs., 59 mins., 59 secs.) Has start/stop (time-out)/reset buttons. Accurate alarm clock! 3 AA batts.

No. 1692AV (2.8 x 4.3 x 1 1/4).....\$49.95 Ppd.

ELECTRONIC SOUND COLLECTOR



Tune in a whisper at 20 ft., normal conversations up to 100 ft., birdcalls & high freq. sounds at almost 200 ft. Nearly twice as far over water! Check on baby, birds! 18" refl. disc, mike, etc.
No. 80,176AV \$32.25 Ppd.

QUALITY DETECTOR UNDER \$40



Our fully transistorized BFO unit can locate a quarter at 18". Powerful 6 trans.-oscillator-amplifier circuit. Comp. to others priced 50% more! Aluminum, just 2 lb.
No. 80,222AV \$39.95 Ppd.

EDMUND SCIENTIFIC CO.

300 Edscorp Bldg., Barrington, N.J. 08007 • (609) 547-3488
America's Greatest Science • Optics • Hobby Center

THERE IS NO OTHER TELESCOPE LIKE IT!

THE NEW EDMUND 4 1/4", 1/4 NEWTONIAN WIDE FIELD REFLECTOR TELESCOPE

Clear, bright, spectacular wide angle views of stars, moon, comets... easy to use... portable!



Patent Pending

IN SECONDS YOU'RE SCANNING THE ASTOUNDING UNIVERSE, able to see and study the breath-taking cosmos as perhaps you never have before... awesome vastness, unbelievable orderliness, stark silent beauty. All the fascinating heavenly mysteries are yours to enter and explore. This new reflector telescope makes it easy for everyone to span a thousand light-years to space-age enjoyment of the heavens and outdoors. No complicated set up! Just insert the eyepiece, focus, and its big 3 1/2" field of view gives you more stars in a single view than any other type of telescope. Bright, crisp, finely resolved images to capture your interest and imagination. It's probably the easiest to use telescope ever... over your shoulder, in your lap, on a tripod. Or just rotate the spherical base on its own mount for use on a table, car hood. Take it anywhere (only 17" 10 lb.) Top quality optical system: 4 1/4", 1/4" parabolic primary mirror (1/4 wave), 17" F.L. 3" pre-galvanized 1/4 wave diagonal on a coated optical window seals optics from moisture and dust. 28mm Kellner eyepiece (gives 15X, higher without other eyepiece or Barlow). Fast focusing (25 to infinity). Bright Scharfianian red (down 1 m.p.m. night vision), adj. carrying strap. A first scope must be an ideal second scope!

There is no other telescope like it.

NO. 2001AV \$149.95 Ppd.

The Edmund BIOSONE II

turns brainwaves into an audible or visual signal. \$149.95

KNOW YOUR ALPHA FROM YOUR THETA!

For greater relaxation, concentration... monitor your alpha/theta brainwaves.

Features Normally Found Only In Units Selling For More Than \$200.00—And 3 Feedback Modes.

The portable, professional quality Edmund Biosone II boasts 3 feedback modes—LED FM tone, threshold tone; a test mode to check overall system of operation. Easy to use, this beautiful 4-pound, simulated walnut unit (9 1/2 x 5 1/2 x 4 1/4") can be operated at home, in office or clinic. It gives you outputs to allow further monitoring of logic signal, raw EEG, filter output, meter, and FM. Total brainwave monitoring capability, incl. filter select feedback, with wide range calibration sensitivity control (5-100 microvolts). Completely safe, the Edmund Biosone II is similar to an electroencephalograph (EEG), enabling you to identify the electrochemical activity that exists at all times in the human brain. In addition to letting you know when you're most relaxed, Biosone II is a great conversation piece. Included at its low price are a set of electrodes, an earphone jack for private use. Uses latest advances in linear circuitry, runs on two 9v transistor batteries (not included).

STOCK NO. 1668AV Just \$149.95 ppd.
LOW COST STARTERS' UNIT, No. 71,809AV\$59.95 ppd.

"SEE" MUSIC IN PULSATING COLOR



ASSEMBLED \$18.50 Ppd.
No. 42,309AV

UNASSEMBLED, IN KIT FORM \$15.95 Ppd.
No. 42,336AV ONLY

The Edmund 3-Channel Color Organ \$18.50

COMPLETELY ASSEMBLED! LESS THAN HALF THE PRICE OF OTHER MODELS!

Create your own audio "light show", add a new dimension to your music listening pleasure with the bargain-priced Edmund 3-Channel Sound To Light Control. Lets you modulate 3 independent strings of colored lamps with the intensity of your music. They flash and vary in brightness related to the music's rhythm, pitch and volume—a pulsating light performance to music! You get volume and frequency sensitivity to a peak rating of 300 watts per channel. Just plug in your favorite colored flood or spotlight, and turn on! Great price, too. This high quality, fully assembled unit in metal housing, with 3 individually controlled circuits, is priced at less than half that of others. Complete instructions are included with this terrific value.

GIANT FREE 164 PG. CATALOG



4000 UNUSUAL BARGAINS FOR HOBBYISTS, SCHOOLS, INDUSTRY

COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007

Send me the following:

Stock No.	Quantity	Price Ea.

Interbank No. _____ Add handling charge \$ 1.00

Card No. _____ Enclosed is _____ check, M.O. in amount of \$ _____

Expiration Date _____ Signature _____

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.

Address _____

City, State, Zip _____

The source of perfection in stereo sound... Pickering's new XSV/3000



The reviewers applaud as never before!

"... we don't see how you can do better at any price."
Hirsch-Houck Laboratories. Stereo Review. February 1977

"The new unit offers the stereo performance of the XUV/4500Q (or perhaps a little better than that) at a lower price. It seems hard to go wrong with such a combination."

CBS Technology Center. High Fidelity. February 1977

"Congratulations to all concerned on a fine contender amongst the world's best stereo pick-ups."

John Borwick. Gramophone. United Kingdom 1977

Pickering's new XSV/3000 is a remarkable development. It possesses a totally new and different design that makes it the precursor of a whole new generation of sophisticated, advanced stereo cartridges.

This has been made possible by technological advances in two areas. **First**, it has an unusually tiny, samarium cobalt (rare earth) magnet of remarkably high power that

permits extremely low mass, and also offers high output. **Second**, this cartridge features the new Stereohedron™ stylus tip, a Pickering first! This extraordinary shape has a far larger bearing radius, which provides increased contact area in the record groove. This assures gentler treatment of the record groove, longer record life, and also, far longer stylus life.

This cartridge provides remarkably smooth and flat frequency response; its channel separation is exceptional, its transient response possesses superb definition.

Truly, Pickering's XSV/3000 represents a whole new concept of excellence in stereo cartridges... the true **Source** of perfection in stereo sound.

For further information write to
Pickering & Co., Inc. Dept. PE,
101 Sunnyside Blvd., Plainview,
New York 11803



PICKERING & CO., INC., COPYRIGHT 1977

CIRCLE NO 38 ON FREE INFORMATION CARD



When you've got a Pace CB radio,



you've got the world by the ears.

There are millions out there with their ears on waiting to talk to you Pace to Pace.

And with a Pace CB two-way radio you've got every bit of power the law allows. And features to cut through interference and "bleeders" from other channels.

What's more, it's assembled with computerized circuitry and it's 100% solid state, so it's as trouble-free as a CB can be.

It all adds up to your voice getting out

there clearer and with less distortion, and the other guy's voice coming back just as clear.

To learn more, drop into a Pace place near you. The dealer will tell you just how economical and easy-to-install a Pace is. He'll help you choose the one that's just right for you, too.

Ask him for the world by the ears. He'll know which CB you're talking about.



PACE CB 8015

pace

PACE CB / PACE TWO-WAY RADIO PRODUCTS
BY PATHCOM INC., HARBOR CITY, CA 90710